

E151 Lecture 15 – References

Matthew Spencer
Harvey Mudd College
ENGR151


1

Disclaimer


These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

2

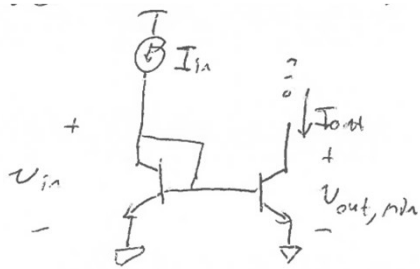How Do We Make Current Sources in Mirrors?



"Simple Mirror"

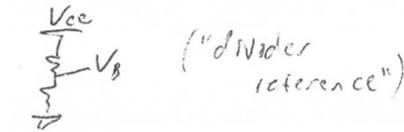

("divider reference")

eg:

("op-amp reference")

- Need analysis tools to measure "how good" V or I reference is
- References need to be supply and temperature invariant (PVT is big)

4


Measure Quality of Reference with Sensitivity

CA 11801 SENSITIVITY

$$S_{\text{of } Y(X)} \text{ to } X \equiv S_X \equiv \lim_{\Delta X \rightarrow 0} \frac{\Delta Y/Y}{\Delta X/X} = \frac{X}{Y} \frac{\partial Y}{\partial X}$$

fractional change of Y w/rt X


eg: divider reference in simple mirror

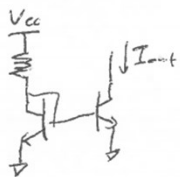

$$S_{V_{cc}}^{I_{out}} = \frac{V_{cc}}{I_{out}} \frac{\partial}{\partial V_{cc}} \left[\left(\frac{\beta}{\beta+2} \right) \cdot \left(\frac{V_{cc} - V_{be,on}}{R} \right) \right]$$

$$= \frac{\beta}{\beta+2} \cdot \frac{V_{cc}}{R} \cdot \frac{1}{\left(\frac{\beta}{\beta+2} \right) \left(\frac{V_{cc} - V_{be,on}}{R} \right)}$$
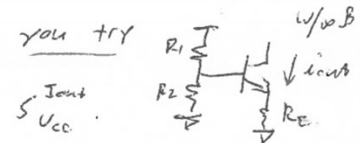
$$\approx \frac{1}{\left(1 - \frac{V_{be,on}}{V_{cc}} \right)} \approx 1 \quad \text{very sensitive!}$$




$$I_{out} = \left(\frac{R_2}{R_1 + R_2} V_{cc} - V_{be,on} \right) \cdot \frac{1}{R_E}$$

$$\frac{\partial I_{out}}{\partial V_{cc}} = \frac{R_2}{R_E} \cdot \frac{1}{R_1 + R_2}$$

$$S_{V_{cc}}^{I_{out}} = \frac{1}{\left(1 - \left(1 + \frac{R_1}{R_2} \right) \frac{V_{be,on}}{V_{cc}} \right)} \approx 1$$

5

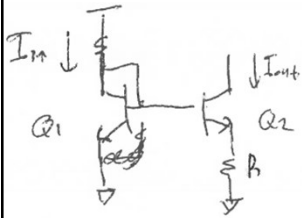“Widlar Current Source” Reference if Time



Interested in $I_{out}(\bar{I}_{in})$

$$- V_{be1} = V_{be2} + I_{out} R - \frac{\beta}{\beta+1}$$

$$- I_{S1} e^{V_{be1}/\phi_T} = \beta I_{S1} \rightarrow V_{be1} = \phi_T \ln \frac{\beta I_{S1}}{I_{S1}}$$

$$- \phi_T \ln \frac{I_{in}}{I_{out}} \approx I_{out} R$$

• Note can't assume 0.7V here

• Need on $1/\beta$ for V_{be} (bug last lecture)

- Logarithmic compression of I_{in} , so called a reference

6

“Widlar Current Source” Reference if Time

- Sensitivity w/ 1mA and 1k this is a factor of 40 better

$$\text{Sensitivity} \sim \phi_T \frac{\partial}{\partial V_{cc}} \ln \frac{I_{in}}{I_{out}} = R \frac{\partial I_{out}}{\partial V_{cc}}$$

$$\phi_T \left(\frac{1}{I_{out}} \frac{\partial I_{in}}{\partial V_{cc}} - \frac{I_{in}}{I_{out}^2} \frac{\partial I_{out}}{\partial V_{cc}} \right) = R \frac{\partial I_{out}}{\partial V_{cc}}$$


$$\frac{\partial I_{out}}{\partial V_{cc}} = \left(\frac{1}{1 + \frac{I_{out} R}{\phi_T}} \right) \cdot \frac{I_{out}}{I_{in}} \cdot \frac{\partial I_{in}}{\partial V_{cc}}$$

$$S_{V_{cc}}^{I_{out}} = \frac{V_{cc}}{I_{out}} \cdot \frac{\partial I_{out}}{\partial V_{cc}} = \left(\frac{1}{1 + I_{out} R / \phi_T} \right) \cdot S_{V_{cc}}^{I_{in}} \approx \left(\frac{1}{1 + \frac{I_{out} R}{\phi_T}} \right)$$

7

Vbe Reference if Time

You try Vbe reference

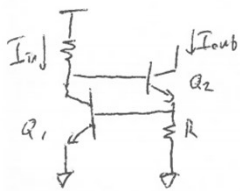

$$I_{out} = V_{be} / R$$

$$= \frac{\phi_T}{R} \ln \frac{I_{in}}{I_{S1}}$$

$$\frac{\partial I_{out}}{\partial V_{cc}} = \frac{\phi_T}{R} \cdot \frac{I_{S1}}{I_{in}} \cdot \frac{\partial V_{be}}{\partial V_{cc}} = \frac{1}{I_{S1}} \cdot \frac{\partial I_{in}}{\partial V_{cc}}$$

$$S_{V_{cc}}^{I_{out}} = \frac{\phi_T}{R} \cdot \frac{I_{S1}}{I_{in}} \cdot \frac{\partial I_{in}}{\partial V_{cc}} = \frac{V_{cc}}{I_{out}} = \frac{\phi_T}{V_{be,ref}} \cdot S_{V_{cc}}^{I_{in}}$$

-Note: pretty good vs Vcc

$$S = \frac{26 \text{ mV}}{100 \text{ mV}} = 2.7\%$$


$$\text{bc } I_{out} R = V_{be,ref}$$

$$\text{so } \frac{V_{cc}}{I_{in}} \frac{\partial I_{in}}{\partial V_{cc}} = S_{V_{cc}}^{I_{in}}$$

- I like this one, easy to implement, easy to analyze, good vs. supply

8

Self-Biasing for Supply Insensitivity

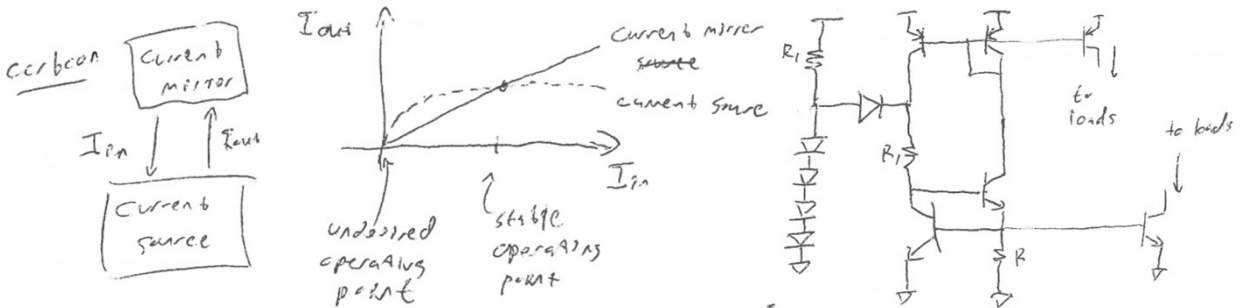

- Get away from dropping Vcc over R ... big sensitivity benefit
- Need startup circuit because undesired stable point (eg: 4Vbe vs. 3)
- Want startup circuits to shut themselves off (eg: rev. bias b/c of Rx)

9


Temperature Sensitivity

$$TC^{I_{out}} = \frac{1}{I_{out}} \frac{\partial I_{out}}{\partial T}$$

- Model w/ temperature coefficient (sensitivity to temp, % change/deg)
- Big issues: Resistors (+1100 ppm/C), V_{be} (-2mV/C), ϕ_T (3300 ppm/C)
- Cancel OK in Widlar, bad issue in V_{be} , assorted self-bias tricks
- Sometimes need reference V constant w/ both supply and temp (eg: regulators) \rightarrow Band Gap


10

Band Gap Reference

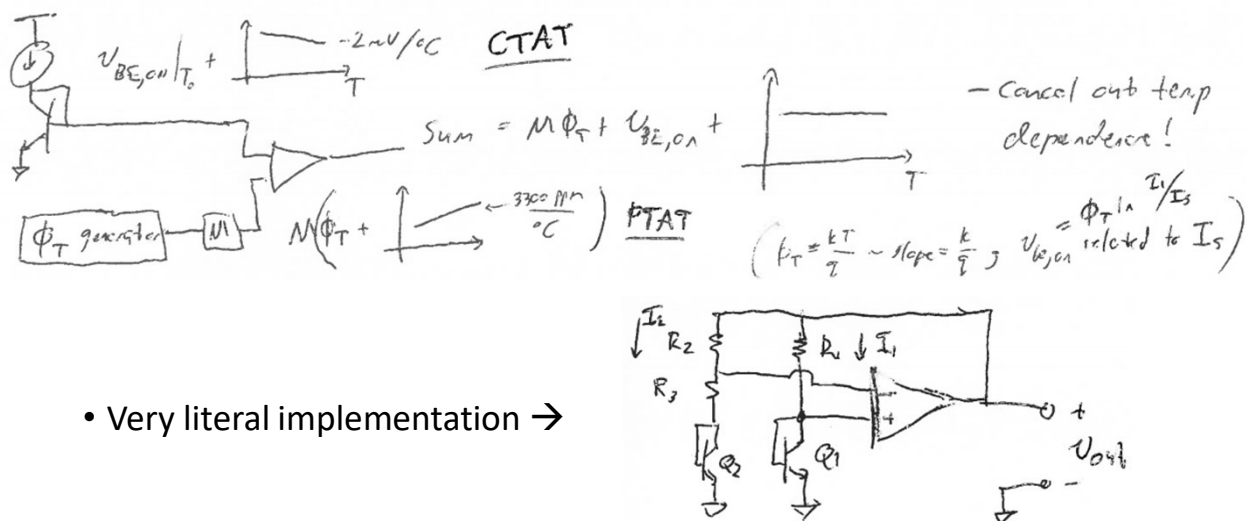

- Very literal implementation \rightarrow

11

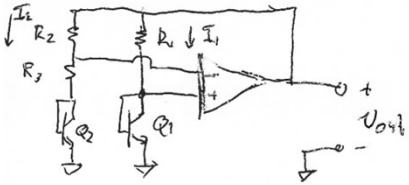

- OP-amp forces $V_{R1} = V_{R2}$

- so $\frac{I_1}{I_2} = \frac{R_2}{R_1}$

- ϕ_T generated, can get it from ΔV_{be}

$$V_{R3} = \underbrace{V_{be1} - V_{be2}}_{\Delta V_{be}} = \phi_T \ln \frac{I_1}{I_2} - \phi_T \ln \frac{I_2}{I_1} = \phi_T \ln \frac{R_2}{R_1} \frac{I_{S2}}{I_{S1}}$$

• same current in R_2 & R_3 , so $V_{R2} = \frac{R_2}{R_3} V_{R3}$

Finally, do KVL, $V_{out} = V_{be2} + V_{R2} + V_{R3}$


$$= V_{be2} + \left(1 + \frac{R_2}{R_3}\right) \phi_T \ln \frac{R_2}{R_1} \frac{I_{S2}}{I_{S1}}$$

$$= V_{be2} + M \phi_T \quad \text{where } M = \left(1 + \frac{R_2}{R_3}\right) \ln \frac{R_2}{R_1} \frac{I_{S2}}{I_{S1}}$$

12

Band Gap Details

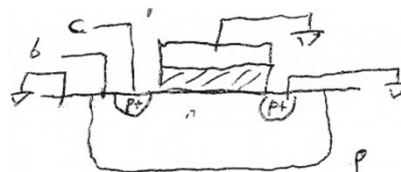- $V_{OUT} = 1.26V$, about the band gap of silicon in eV (but unrelated)
- Temperature variation: parabolic, concave down, a few mV over 100C
- Implement in CMOS w/ parasitic substrate PNP



13