

# E151 Lecture 17 – CE Dynamics and Miller

Matthew Spencer  
Harvey Mudd College  
ENGR151

## Disclaimer


These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

## Describe BJT Small Signal Speed Limit with $f_T$

How fast can we go?

→ often measured w/  $f_x$ , frequency where  $A_i$  drops to 1

$f_{max}$  where power gain = 1

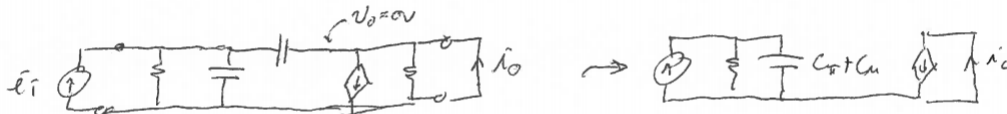


$$i_o = \beta i_{be}$$

$$v_{be} = i_i \cdot \frac{R / (C_{\pi} + C_{\mu})s}{R + 1/(C_{\pi} + C_{\mu})s} = \frac{r_{\pi}}{1 + r_{\pi}(C_{\pi} + C_{\mu})s}$$

$$So A_{VT} = \frac{\beta}{1 + \beta \left( \frac{C_{\pi} + C_{\mu}}{g_m} \right) s}$$

$$\rightarrow f_T \approx \frac{1}{2\pi} \frac{g_m}{r_{\pi} + r_{\mu}}$$

## Dynamic Model of CE Amplifier

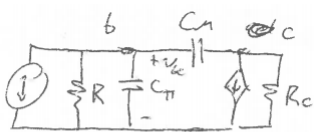

$$R = R_S \parallel r_{\pi}$$

$$i_i = v_i / R_S$$

Let  $R_C$  stand for  $R_C \parallel r_o$

kCL @ b

$$i_i = \frac{v_b}{R} + v_b C_{\pi} s + (v_b - v_c) C_{\mu} s$$

kCL @ c

$$(v_b - v_c) C_{\mu} s = g_m v_b + \frac{v_c}{R_C}$$

$$\frac{v_c}{v_i} = -g_m R_C \frac{r_{\pi}}{R_S + r_{\pi}} \cdot \frac{1 - s \frac{C_{\mu}}{g_m}}{1 + s(C_{\mu}(R_C + R_{L||\pi}) + g_m R_L R_S || \pi) + s^2 C_{\mu} C_{\pi} R_C R_L R_S || \pi}$$

Terrible Algebra Ahead!

- Separates into gain + dynamics, get gain from DC circuit
- RHP zero → negative feedthrough
- This is unsustainable ... need approximation methods

For Clarity: 
$$\frac{\left(1 - \frac{s C_{\mu}}{g_m}\right)}{1 + s(C_{\mu}(R_L + R_S || \pi) + g_m R_L R_S || \pi) + C_{\pi} R_S || \pi} + s^2 C_{\mu} C_{\pi} R_L R_S || \pi}$$

## First Simplification: CE Amplifier PZ Plot

- We can simplify our life by noticing poles are real & widely separated

↳ poles usually real & widely separated

$$D(s) = (1 + z_1 s)(1 + z_2 s) = 1 + (z_1 + z_2)s + z_1 z_2 s^2 \approx 1 + z_1 s + z_1 z_2 s^2$$


dominant pole is slow

$$P_1 = \frac{1}{z_1} = C_{\pi} R_{\text{in}} / r_{\pi} + C_{\mu} (R_{\text{in}} + R_{\text{out}}) / (R_{\text{in}} R_{\text{out}})$$

$$P_2 = \frac{1}{z_2} = \frac{1}{R_{\text{out}} C_{\mu}} + \frac{1}{R_{\text{in}} C_{\mu}} + \frac{1}{R_{\text{out}} C_{\pi}} + \frac{g_m}{C_{\pi}}$$

- Communicating caps ... icky ... can't just thevenize
- Assumed  $\tau_1 \gg \tau_2$  so we can pull  $\tau_1$  straight from s coefficient
  - True because of  $g_m \cdot R_I$  term
  - Why is our voltage gain in here?

## The Miller Effect

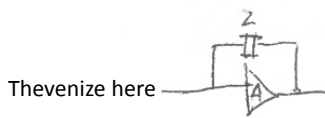


$$\tilde{v} = \frac{v_i - v_o}{Z}$$

$$= \frac{v_i}{Z} \cdot (1 - A)$$


$$\frac{v}{i} = Z_{\text{eff}} = \frac{Z}{1 - A}$$

- Thevenin impedance is boosted by gain across a feedback element!
- Caps in feedback around negative gain appear bigger by  $1 + A$

## The Miller Approximation for a CE

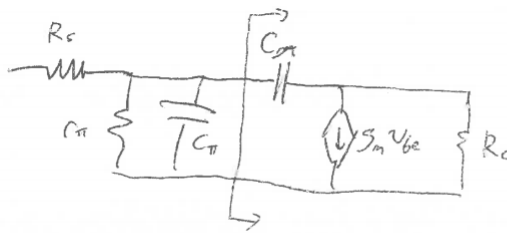


Find thevenin here

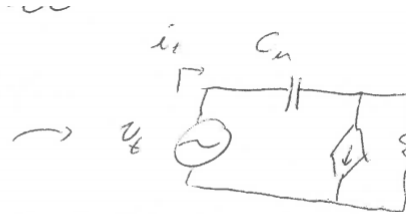

$$\frac{v_E - v_o}{1/C_{\mu} s} = i_i = C_{\mu} s (v_E - v_o)$$

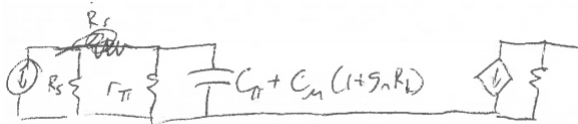- Let's just calculate the first pole & assume that  $C_{\mu}$  sees the DC gain



$$P_1 = (R_s \parallel r_{\pi}) (C_{\pi} + C_{\mu} (1 + g_m R_c))$$

$$v_o = -g_m R_c \frac{R_s \parallel r_{\pi}}{1 + \tau_1 s} \cdot \frac{v_i}{R_s}$$

## Issues with Miller Approximation

- Not conservative:
  - lose zero and 2<sup>nd</sup> pole, so ignore lots of stability implications
  - Approximation of  $\tau_1$  loses a  $C_{\mu} R_c$  term, appears a bit faster
- Kind of CE specific,
  - relies on  $a_v$  falling across tricky feedback cap
  - lets us convert  $C_{\mu}$  to grounded
- Even so, gives good intuition about caps in feedback!