

E151 Lecture 25 – Wrap Up

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

Administrative

- Assessment – in class right now, out of class as final review
- Final is Monday 5/11, 2-5PM. Allowed 2 8.5”x11” cheat sheets.
(More details to follow in email, including review resources & Zoom)
- We’re going to fill out course evaluations today.

Stability Analysis Practice


- Consider an uncompensated amplifier with two poles at $p_1=1\text{MHz}$ and $p_2=10\text{MHz}$. What is the maximum open loop gain the amplifier can have and still be unity gain stable?
- Answer:
 - reach 180deg phase at 100MHz.
 - Have 1 decade (1MHz-10MHz) of 20dB rolloff
 - Have 1 decade (10MHz-100MHz) of 40dB rolloff
 - Therefore max stable gain is 60dB \rightarrow 1000


Stability Analysis Practice, Round 2

- Consider an uncompensated amplifier with two widely separated poles. One at low frequency and the second at crossover. What is the phase margin of this amplifier?
- Answer:
 - Leave as exercise to reader


Op-Amp Quiz Follow Up


- Output and input swing calculations may be rusty, esp class B/AB
- Bandwidth and/or transfer function estimation is a good skill
 - Usually only need to find one OCTC or calculate rout into Ccomp,eff
- Natural followup would be to use Xfer function to ask about stability
- DC coupling didn't require a level shift here
- Must degenerate CE stage because emitter bypass doesn't work at DC
- r_{in} of the class AB is small ... careful of loading

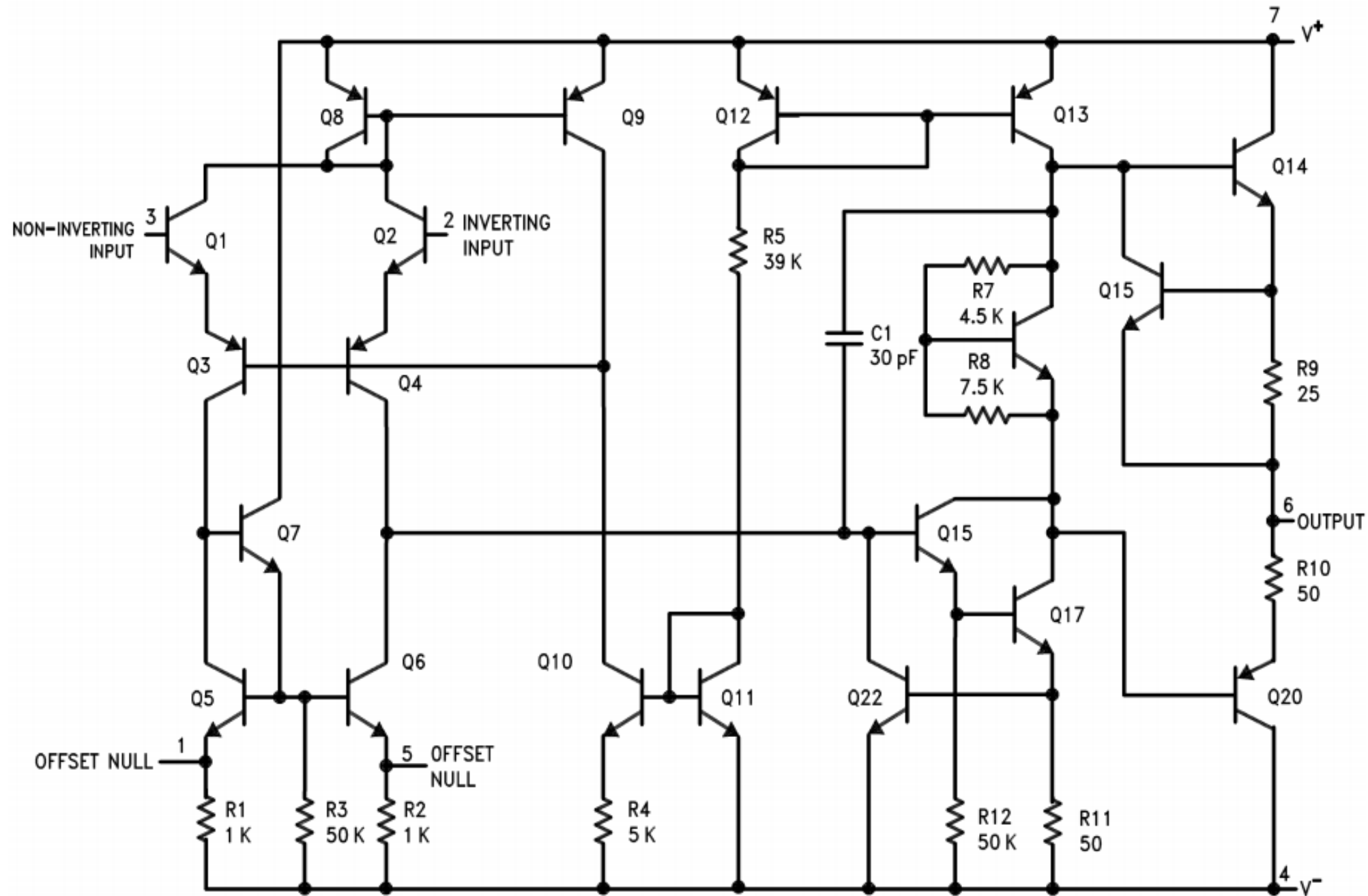

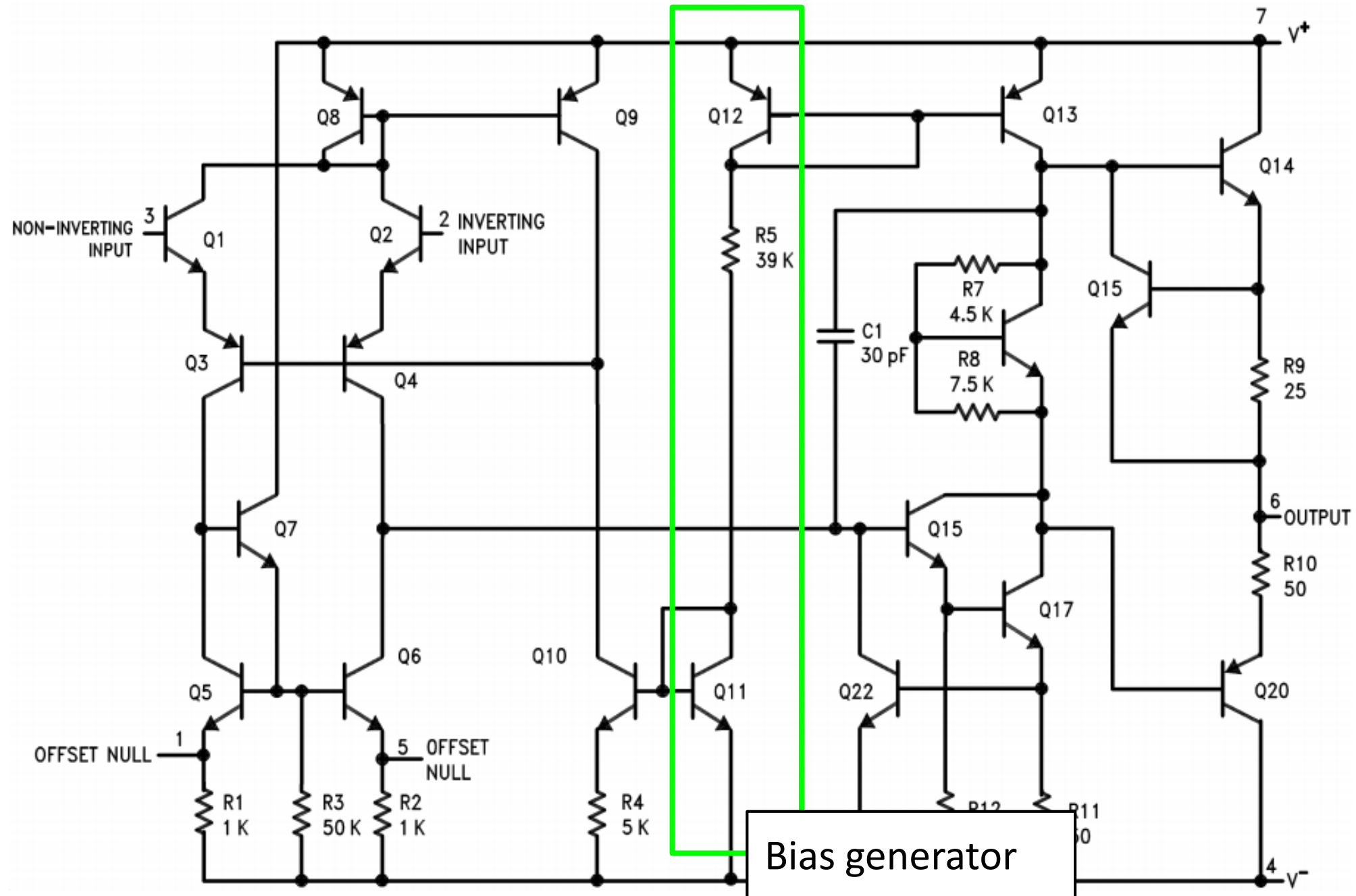


Cascoded Diff EF Input

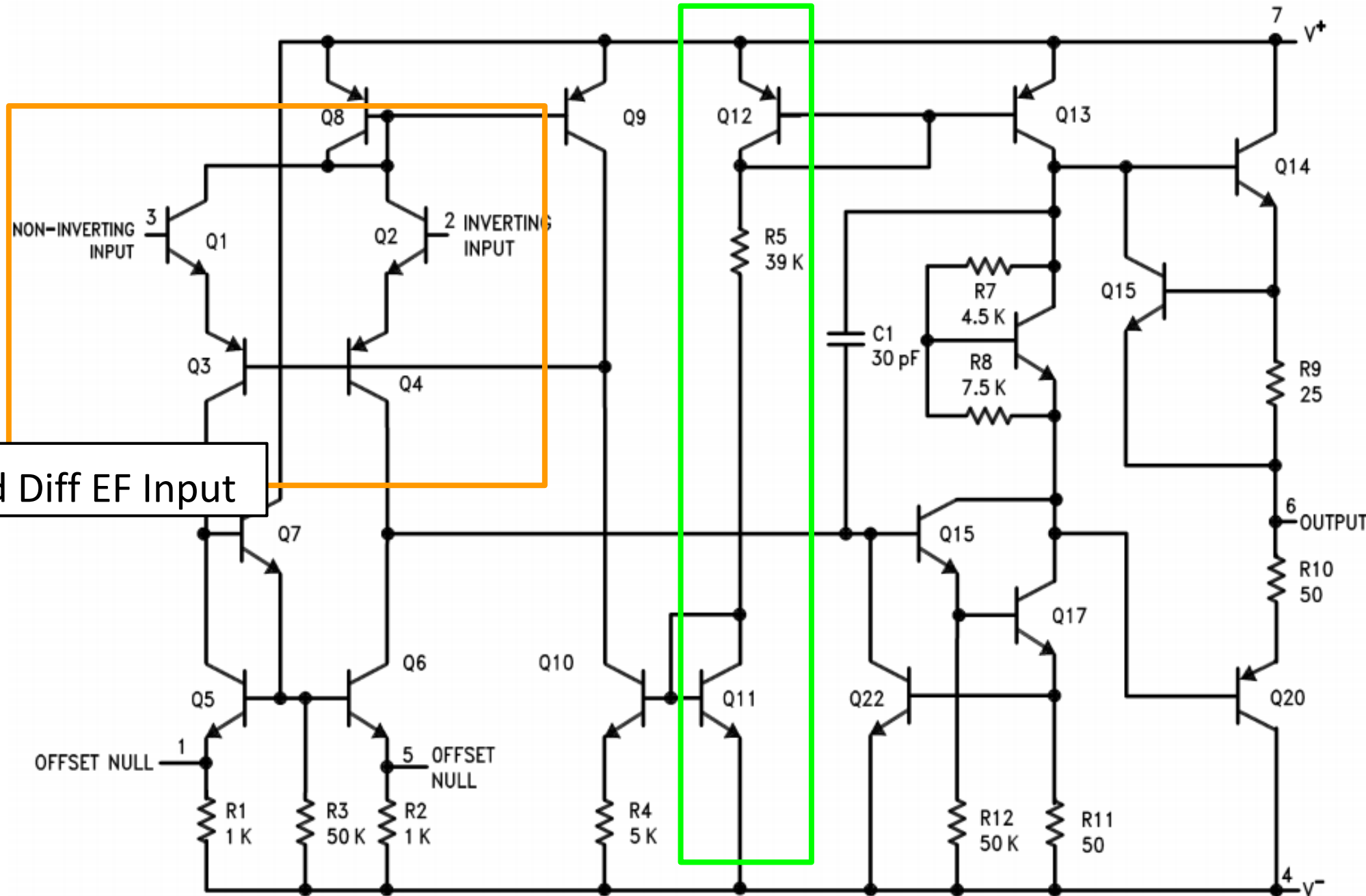


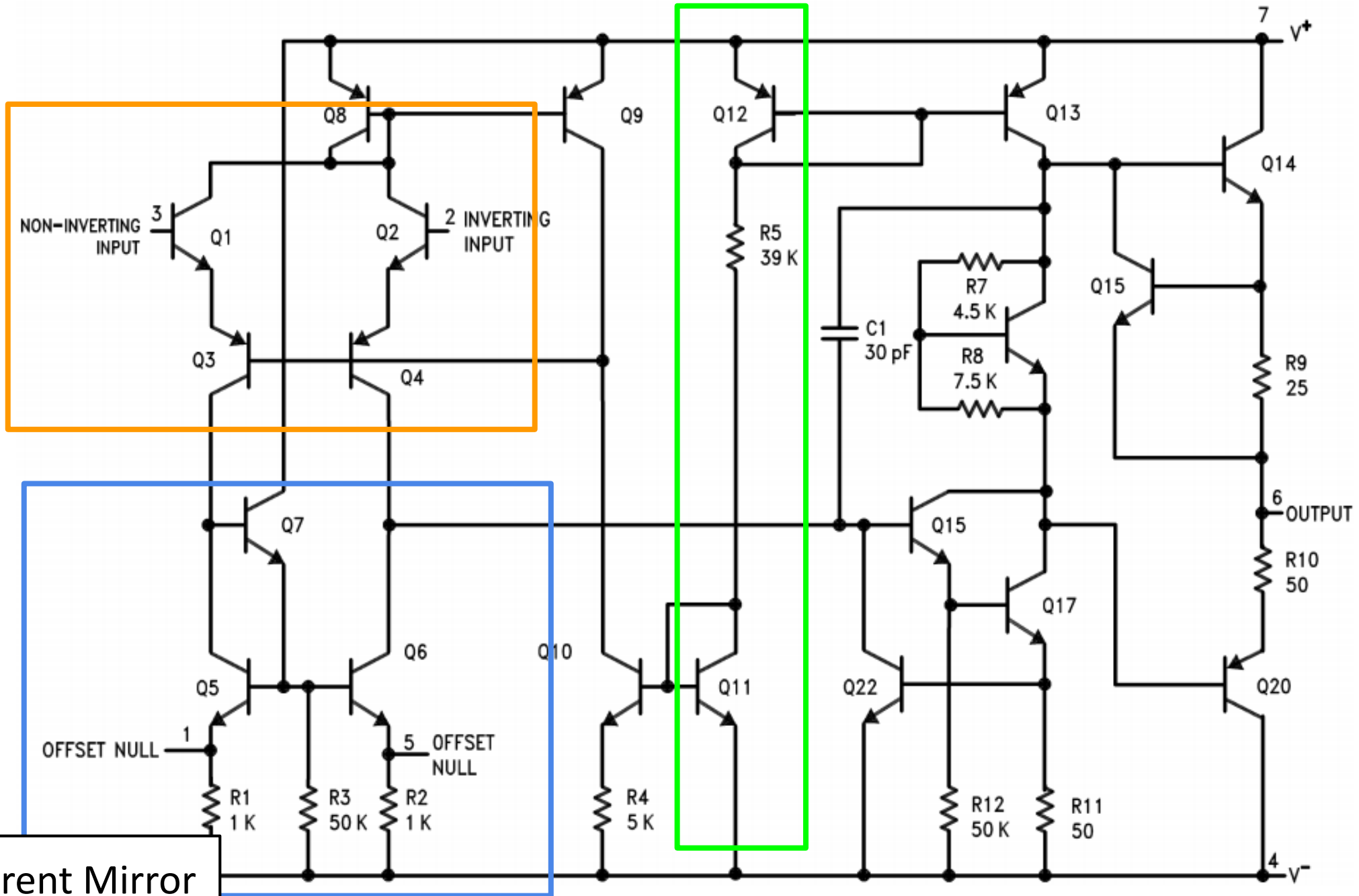



Fancy Current Mirror

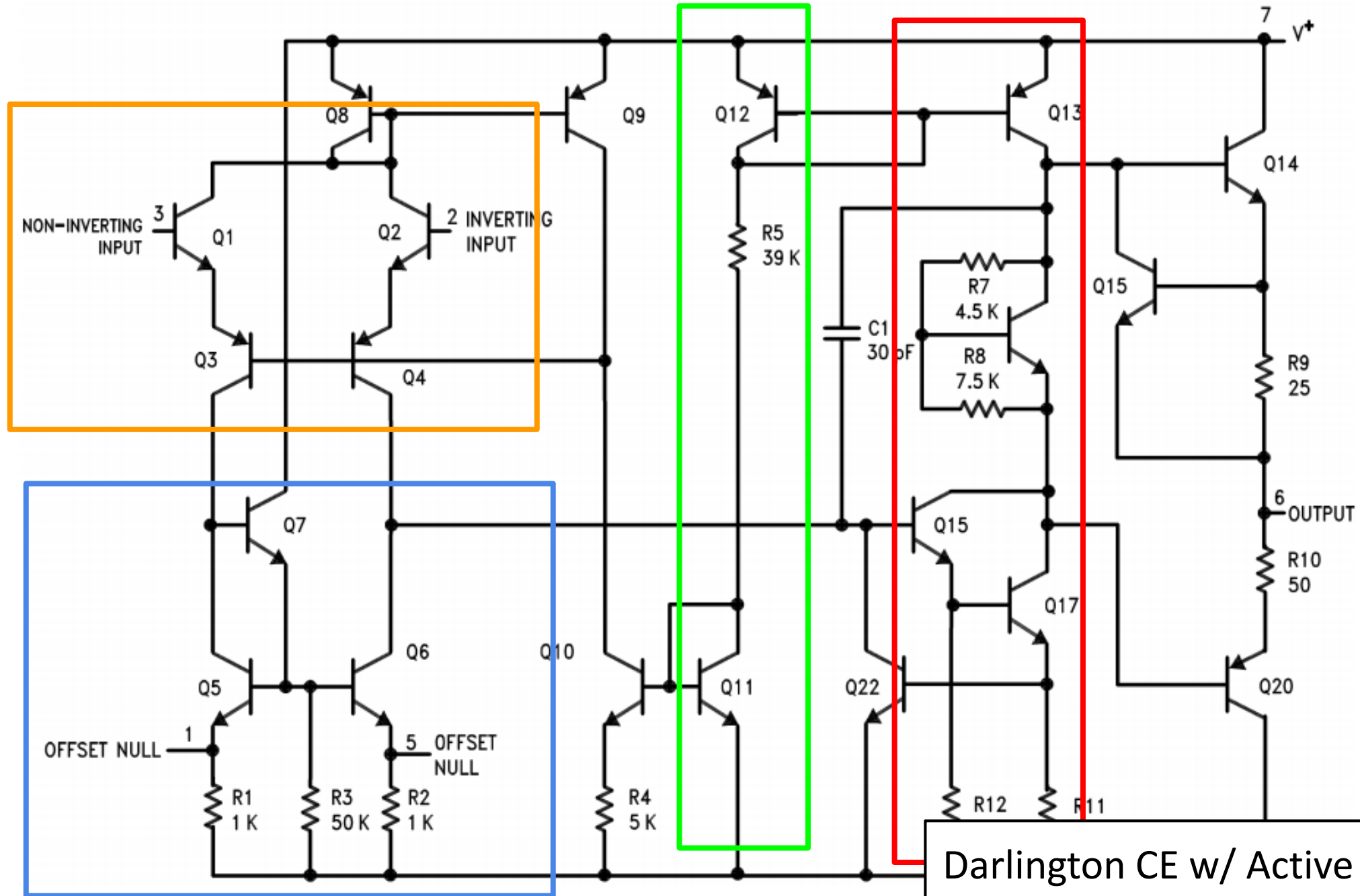

Darlington CE w/ Active Load

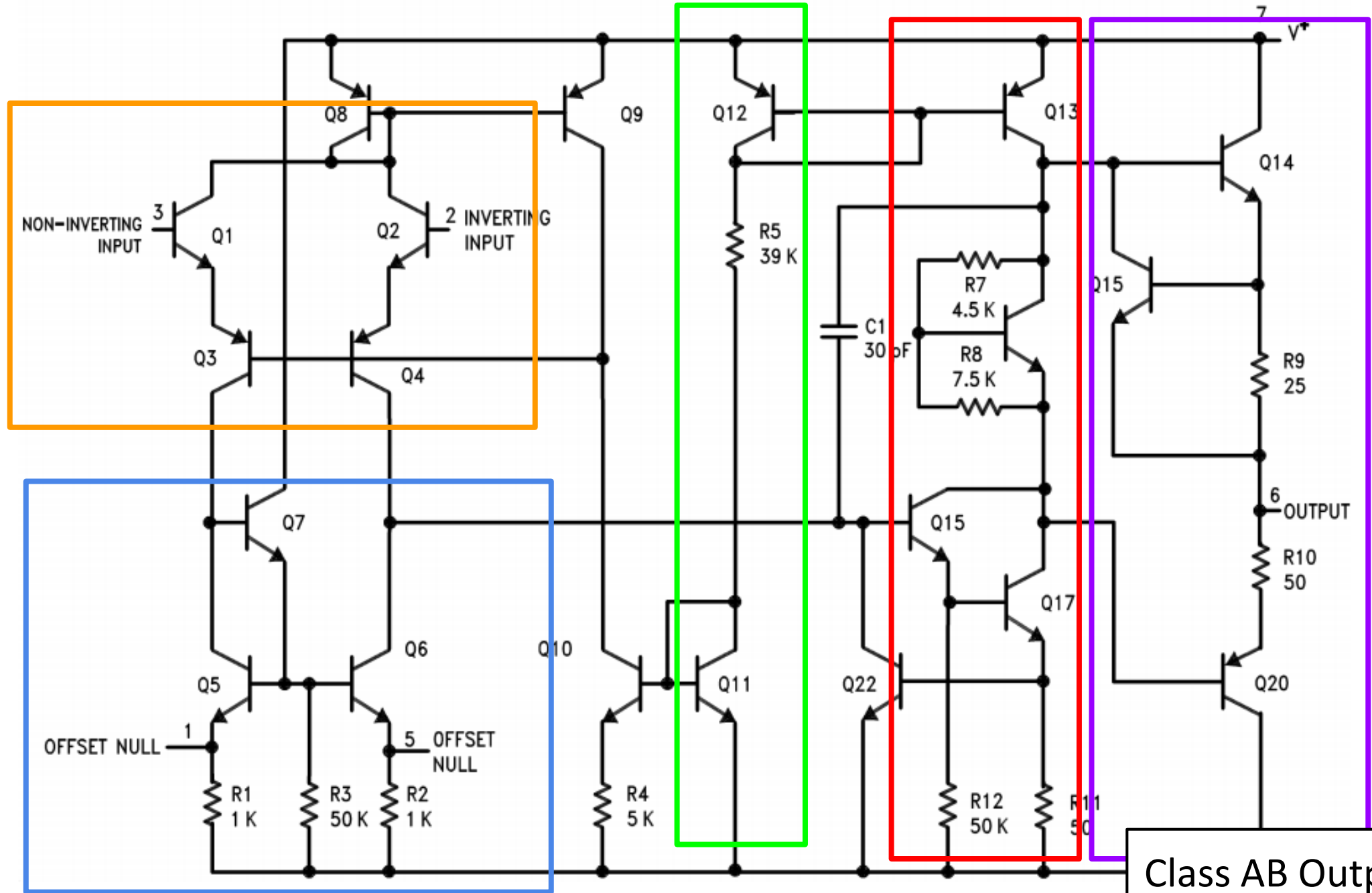

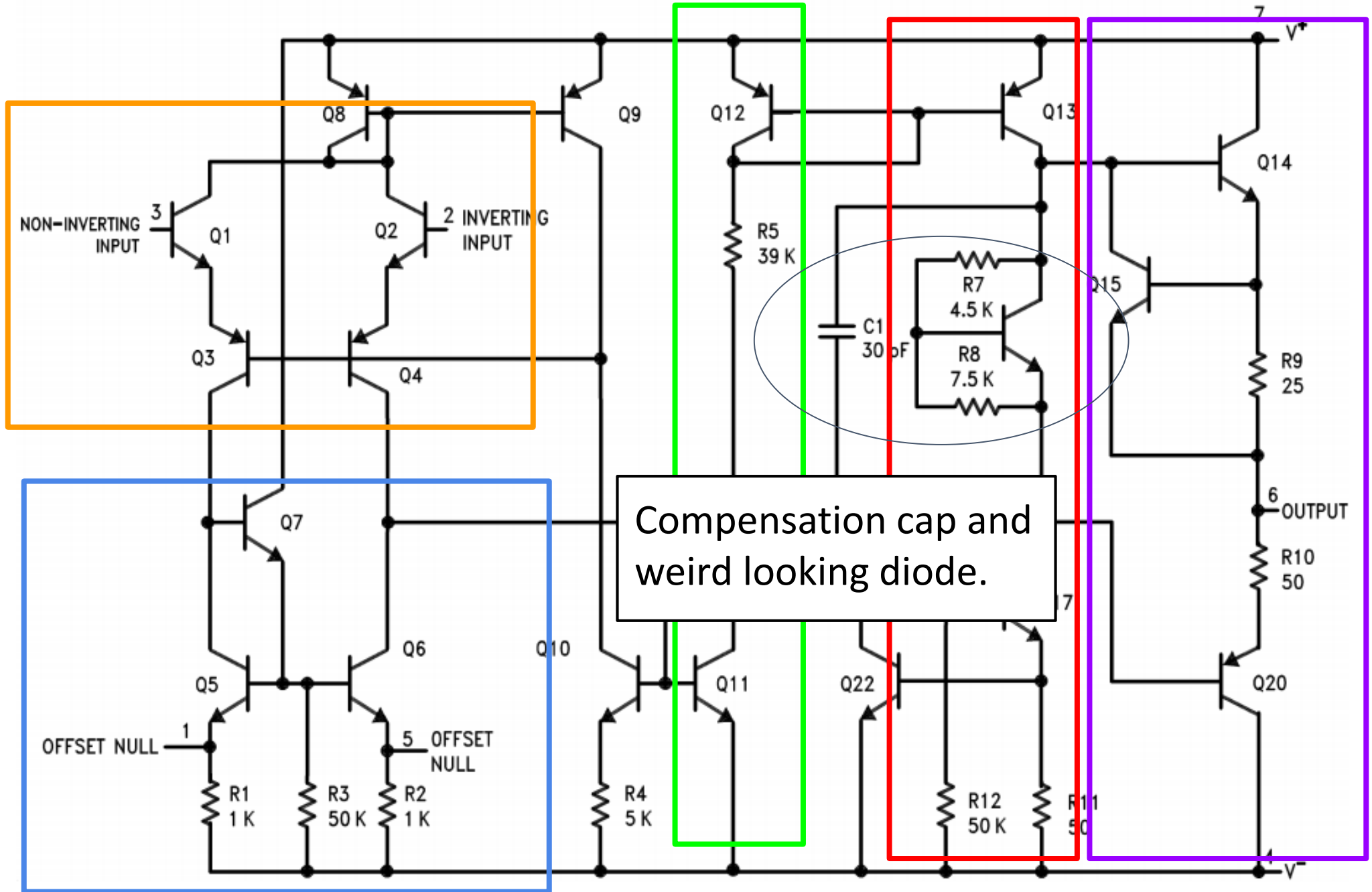

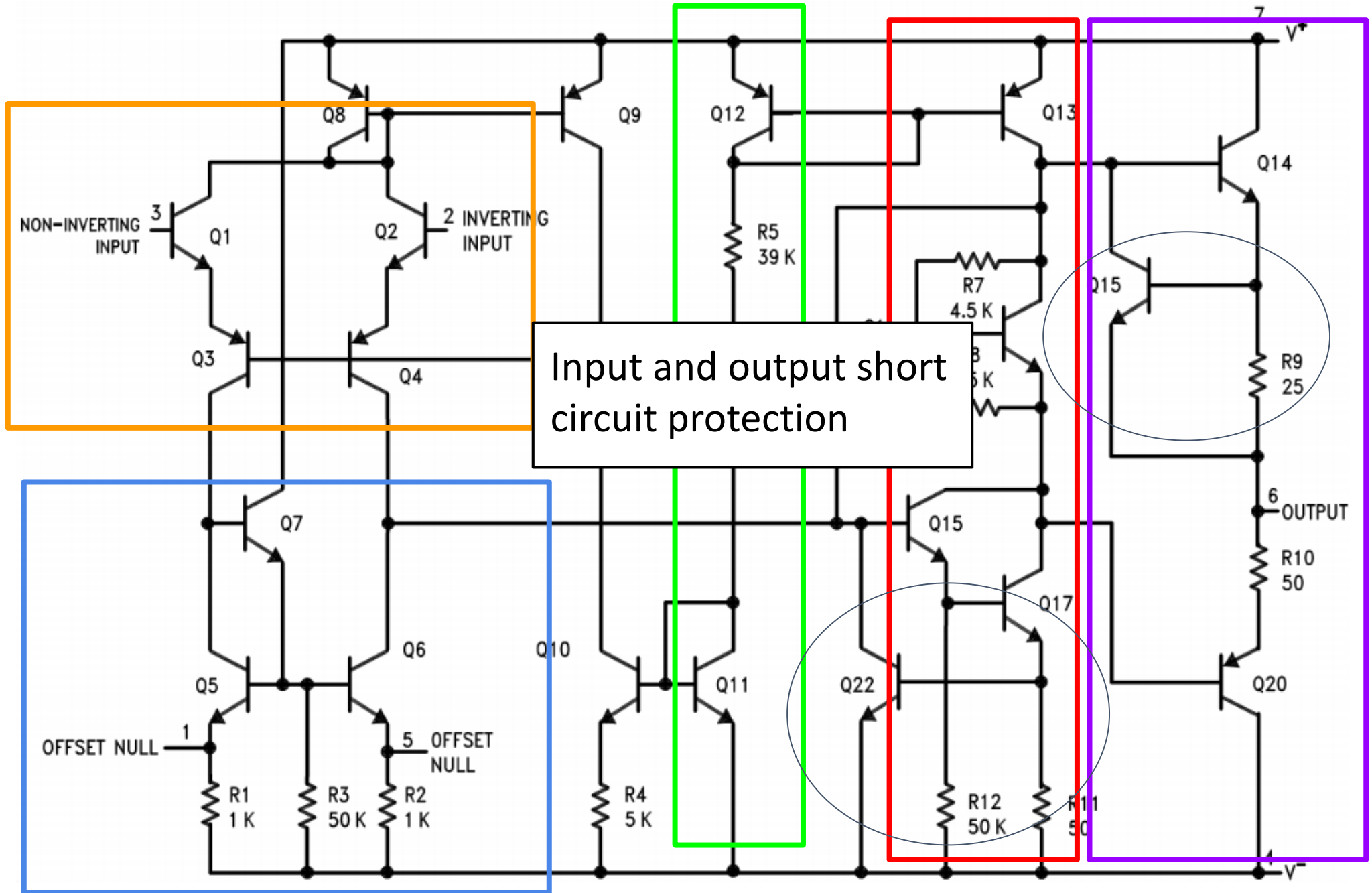

Input and output short circuit protection