

Multistage Amplifiers and Emitter Followers

Matthew Spencer
Harvey Mudd College
E151 – Analog Circuit Design

1

Up until now we've only looked at common emitter amplifiers, and while they're a fine place to start amplifier design, they can't do all of the things we'd like amplifiers to do. In this video series we're going to talk about combining amplifiers to achieve specs that we would otherwise be unable to achieve with common emitters, and we'll also be introducing a new amplifier called the emitter follower. This video series has some important organizational and motivational content for the next few lectures, where we'll be learning about different types of amplifiers that we can use in our multistage designs. We're also going to be analyzing some small signal circuits that turn up over and over again, so you'll need to pay attention both to our process and our results because I want you both to be able to analyze new small signal circuits and to use results that we derive here in bigger designs.

Multistage Amplifiers

Matthew Spencer

Harvey Mudd College


E151 – Analog Circuit Design

2

In this video we're going to set our direction for the next few weeks, so it's an important organizational video. We're also going to introduce modeling techniques that let us analyze collections of amplifiers easily.

We Can't Make a CE to Solve Every Problem

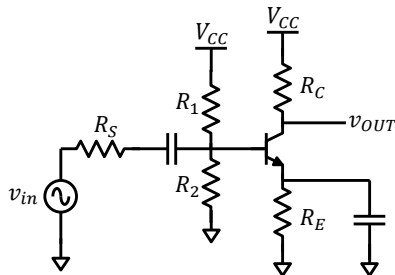- Problem: want 10,000x (80dB) voltage gain and 2V output swing.



$$V_{CC} - V_O = I_C R_C = \frac{V_{SW}}{2} \quad \text{if limited on high side}$$

$$a_v = g_m R_C = \frac{I_C R_C}{\phi_{th}} = \frac{V_{CC} - V_O}{\phi_{th}}$$

$$\text{For } a_v = 10,000 \text{ need } V_{CC} - V_O = 40\text{kV}$$

3

OK, so we're armed with enough amplifier knowledge to be dangerous, let's put it to use. Say a client comes to you requesting an amplifier with a gain of 10,000 and a measly 2V of output swing. This seems like something you can tackle. As a quick aside before we start, some circles will refer to a voltage gain of 10,000 as 80dB of gain, using the formula $20 \cdot \log(V_{out}/V_{in})$. I don't love that definition because of some subtleties about the source and load impedance, but don't forget dBs, they come up often when you're designing around large numbers in amplifiers.


CLICK OK, so let's get into this design. We know that the large signal voltage drop across R_C is given by $I_C \cdot R_C$, and that sets V_O . You should note that if V_O is closer to V_{OMAX} than V_{OMIN} , this value is also $V_{SW}/2$.

CLICK However, you might note with dismay that our voltage gain is equal to $g_m \cdot R_C$, and if we sub in for g_m then we find the gain is $I_C \cdot R_C / \phi_{th}$, and substituting in the previous line reveals that our voltage gain is directly proportional to the voltage drop across R_C . This relation is true regardless of what I_C and R_C you pick, so we know that every volt of drop across R_C turns into a voltage gain of about 40. (because $1/25\text{mV}$ is about 40 $1/V$)


CLICK The consequences of that become clear if we calculate how much dropout we'd need to achieve a gain of 10,000. Rearranging the equation above shows that $V_{CC} - V_O$ would

have to be 40kV in order to get a gain of 10,000. That's implausible for a wide variety of reasons, so it looks like the common emitter can't be used to make this amplifier design work.

Combining Amp Stages Makes Super Amps

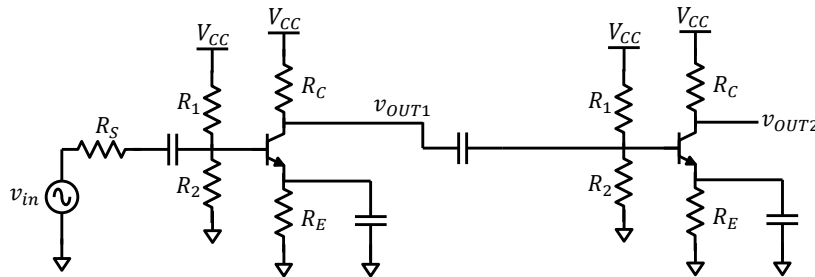

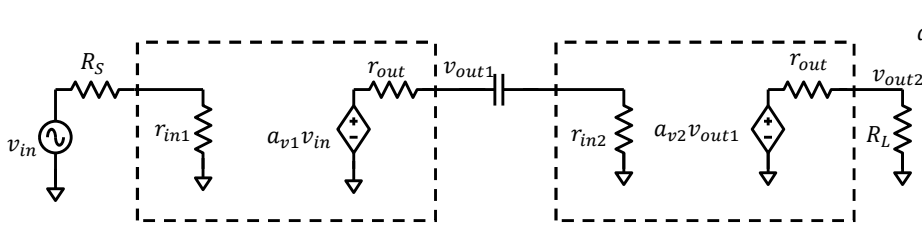$a_v = 200$ implies $V_{CC} - V_O = 5V$
 Two stages:
 $a_v \approx 20,000$ with 10V swing
 (depending on r_{out} and r_{in})
 Meets our design spec!



$$a_{v,multi} = a_{v1} \frac{r_{in2}}{r_{out1} + r_{in2}} a_{v2}$$

$$r_{in,multi} = r_{in,1}$$

$$r_{out,multi} = r_{out,2}$$

OK, that's rough, but what if we stuck two common emitter amplifiers together? Maybe this would produce the gain we needed without needing a crazy VCC value. It certainly looks like a nice idea, but the idea of re-analyzing some big structure with two small signal models inside of it seems like a pain. Notice that I've coupled the amplifiers together with a capacitor, so they can each have different DC bias points.

CLICK Fortunately, we can use our generic amplifier model to make our lives much easier. If we know r_{in} , r_{out} and a_v for each amplifier then we can convert them to this generic form, and it's really easy to calculate the gains and impedances associated with this multistage amplifier.

CLICK The gain of the multistage amplifier is given by the product of the gain of each amplifier multiplied by the voltage dividers formed between each stage, called interstage loading. When this multistage amplifier is put in a circuit, it will see extra dividers at the load and the source as usual. The output impedance of the combined amplifier is given by the output impedance of the last stage, and the input impedance is given by the input impedance of the first stage.

CLICK Taking that back to our two common emitters, we can design each with a_v of 200, which means we'll have a 5V drop from VCC on each of them.

CLICK That means if the rout of the first stage is similar to the rin of the second stage, we'll pick up a gain of $\sim 20,000$ from these two amplifiers with around 10V of swing. Nice!

This is called a multistage model

Heterogeneous Multistage Allows Even More

Issue with CE Amp

r_{out} often high and r_{in} is modest

Poor linearity / gain depends on g_m

Gain and swing are coupled

a_v isn't super high

Amplifier to Fix It

Emitter Follower

CE with Degeneration Resistor

CE w/ Degeneration, Active Load

Cascodes with active loads

We can go even further with multistage amplifiers by replacing some of the common emitter stages with other amplifiers. On this slide I've listed issues with common emitters and the amplifiers that we're going to use instead of common emitters to fix them. For instance, we can get better r_{out} and r_{in} from emitter follower amplifiers than we can with common emitters, and we can fix that lingering g_m non-linearity for large gains by using something called a common emitter with degeneration resistance. There are other problems we'll address too: we'll look at a few ways to fix the coupling of gain and swing, including the aforementioned common emitter with degeneration and also something called an active load, and we'll find something called a cascode can make comically high voltage gains.

All of this is hopefully interesting foreshadowing. But the main takeaway is that we're going to study some other amplifiers that we can include in our multistage amplifier model in the next few lectures.

Summary

- Common emitter amplifiers can't do everything, partially because of a fixed relationship between gain and swing:

$$a_v = \frac{V_{CC} - V_O}{\phi_{th}}$$

- Using multistage amplifiers lets us combine properties from many amplifiers:

$$r_{in,multi} = r_{in,1}$$

$$a_{v,multi} = a_{v1} \frac{r_{in2}}{r_{out1} + r_{in2}} a_{v2}$$

$$r_{out,multi} = r_{out,2}$$

- We're learning about new amplifiers with new properties next.

Emitter Followers

Matthew Spencer

Harvey Mudd College


E151 – Analog Circuit Design

7

In this video we're going to find the small signal parameters of an amplifier called the emitter follower. This might sound simple, and that's true in the sense that each step in the following slides is pretty easy, but this video is going to cover a lot of ground. That's particularly true because I want you to remember both how we analyzed the emitter follower small signal model and the results of the analysis. There are only two videos today, so it's important that you take this one slowly and absorb it. Also pause and work problems when requested.

Emitter Follower: Emitter Not Grounded

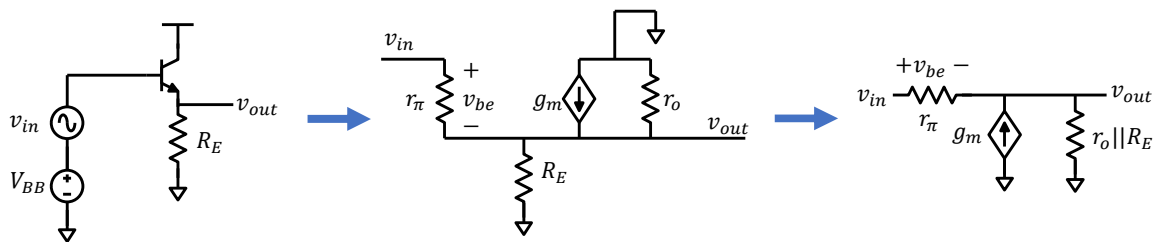- AKA Common Collector b/c collector is grounded.
- Will find they have high r_{in} , low r_{out} , $a_v \approx 1$.
- Good as voltage buffers, reduce loading effects.



8

I've drawn an emitter follower on the left of this slide and listed a few of its notable or desirable properties on the left. A handful of people call the emitter follower a common collector amplifier because the collector is small signal grounded by being connected to VCC. Importantly, that means the emitter is not grounded, which makes calculating input and output resistances much more complex. When we calculate the amplifier parameters we'll find that r_{in} of an emitter follower is very high, r_{out} is very low and a_v is about one. That makes emitter followers great voltage buffers: they can make copies of voltages and drive them with low output impedance.


We need to draw a small signal model of the emitter follower to start calculating those amplifier parameters. I'd like you to pause the video and draw a small signal model for an emitter follower.

CLICK Here's my rendition. Note that the collector is grounded, the emitter is now free to move around, which is important because it's the output node of this amplifier.

CLICK We can clean this schematic up considerably by getting rid of some of the extra 90 degree angles and combining r_o and R_E in parallel. We'll use this model to find r_{in} , r_{out} and a_v .

Emitter Follower r_{in}

- Set $R_S = 0$, R_L proper value
- R from v_{out} to ground is $R_E || r_o || R_L$
- Use i_{in} as test source: easier than v_{in}

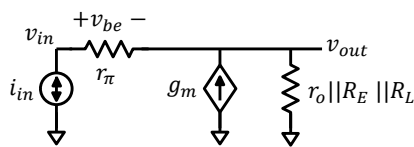

$$v_{be} = i_{in}r_{\pi}$$

$$v_{out} = (i_{in} + i_{gm})(R_E || r_o || R_L)$$

$$= i_{in}(1 + g_m r_{\pi})(R_E || r_o || R_L)$$

$$v_{in} = v_{out} + v_{be}$$

$$= i_{in}(1 + g_m r_{\pi})(R_E || r_o || R_L) + i_{in}r_{\pi}$$

$$r_{in} = r_{\pi} + (\beta + 1)(r_o || R_E || R_L) \approx \beta R_E$$

We set up our analysis to find r_{in} by remembering the test conditions we use for r_{in} . We set R_S to zero so it doesn't add to the r_{in} that we calculate, and we set R_L to an appropriate value so that any feedback effects in our amplifier get captured by r_{in} . Because R_L would be connected between v_{out} and ground, it just falls in parallel with our $r_o || R_E$ resistor from the previous page.

Because this model is more complex than the common emitter, we can find the Thevenin resistance that represents r_{in} just by calculating equivalent resistances. The dependent source means we need to apply a test source. We've opted to use an input test current to find r_{in} because it happens to be easier. Remember that you have the freedom to use either input test currents or input test voltages.

Given this setup, I'd like you to pause the video and try to find r_{in} . You might thrash with the algebra a bit, and that's perfectly normal when you're getting used to small signal model analysis.

CLICK First we notice that our g_m control variable, v_{be} , is equal to $i_{in}r_{\pi}$. That's super handy because it means we can sub in expressions for our dependent source current in terms of our input. Finding your dependent source control variable as soon as possible is always a good idea.

CLICK We want to calculate the output node voltage because we can add it to v_{be} to find v_{in} . It's given by the sum of the g_m current and the r_{pi} current being driven through the resistor to ground.

CLICK We know the g_m current is given by $g_m \cdot v_{be}$, and v_{be} is given by $i_{in} \cdot r_{pi}$, so substituting both of those relationships in here and factoring out i_{in} gives us this expression.

CLICK Great, we know v_{in} is equal to $v_{out} + v_{be}$,


CLICK and we have expressions for each of those voltages we can substitute here.

CLICK and we finally divide i_{in} off the right side to find that r_{in} is equal to $r_{pi} + (\beta + 1)(r_o \parallel R_E \parallel R_L)$. That's a very good expression for r_{in} , but if you're in lab and don't want to memorize the whole thing then you can use the very quick and dirty approximation that r_{in} is about $\beta \cdot R_E$. This is a great expression for doing math in your head, which I recommend, but you'll want to use the more exact expression for matching to simulations and measurements.

Here's an expression and a super-abbreviated expression ...

Emitter Follower a_v

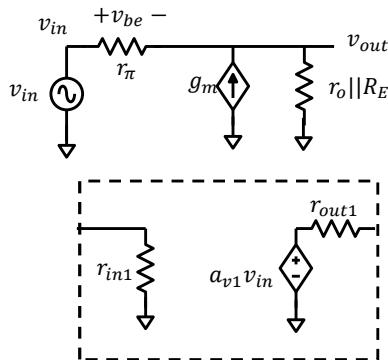- Set $R_S = 0, R_L = \infty$
- Must use test voltage



$$\begin{aligned}
 v_{out} &= (i_{in} + i_{gm})(R_E || r_o) \\
 &= i_{in}(1 + \beta)(R_E || r_o) \\
 &= \frac{v_{in}}{r_{in}}(1 + \beta)(R_E || r_o) \\
 a_v &= \frac{(\beta + 1)(R_E || r_o)}{r_{\pi} + (\beta + 1)(R_E || r_o)} \approx 1
 \end{aligned}$$

This makes sense because $v_E = v_B - V_{BEON}$

Now we're going to find the voltage gain of the emitter follower. We recall that we calculate voltage gain as small signal v_{out} over small signal v_{in} with zero source resistance and infinite load resistance. We set the resistances that way so that we're not measuring either the source or load divider by accident. I've set that up in the small signal model below, note that the resistor from v_{out} to ground has gone back to $r_o || R_E$ because we removed the load. Pause the video and try to find the gain of this amplifier.

CLICK OK, we can start by finding an expression for v_{out} . This one ought to look familiar from last slide: we know the current through r_{π} and the current through g_m have to go to ground through the $r_o || R_E$ resistance, which creates the output voltage.

CLICK A little factoring and recalling that v_{be} is equal to $i_{in} * r_{\pi}$ and β is $g_m * r_{\pi}$ gets us to this expression. However, we've got a problem, we don't know i_{in} like we did when we had a test current source.

CLICK So we're going to play a cheeky trick. We know that this amplifier can be effectively represented by its small signal model, and that r_{in} describes the relationship between v_{in} applied to the base and current into the base.

CLICK So we can just say that i_{in} is equal to v_{in} / r_{in} from the previous slide. This is fun,

we've jumped back and forth between our amplifier model and our transistor model to figure out the current into the base. However, I've also seen students get tripped up because this trick only works because of our silly biasing. We needed the current through r_{pi} (into the base) to plug into this second expression, and I've seen people get confused and use a current through a bias network in this step instead. So this is another reminder that we find our amplifier parameters assuming silly voltage source biasing, and you need to modify these expressions to account for bias networks.


CLICK Subbing in our expression from the previous page, we find that the voltage gain is given by $(\beta+1)r_{e} \parallel r_o / (\beta+1)r_{e} \parallel r_o + r_{pi}$. If βr_{e} is bigger than r_{pi} , then this gain is quite close to one, which is the quick and dirty in the lab approximation for emitter follower gain.

CLICK The gain of one makes particular sense with emitter followers because the total signal relation between input and output voltages in an emitter follower is that v_E is just a V_{BEON} drop below v_B . If we assume V_{BEON} is constant, then plotting v_E vs. v_B has a slope of one. If the total signal relationship has a gain of about one, the small signal relationship has to have that behavior too.

Careful with this trick! This is r_{in} looking into a base

Emitter Follower r_{out}

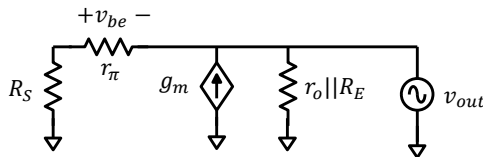- Set $R_L = \infty$, R_S to proper value
- Test v_{out} happens to be easier than i_{out}



$$i_{out} = \frac{v_{out}}{r_o} + \frac{v_{out}}{R_E} + g_m \frac{r_\pi}{R_S + r_\pi} v_{out} + \frac{v_{out}}{R_\pi + R_S}$$

$$r_{out} = \frac{1}{\frac{1}{r_o} + \frac{1}{R_E} + \frac{g_m r_\pi + 1}{R_S + r_\pi}}$$

$$r_{out} = r_o \parallel R_E \parallel \left(\frac{R_S + r_\pi}{\beta + 1} \right) \approx \frac{1}{g_m} + \frac{R_S}{\beta}$$

$1/g_m$ looks like a resistance because we directly control v_{be} .

11

Finally, we're going to find r_{out} of the emitter follower. Our r_{out} test conditions are an infinite load resistance, so it doesn't steal any current from our output, and an R_S that is normal for the amplifier. We're choosing to use a test voltage source for this analysis because it makes our life easier. Pause the video and try to find r_{out} .

CLICK We start by writing that i_{out} is the sum of current in a bunch of parallel branches: resistive current in the r_o , R_E and R_S+r_π branches, and a g_m current that is controlled by a voltage divider between r_π and R_S . We played a few tricks here. First we wanted the voltage on the top resistor in the voltage divider, which means r_π is on top. Second, v_{be} is activated in a negative direction when v_{out} increases, but that also causes the g_m source to inject current to enter the v_{out} node. We can switch the signs on v_{be} and the direction of the arrow on g_m and wind up with the same result. This has the effect of just cancelling a few negative signs in the g_m term.

CLICK We factor out v_{out} and divide through, then invert the equation to find r_{out} . Note that I merged the two terms with R_S+r_π in their denominators. Not also that r_{out} looks like the inverse of a bunch of inverse resistances.

CLICK So that means we can rewrite r_{out} as a parallel combination of r_o , R_E and this weird pseudo-resistance that is $(R_S+r_\pi)/(\beta+1)$. We can make a lab-worthy approximation for

this of $1/g_m + R_S/\beta$, by assuming the pseudo-resistance term is the smallest in our equation, saying β is pretty close to $\beta + 1$, splitting up the numerator, and remembering β is equal to $g_m \cdot r_{\pi}$. This is often shortened further to r_{out} being equal to $1/g_m$, but don't forget about the effect of R_S/β if your source resistance is big or your r_{out} constant is tight.

CLICK One fun note is that $1/g_m$ is showing up here as a resistance. At first glance, that's cute because the units are right. At second glance, it makes even more sense: we're moving v_{out} up and down, which directly affects the control variable for g_m . In response, g_m is injecting a linear amount current into the out node. A resistor is an element that has a linear current-voltage relationship to changes in one node, so the arrangement of the control variable here makes g_m behave like a resistor. That means any time we wiggle an emitter around, we should expect to see an impedance that looks something like $1/g_m$.

That last fact implies that we'll wiggle emitters around in other circuits, which is true. As a result, it can help to remember how we solved this particular circuit to re-apply it in the future. The same is true of the emitter follower input resistance. I call these common dependent source and resistor arrangements small signal patterns, and we're going to meditate on them for a bit in future videos.

Summary

- Emitter followers are good voltage buffers: high r_{in} , low r_{out} , $a_v \approx 1$

- Emitter follower amplifier parameters

$$r_{in} = r_{\pi} + (\beta + 1)(r_o \parallel R_E \parallel R_L) \approx \beta R_E$$

$$r_{out} = r_o \parallel R_E \parallel \left(\frac{1}{g_m} + \frac{R_S}{\beta} \right) \approx \frac{1}{g_m} + \frac{R_S}{\beta}$$

$$a_v = \frac{(\beta + 1)(R_E \parallel r_o)}{r_{\pi} + (\beta + 1)(R_E \parallel r_o)} \approx 1$$

- Saw two small-signal circuit solving patterns that will show up again.