


E151 Lecture 23 – Op-Amp Design

Matthew Spencer
Harvey Mudd College
ENGR151

1

We Can Make an Op-Amp from Our Pieces

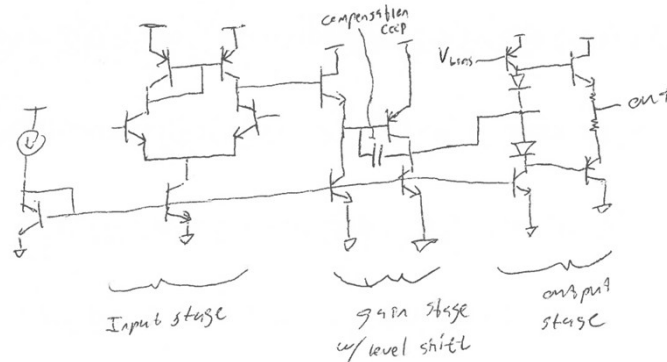- Already have differential input and 0 output impedance (for large v_O)
- Need infinite gain and DC coupling (use level shifts to achieve that)
- Input common mode range (b/c feedback shrinks DM, rail-to-rail)
- Input bias current
- Input offset voltage
- Output swing (rail-to-rail)
- Mirror biasing is handy




2

Compensation Capacitance and Slew Rate

- Op-amps always in feedback (why we care about input CM range)
- If you hear feedback, always think stability → CC makes look 1st order
- But big caps limit dV/dt at op-amp output, called slew rate

~ slewing behavior

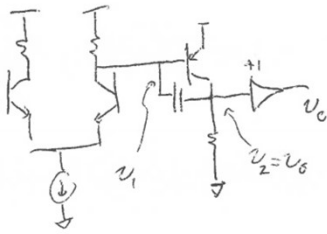

~ straight lines (ramp)
except where slope
small

$$\frac{dv_o}{dt} = \frac{dv_2}{dt} \approx v_1 + CQ \quad \text{SO}$$

$$\begin{aligned} SR_{\text{output}} &= I_{\text{out}}/C_L \\ \text{OR} \\ SR_{CC, \text{mirror}} &= I_{\text{tail}}/C_C \\ \text{OR} \\ SR_{CC, \text{resistor}} &= I_{\text{tail}}/2C_C \end{aligned}$$