

E157 Lecture 8 Day Plan

Any questions before quiz

Quiz + Team Quiz + Talk through solution

Design a L-match checking against <https://www.smithchart.net>

- 5Grad/s , $Rl=10\text{ ohm}$
- $Q_{\text{desired}} = \text{sqrt}(3)$
- $L_{\text{series}} = 4\text{nH}$, $C_{\text{shunt}} = 8\text{pF}$

Lab practice discussion – designing a match empirically.

Parasitics discussion – amplifiers have shunt C, and vias have series L

Matching networks with transmission lines – impedance cancellation, single stub

Tapped Capacitors, Tapped Inductors and Transformers

Design a T-match checking against <https://www.smithchart.net> – note compound Q=

Check-in, office hours