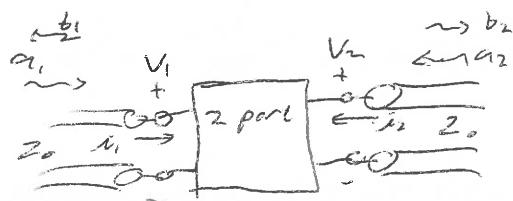


- Port I & V
 - Power flow
 - ↳ complex power
 - ↳ P_{in} resistor
 - ↳ 2 port
 - VNA operation
 - ↳ dir coupler
 - ↳ block
 - VNA practicalities
 - ↳ open worse than short
 - ↳ phase ...
 - ↳ checks 2nd
 - ↳ ref. plane

Talking about S-parameters

↳ type of 2 port parameters expressing how waves bounce off block box.

↳ contrast w/ Z-params ~ talk about voltages induced by currents



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = Z \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \text{vs.} \quad \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = S \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} / Z_{11} \quad \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} / Z_{11}$$

• measure by setting $I_2 = 0$
(terminate w/ open)

• measure by terminating
w/ Z_0 to kill b_1 or b_2

- ~ Want to:
 - figure out measurement techniques & interpretation
 - relate to circuit calculations we already knew
 - relate to power delivery

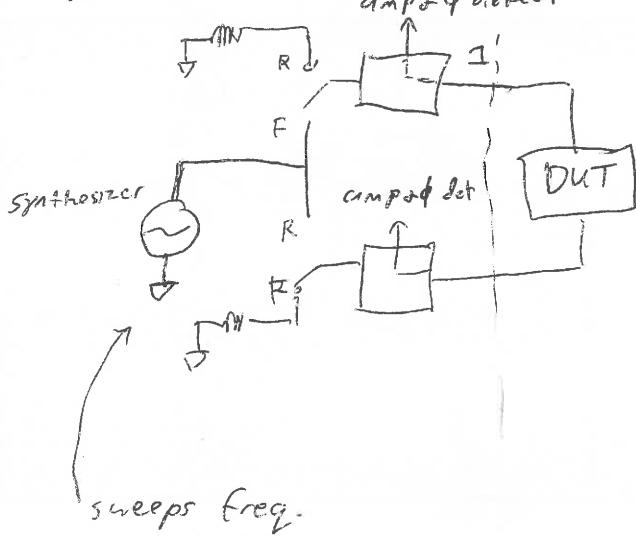To measure S-params we use a Vector Network Analyzer



- Relies on directional couplers
 - ↳ split waves into fwd & rev components, more later
 - ↳ observe reflected waves on one & fwd. waves on other for direct S-param measure

- VNA only takes good measurements when calibrated
- ↳ calibrate w/ cal. standards short, open, load, thru

↳ short
to find
ref. plane



$$S_{VNA} = \begin{bmatrix} e^{\jmath \beta Z_1} & \\ & e^{\jmath \beta Z_2} \end{bmatrix} S_{DUT}$$

↳ reference plane

- Need to define where $Z=0$ is, i.e.: measure Z_1 & Z_2


- O/w have a lot of excess phase: $\phi = \beta Z_1 = \frac{2\pi}{\lambda} Z_1 = \omega \cdot \frac{Z_1}{v}$

will see phase plot




arc parameterized
in co

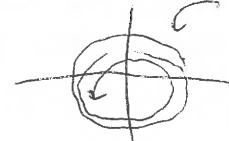You guys - what will Smith chart look like



- why not open? capacitance & radiation lead to worse results

- going on to PCB

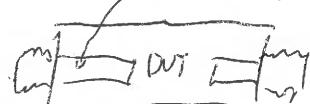

extra ϕ on this t. line

options: cal. in place

port extension

short sets $Z=0$ here

open & Load

re-reflection fwd. leakage

- source mismatch & directivity errors


- open is an independent reflection, load should be no reflection

thru


- frequency response of fixturing

- post cal checks

- short S11 or S22

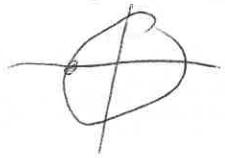

- open S11 or S22

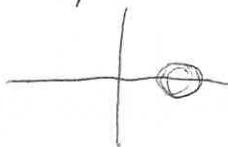

- thru




- Not as good w/o shunt cap



• look @ delcar too, nearly 0

• Hard to nap over a few 100 MHz

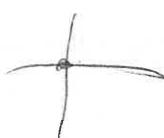

- control of port 2 connector protector

- only screw in turtle-neck so you don't break internal pins


- Debugging ~ check cables & connectors. Wiggle to find bad ones
~ sanity check -- am I seeing a signal?

- when to recalibrate → change in sweep of ω
→ change in fixturing

Notes on PCB parasitics - via has inductance ~1 nH in series to ground

- pad has cap

- in shunt to ground

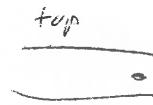

- Extract w/ VNA by making resonant

↳ @ resonance series → short & ff → open

↳ big phase change, magnitude changes, but reflects @ res and off res.

Can express port $I \& V$ in terms of S parameters

→ can invert to get screwy definition of a & b , beware!

$$V_1 = V_{21} + V_{r1} \quad I_1 = (V_{11} - V_{21})/Z_0$$

$$= \sqrt{Z_0} (a_1 + b_1)$$

$$= \frac{a_1 - b_1}{\sqrt{Z_0}}$$


$$a_1 = \frac{V_1 + Z_0 I_1}{\sqrt{Z_0}}$$

$$b_1 = \frac{V_1 - Z_0 I_1}{\sqrt{Z_0}}$$

~~Analytic power~~

• Relating S-params to ckt

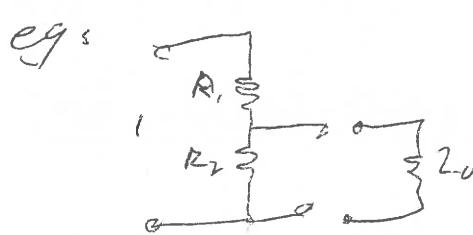- S_{11} & S_{22} easy enough to calculate ~ reflection coeff of load on port



$$S_{11} = \frac{R_1 + R_2 \parallel Z_0 - Z_0}{R_1 + R_2 \parallel Z_0 + Z_0} \quad \text{and} \quad S_{22} = \frac{R_2 \parallel (R_1 + Z_0) - Z_0}{R_2 \parallel (R_1 + Z_0) + Z_0}$$

- Get S_{21} & S_{12} from port voltage def¹ of a, b, g

- S_{21} & S_{12} a bit more involved, but can be calculated from Z params

$$S = (Z - Z_0 I)(Z + Z_0 I)^{-1} \quad \leftarrow \text{matrix form of } \Gamma$$

$$Z = (I - S)^{-1}(I + S)Z_0$$

↳ formulas for $S_{21} = \frac{2Z_0 Z_{21}}{(Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12} Z_{21}}$

$\underbrace{\qquad\qquad\qquad}_{\text{call this } \Delta}$

$$S_{12} = \frac{2Z_0 Z_{12}}{\Delta}$$

• Complex power

$\hookrightarrow P = \operatorname{Re}\{V I^*\}$ b/c we're representing sinusoidal V as $V e^{j\omega t}$


↳ Need voltage & current in phase to have power eg: $Z_{load} = j0$

• Power in wave is $\frac{1}{2}|a|^2$ & power into 2 port is $\frac{1}{2}|a|^2 - \frac{1}{2}|b|^2 = \operatorname{Re}\{V I^*\}$

$$\left\{ \frac{|V_{11}|^2}{2Z_0} \right.$$

• Lossy, 2 ports won't send all their power out in b_2 \Rightarrow Hermitian matrices

eg: 1 port

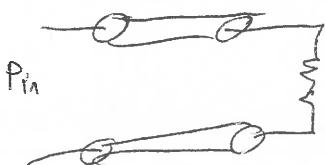

$$\text{Preflected} = |\Gamma|^2 P_{in}$$

$$P_{load} = (1 - |\Gamma|^2) P_{in}$$

- More to come re: S_{11}

Filters next time b/c last 3