

Problem Set Extra

April 17, 2015

1

Consider an amplifier with a gain of A , and two poles at frequencies p_1 and p_2 . Express the crossover frequency of the amplifier as ω_c . $p_1 < p_2$.

1.1

What is the phase margin of this amplifier under the following conditions: $p_2 > 10\omega_c$, $\omega_c < p_2 < 10\omega_c$, $p_2 = \omega_c$, $0.1\omega_c < p_2 < \omega_c$.

1.2

What is the closed loop bandwidth of the amplifier with a feedback factor of f and $p_2 \ll \omega_c$.

2

Make a block diagram for the transimpedance amplifier from PS2. Find the closed loop gain using black's formula. Does it agree with the calculations from PS2.

3

Draw an op-amp with a PMOS input stage. You may use NMOS devices, PMOS devices and one current source.

4

An op-amp compensation network is made of a series RC circuit instead of a capacitor.

4.1

What is the transfer function of the feedback network?

4.2

What is the compensated transfer function of the op-amp?

5

Each stage of an op-amp generates noise at its output, and we can use our usual analog tradeoff (increase C , decrease R , increase g_m) to reduce the noise from each stage. If each stage has the same relationship between noise and current, how should the current in the op-amp be distributed to minimize power at a given noise level and bandwidth?