

# Problem Set 4

February 13, 2015

## 1

### 1.1

Two devices of width  $W$  and length  $L$  are connected in parallel as pictured in Figure 1a. Calculate the Id-Vg characteristic for the pair of devices. Could they be replaced by a single device?

### 1.2

Two devices of width  $W$  and length  $L$  are connected in series as pictured in Figure 1b. Calculate the Id-Vg characteristic for this pair of devices. Could they be replaced by a single device?

## 2

### 2.1

A NAND2 gate is pictured in Figure 2. Calculate the leakage current in the gate for each value of  $A$  and  $B$ . The gate is sized to match the pull-down delay of an inverter with width  $W$ .

### 2.2

If inputs  $A$  and  $B$  each have a 50% chance of being one each cycle, what is the average leakage energy per cycle through the gate? The logic is being run at a frequency  $f_s$ .

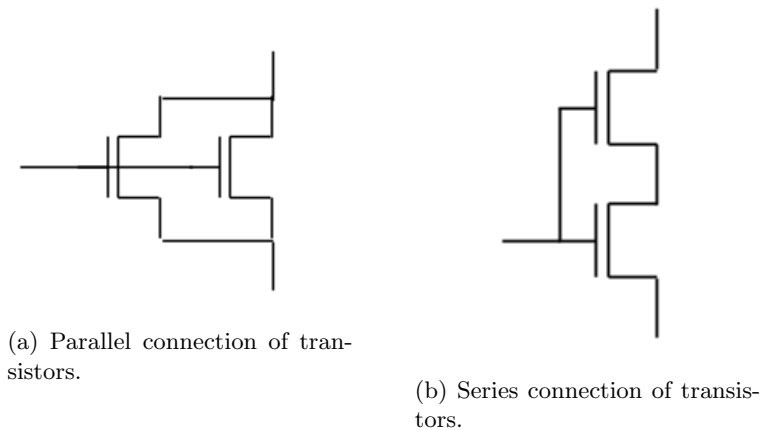


Figure 1: Interesting transistor connections.

 


Figure 2: A NAND2 gate.

### 3

#### 3.1

Draw the band diagram for a NPN transistor in all three modes of operation and indicate the qualitative directions and magnitudes of carrier flow. As background, npn transistors consist of two back-to-back  $pn$  junctions with the  $p$  region being very small. It is doped as  $n_+$ ,  $p$ ,  $n$ .

#### 3.2

Repeat for a PNP transistor.

### 4

#### 4.1

Find an expression for electron concentration and hole concentration as a function of doping by using the law of mass action for electrons and holes ( $np = n_i^2$ ) and the law of charge conservation for electrons and holes.

#### 4.2

What do these expressions simplify to if  $N_A \gg N_D$ .