

**RISC-V**

**System-on-Chip Design**

**Harris, Stine, Thompson, & Harris**

# **Chapter 15:**

# **Multiply & Divide**

# Chapter 15 :: Topics

## **Extensions: M (Multiply & Divide)**

12.1 Principles

12.2 RISC-V Practices: M-extension

12.3 Test Plan

12.4 Wally Implementation

# Principles

- **Signed/Unsigned Multiplication**
- **Carry-Save Adders**
- **Multiplication**
  - Array Multiplier
  - Signed Multiplication
  - Booth Encoding
  - Multiplier Synthesis
- **Division**
  - Radix-2 Division
  - Signed Division

# Intro to Multiplication

- Multiplication of **XLEN** operands produces **2 XLEN** result.
- Unlike addition, multiplication **result** differs depending on operand **signs**.

# Signed / Unsigned Multiplication

## Example: XLEN = 4

- $1111 \times 1111$
- Signed x Signed:
  - $1111 = -1$
  - $-1 \times -1 = 1$ :         $0000$  **0001**
- Unsigned x Unsigned:
  - $1111 = 15$
  - $15 \times 15 = 225$ :     $1110$  **0001**
- Signed x Unsigned:
  - $1111 = -1, 1111 = 15$
  - $-1 \times 15 = -15$ :     $1111$  **0001**

The bottom XLEN (4) bits are the same independent of sign.

# RISC-V Multiply Instructions

- **Lower XLEN bits:** `mul`
- **Upper XLEN bits:**
  - Signed/Signed: `mulh`
  - Unsigned: `mulhu`
  - Signed/Unsigned: `mulhsu`

# Chapter 15: Multiply & Divide


## **Adders**

# Carry-Save Adders (CSAs)

- **Used to add multiple words** (i.e., partial products in multipliers)


- **CSA operation:**

 - **3 inputs:**  $X$ ,  $Y$ ,  $Z$  (operands)
- **2 outputs:**  $S$  (sum),  $C$  (carry out)
- **Function:**  $\{C, S\} = X + Y + Z$ 
  - Carry out ( $C$ ) has double the weight of the sum ( $S$ )
  - To produce the actual sum, add  $2C + S$  using regular carry-propagate adder (CPA)
- Also called 3:2 adder






# N-bit CSA

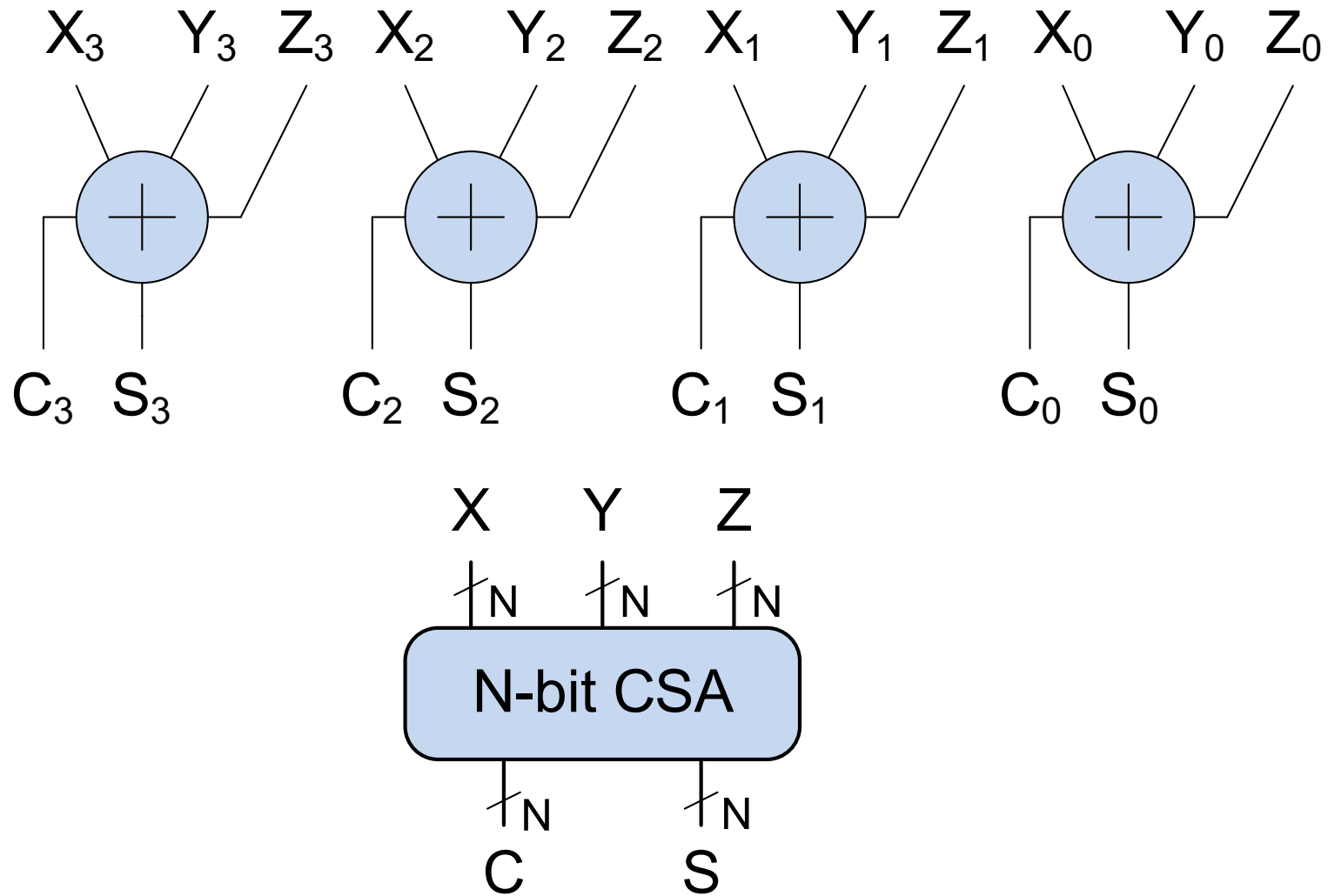


# Addition of Four 4-bit Operands

## CSA (Carry-Save Adder)

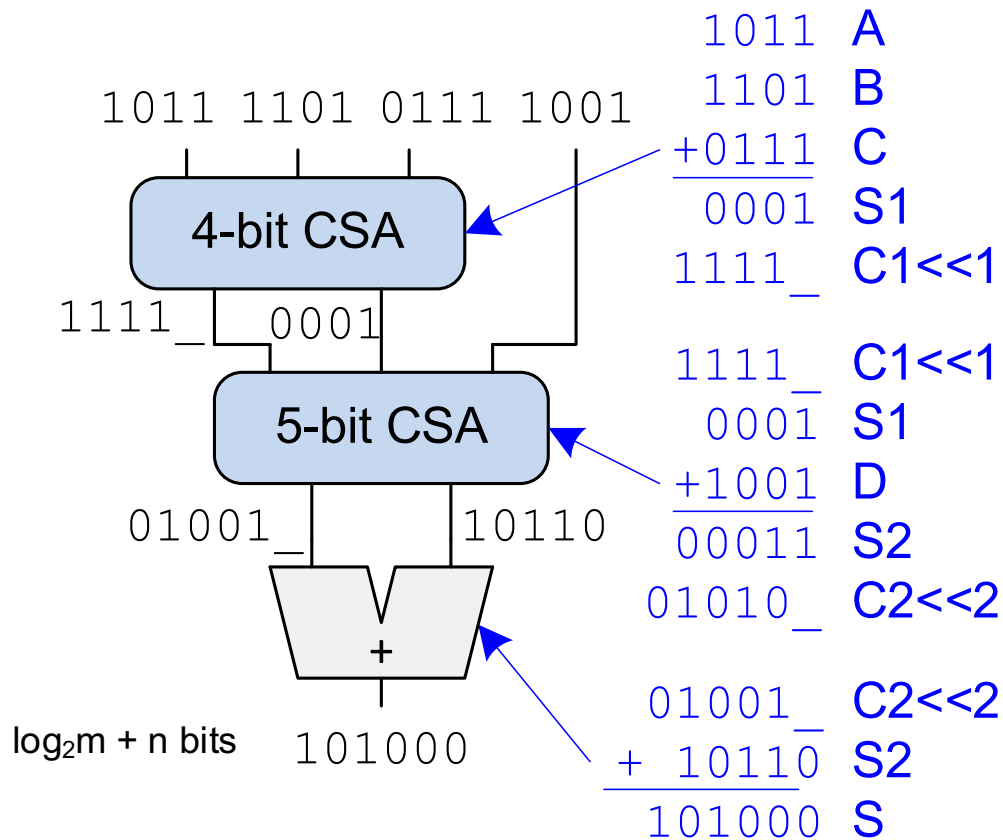


## CPA (Carry-Propagate Adder)

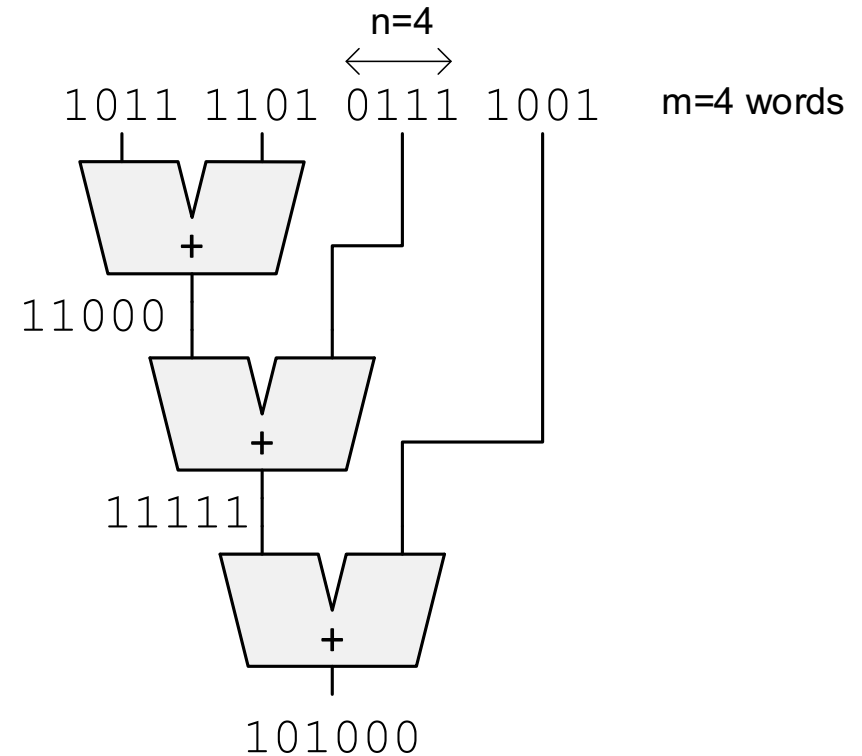


## Addition of Four 4-bit Operands

## CSA

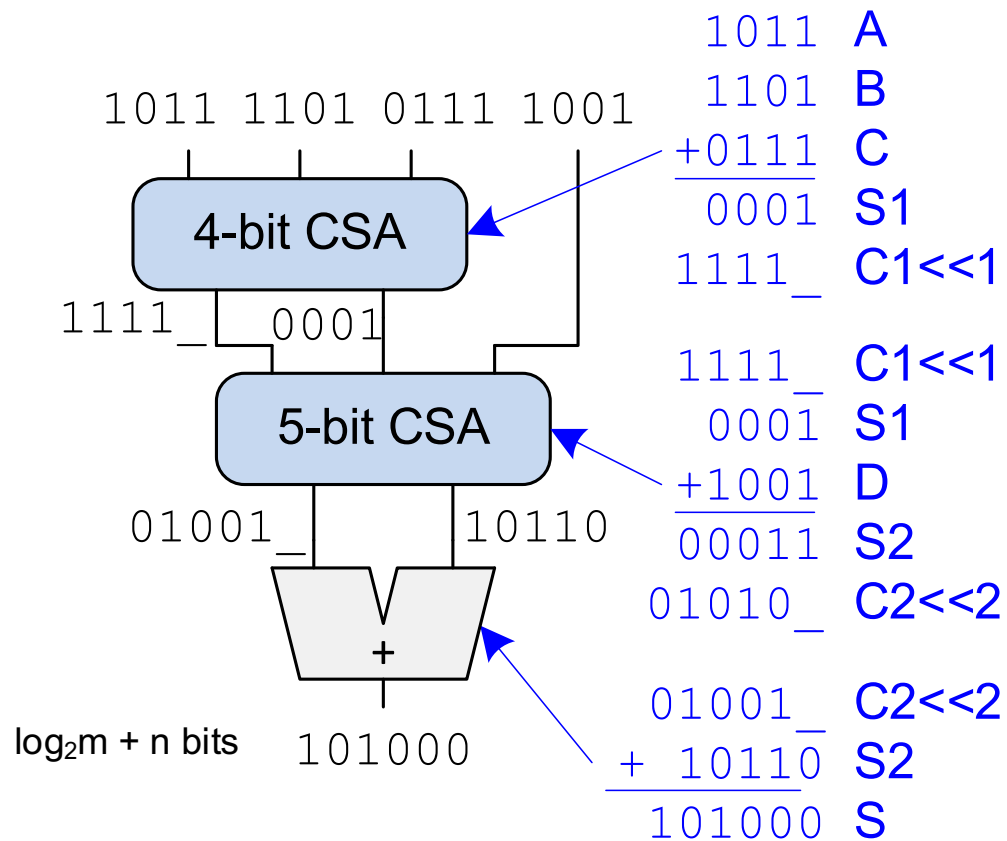

# CSA Implementation

 

# Chapter 15: Multiply & Divide

## **Multipliers**

# Multiplication

$$P = Y \times X$$

- **Y**:  $M$ -bit Multiplicand  $\{y_{M-1}, y_{M-2}, \dots, y_1, y_0\}$
- **X**:  $N$ -bit Multiplier  $\{x_{M-1}, x_{M-2}, \dots, x_1, x_0\}$
- **P**:  $M+N$ -bit product

$$P = \left( \sum_{j=0}^{M-1} y_j 2^j \right) \left( \sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

# Multiplication

$$P = Y \times X$$

- ***Y***:  $M$ -bit Multiplicand  $\{y_{M-1}, y_{M-2}, \dots, y_1, y_0\}$
- ***X***:  $N$ -bit Multiplier  $\{x_{M-1}, x_{M-2}, \dots, x_1, x_0\}$
- ***P***:  $M+N$ -bit product

## Example: 4x4 unsigned multiplication

				$y_3$	$y_2$	$y_1$	$y_0$	
				$x_3$	$x_2$	$x_1$	$x_0$	
				$x_0y_3$	$x_0y_2$	$x_0y_1$	$x_0y_0$	[
			$x_1y_3$	$x_1y_2$	$x_1y_1$	$x_1y_0$		
		$x_2y_3$	$x_2y_2$	$x_2y_1$	$x_2y_0$			
	$x_3y_3$	$x_3y_2$	$x_3y_1$	$x_3y_0$				
$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$	

multiplicand

multiplier


partial products

product

$1011$	$:$	$11_{10}$
$\times 0101$	$:$	$5_{10}$
$1011$ $0000$ $1011$ $+ 0000$		
$0110111$	$:$	$55_{10}$
 
# Multiplication: Dot Notation

**Dot notation** is useful for larger multiplications.




**Example: 16 x 16 unsigned multiplier**

## Chapter 15: Multiply & Divide


# **Array Multiplier**



# Array Multiplier

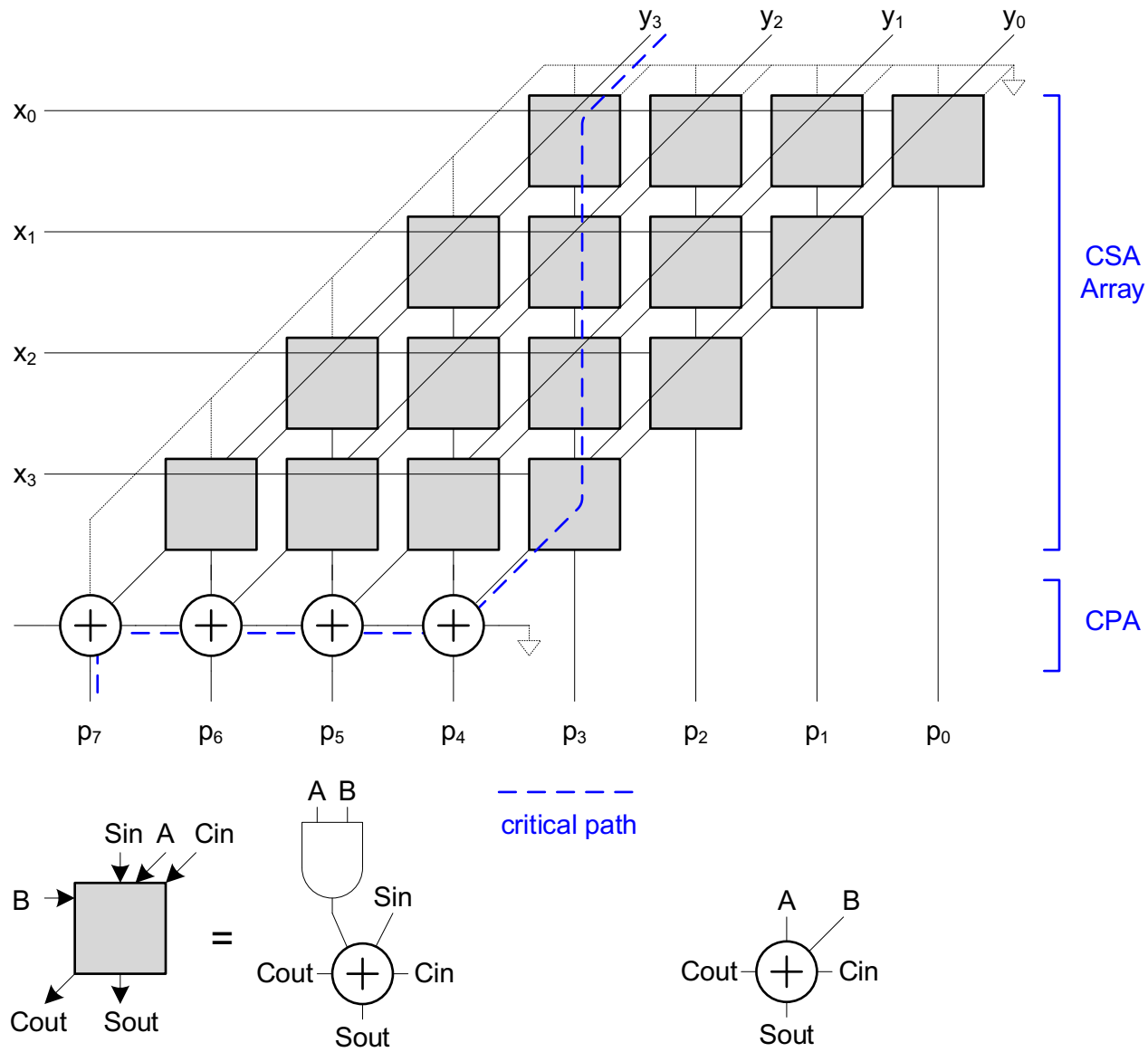

# Array Multiplier: Square Format

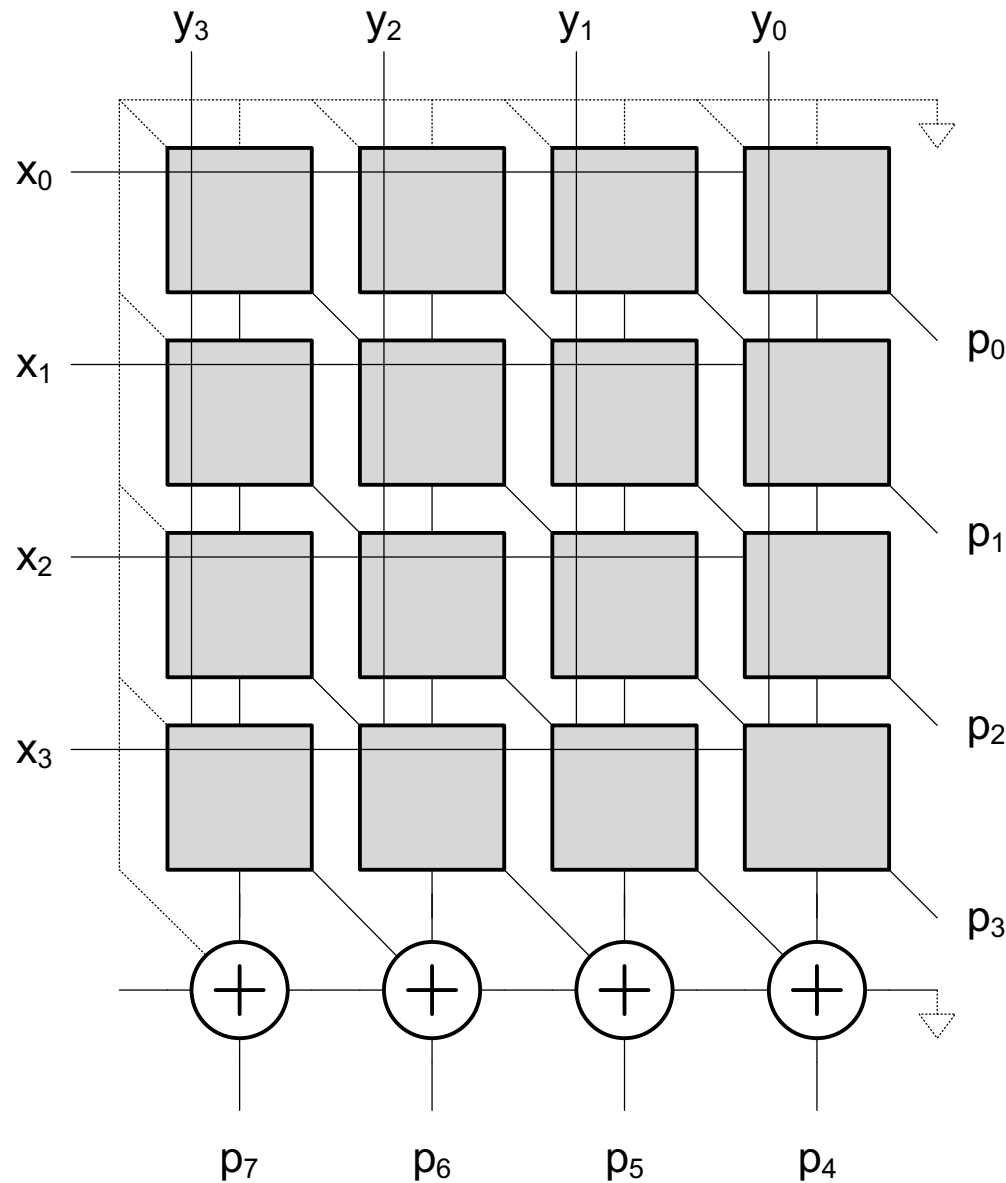

Square format fits  
better on a chip


## Chapter 15: Multiply & Divide

# **Signed Multiplication**

# Signed Multiplication

Two of the partial products may be negative

- when  $x_{M-1}$  or  $x_{N-1}$  are 1 (not 0)
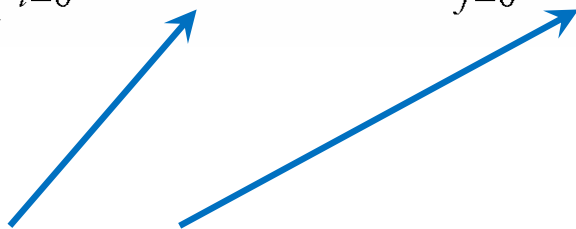
$$P = \left( -y_{M-1} 2^{M-1} + \sum_{j=0}^{M-2} y_j 2^j \right) \left( -x_{N-1} 2^{N-1} + \sum_{i=0}^{N-2} x_i 2^i \right)$$
$$= \sum_{i=0}^{N-2} \sum_{j=0}^{M-2} x_i y_j 2^{i+j} + x_{N-1} y_{M-1} 2^{M+N-2} - \left( \sum_{i=0}^{N-2} x_i y_{M-1} 2^{i+M-1} + \sum_{j=0}^{M-2} x_{N-1} y_j 2^{j+N-1} \right)$$


**Partial products  
may be negative.**

# Signed Multiplication

[illegible]

$$= \sum_{i=0}^{N-2} \sum_{j=0}^{M-2} x_i y_j 2^{i+j} + x_{N-1} y_{M-1} 2^{M+N-2} - \left( \sum_{i=0}^{N-2} x_i y_{M-1} 2^{i+M-1} + \sum_{j=0}^{M-2} x_{N-1} y_j 2^{j+N-1} \right)$$

# Simplified Partial Products

$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$
$\overline{x_5}y_0$	$x_0y_4$	$x_0y_3$	$x_0y_2$	$x_0y_1$	$x_0y_0$
$\overline{x_5}y_1$	$x_1y_4$	$x_1y_3$	$x_1y_2$	$x_1y_1$	$x_1y_0$
$\overline{x_5}y_2$	$x_2y_4$	$x_2y_3$	$x_2y_2$	$x_2y_1$	$x_2y_0$
$\overline{x_5}y_3$	$x_3y_4$	$x_3y_3$	$x_3y_2$	$x_3y_1$	$x_3y_0$
$\overline{x_5}y_4$	$x_4y_4$	$x_4y_3$	$x_4y_2$	$x_4y_1$	$x_4y_0$

The diagram illustrates the carry propagation in a 6-bit ripple-carry adder. The carry chain starts at  $p_{11}$  (1) and propagates through  $p_{10}$  (1),  $p_9$  (1),  $p_8$  (1),  $p_7$  (1),  $p_6$  (1),  $p_5$  (1),  $p_4$  (1),  $p_3$  (1),  $p_2$  (1),  $p_1$  (1), and  $p_0$  (1). The carry propagation function is defined by the truth table above. The carry chain is shown as a sequence of logic gates (AND and OR) that propagate the carry from  $p_{11}$  to  $p_0$ . The carry chain is shown as a sequence of logic gates (AND and OR) that propagate the carry from  $p_{11}$  to  $p_0$ .

# Simplified Partial Products, Cont'd

The diagram illustrates the multiplication of two 6-bit numbers,  $x_5x_4x_3x_2x_1x_0$  and  $y_5y_4y_3y_2y_1y_0$ . The partial products are arranged in a triangular fashion, with the most significant bit of each product shifted to the left. The partial products are:

- $x_5y_0$  (blue)
- $x_4y_0$  (black)
- $x_3y_0$  (black)
- $x_2y_0$  (black)
- $x_1y_0$  (black)
- $x_0y_0$  (black)
- $x_5y_1$  (blue)
- $x_4y_1$  (black)
- $x_3y_1$  (black)
- $x_2y_1$  (black)
- $x_1y_1$  (black)
- $x_0y_1$  (black)
- $x_5y_2$  (blue)
- $x_4y_2$  (black)
- $x_3y_2$  (black)
- $x_2y_2$  (black)
- $x_1y_2$  (black)
- $x_0y_2$  (black)
- $x_5y_3$  (blue)
- $x_4y_3$  (black)
- $x_3y_3$  (black)
- $x_2y_3$  (black)
- $x_1y_3$  (black)
- $x_0y_3$  (black)
- $x_5y_4$  (blue)
- $x_4y_4$  (black)
- $x_3y_4$  (black)
- $x_2y_4$  (black)
- $x_1y_4$  (black)
- $x_0y_4$  (black)
- $x_5y_5$  (black)
- $x_4y_5$  (black)
- $x_3y_5$  (black)
- $x_2y_5$  (black)
- $x_1y_5$  (black)
- $x_0y_5$  (black)

The partial products are summed to produce the final 12-bit result,  $p_{11}p_{10}p_9p_8p_7p_6p_5p_4p_3p_2p_1p_0$ . The sum is calculated as:

$$32 + 16 + 8 + 4 + 4 = 64$$

The final result is shown in a red box, with the sum of the partial products calculated as 64.

## Simplified Partial Products, Cont'd

[illegible]



## Simplified Partial Products, Cont'd

The diagram illustrates the addition of two 1024-bit numbers to produce a 2048-bit result. The top part shows two 1024-bit numbers, each with a leading '1' in the 1024th bit position. These are added to produce a 2048-bit result, with the leading '1' in the 2048th bit position. The diagram uses a grid of bits to show the carry propagation from the 1024th bit to the 2048th bit.



	$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$	
1	$\overline{x_5 y_0}$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$
	$\overline{x_5 y_1}$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$
		$\overline{x_5 y_2}$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$
			$\overline{x_5 y_3}$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$
				$\overline{x_5 y_4}$	$x_4 y_4$	$x_4 y_3$
					$\overline{x_5 y_5}$	$x_5 y_5$

1024 + 1024 = 2048

# Simplified Partial Products, Cont'd

							$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
							$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$
						1	$\overline{x_5 y_0}$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$
					$\overline{x_5 y_1}$		$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$	
				$\overline{x_5 y_2}$	$x_2 y_4$		$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$		
			$\overline{x_5 y_3}$	$x_3 y_4$	$x_3 y_3$		$x_3 y_2$	$x_3 y_1$	$x_3 y_0$			
		$\overline{x_5 y_4}$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$		$x_4 y_1$	$x_4 y_0$				
1	$x_5 y_5$	$\overline{x_4 y_5}$	$\overline{x_3 y_5}$	$\overline{x_2 y_5}$	$\overline{x_1 y_5}$	$\overline{x_0 y_5}$						
$p_{11}$	$p_{10}$	$p_9$	$p_8$	$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$	

# Signed Multiplier

  

## Chapter 15: Multiply & Divide

# Booth Encoding

# Multiplication Radix

- **Radix 2:** one partial product for each bit
  - **Partial product:**
    - $x_i = 0$ :  $P = 0$
    - $x_i = 1$ :  $P = Y$
- **Radix 4:** one partial product for every 2 bits
  - **Partial products:**
    - $\{x_{2i+1}, x_{2i}\} = 00$ :  $P = 0$
    - $\{x_{2i+1}, x_{2i}\} = 01$ :  $P = Y$
    - $\{x_{2i+1}, x_{2i}\} = 10$ :  $P = 2Y$
    - $\{x_{2i+1}, x_{2i}\} = 11$ :  $P = 3Y$

But **3Y** is hard to produce.

# Booth Encoding

- **Radix 4:**

- **Partial products:**

- $\{x_{2i+1}, x_{2i}\} = 00:$   $P = 0$
    - $\{x_{2i+1}, x_{2i}\} = 01:$   $P = Y$
    - $\{x_{2i+1}, x_{2i}\} = 10:$   $P = 2Y = -2Y (+ 4Y)$
    - $\{x_{2i+1}, x_{2i}\} = 11:$   $P = 3Y = -Y (+ 4Y)$

**Instead:**

**Subtract:**  $-2Y$  and  $-Y$

Then, next pair of bits adds  $4Y$

# Booth Encoding

- **Radix 4:**

- **Partial products:**

- $\{x_{2i+1}, x_{2i}\} = 00:$   $P =$  **0**
    - $\{x_{2i+1}, x_{2i}\} = 01:$   $P =$   **$Y$**
    - $\{x_{2i+1}, x_{2i}\} = 10:$   $P =$   **$-2Y$**
    - $\{x_{2i+1}, x_{2i}\} = 11:$   $P =$   **$-Y$**

**Subtract:**  $-2Y$  and  $-Y$  (for 10 and 11 cases)

Then, next pair of bits adds  **$4Y$**

So, if msb of current pair is 1 ( $x_{2i+1} = 1$ ),  
then will add  **$4Y$**  to the next pair.

# Booth Encoding

- **Radix 4:**

- Partial products, considering **msb** of previous pair:

• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 00\mathbf{0}$ :	$P =$	<b>0</b>		
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 01\mathbf{0}$ :	$P =$	<b>Y</b>		
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 10\mathbf{0}$ :	$P =$	<b>-2Y</b>		
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 11\mathbf{0}$ :	$P =$	<b>-Y</b>		
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 00\mathbf{1}$ :	$P = Y +$	<b>0</b>	<b>=</b>	<b>Y</b>
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 01\mathbf{1}$ :	$P = Y +$	<b>Y</b>	<b>=</b>	<b>2Y</b>
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 10\mathbf{1}$ :	$P = Y +$	<b>-2Y</b>	<b>=</b>	<b>-Y</b>
• $\{x_{2i+1}, x_{2i}, x_{2i-1}\} = 11\mathbf{1}$ :	$P = Y +$	<b>-Y</b>	<b>=</b>	<b>0</b>

Adding **Y** in current pair is like adding **4Y** in previous pair (because of left shift by 2 bits)



# Booth Encoding

Inputs			Partial Products	Booth Selects		
$x_{2i+1}$	$x_{2i}$	$x_{2i-1}$	$PP_i$	$Single_i$	$Double_i$	$Neg_i$
0	0	0	0	0	0	0
0	1	0	$Y$	1	0	0
1	0	0	$-2Y$	0	1	1
1	1	0	$-Y$	1	0	1
0	0	1	$Y (= Y + 0)$	1	0	0
0	1	1	$2Y (= Y + Y)$	0	1	0
1	0	1	$-Y (= Y - 2Y)$	1	0	1
1	1	1	$0 (= Y - Y = -0)$	0	0	1


# Booth Encoding Example

$$100111 \times 011001 = 001111001111$$


$$(39 \times 25 = 975)$$

Sign


Extension

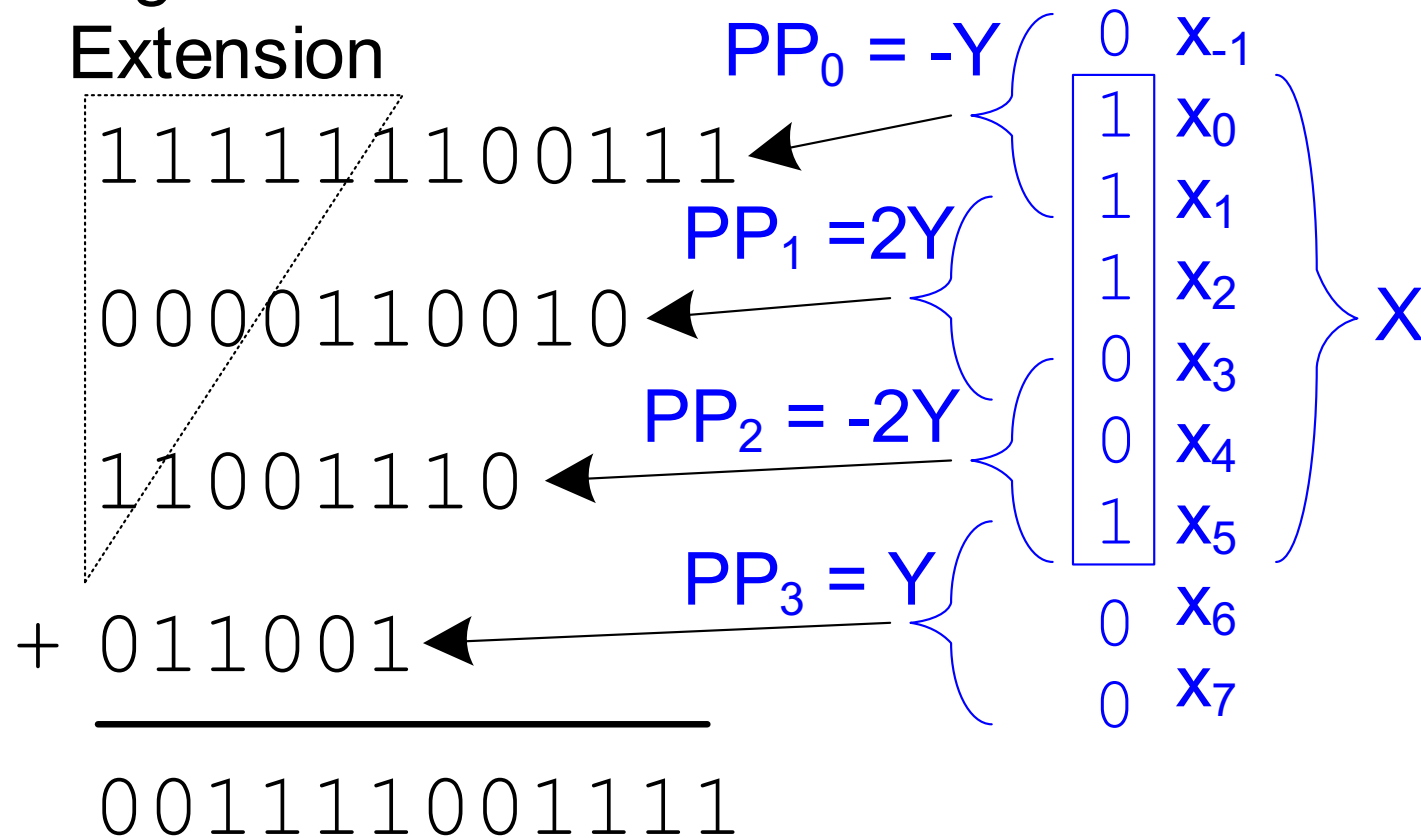


# Booth Encoding Hardware

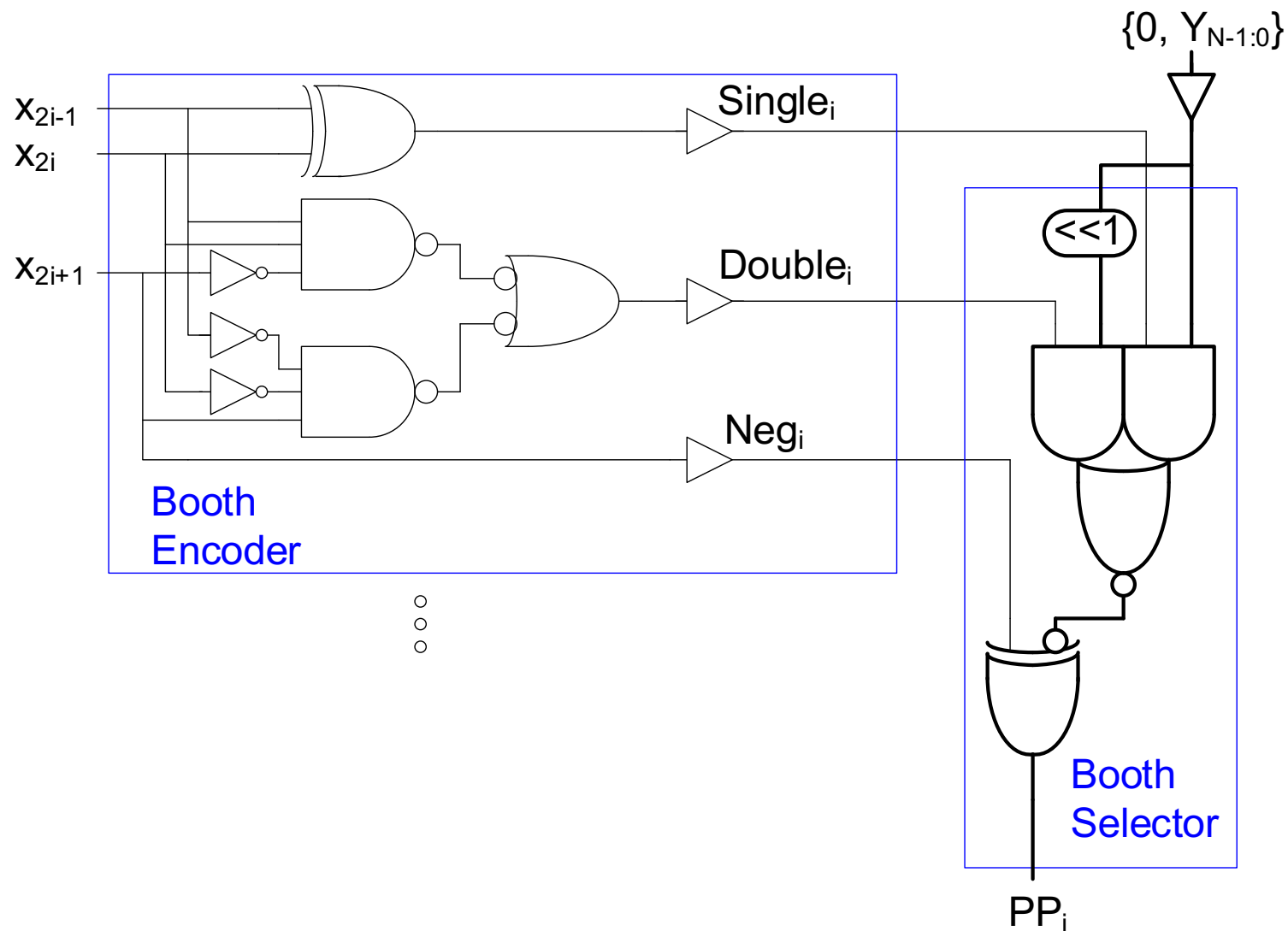

# Booth Encoding w/ Sign Extension

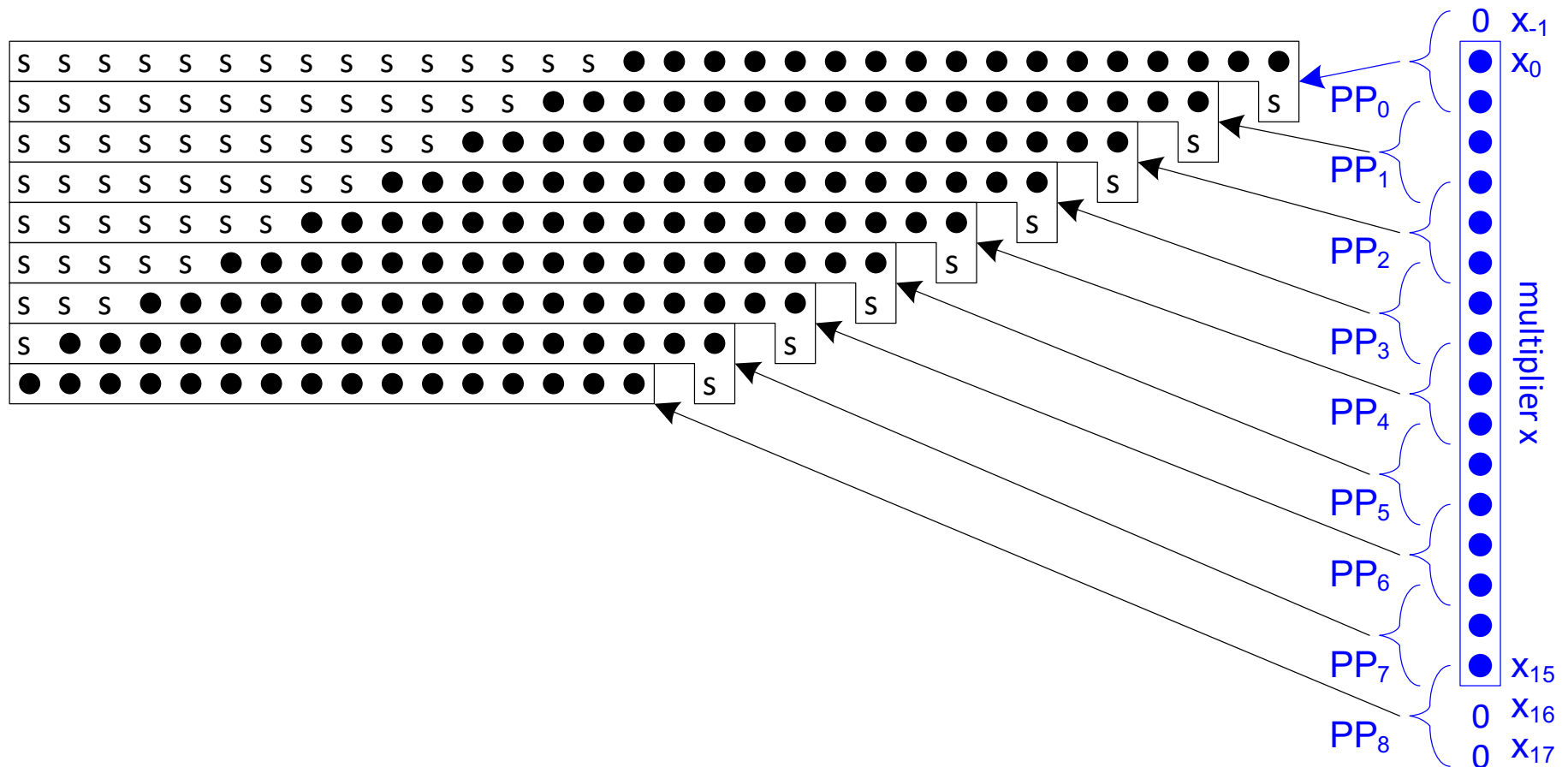

# Simplified Sign Extension

 

# Multiplier synthesis

```
assign p = x * y;
```

```
// Synthesis tool optimizes
```

# Chapter 15: Multiply & Divide

## **Division**

# Intro to Division

$$X/D = Q + \text{REM}/D$$

or

$$X = Q \times D + \text{REM}$$

- **Dividend:** X
- **Divisor:** Y
- **Quotient:** Q
- **Remainder:** REM (same sign as X)

$$Q = \sum_{i=0}^{N-1} q_i 2^{N-1-i} \quad X = \sum_{i=0}^{N-1} x_i 2^{N-1-i}$$



# Division Algorithm

$$Q = \sum_{i=0}^{N-1} q_i 2^{N-1-i} \quad X = \sum_{i=0}^{N-1} x_i 2^{N-1-i}$$

**For division:**

Using big-endian bit numbering (bit 0 is msb and bit  $N-1$  is lsb)

$W = 0$

for  $i = 0$  to  $N-1$

$W = \{W \ll 1, x_i\}$

$W' = W - D$

if ( $W' \geq 0$ )

$q_i = 1, W = W'$

else


$q_i = 0$

**At end of algorithm:**

Q = quotient

W = remainder

# Radix-2 Unsigned Integer Divider

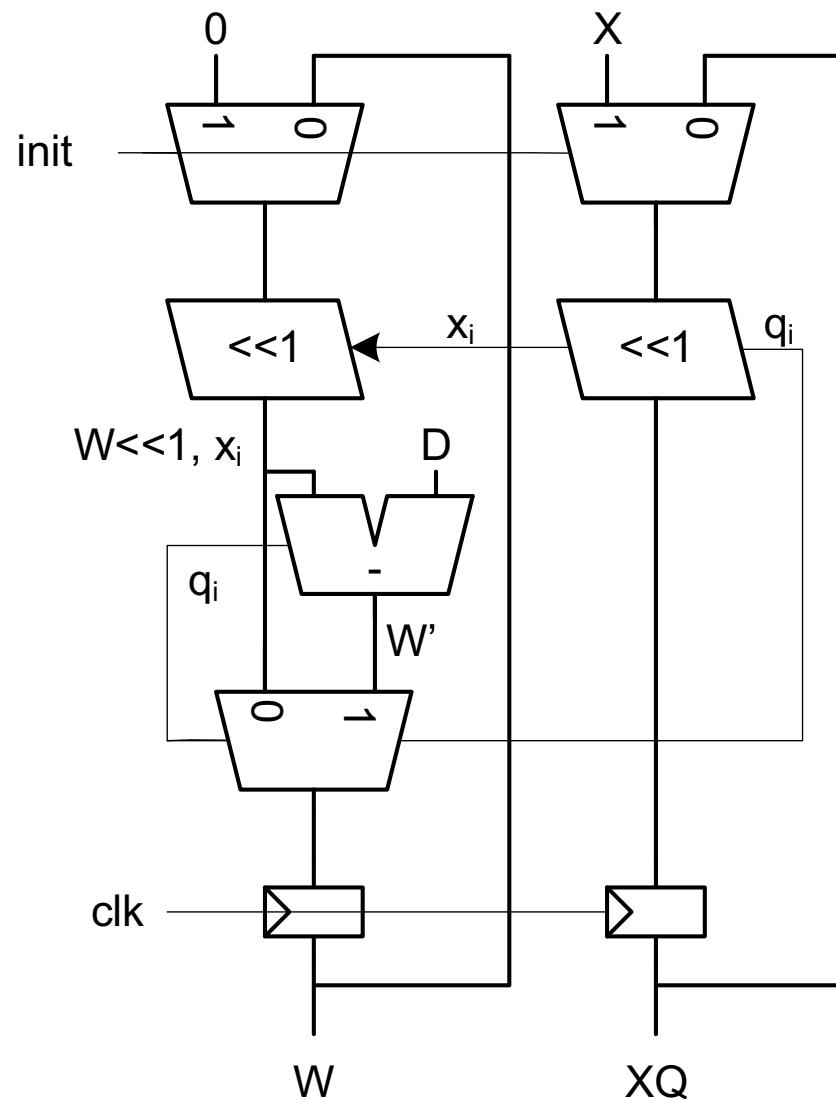

# Unsigned Integer Division Example

$i$	$W \ll 1, x_i$	$q_i$	$W$ output	$XQ$ output
init			0000	1101
0	0001	0	0001	1010
1	0011	1	0001	0101
2	0010	1	0000	1011
3	0001	0	0001	0110

$W = 0$

for  $i = 0$  to  $N-1$

$W = \{W \ll 1, x_i\}$

$W' = W - D$

if  $(W' \geq 0)$        $q_i = 1, W = W'$

else       $q_i = 0$

# Signed Division

## Examples:

X`	D	Q	REM
13	2	6	1
13	-2	-6	1
-13	2	-6	-1
-13	-2	6	-1

## Signed division:

- Take absolute value of inputs
- Perform unsigned integer division
- If signs of  $X$  and  $D$  differ, negate  $Q$
- If the sign of  $X$  is negative, negate  $REM$

## Chapter 15: Multiply & Divide

# **RISC-V Practices**

# M-Extension

op	funct3	funct7	Type	Instruction	Description	Operation
0110011 (51)	000	0000001	R	mul rd, rs1, rs2	multiply	$rd = (rs1 * rs2)_{XLEN-1:0}$
0110011 (51)	001	0000001	R	mulh rd, rs1, rs2	multiply high signed signed	$rd = (rs1 * rs2)_{2*XLEN-1:XLEN}$
0110011 (51)	010	0000001	R	mulhsu rd, rs1, rs2	multiply high signed unsigned	$rd = (rs1 * rs2)_{2*XLEN-1:XLEN}$
0110011 (51)	011	0000001	R	mulhu rd, rs1, rs2	multiply high unsigned unsigned	$rd = (rs1 * rs2)_{2*XLEN-1:XLEN}$
0110011 (51)	100	0000001	R	div rd, rs1, rs2	divide (signed)	$rd = rs1 / rs2$
0110011 (51)	101	0000001	R	divu rd, rs1, rs2	divide unsigned	$rd = rs1 / rs2$
0110011 (51)	110	0000001	R	rem rd, rs1, rs2	remainder (signed)	$rd = rs1 \% rs2$
0110011 (51)	111	0000001	R	remu rd, rs1, rs2	remainder unsigned	$rd = rs1 \% rs2$

RV64M adds mulw, divw, remw, divuw, remuw with op = 59. These operate on only the lower 32 bits of a register.

- Multiply, divide, and remainder instructions
- Operate on XLEN-bit words
- Treated as signed or unsigned values
- RV64M adds operations using the lower 32 bits of the registers

# Chapter 15: Multiply & Divide

## **Test Plan**

# Test Plan: riscv-arch-test


Instruction	RV32M Tests	RV64M Tests
div	587	675
divu	722	821
divuw		820
divw		667
mul	583	680
mulh	583	673
mulhsu	645	740
mulhu	719	811
mulw		670
rem	582	662
remu	720	819
remuw		815
remw		672
<b>Total</b>	<b>5141</b>	<b>9525</b>



## Chapter 15: Multiply & Divide

# **Wally Implementation**

# Wally Multiply/Divide Unit (MDU)

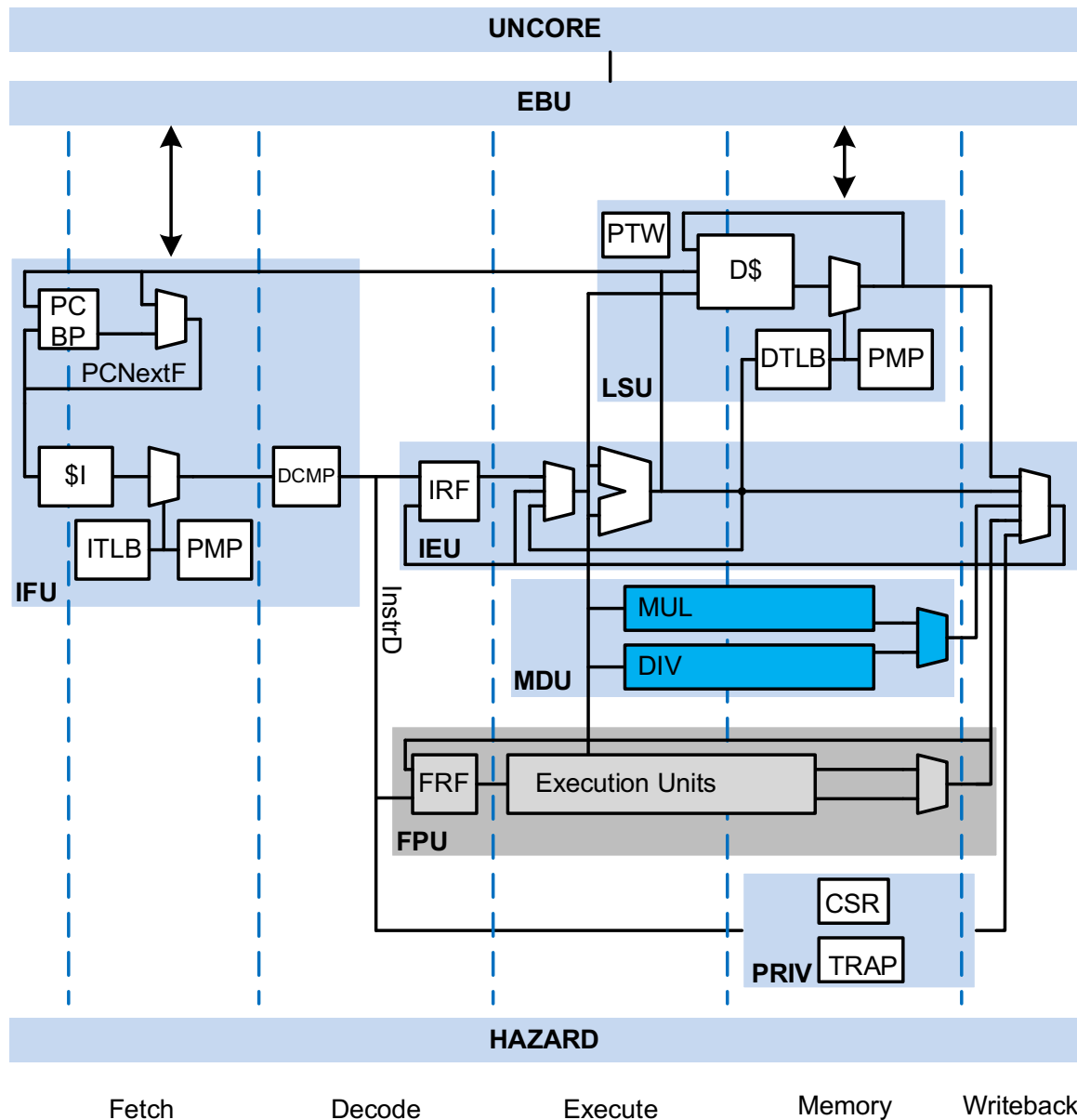

# Multiplication: Partial Products

Term	Definition	Comments
$P'$	$X' \times Y'$	$N-1 \times N-1$ bit multiplication
$PX$	$Y_{n-1} \times X'$	$N-1$ bit partial product
$PY$	$X_{n-1} \times Y'$	$N-1$ bit partial product
$P_{\text{msb}}$	$X_{n-1} \times Y_{n-1}$	1-bit partial product

# Signed & Unsigned Multiplication

Flavor	$X$	$Y$
<code>mulhu</code>	Unsigned	Unsigned
<code>mulh</code>	Signed	Signed
<code>mulhsu</code>	Signed	Unsigned

# Pre-Adding 1s in Dot Diagram


$$\begin{array}{r}
 \begin{array}{cccccccc}
 & & P'_5 & P'_4 & P'_3 & P'_2 & P'_1 & P'_0 & P' \\
 1 & 1 & \overline{PX}_2 & \overline{PX}_1 & \overline{PX}_0 & & & & \\
 & & & & 1 & & & & -PX2^{N-1} \\
 1 & 1 & \overline{PY}_2 & \overline{PY}_1 & \overline{PY}_0 & & & & -PY2^{N-1} \\
 & & & & 1 & & & & \\
 & & & & & & & & P_{msb}2^{2N-2} \\
 (a) \quad \hline
 & & P'_5 & P'_4 & P'_3 & P'_2 & P'_1 & P'_0 & P1 \\
 & & \overline{PX}_2 & \overline{PX}_1 & \overline{PX}_0 & & & & P2 \\
 & & \overline{PY}_2 & \overline{PY}_1 & \overline{PY}_0 & & & & P3 \\
 1 & P_{msb} & & 1 & & & & & P4 \\
 (b) \quad \hline
 \end{array}
 \end{array}$$

# Signed & Unsigned Multiplication

Flavor	$P1$	$P2$	$P3$	$P4$
<code>mulhu</code>	$P'$	$(PX)2^{N-1}$	$(PY)2^{N-1}$	$P_{\text{msb}}2^{2N-2}$
<code>mulh</code>	$P'$	$(\overline{PX})2^{N-1}$	$(\overline{PY})2^{N-1}$	$P_{\text{msb}}2^{2N-2} + 2^{2N-1} + 2^N$
<code>mulhsu</code>	$P'$			<exercise to reader>

# Wally Integer Multiplier Unit

mul

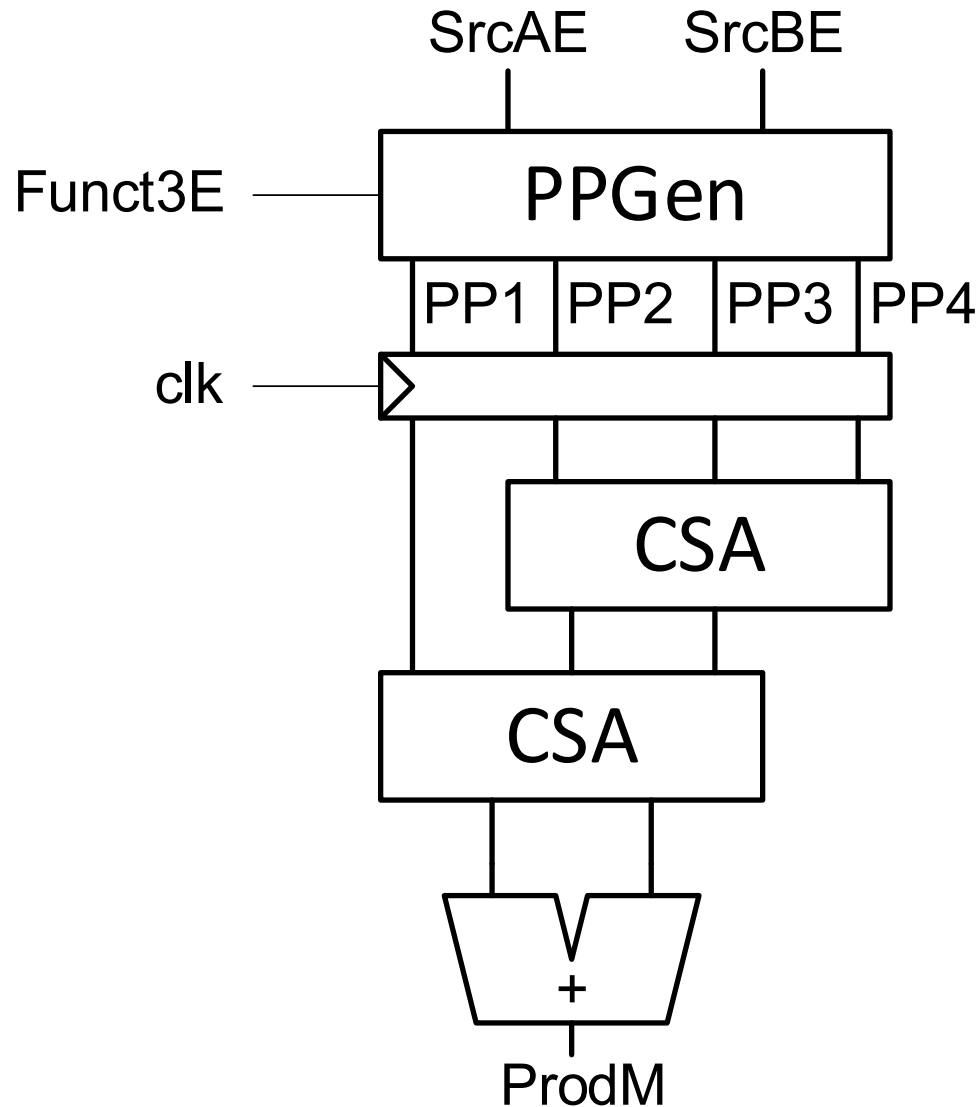


div







# Integer Divider Timing

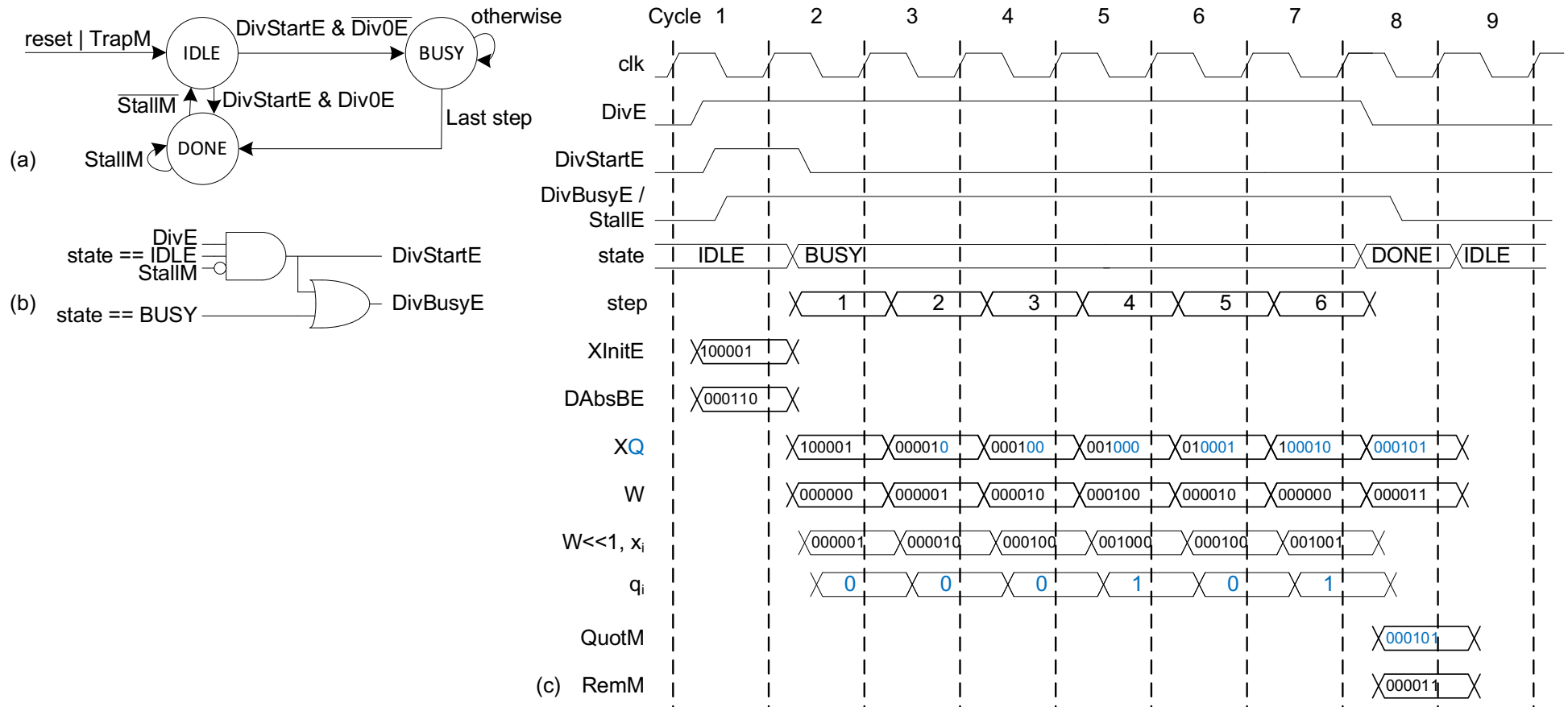

# MDU

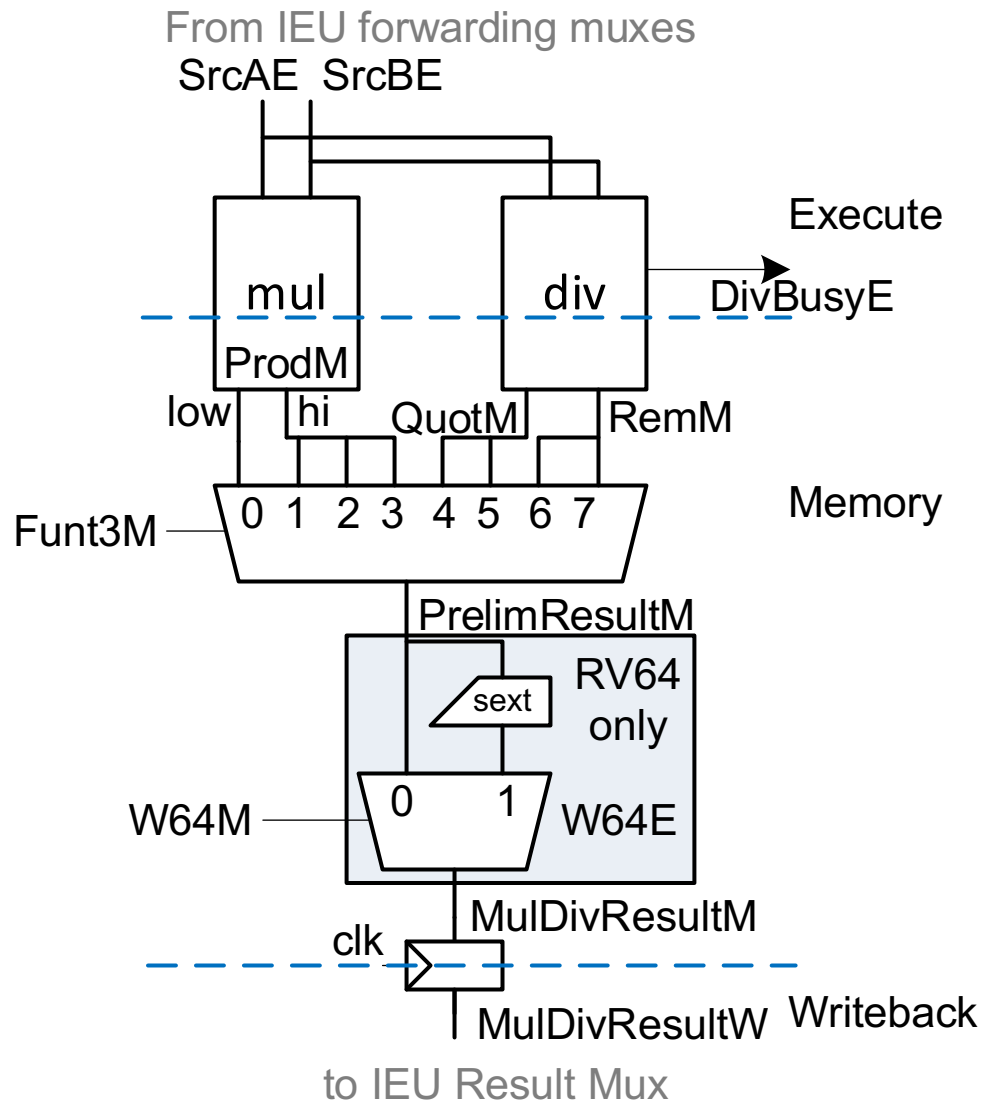

# Hazard Unit

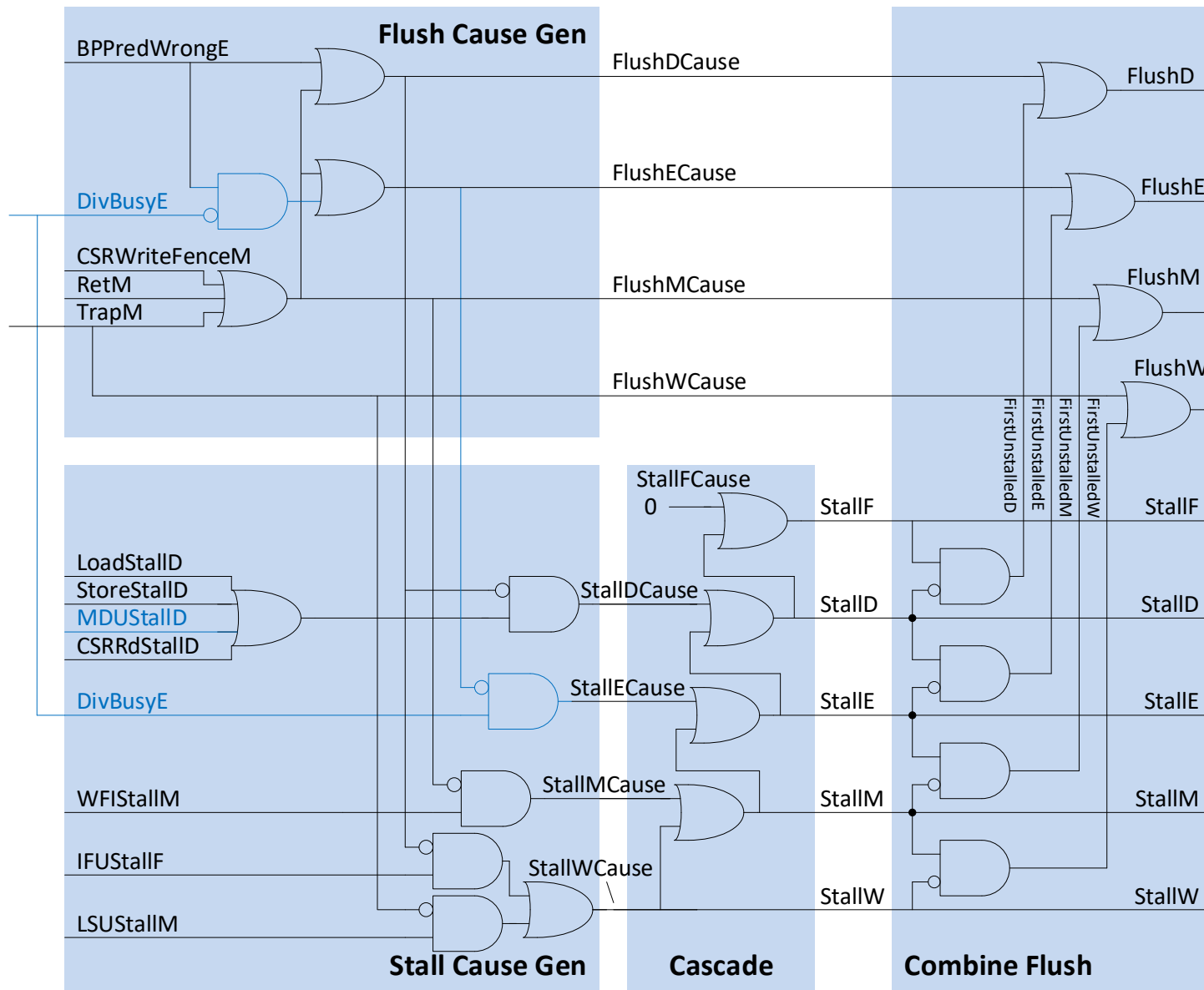

# About these Notes

**RISC-V System-on-Chip Design Lecture Notes**

**© 2025 D. Harris, J. Stine, R. Thompson, and S. Harris**

**These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.**