

**RISC-V**

**System-on-Chip Design**

**Harris, Stine, Thompson, & Harris**

**Chapter 4:**

**HDL Design Practices**

# Chapter 4 :: Topics

## Hardware Description Language (HDL) Design Practices

- 4.1 HDL Design Methodology
- 4.2 Hardware Design with SystemVerilog
- 4.3 Wally Style Guidelines

# Chapter 4: HDL Design Practices

## **HDL Design Methodology**

# Design Approach

- **Write specification before coding**
- **Block diagrams**
  - Start at top level
    - Sketch inputs, outputs, sub-blocks and their connections
  - Repeat recursively until done
- **Different designers own different blocks**
  - Rely on well-defined interfaces
- **Think of the hardware you want**
  - Write HDL idioms that generate that hardware
    - Use the synthesizable subset of the language
  - Don't write like it's a computer (software) program
  - Beware of bad examples on the Internet
  - Use the idioms from this chapter

# Project Management Methods

## Waterfall

- Traditional approach
- Divide project into tasks:
  - conception, design, build, test, deploy
- Review each step and freeze before next step
- Works well for industries like construction where steps are predictable
- Fails catastrophically on software and HDL because bugs aren't found until very late

## Agile

- Iterative design process
- Frequent working prototypes
  - Start with key features
- Frequent customer feedback

# Version Control

- **Essential for complex projects**
  - Provides backups
  - Allows one to roll back to the last working version
  - Allows teams to collaborate without overwriting
  - Allows experimenting in a branch before rolling into the main development
- **Git has taken over version control**

# Verification

- **Verification is more time consuming and expensive than SoC design**
- **Must start with the goal of verification in mind**
- **Develop test cases before or concurrent with HDL**
  - So code can be tested as soon as it is written
- **Regression suite**
  - Repeatedly run on code each time it is modified
  - Longer regression run nightly
  - Early notification of trouble
- **Danger: don't hack until the tests pass!**

Chapter 4: HDL Design Practices

**Hardware Design**

**With**

**SystemVerilog**



# Hierarchical Design

- **Decompose complex systems hierarchically**
- **Upper levels are described structurally**
  - In terms of simpler modules
- **Bottom levels are described behaviorally**
  - Boolean equations, truth tables, FSMs, etc.

# Combinational & Sequential Logic

- **Combinational Logic:**
  - Outputs depend on current inputs only
- **Sequential Logic:**
  - Outputs depend on current and previous inputs
  - Has memory
- **State:**
  - Minimum information about previous inputs needed to predict future outputs
- **Synchronous Sequential Logic:**
  - Every element is combinational logic or a flip-flop
  - All flip flops use the same clock (clk)
  - All feedback passes through a flip-flop

**A large majority of digital design is synchronous sequential.**

- Easy to design and verify

# Chapter 4: HDL Design Practices

## **Combinational Logic**




# Modules

- **Module name**
- **Inputs & Outputs**
- **Behavioral or structural description**

## Behavioral full adder example:

```
module fulladder(input  logic a, b, c,
                 output logic s, cout);

    assign s = a ^ b ^ c;
    assign cout = (a & b) | (a & c) | (b & c);
endmodule
```

   

# Operator Precedence

Only parenthesize when necessary or helpful

Precedence	Operator	Meaning
Highest	~	NOT
	*, /, %	Multiply, divide, modulo
	+, -	Add, subtract
	<<, >>	Logical left/right shift
	<<<, >>>	Arithmetic left/right shift
	<, <=, >, >=	Relative comparison
	==, !=	Equality comparison
	&, ~&	AND, NAND
	^, ~^	XOR, XNOR
	, ~	OR, NOR
Lowest	? :	Conditional (ternary)


# Combinational Logic using `assign`

## Express Boolean equations using `assign`

- **Bitwise operators** take N bits in and out
- **Reduction operators** take N bits in, 1 bit out

```
module eqcmp(input  logic [3:0] a, b,
             output logic      eq);

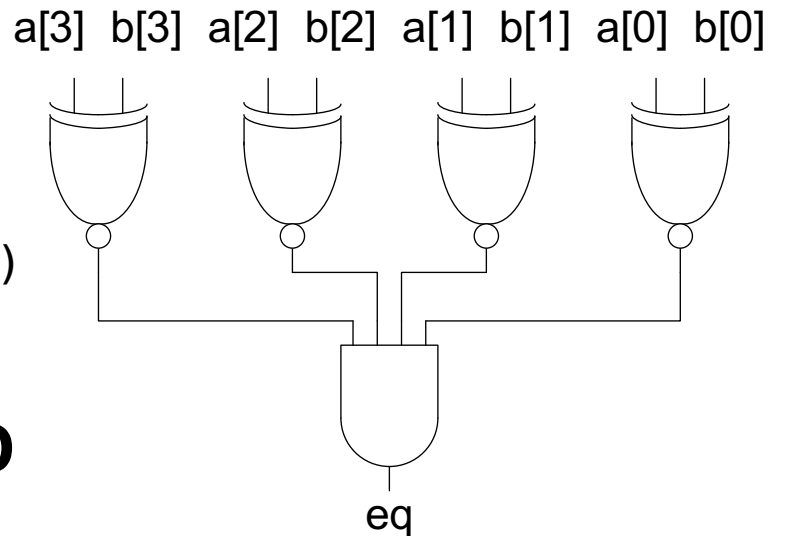    assign eq = &(a ~^ b);
    // equivalent to assign eq = (a == b)
endmodule
```



- **Bitwise XNOR, reduction AND**


# Multiplexer: Ternary Operator

**Ternary operator ? : is more readable than gates**

```
module mux2(input  logic [63:0] d0, d1,  
            input  logic          s,  
            output logic [63:0] y);
```

```
    assign y = s ? d1 : d0;
```

```
    /* alternative implementation using gates  
    logic [63:0] s64;  
    assign s64 = {64{s}}; // replicate s 64 times  
    assign y = ~s64 & d0 | s64 & d1; */  
endmodule
```

 


# Mux4: Structural Implementation

```
// 4:1 mux
module mux4 #(parameter WIDTH = 64) (
    input  logic [WIDTH-1:0] d0, d1, d2, d3,
    input  logic [1:0] s,
    output logic [WIDTH-1:0] y);

    logic [WIDTH-1:0] d01, d23;

    // structural implementation using 2:1 muxes
    mux2 #(WIDTH) lsbmux(d0, d1, s[0], d01);
    mux2 #(WIDTH) msbmux(d2, d3, s[0], d23);
    mux2 #(WIDTH) finalmux(d01, d23, s[1], y);

endmodule
```

 



# Mux4: Other Implementations

```
module mux4 ...
```

```
/* alternative behavioral implementation using assign statement  
assign y = s[1] ? (s[0] ? d3 : d2) : (s[0] ? d1 : d0); */
```

```
/* alternative behavioral implementation using case statement  
always_comb  
  case(s)  
    0: y = d0;  
    1: y = d1;  
    2: y = d2;  
    3: y = d3;  
  endcase */
```


```
/* alternative behavioral implementation using if statements  
always_comb  
  if (s == 2'b00) y = d0;  
  else if (s == 2'b01) y = d1;  
  else if (s == 2'b11) y = d2;  
  else y = d3; */  
endmodule
```

# Combinational Logic with Always
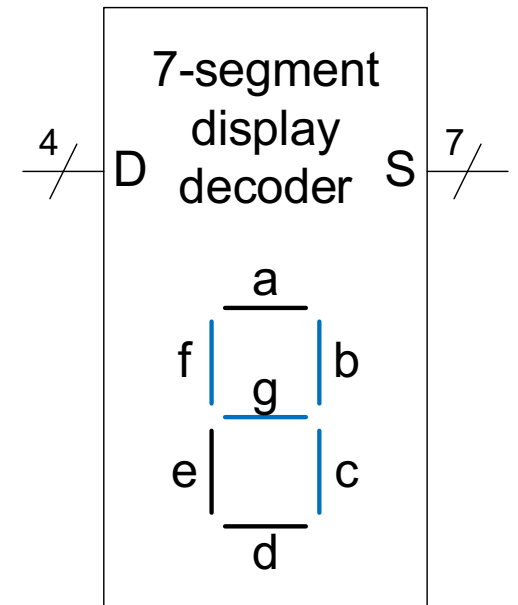
## case statements for truth tables

```
module sevensseg(input  logic [3:0] digit,
                 output logic [6:0] segments);

    always_comb
        case(digit)
            // abc_defg
            0:    segments = 7'b111_1110;
            1:    segments = 7'b011_0000;
            2:    segments = 7'b110_1101;
            3:    segments = 7'b111_1001;
            4:    segments = 7'b011_0011;
            5:    segments = 7'b101_1011;
            6:    segments = 7'b101_1111;
            7:    segments = 7'b111_0000;
            8:    segments = 7'b111_1111;
            9:    segments = 7'b111_0011;
            default: segments = 7'b000_0000;
        endcase
endmodule
```



# Combinational Logic with Always

## casez statements for truth tables with don't care

```
module priorityckt(input  logic [3:0] a,  
                  output logic [3:0] y);
```

```
    // casez implementation
```

```
    always_comb
```

```
        casez(a)
```

```
            4'b1???: y = 4'b1000;
```

```
            4'b01??: y = 4'b0100;
```

```
            4'b001?: y = 4'b0010;
```

```
            4'b0001: y = 4'b0001;
```

```
            default: y = 4'b0000;
```

```
        endcase
```

```
    /* if implementation:
```

```
    always_comb
```

```
        if      (a[3]) y = 4'b1000;
```


```
        else if (a[2]) y = 4'b0100;
```

```
        else if (a[1]) y = 4'b0010;
```

```
        else if (a[0]) y = 4'b0001;
```

```
        else          y = 4'b0000; */
```

```
endmodule
```

 


## Chapter 4: HDL Design Practices

# **Sequential Logic: Elements**
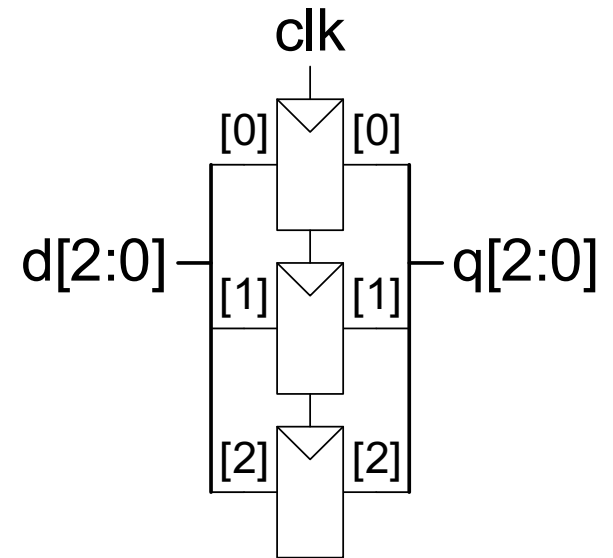
# Flip-Flops

On rising edge of clock, copy D to Q

```
module flop #(parameter WIDTH = 3) (  
    input  logic          clk,  
    input  logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] q);  
  
    always_ff @(posedge clk)  
        q <= #1 d;  
endmodule
```




# Resettable Flip-Flops

```
module flopr #(parameter WIDTH = 8) (  
    input  logic          clk, reset,  
    input  logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] q);
```

```
    always_ff @(posedge clk, posedge reset) // asynchronous reset  
        if (reset) q <= #1 0;  
        else      q <= #1 d;  
endmodule
```

```
module flopc #(parameter WIDTH = 8) (  
    input  logic          clk, clear,  
    input  logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] q);
```
 
```
    always_ff @(posedge clk)  
        if (clear) q <= #1 0; // synchronous clear  
        else      q <= #1 d;  
endmodule
```





# Enabled Flip-Flops

```
module flopen #(parameter WIDTH = 8) (  
    input  logic          clk, en,  
    input  logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] q);
```

```
    always_ff @(posedge clk)  
        if (en) q <= #1 d;  
endmodule
```

```
module flopenrc #(parameter WIDTH = 8) (  
    input  logic          clk, reset, clear, en,  
    input  logic [WIDTH-1:0] d,  
    output logic [WIDTH-1:0] q);
```

  
```
    always_ff @(posedge clk, posedge reset)  
        if (reset)    q <= #1 0;  
        else if (en)  
            if (clear) q <= #1 0;  
            else       q <= #1 d;  
endmodule
```



# Blocking vs. Nonblocking Assignments

 
## Nonblocking

```
always_ff @(posedge clk) begin
    b <= a;
    c <= b;
end
```


 
## Blocking

```
always_ff @(posedge clk) begin
    b = a;
    c = b;
end
```




- **Nonblocking** are appropriate for **sequential logic**
- **Blocking** are more efficient for **combinational logic**



# Latches
 
## When $\text{clk} = 1$ , copy $d$ to $q$

```
module latch #(parameter WIDTH = 8) (  
  input  logic          clk,  
  input  logic [WIDTH-1:0] d,  
  output logic [WIDTH-1:0] q);  
  
  always_latch  
    if (clk) q <= #1 d;  
endmodule
```





# Chapter 4: HDL Design Practices

## **Sequential Logic:**


### **FSMs**
 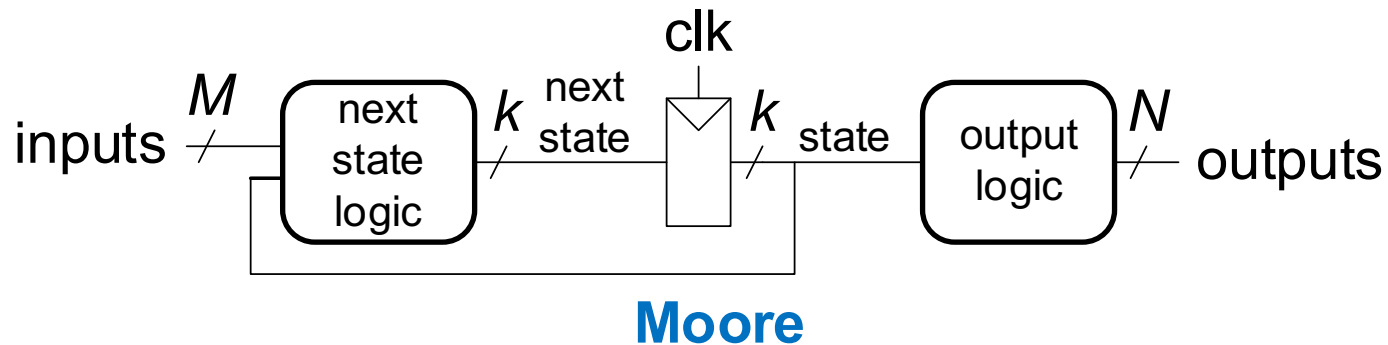
# Finite State Machines

- **Moore:** Output depends on **current state**
- **Mealy:** Output depends on **current state & inputs**



# Moore Example: 2-bit branch predictor

 

# Moore Example: 2-bit branch predictor

```

module twobitbranchpredictor(input logic clk, reset,
                             input logic t,
                             output logic p);

    typedef enum logic [1:0] {SNT, WNT, WT, ST} statetype;

    statetype state, nextstate;


    // state register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= WT;
        else state <= nextstate;

    // next state logic
    always_comb
        case (state)
            SNT: if (t) nextstate = WNT;
                 else nextstate = SNT;
            WNT: if (t) nextstate = WT;
                 else nextstate = SNT;
            WT:  if (t) nextstate = ST;
                 else nextstate = WNT;
            ST:  if (t) nextstate = ST;
                 else nextstate = WT;
            default: nextstate = WT;
        endcase

    // output logic
    assign p = (state == WT) | (state == ST);
endmodule

```

State	Encoding S[1:0]
SNT	00
WNT	01
WT	10
ST	11

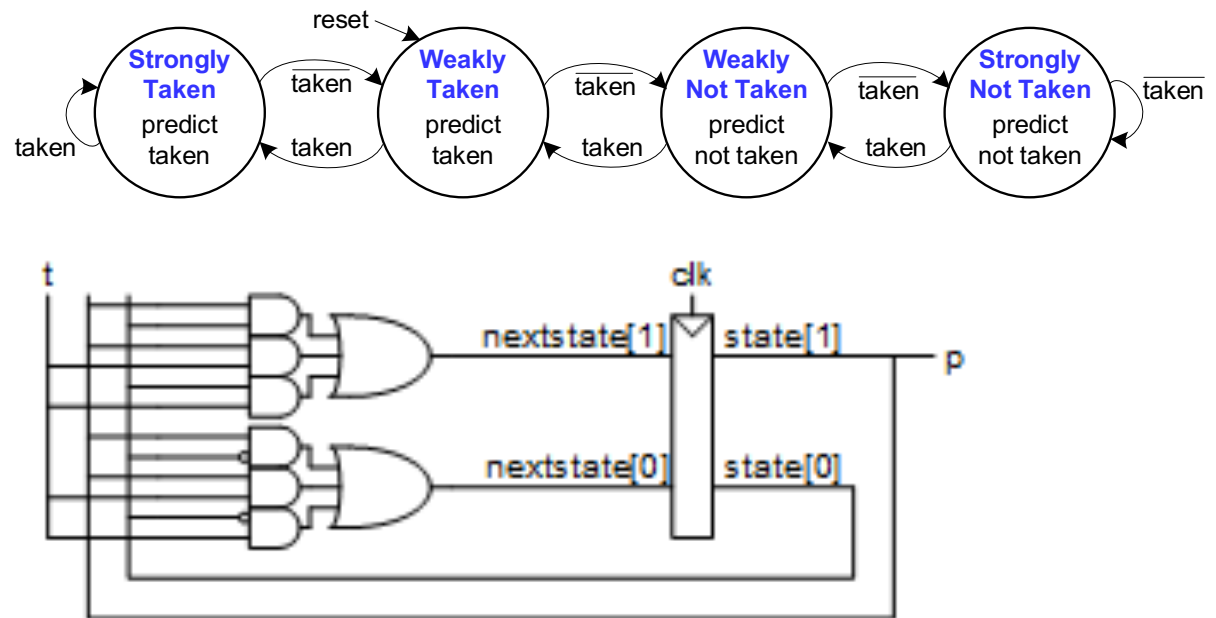


# Mealy Example: Divider Controller

```
module dividercont (input  logic clk, reset,  
                  input  logic div,  
                  output logic start, busy);
```

```
typedef enum logic [1:0] {IDLE, BUSY, DONE} statetype;  
statetype state;  
logic [5:0] step;
```

```
always_ff @(posedge clk)  
  if (reset) state <= IDLE;  
  else case (state)  
    IDLE: if (div) begin  
           state <= BUSY;  
           step  <= 1;  
         end  
    BUSY: begin  
           if (step[5]) state <= DONE;  
           step  <= step + 1;  
         end  
    DONE: state <= IDLE;  
  endcase
```

```
assign start = div & (state == IDLE);  
assign busy  = start | (state == BUSY);  
endmodule
```

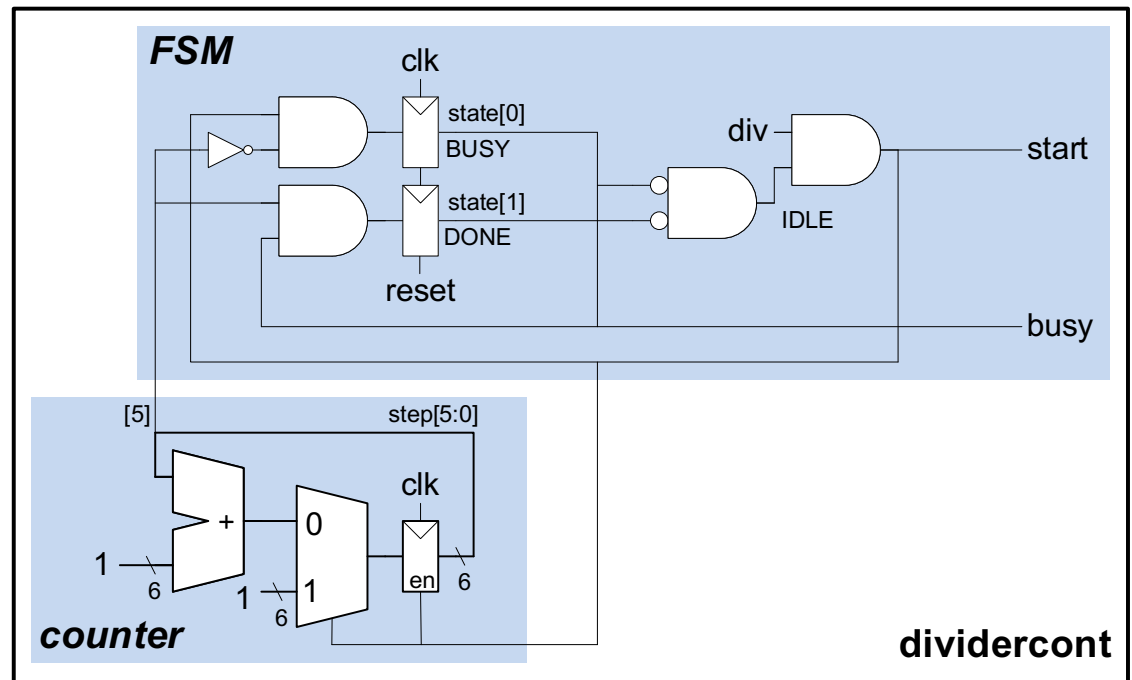


## Chapter 4: HDL Design Practices

# **Sequential Logic: Memories**
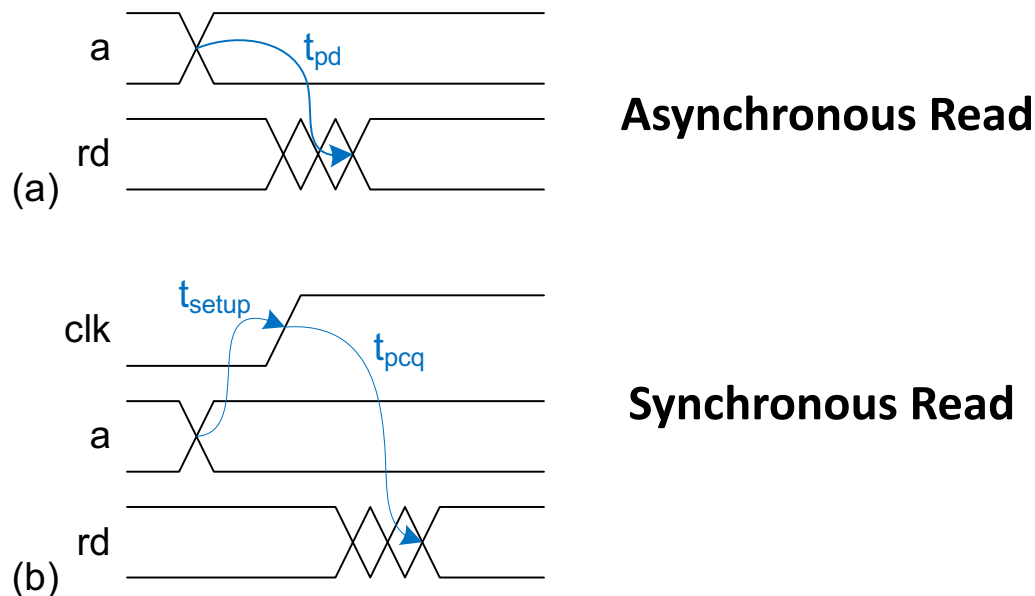
# Memories


- $2^M$  words x N bits
- Read and write ports
- Optional byte and chip enables
- Synchronous or asynchronous read
- Synchronous write




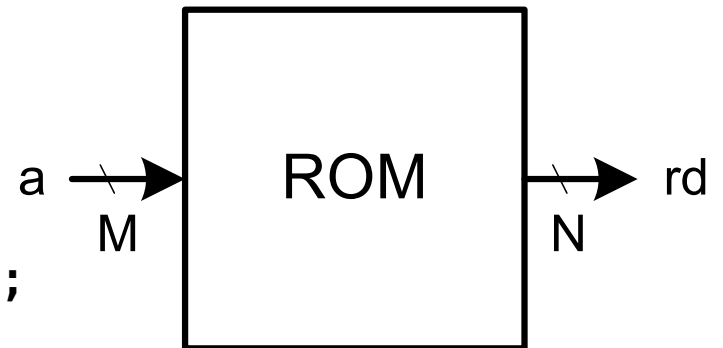
# ROM: Read Only Memory

```
module rom1p1r #(parameter M=3, N=16) (  
    input  logic [M-1:0] a,  
    output logic [N-1:0] rd);  
  
    logic [N-1:0] mem[2**M];  
  
    initial $readmemh("romfile.dat", mem);  
  
    assign rd = mem[a]; // asynchronous read  
endmodule
```




```
romfile.dat  
0000  
FFFF  
A5A5  
0001  
DEAD  
BEEF  
ABCD  
0123
```
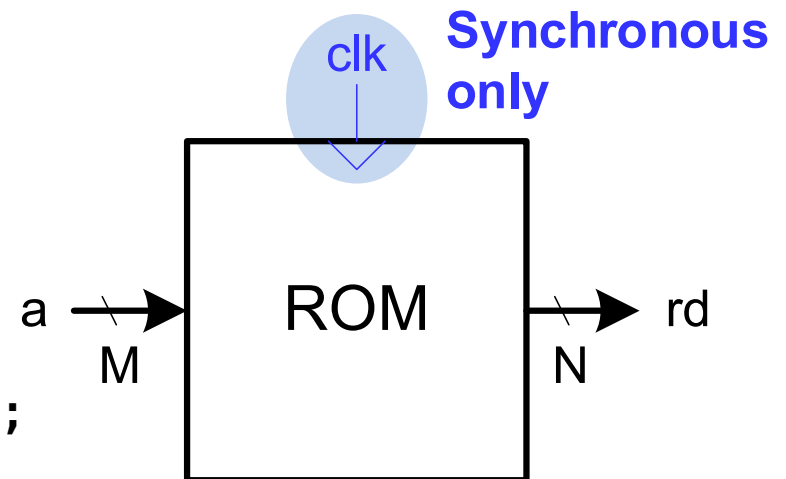
# ROM: Read Only Memory

```
module rom1p1r #(parameter M=3, N=16) (  
    input  logic [M-1:0] a,  
    output logic [N-1:0] rd);  
  
    logic [N-1:0] mem[2**M];  
  
    initial $readmemh("romfile.dat", mem);  
  
    always_ff @(posedge clk)  
        rd <= mem[a]; // synchronous read  
endmodule
```


```
romfile.dat  
0000  
FFFF  
A5A5  
0001  
DEAD  
BEEF  
ABCD  
0123
```



# Static Random Access Memory (SRAM)
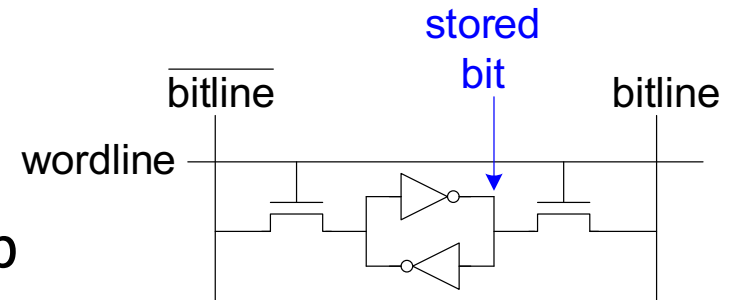
## Read:

Precharge bitline & bitlineb high  
Raise wordline  
Either bitline or bitlineb will drop



## Write:

Drive bitline to write value and bitlineb to its complement  
Raise wordline  
Bitlines will overpower inverters and store into cell

## Large SRAMs use SRAM bit cells


- Along with decoders, bitline circuits

## Small SRAMs use flip-flops or latches
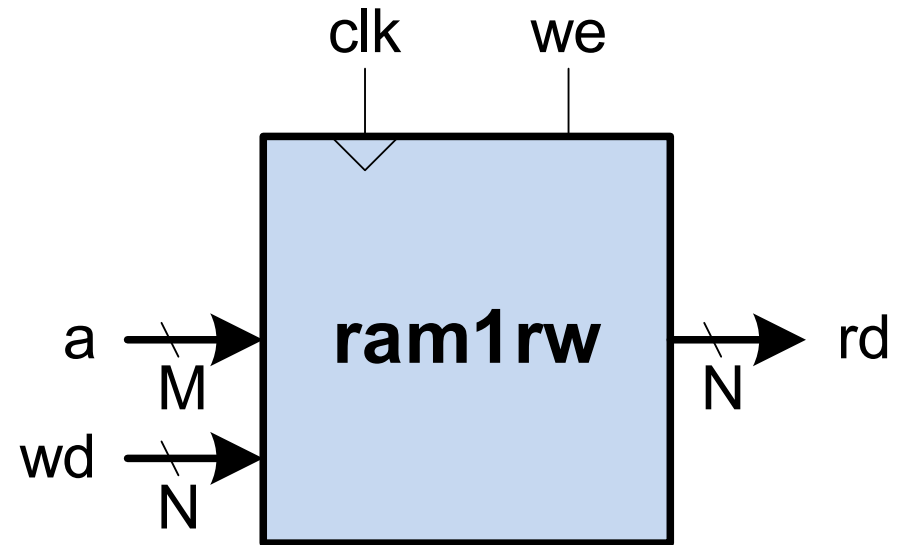
# Single-port SRAM

```
module ram1p1rw_async #(parameter M = 6, N = 32) (  
    input  logic      clk,  
    input  logic      we,  
    input  logic [M-1:0] a,  
    input  logic [N-1:0] wd,  
    output logic [N-1:0] rd);  
  
    logic [N-1:0] mem[2**M];  
  
    assign rd = mem[a];          // asynchronous read  
    always_ff @(posedge clk)  
        if (we) mem[a] <= wd;  
endmodule
```

```
module ram1p1rw #(parameter M = 6, N = 32) (  
    input  logic      clk,  
    input  logic      we,  
    input  logic [M-1:0] a,  
    input  logic [N-1:0] wd,  
    output logic [N-1:0] rd);  
  
    logic [N-1:0] mem[2**M];  
  
    always_ff @(posedge clk) begin  
        rd <= mem[a];          // synchronous read  
        if (we) mem[a] <= wd;  
    end  
endmodule
```



# SRAM with Byte Enable

## Only write byte when its we = 1

```
module ram1p1rwb #(parameter M = 6, N = 32) (  
    input  logic          clk,  
    input  logic [N/8-1:0] we,  
    input  logic [M-1:0]  a,  
    input  logic [N-1:0]  wd,  
    output logic [N-1:0]  rd);  
  
    logic [N-1:0] mem[2**M];  
    genvar i;  
  
    always_ff @(posedge clk)  
        rd <= mem[a];  
  
    for(i=0; i<M/8; i++) // byte writes  
        always_ff @(posedge clk)  
            if (we[i])  
                mem[a][i*8+7:i*8] <= wd[i*8+7:i*8];  
endmodule
```

# SRAM with Chip & Byte Enable


## Disable write & retain old output when ce = 0

```
module ram1p1rwbe #(parameter M = 6, N = 32) (  
    input  logic          clk,  
    input  logic          ce,  
    input  logic [N/8-1:0] we,  
    input  logic [M-1:0]  a,  
    input  logic [N-1:0]  wd,  
    output logic [N-1:0]  rd);  
  
    logic [N-1:0] mem[2**M];  
    genvar i;  
  
    always_ff @(posedge clk)  
        if (ce) rd <= mem[a];  
  
    for(i=0; i<N/8; i++) // byte writes  
        always_ff @(posedge clk)  
            if (ce & we[i])  
                mem[a][i*8+7:i*8] <= wd[i*8+7:i*8];  
    end  
endmodule
```

# Dual-Ported SRAM
 
## 2 ports: 1 read and 1 write port


```
module ram2p1r1w #(parameter M = 6, N = 32) (  
    input  logic      clk,  
    input  logic      we2,  
    input  logic [M-1:0] a1, a2,  
    input  logic [N-1:0] wd2,  
    output logic [N-1:0] rd1);  
  
    logic [N-1:0] mem[2**M];  
  
    always_ff @(posedge clk) begin  
        rd1 <= mem[a1];  
        if (we2) mem[a2] <= wd2;  
    end  
endmodule
```



# Dual-Ported SRAM
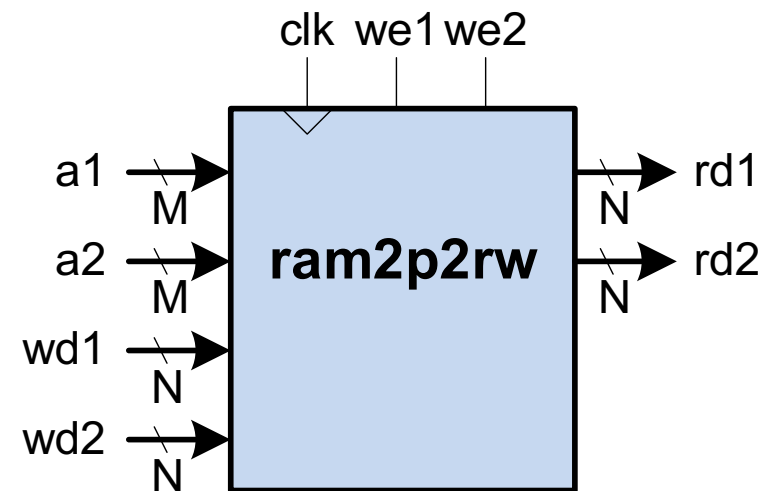
## 2 ports: 2 read/write ports

```
module ram2p2rw #(parameter M = 6, N = 32) (  
    input  logic      clk,  
    input  logic      we1, we2,  
    input  logic [M-1:0] a1, a2,  
    input  logic [N-1:0] wd1, wd2,  
    output logic [N-1:0] rd1, rd2);  
  
    logic [N-1:0] mem[2**M];  
  
    always_ff @(posedge clk) begin  
        rd1 <= mem[a1];  
        rd2 <= mem[a2];  
        if (we1) mem[a1] <= wd1;  
        if (we2) mem[a2] <= wd2;  
    end  
endmodule
```






# Triple-Ported Register File
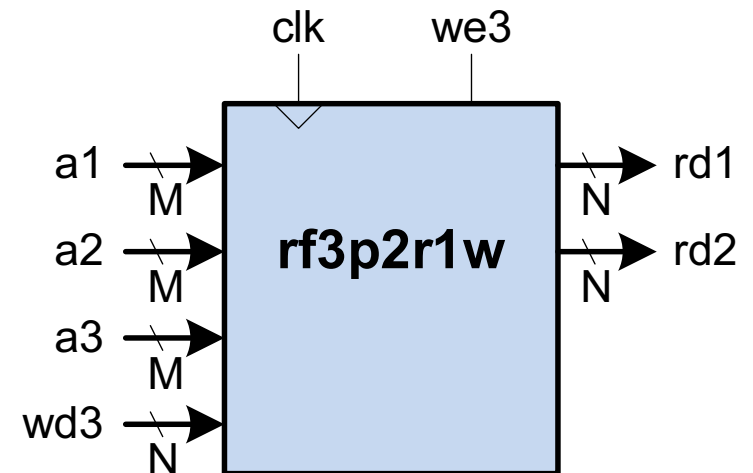
## 3 ports: 2 read ports, 1 write port

```
module rf3p2r1w #(parameter M = 5, N = 32) (  
    input  logic          clk,  
    input  logic          we3,  
    input  logic [M-1:0] a1, a2, a3,  
    input  logic [N-1:0] wd3,  
    output logic [N-1:0] rd1, rd2);  
  
    logic [N-1:0] mem[2**M];  
  
    // asynchronous read on ports 1, 2  
    assign rd1 = mem[a1];  
    assign rd2 = mem[a2];  
  
    // synchronous write on port 3  
    always_ff @(posedge clk)  
        if (we3) mem[a3] <= wd3;  
endmodule
```



# Chapter 4: HDL Design Practices

## **Verilog Syntax**

# Constants

## N' Bvalue

- **N** = size in bits
- **B** = base (b binary, d decimal, h hexadecimal)

Number	Bits	Base	Decimal Value	Stored
3'b101	3	2	5	101
8'b1010_1011	8	2	171	10101011
8'b11	8	2	3	00000011
3'd6	3	10	6	110
8'hAB	8	16	171	10101011

# Bit Swizzling

```
// Create 64-bit bus of all 0 or all 1 depending on s
```

```
logic [63:0] s64;  
assign s64 = {64{s}};
```

```
// Create 8-bit bus of all x or all 1s
```

```
logic [7:0] data0, data1;  
assign data0 = 'x;      // data0 = xxxxxxxx  
assign data1 = '1;      // data1 = 11111111
```

```
// Join together two 32-bit values to form a 64-bit value
```

```
logic [31:0] upper, lower;  
logic [63:0] entire;  
assign entire = {upper, lower};
```

```
// Form bus containing constants and parts of other busses
```

```
// y = a[2] a[2] b[2] b[1] b[0] a[1] a[0] 1 0 1  
logic [2:0] a, b;  
logic [9:0] y;  
assign y = {{2{a[2]}}, b, a[1:0], 3'b101};
```

```
// Add 2 32-bit numbers: produce 32-bit sum, 1-bit carry out
```

```
logic [31:0] a, b, sum;  
logic      cout;  
assign {cout, sum} = a + b;
```

# Gating one bit with many

```
logic          reset;
logic [N-1:0] a, y1, y2;

// equivalent methods
assign y1 = reset ? '0 : a;
assign y2 = {N{~reset}} & a;
```

# Delays

- **Handy to track causality in simulation**
  - Especially on flip-flop outputs
- **Necessary to create clocks in testbench**
- **Ignored for synthesis**


```
module fulladder(input  logic a, b, c,  
                output logic s, cout);  
  
    assign #3 s = a ^ b ^ c;  
    assign #2 cout = (a & b) | (a & c) | (b & c);  
endmodule
```

# Tristate and Bidirectional I/O
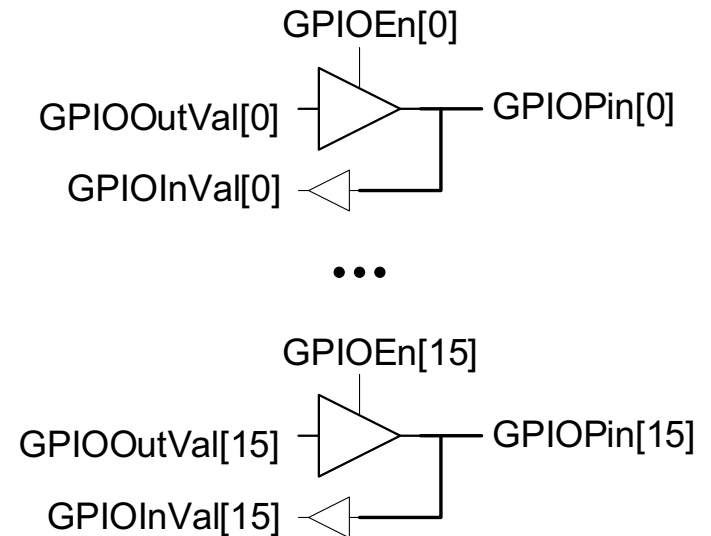
## Z indicates floating (undriven) value

```
module tristate #(parameter WIDTH=32) (  
    input  logic [WIDTH-1:0] a,  
    input  logic          en,  
    output tri   [WIDTH-1:0] y);  
  
    assign y = en ? a : 'z;  
endmodule
```

```
module gpio #(parameter WIDTH=16) (  
    input  logic [WIDTH-1:0] GPIOOutVal, GPIOEn,  
    output logic [WIDTH-1:0] GPIOInVal,  
    inout  tri   [WIDTH-1:0] GPIOPin);  
  
    assign GPIOInVal = GPIOPin;  
    tristate #(1) ts[WIDTH-1:0](GPIOOutVal, GPIOEn, GPIOPin);  
endmodule
```



# Port Connections

- **.sig** connects signal with same name
- **.sig(sig2)** connects **sig2** to **sig** port
- **.\*** connects all ports
  - **Avoid** because it makes code hard to trace

```
module reg4(input logic clk,
            input logic reset,
            input logic [3:0] x,
            output logic [3:0] y);

    flopr #(1) f0(clk, reset, x[0], y[0]);
    flopr #(1) f1(.clk(clk),
                 .reset(reset),
                 .d(x[1]),
                 .q(y[1]));
    flopr #(1) f2(.clk, .reset, .d(x[2]), .q(y[2]));
    flopr #(1) f3(.d(x[3]), .q(y[3]), .*);
endmodule
```



# Assertions

## Check properties during simulation

```
always_comb
  assert (`U_SUPPORTED | (`S_SUPPORTED == 0))
    else $error ("S supported only if U is too");
```

`$warning` is also available

## Chapter 4: HDL Design Practices

# **Configurable Hardware**

# `define

Place configuration values in a `.vh` header file

- ``include 'wally-config.vh'` in each `.sv` file

```
`define XLEN 32  
`define PPN_BITS (`XLEN==32 ? 22 : 44)
```

# Configurable Widths

## Use `{size{val}}` to create configurable busses

```
`include "wally-config.vh"

// Create XLEN-bit bus of all 0 or all 1 depending on s
logic [`XLEN-1:0] sx;
assign sx = `{XLEN{s}};

// Sign extend D[31:20] to `XLEN bits
logic [`XLEN-1:0] extend;
assign extend = {{(`XLEN-12){Instr [31]}}, Instr[31:20]};

// LT in the bottom bit and WIDTH-1 0s in the upper bits
logic [`XLEN-1:0] SLT;
assign SLT = {{(`XLEN-1){1'b0}}, LT};
```

# Conditional Hardware

## Turn off signals based on configuration

- **Example:** WriteMSTATUSHM = 0 when `XLEN is not 32

```
`include "wally-config.vh"
assign WriteMSTATUSHM = CSRMWriteM & (CSRAdrM == MSTATUSH) &
    (`XLEN==32);
```

## Instantiate module based on configuration



- **Example:** Make MDU when `M\_SUPPORTED
- Otherwise tie outputs to 0

```
logic [`XLEN-1:0] MulDivResultW;
logic          DivBusyE;
if (`M_SUPPORTED) begin: mdugen
    mdu mdu(.clk, .reset, .ForwardedSrcAE, .ForwardedSrcBE,
        .Funct3E, .Funct3M, .MulDivE, .W64E,
        .MulDivResultW, .DivBusyE, .StallM, .StallW, .FlushM, .FlushW);
end else begin // no M instructions supported
    assign MulDivResultW = 0;
    assign DivBusyE = 0;
end
```

# Generate Loops
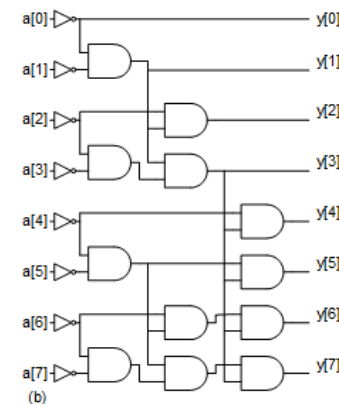 
## Loop to describe each bit

```
module prioritythermometer #(parameter N = 8) (  
    input logic [N-1:0] a,  
    output logic [N-1:0] y);  
  
    // create thermometer code mask  
    genvar i;  
    assign y[0] = ~a[0];  
    for (i=1; i<N; i++) begin: therm  
        assign y[i] = y[i-1] & ~a[i];  
    end  
endmodule
```



# Arrays of Modules

```
module tlbram #(parameter TLB_ENTRIES = 8) (  
    input  logic          clk, reset,  
    input  logic  [`XLEN-1:0]    PTE,  
    input  logic  [TLB_ENTRIES-1:0]  Matches, WriteEnables,  
    output logic  [`PPN_BITS-1:0]    PPN,  
    output logic  [7:0]            PTEAccessBits,  
    output logic  [TLB_ENTRIES-1:0]  PTE_Gs  
);  
  
    logic  [`PPN_BITS+9:0] RamRead[TLB_ENTRIES];  
    logic  [`PPN_BITS+9:0] PageTableEntry;  
  
    // RAM implemented with array of flops and AND/OR read logic  
    tlbramline #(`PPN_BITS+10) tlbramline[TLB_ENTRIES-1:0]  
        (.clk, .reset, .re(Matches), .we(WriteEnables),  
        .d(PTE[`PPN_BITS+9:0]), .q(RamRead), .PTE_G(PTE_Gs));  
    or_rows #(TLB_ENTRIES, `PPN_BITS+10) PTEOr(RamRead, PageTableEntry);  
  
    // Rename the bits read from the TLB RAM  
    assign PTEAccessBits = PageTableEntry[7:0];  
    assign PPN = PageTableEntry[`PPN_BITS+9:10];  
endmodule
```

```
module tlbramline #(parameter WIDTH = 22)  
    (input  logic          clk, reset,  
     input  logic          re, we,  
     input  logic  [WIDTH-1:0] d,  
     output logic  [WIDTH-1:0] q,  
     output logic          PTE_G);  
  
    logic  [WIDTH-1:0] line;  
  
    flopenr #(WIDTH) pteflop(clk, reset, we, d, line);  
    assign q = re ? line : 0;  
    assign PTE_G = line[5]; // send global bit to CAM as part of ASID matching  
endmodule
```

How do signals connect to an array?

```
module or_rows #(parameter ROWS = 8, COLS=2) (  
    input  var logic  [COLS-1:0] a[ROWS],  
    output logic  [COLS-1:0] y);  
  
    genvar row;  
    if(ROWS == 1)  
        assign y = a[0];  
    else begin  
        logic  [COLS-1:0] mid[ROWS-1:1];  
        assign mid[1] = a[0] | a[1];  
        for (row=2; row < ROWS; row++)  
            assign mid[row] = mid[row-1] | a[row];  
        assign y = mid[ROWS-1];  
    end  
endmodule
```

# Chapter 4: HDL Design Practices

## **Testbenches**



# Self-checking Testbench

- Instantiate device under test (DUT)
- Generate clock and reset inputs
- Read a set of *testvectors* (inputs and expected outputs) from a file
- Apply the inputs on successive clock cycles and check the outputs
- Log any mismatches

# fulladder testbench

```
module testbench();
  logic      clk, reset;
  logic      a, b, c, s, cout, sexpected, coutexpected;
  logic [31:0] vectornum, errors;
  logic [4:0] testvectors[10000:0];

  // instantiate device under test
  fulladder dut(a, b, c, s, cout);

  // generate clock
  always
  begin
    clk = 1; #5; clk = 0; #5;
  end

  // at start of test, load vectors and pulse reset
  initial
  begin
    $readmemb("fulladder.tv", testvectors);
    vectornum = 0; errors = 0;
    reset = 1; #22; reset = 0;
  end

  // apply test vectors on rising edge of clk
  always @(posedge clk)
  begin
    #1; {a, b, c, coutexpected, sexpected} = testvectors[vectornum];
  end
end
```

fulladder.tv

```
// abc_cout s
000_00
001_01
010_01
011_10
100_01
101_10
110_10
111_11
```

# fulladder testbench (continued)

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset) begin // skip during reset
    if (s !== sexpected | cout !== coutexpected) begin // check result
      $display("Error: inputs = %b", {a, b, c});
      $display("  outputs cout s = %b%b (%b%b expected)", cout, s, coutexpected, sexpected);
      errors = errors + 1;
    end
    vectornum = vectornum + 1;
    if (testvectors[vectornum] === 'bx) begin
      $display("%d tests completed with %d errors",
              vectornum, errors);
      $stop;
    end
  end
endmodule
```

Use **===** or **!==** for  
Signals that could be  
x or z

# Chapter 4: HDL Design Practices

**Wally**

**Style**

**Guidelines**

# Signals

- Use **flatcase** for `clk` and `reset`.
- Use **UpperCamelCase** for signals.
- Use **suffixes** on all signals associated with pipeline stages.
  - F, D, E, M, W
- Use **prefixes** to distinguish related signals from different sources
  - IEUResultM, MDUResultW, SCResultW
- **Declare all internal signals**, including 1-bit signals.
- Only use (bidirectional) **inout pins at the top-level** chip module.
  - Define them as `inout tri`.
- Declare all other signals as **logic**.
- Declare busses as **little-endian**
  - `bus[31:0]`, not `bus[0:31]`
- **Avoid passing arrays through ports** if possible, but declare the port as `var logic` if necessary.
  - `input var logic [7:0]`  
`PMPCFG_ARRAY_REGW[`PMP_ENTRIES-1:0]`

# Port Connections

- **Connect ports by order for simple generic modules** such as flip-flops and multiplexers.
- Guideline 3.12 **Connect ports by name** for other modules.
- Guideline 3.13 For non-generic modules used only once, **use the same name** inside and outside of the module.
- Guideline 3.14 **Avoid** .\* notation except in wrapper modules
- Guideline 3.15 Pack **multiple port connections on one line** of the instantiation.

## Example:

```
mux2 #(`XLEN) ieureultmux(ALUResultE, AltResultE, ALUResultSrcE,  
                          IEUResultE);  
mmu #(.TLB_ENTRIES(`DTLB_ENTRIES), .IMMU(0)) dmmu(  
    .clk, .reset, .SATP_REGW, .STATUS_MXR, .STATUS_SUM,  
    .STATUS_MPRV, .STATUS_MPP,  
    .PrivilegeModeW, .DisableTranslation(SelHPTW),  
    .PAdr(PreLSUPAdrM),  
    .VAdr(IEUAdrM),  
    .PMPCFG_ARRAY_REGW, .PMPADDR_ARRAY_REGW);
```

# Spacing and Indentation

- **Indent by two spaces** for each level of nesting.
- **Indent using spaces** instead of tabs.
- **Align signal declarations** within a block.
- Leave a **space around operators** and **after if/case/for** statements.
- **Avoid space before** semicolons, commas, closing parentheses, and open parentheses in module instantiations, and inside bus width declarations.
- **Only use begin and end** when more than one statement is required in a block.
- Pack the **begin statements on the same line** where feasible.
- Limit lines to a maximum of **95 characters**
- Use **blank lines sparingly** to logically separate portions of code.
- Use **banner comments sparingly** to separate major portions of code in a complex module when using hierarchy isn't a good alternative.

# Synchronous Design

## Use synchronous sequential design:

- Every component should be: a positive edge-triggered flip-flop, a standard memory, or combinational logic.
- All components share common clock called clk.
- Avoid latches, negative edge-triggered flip-flops, and asynchronous components.
- Exceptions should only occur when essential (e.g., at an interface with an asynchronous peripheral)

## Instantiate memories and flip-flops using modules:

- Facilitates identifying # of state bits
- Provides a consistent built-in delay for simulation
- Enables swapping out synchronous/asynchronous reset, scan, or low-power features
- **Exception:** FSM state registers use enumerated state types



# Modules

- Each module in its own file; **file name = module name**
- Module **name** immediately followed by “(“
- Input and output ports **start on same line** as module name - unless parameterized
- **For parameterized modules:**
  - “(“ and parameters go on same line as module declaration.
  - Input and output ports go on subsequent lines, indented by two spaces
  - Place the closing ); on the same line with the last port declaration.
- **One input or output keyword on a single line** in module declaration; ports with the same polarity (input or output) and width are declared on the same line
- **Align text horizontally**

# System

- Use **behavioral** coding style for **leaf** cells including generic blocks and control blocks.
- Use **structural** coding style for **datapath** blocks.
- Use **hierarchy** so that modules remain small and easy to understand.
- Avoid programming constructs that obscure the hardware being implied.

# Configurable Hardware

- Define **generic configurable** modules where appropriate.
- Use ``define` to define **global parameters** in a `wally-config.vh` file included by all modules.
- Use `#parameter` to define **parameters for individual modules**.
- **Module interfaces should remain the same** whether or not a feature is enabled.
- **Omit** the optional `generate/endgenerate` keywords around conditional generates and generate loops.
- When a **generate block** contains instance or signal declarations, **name the block with a colon** after the `begin` keyword.

# Comments

- **Place a banner comment at the beginning of each file.**
  - Filename, authors name and email, date. This gives you copyright.
  - Purpose of module
  - License (Wally uses SolderPad license, an Apache derivative).
- **Use comments to explain the big picture rather than restate what the code is doing.**

## **Bad Example:**

```
assign ab = ~a; // flip the bits
assign minusa = ab + 1; // add one
```

## **Good example:**

```
// Take the 2's complement to negate a
assign minusa = ~a + 1;
```

# About these Notes

**RISC-V System-on-Chip Design Lecture Notes**

**© 2025 D. Harris, J. Stine, R. Thompson, and S. Harris**

**These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.**