

RISC-V

System-on-Chip Design

Harris, Stine, Thompson, & Harris

**Chapter 7:
Pipelined Core**

Chapter 7 :: Topics

Pipelined Core


7.1 Single-Cycle Core

7.2 Pipelined RV32I Core


Simplified Pipelined Core

- **RV32I or RV64I**
- Assumes **ideal instruction & data memories**
 - IROM instruction read-only memory
 - DTIM: data tightly-integrated memory
- **No bus interface** (for external memory or peripherals)
- **Trivial branch predictor:** predicts not taken
- **No MDU** (multiply-divide unit)
- **No FPU** (floating-point unit)
- **No privileged unit, so:**
 - Always run in machine-mode (M-Mode)
 - No traps
 - No virtual memory
 - Doesn't support CSRs


Simplified Pipelined Core

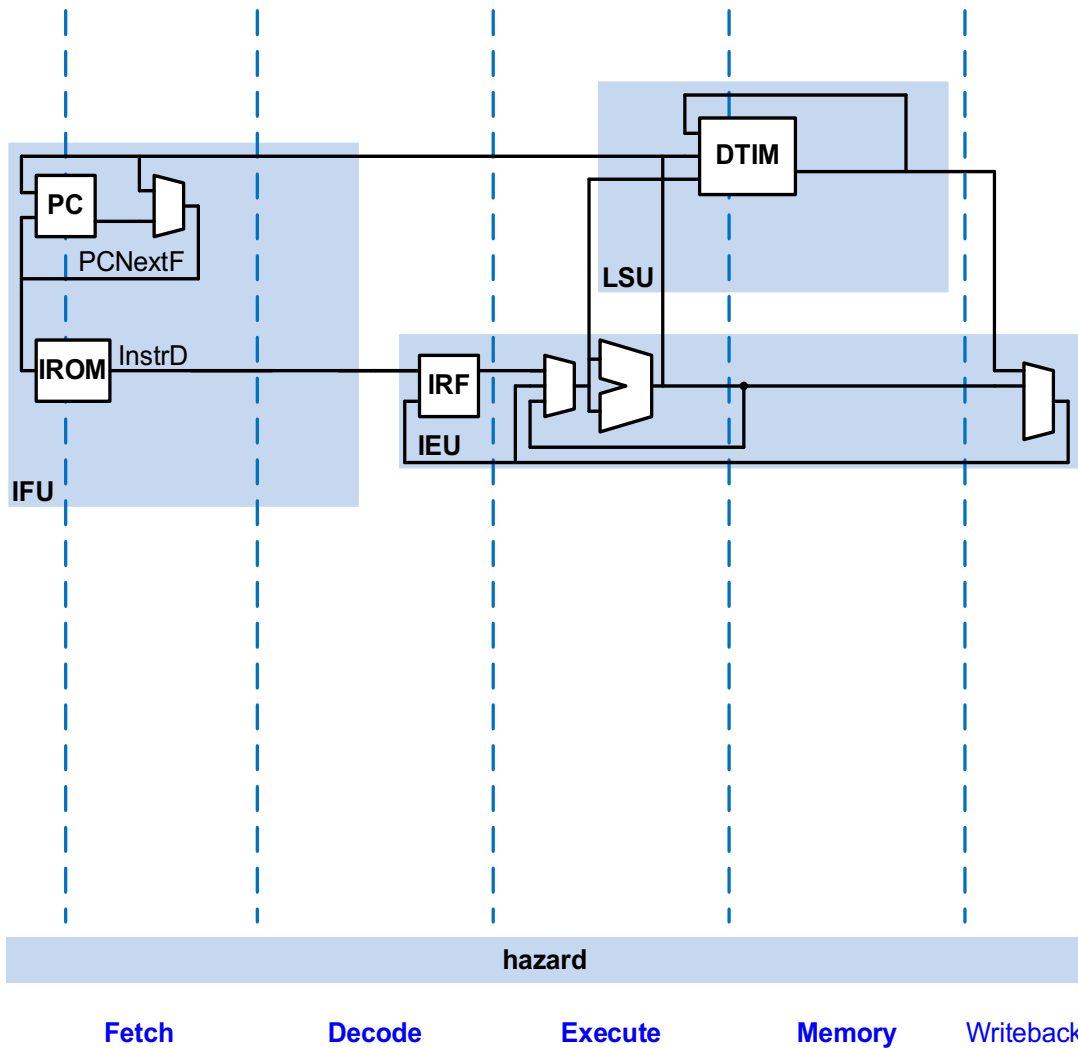

Simplified Pipelined Core

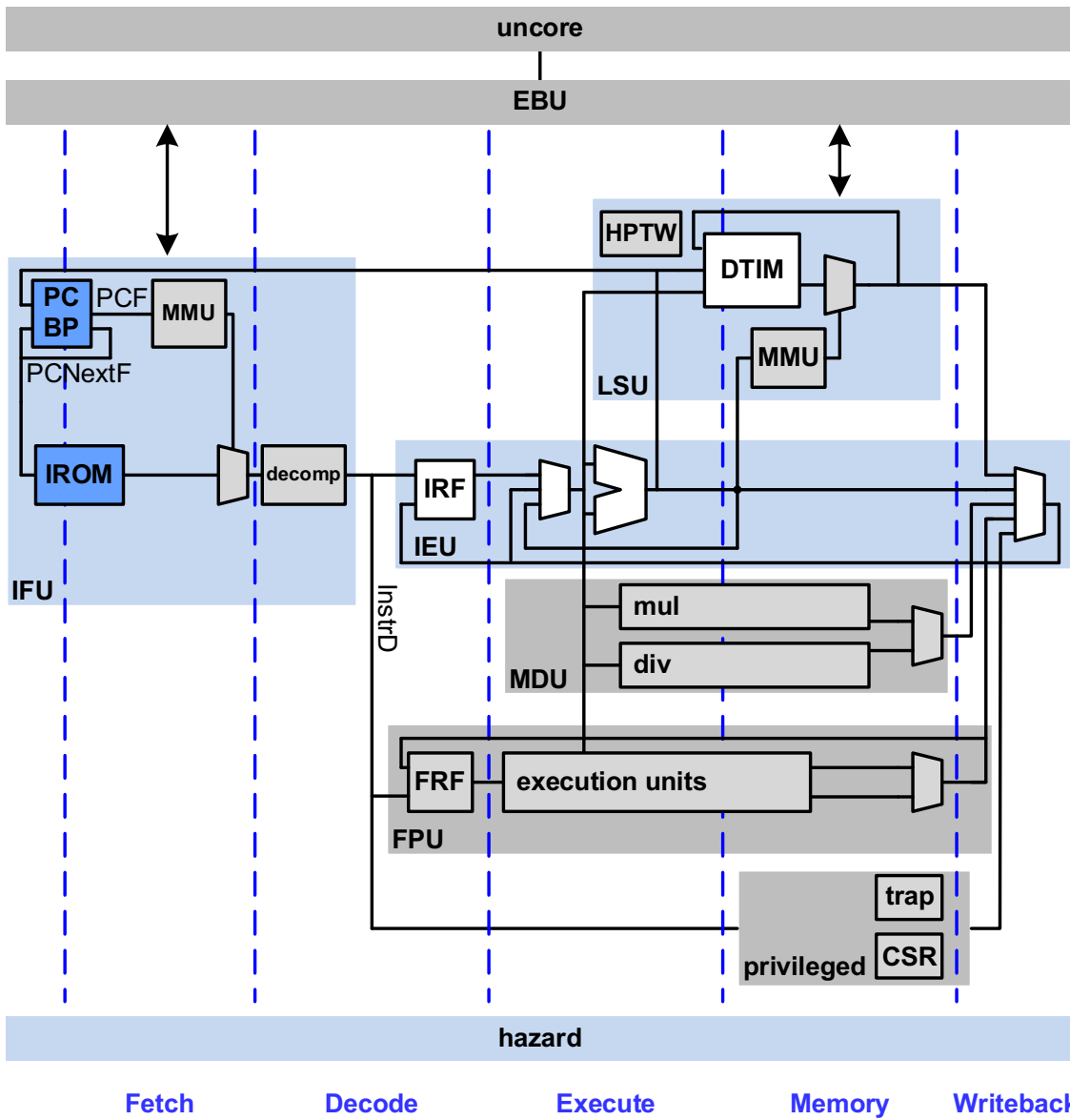


Simplified Pipelined Core

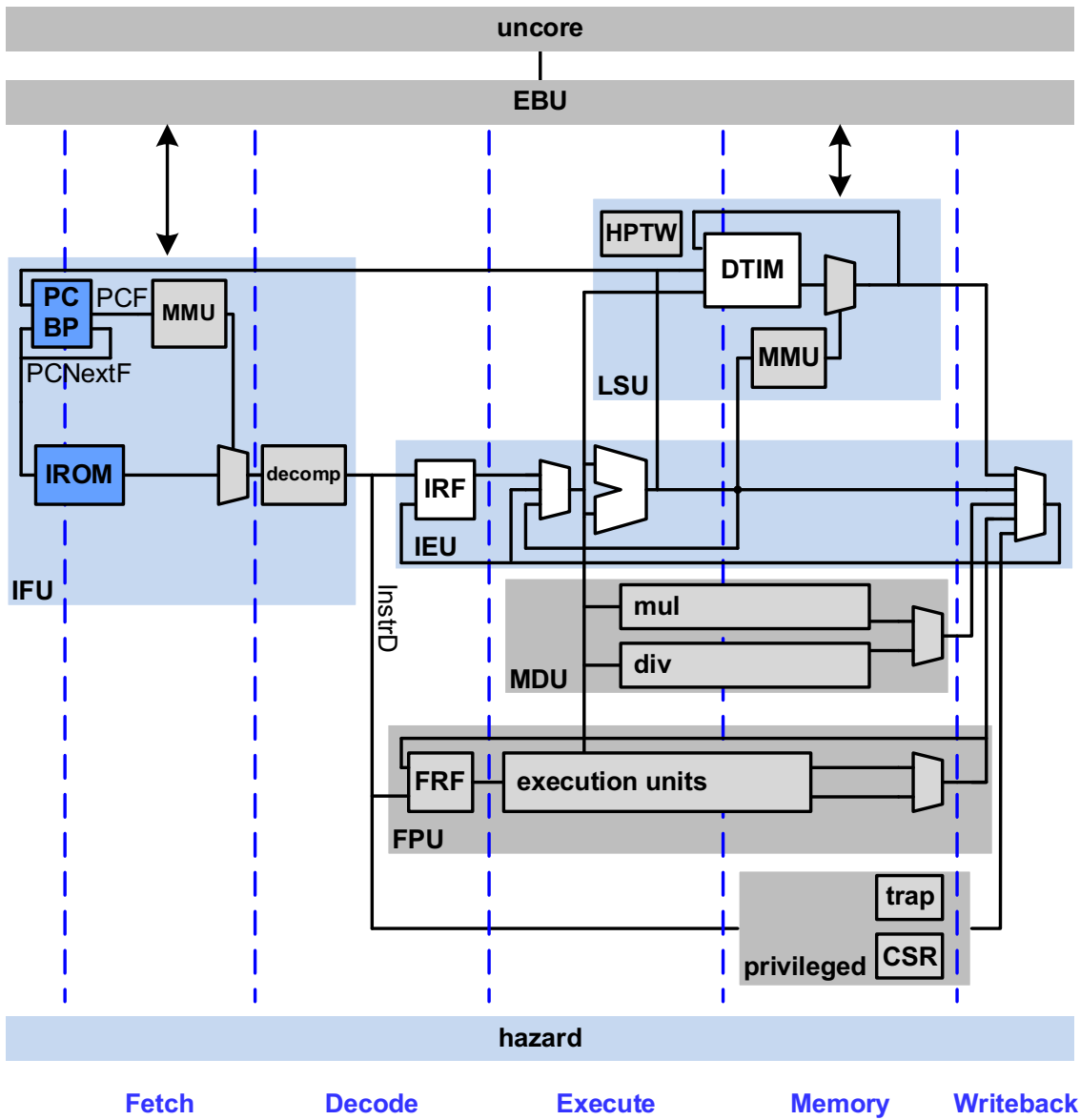

Chapters:

- **8 – PRIV:** Privileged Unit
- **9 – EBU:** External Bus Unit
- **10 – Cache**
- **11 – MMU:** Memory Management Unit
- **12 – LSU:** Load/Store Unit
- **13 – IFU:** Instruction Fetch Unit, branch predictors
- **14-19 – Extensions:**
 - **14 – C:** Compressed
 - **15 – M:** Multiply/Divide
 - **16 – FPU:** Floating-Point
 - **17 – AMO:** Atomic
 - **18 – B/Zk*:** Bit Manip & Crypto
 - **19 – Other Extensions**
- **20 – Peripherals**

Simplified Pipelined Core

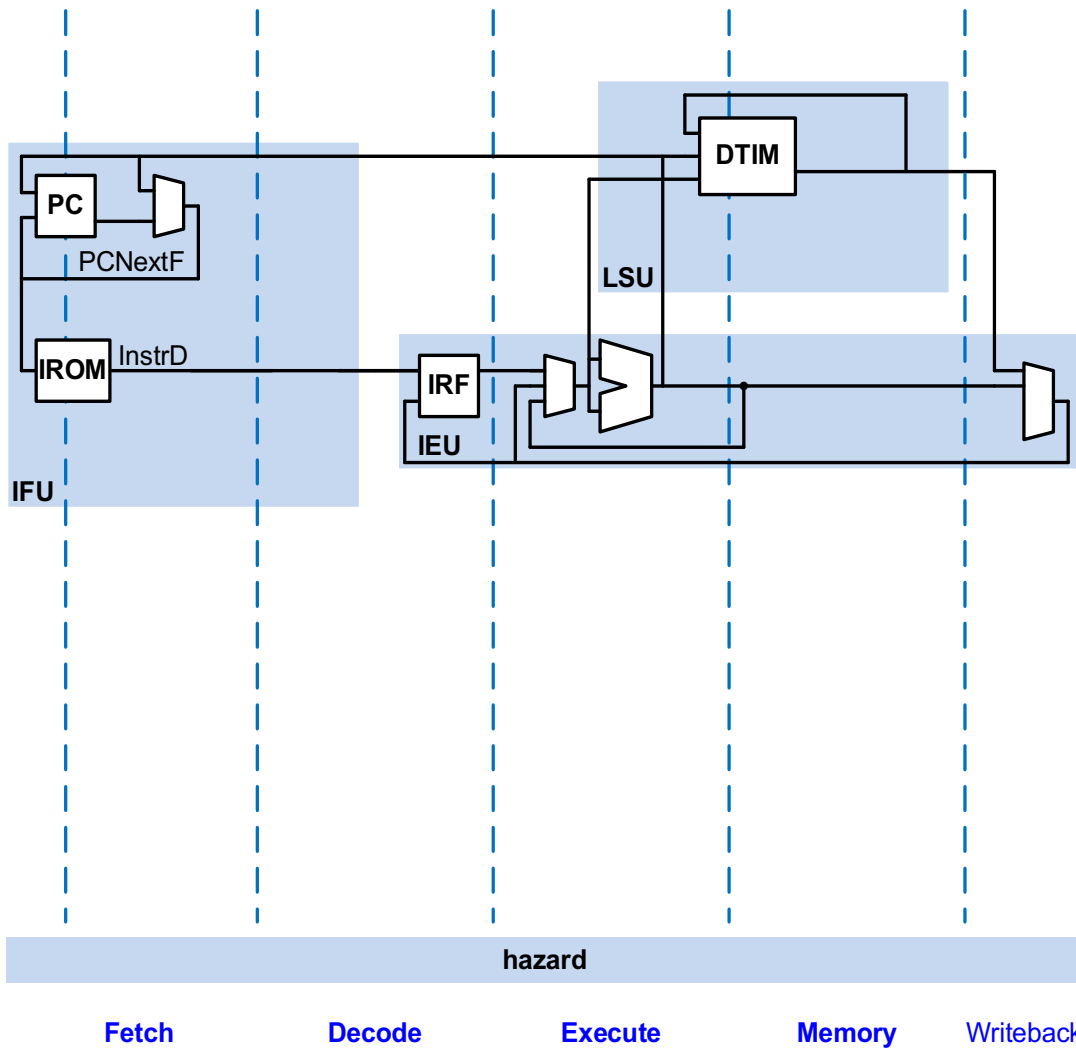

Supports RV32I / RV64I Instructions

Category	Op	Format	RV32I/RV64I	RV64I Extra
R-Type ALU	51 / 59	R	add, sub, and, or, xor, sll, srl, sra, slt, sltu	addw, subw, sllw, srlw, sraw
I-Type ALU	19 / 27	I	addi, andi, ori, xori, slli, srli, srai, slti, sltiu	addiw, slliw, srliw, sraiw
Loads	3	I	lw, lh, lhu, lb, lbu	ld, lwu
Stores	35	S	sw, sh, sb	sd
Branches	99	B	beq, bne, blt, bge, bltu, bgeu	
Jump and Link	111	J	jal	
Jump and Link Register	103	I	jalr	
Load Upper Immediate	55	U	lui	
Add Upper Immediate PC	23	U	auipc	


Single-Cycle → Pipelined Core

- Start by developing a single-cycle core
- Then convert it into a pipelined core

Chapter 7: Pipelined Core

Single-Cycle Core

Simple Single-Cycle Core from Ch. 2

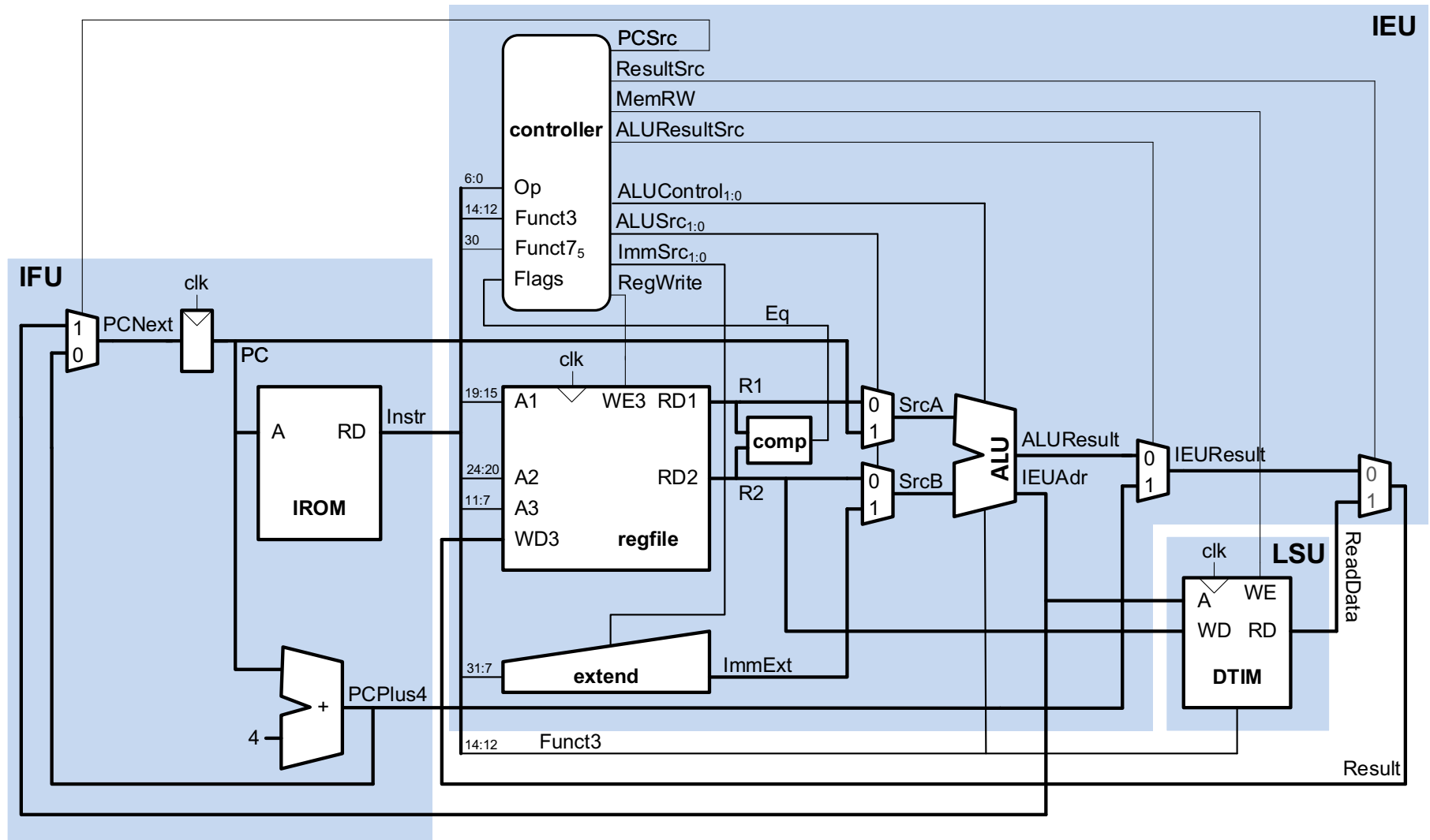

Supports: add, sub, and, or, slt, addi, andi, ori, slti, lw, sw, beq, jal

Extend Simple Core From Ch. 2


Support all RV32I/RV64I Instructions:

- More R- and I-type ALU instructions, including RV64's W instructions, which operate on 32-bit values
- Byte, half-word, and double-word loads and stores
- More flavors of branches
- Upper immediate instructions: `lui` and `auipc`
- Jump and link register: `jlr`

Baseline vs. New Instructions


Category	Op	Format	RV32I/RV64I	RV64I Extra
R-Type ALU	51 / 59	R	<code>add, sub, and, or, xor, sll, srl, sra, slt, sltu</code>	<code>addw, subw, sllw, srlw, sraw</code>
I-Type ALU	19 / 27	I	<code>addi, andi, ori, xori, slli, srli, srai, slti, sltiu</code>	<code>addiw, slliw, srliw, sraiw</code>
Loads	3	I	<code>lw, lh, lhu, lb, lbu</code>	<code>ld, lwu</code>
Stores	35	S	<code>sw, sh, sb</code>	<code>sd</code>
Branches	99	B	<code>beq, bne, blt, bge, bltu, bgeu</code>	
Jump and Link	111	J	<code>jal</code>	
Jump and Link Register	103	I	<code>jalr</code>	
Load Upper Immediate	55	U	<code>lui</code>	
Add Upper Immediate PC	23	U	<code>auipc</code>	

Extended Simple Single-Cycle Core

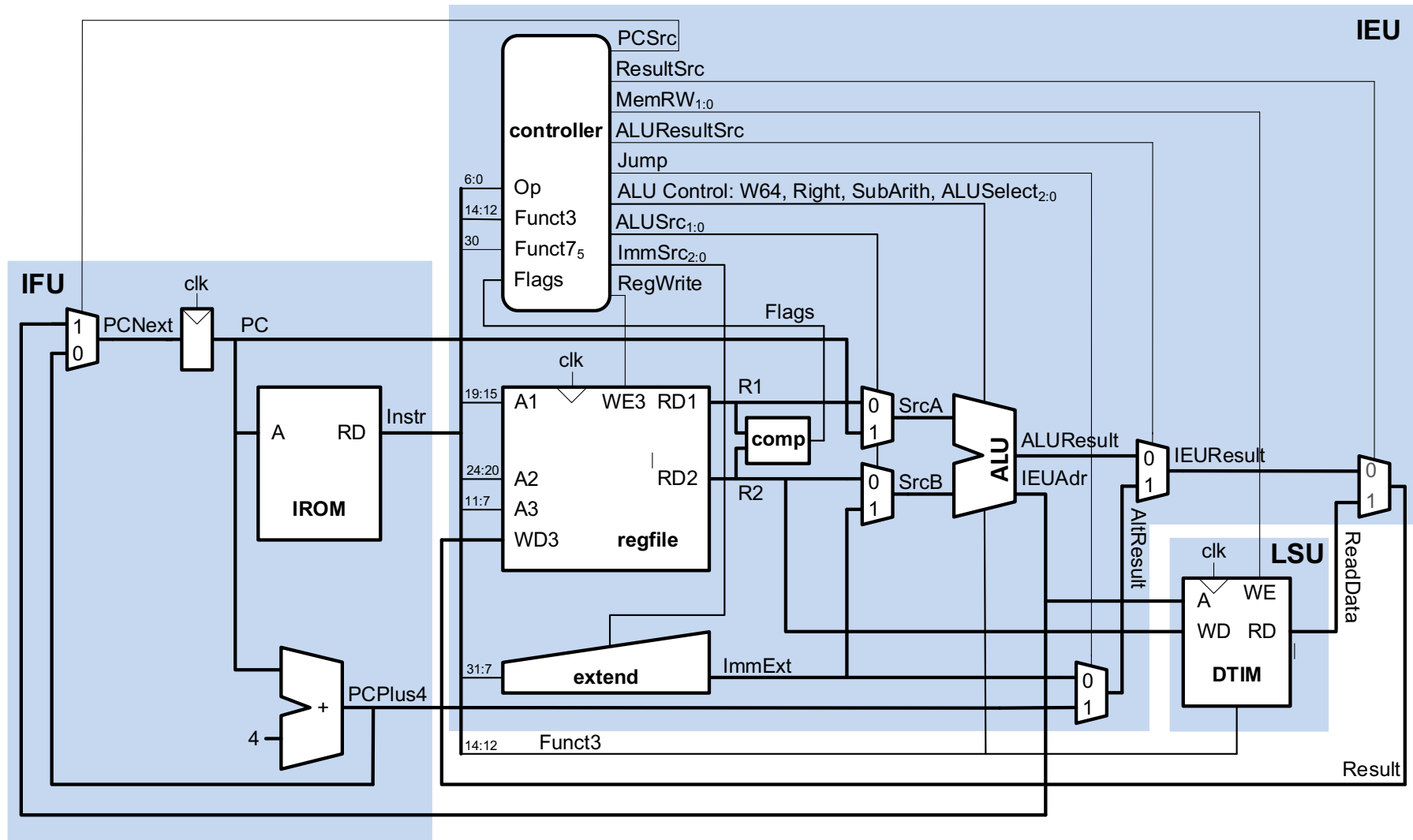

Enhancements

- **Configurable datapath:**
 - XLEN = 32 or 64 bits (for RV32 or RV64)
- **ALU enhanced:**
 - Supports **additional operations**
 - xor, set less than unsigned, shifts
 - Has an **extra bit of ALUControl** to specify RV64's RW/IW instruction
 - e.g. addw and addiw
- LSU adds circuitry for **subword loads and stores**
- Comparator generates **more flags**: equal, less than, less than unsigned (to handle all the flavors of branches)
- Extender enhanced to support **U-format** instructions
- The controller adds entries for the **new instruction categories**: jalr, lui, and auipc.

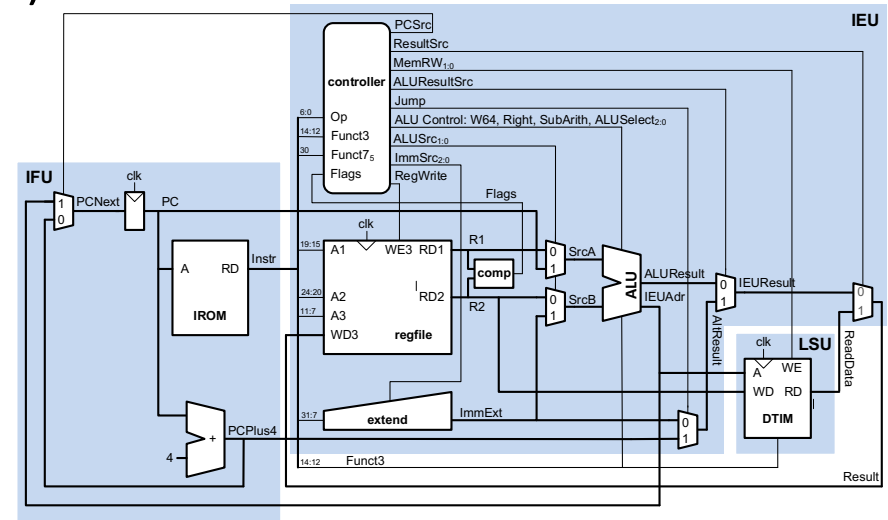

Architectural State

- **PC** (program counter)
- **Integer registers** (x1 - x31)

Immediate Encodings & Extensions

Instruction Bits

Immediate bit	11 10 9 8 7 6 5 4 3 2 1 0	rs1	funct3	rd	I S B U J	
	11 10 9 8 7 6 5	rs2	rs1	funct3 4 3 2 1 0		
	12 10 9 8 7 6 5	rs2	rs1	funct3 4 3 2 1 11		
	31 30 29 28 27 26 25 24 23 22 21 20	19 18 17 16 15 14 13 12				rd
	20 10 9 8 7 6 5 4 3 2 1 11	19 18 17 16 15 14 13 12				rd
31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0						
Instruction bit						

Immediate Extension


Instruction Bit	31	30:25	24:21	20	I S B U J	
	imm[11]		imm[10:0]			
	31	30:25	11:8	7		
	imm[11]		imm[10:0]			
	31	7	30:25	11:8		0
	imm[12]		imm[11:1]			
31	30:20	19:12	0			
imm[31:12]		0				
31	19:12	20	30:25	24:21	0	
imm[20]		imm[19:1]		0		
31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0						
ImmExt Bit						

12-, 13-, 21-, or 32-bit immediates

Immediate Extensions

ImmSrc	ImmExt	Type	Description
000	{{20{Instr[31]}}, Instr[31:20]}	I	12-bit signed
001	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}	S	12-bit signed
010	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}	B	13-bit signed
011	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}	J	21-bit signed
100	{Instr[31:12], 12'b0}	U	32-bit signed


Immediate Extension

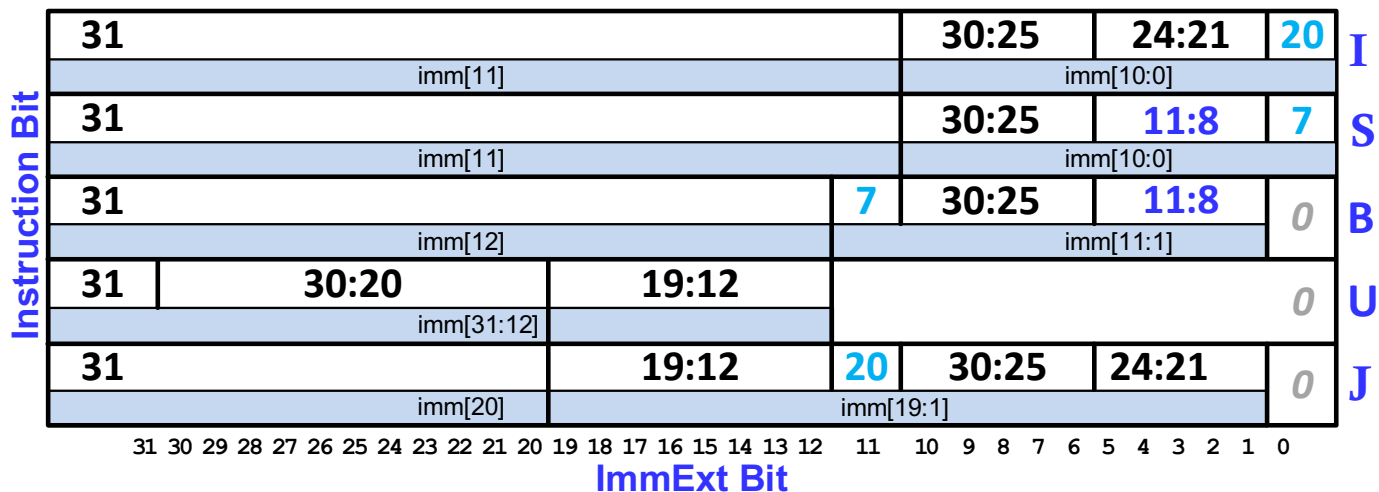

Arithmetic Circuitry

- **ALU:** Perform an arithmetic, shift, or logical operation and address calculation
- **Comparator:** Compare two registers to produce flags used for branches
- **Incrementor:** Increment the PC by 4 to calculate the next PC


Arithmetic blocks

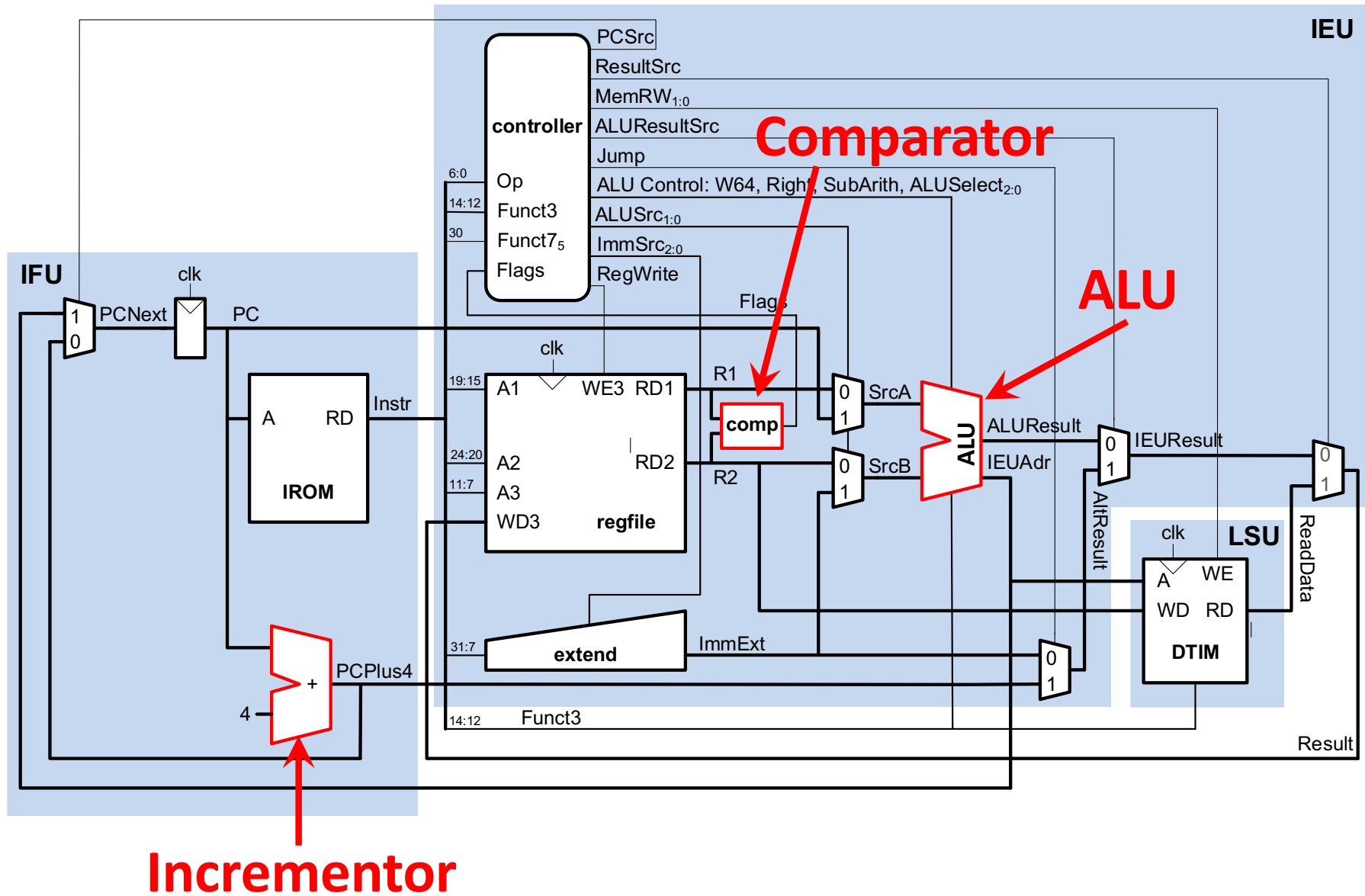

ALU Operations

Category	ALUResult	IEUResult	IEUAdr Destination	Comparator
R-Type ALU	R1 op R2	ALUResult	x	
I-Type ALU	R1 op ImmExt	ALUResult	x	
Loads/Stores	x	x	R1 + ImmExt → LSU	
Branches	x	x	PC + ImmExt → IFU	R1 cmp R2
jal	x	PCPlus4	PC + ImmExt → IFU	
jalr	x	PCPlus4	R1 + ImmExt → IFU	
lui	x	Imm	x	
auipc	PC + ImmExt	ALUResult	x	


ALU Schematic

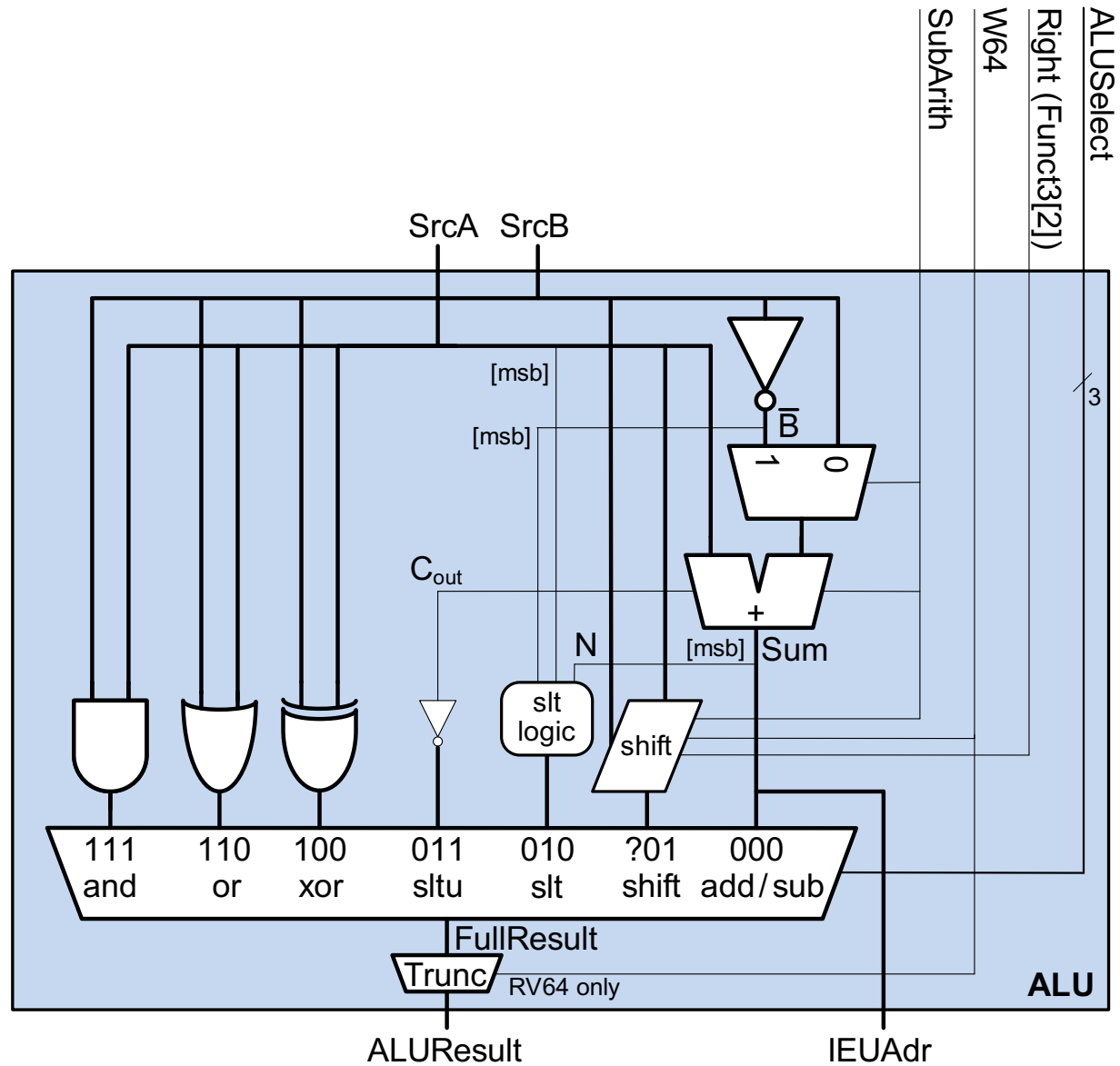

Adder Operations

- SubArith = 0: Adds
- SubArith = 1: Subtracts


$$\text{Sum} = A + \bar{B} + 1$$

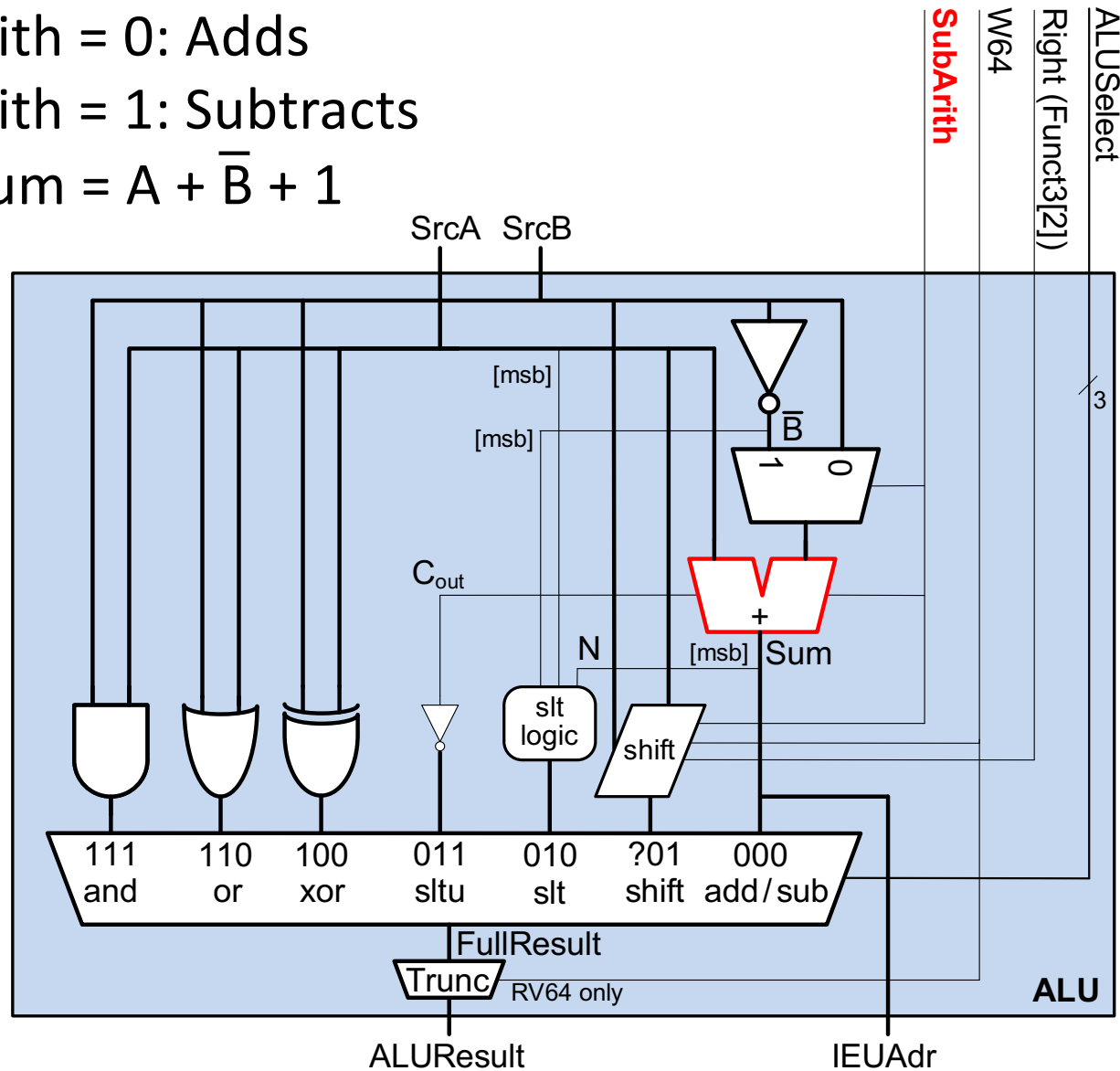

Shifter

- **Funnel shifter**
 - Source generator creates $2N-1$ bit signal Z from A
 - Mux tree funnels down to N -bit result Y

Shift Type	Z	Shift Amount
srl	{63'b0, $A_{63:0}$ }	k
sra	{{63{ A_{63} }}, $A_{63:0}$ }	k
sll	{ $A_{63:0}$, 63'b0}	$\sim k$
srlw	{95'b0, $A_{31:0}$ }	k
sraw	{64'b0, {31{ A_{31} }}, $A_{31:0}$ }	k
sllw	{32'b0, $A_{31:0}$, 63'b0}	$\sim k$

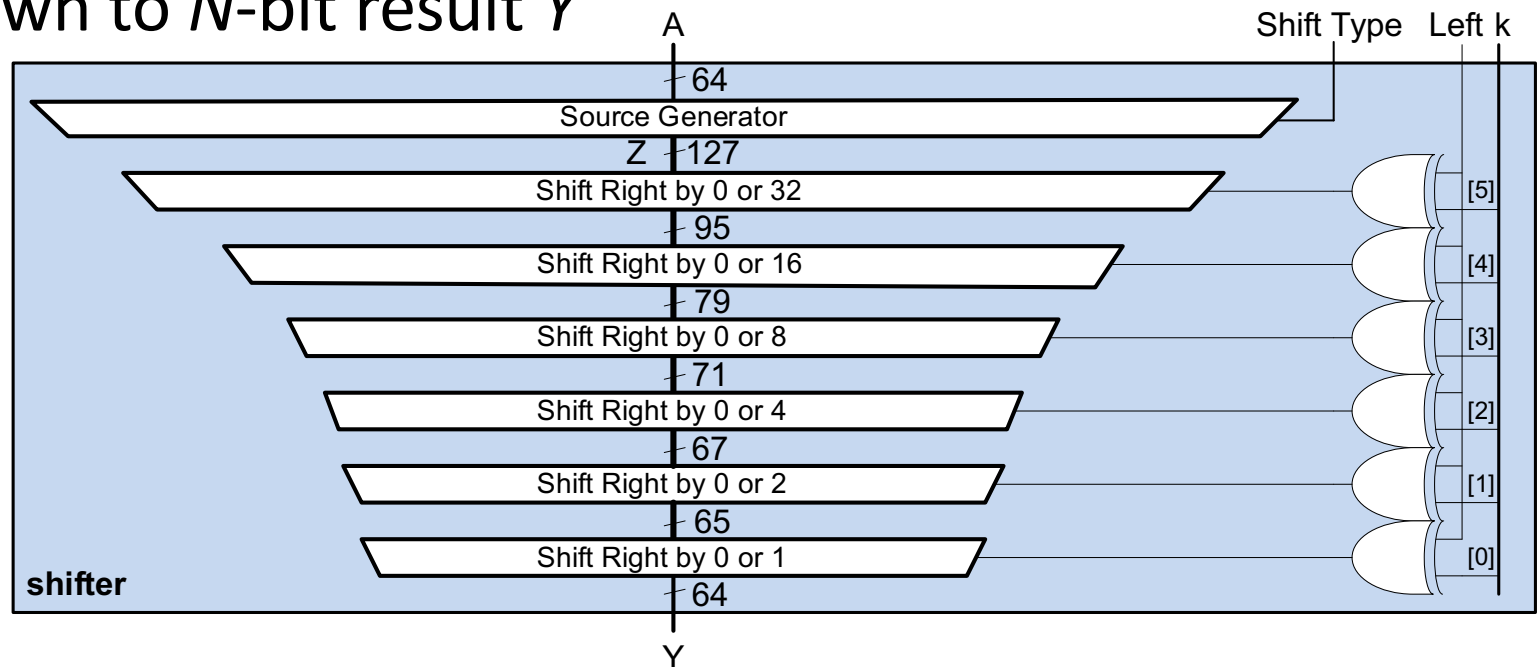


Comparator

- **Handles eq, lt, ltu**
 - Use signed for lt vs. unsigned for ltu

```
module comparator #(parameter WIDTH=64) (  
    input  logic [WIDTH-1:0] a, b, // Operands  
    input  logic sgnd,           // Signed operands  
    output logic [1:0] flags);    // Output flags: {eq, lt}  
  
    logic          eq, lt; // Flags: equal (eq), less than (lt)  
    logic [WIDTH-1:0] af, bf; // Operands with msb flipped when signed  
  
    // For signed numbers, flip most significant bit  
    assign af = {a[WIDTH-1] ^ sgnd, a[WIDTH-2:0]};  
    assign bf = {b[WIDTH-1] ^ sgnd, b[WIDTH-2:0]};  
  
    // Behavioral description gives best results  
    assign eq = (a == b); // eq = 1 when operands are equal, 0 otherwise  
    assign lt = (af < bf); // lt = 1 when a less than b (accounting for sign)  
    assign flags = {eq, lt};  
endmodule
```

Controller

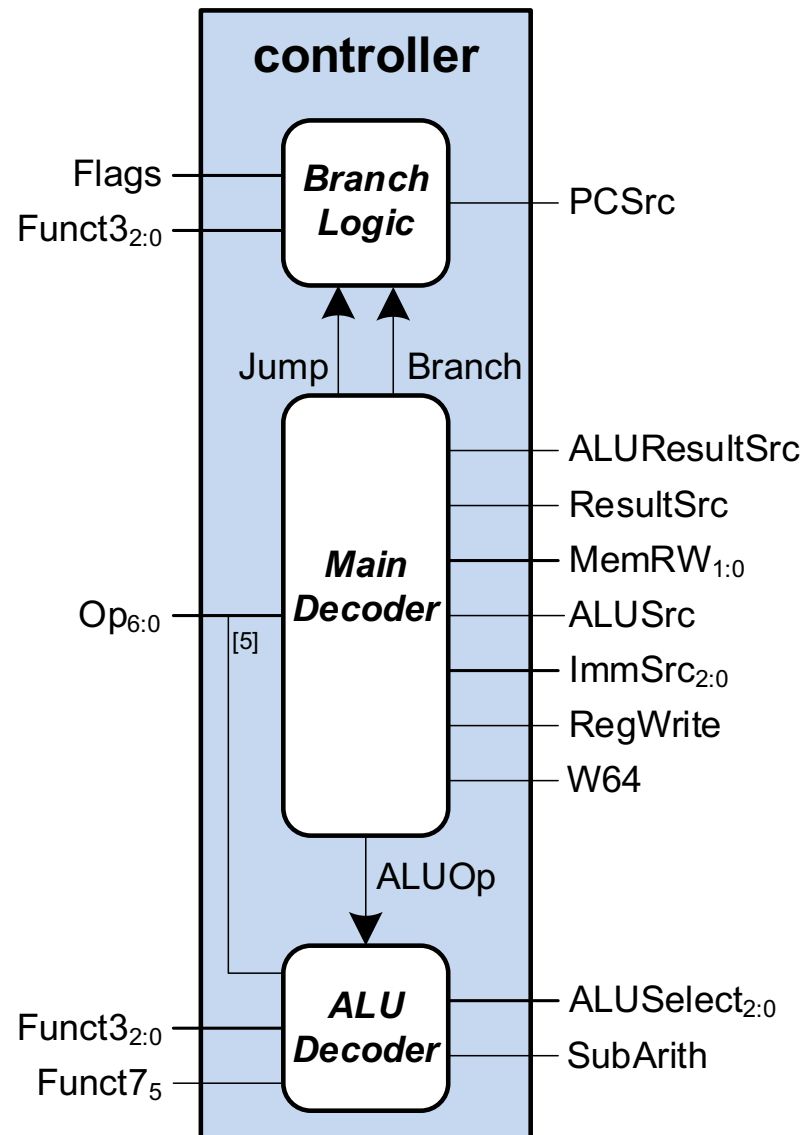


Main Decoder

Category	op	Branch	Jump	ALUSrc	ImmSrc	ALUOp	W64	ALUResultSrc	ResultSrc	RegWrite	MemRW
R-Type ALU	51	0	0	00	xxx	1	0	0	0	1	00
I-Type ALU	19	0	0	01	000	1	0	0	0	1	00
RW-Type ALU*	59	0	0	00	xxx	1	1	0	0	1	00
IW-Type ALU*	27	0	0	01	000	1	1	0	0	1	00
Loads	3	0	0	01	000	0	0	x	1	1	10
Stores	35	0	0	01	001	0	0	x	x	0	01
Branches	99	1	0	11	010	0	0	x	x	0	00
jal	111	0	1	11	011	0	0	1	0	1	00
jalr	103	0	1	01	000	0	0	1	0	1	00
lui	55	0	0	xx	100	x	0	1	0	1	00
auipc	23	0	0	11	100	0	0	0	0	1	00

* Required for RV64 only

Branch Logic


Type	Funct3	BranchTaken
beq	000	eq
bne	001	\sim eq
<undefined>	01x	0
blt	100	lt
bge	101	\sim lt
bltu	110	ltu
bgeu	111	\sim ltu

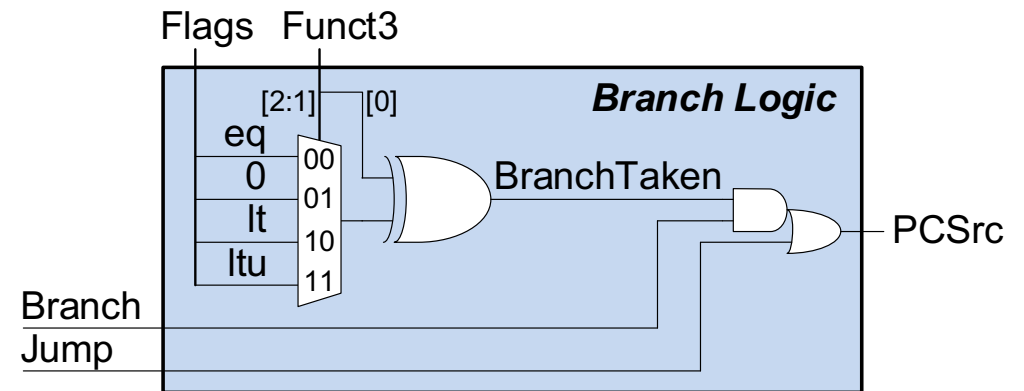

When $\text{Funct3}[0] = 1$, the flag inverts

- **Example:** for bne, $\text{funct3} = 001$, so
BranchTaken = \sim eq (i.e., $\text{eq XOR } 1 = \sim$ eq)

LSU: Load/Store Unit

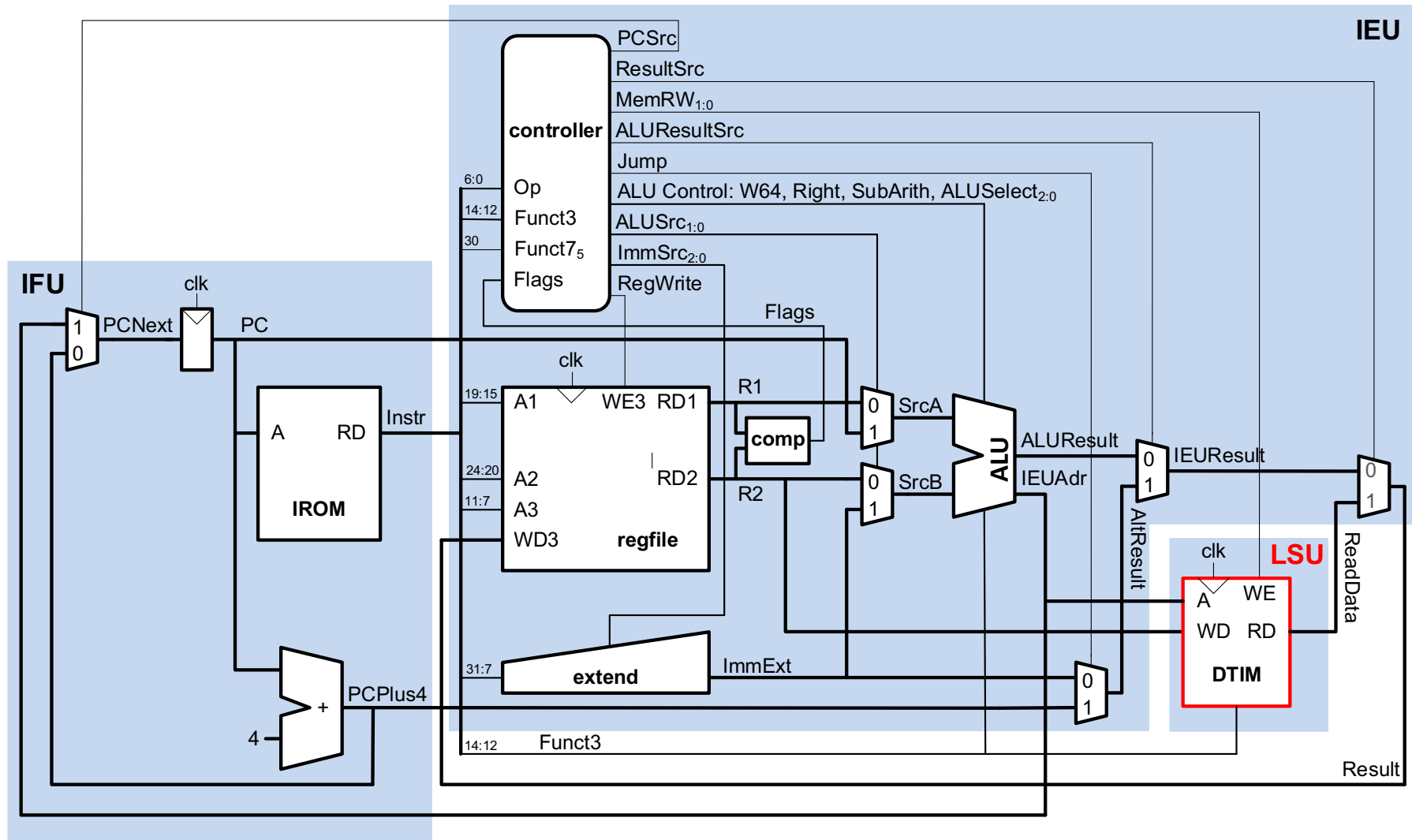


LSU: Load/Store Unit


Contains a **DTIM** (data tightly integrated memory)

- TIMs have single-cycle access
- Reads occur asynchronously
- Writes occur on rising edge of clock
- Subword reads:
 - DTIM reads full word
 - Extracts appropriate byte(s)
 - Places them in least significant byte(s) of result
 - Sign-extends result
- Subword writes:
 - DTIM replicates subword into all positions in its data write signal
 - Asserts byte write signals (that indicate which bytes within word to write)

Detailed LSU

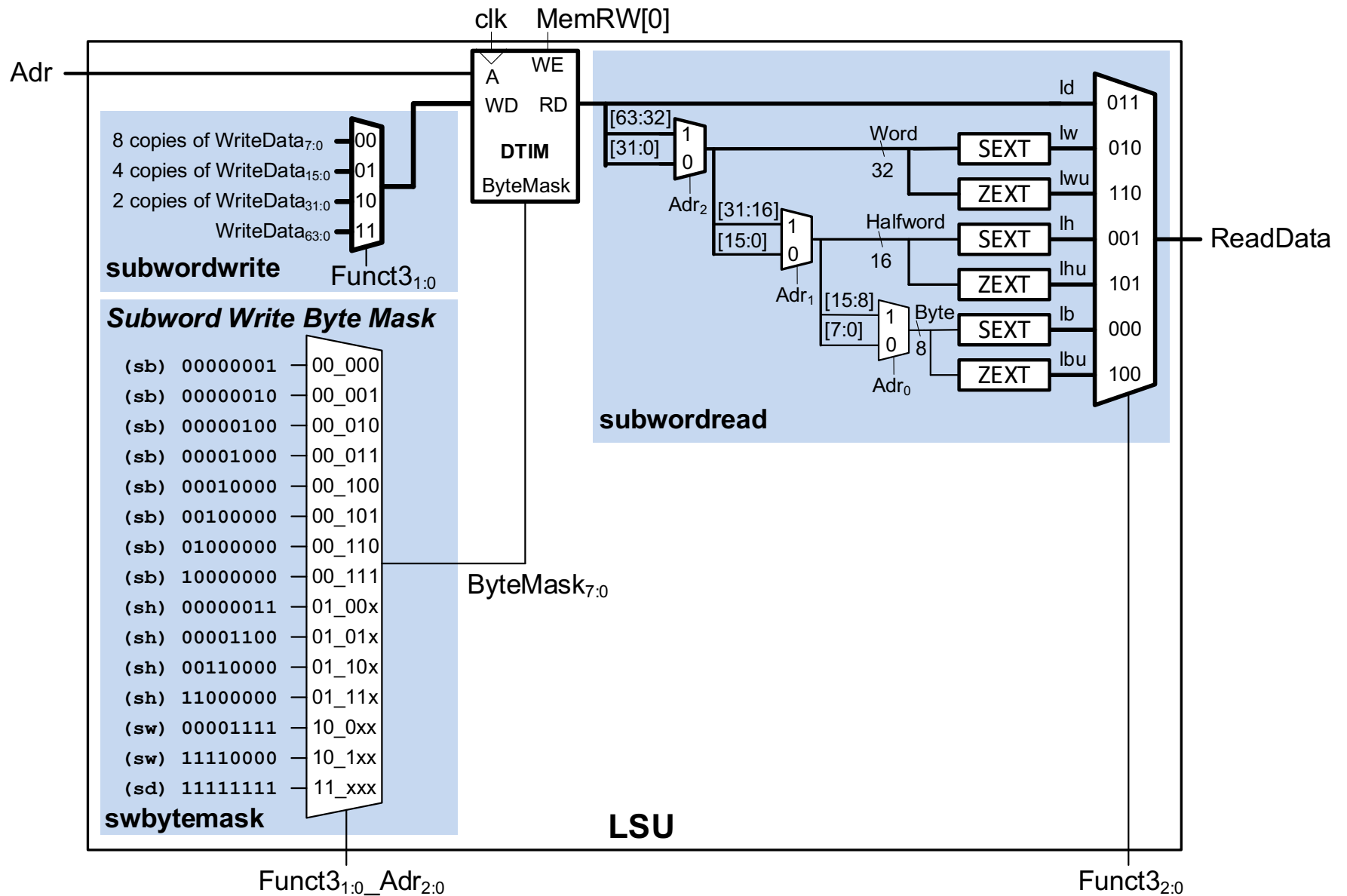

Example Execution

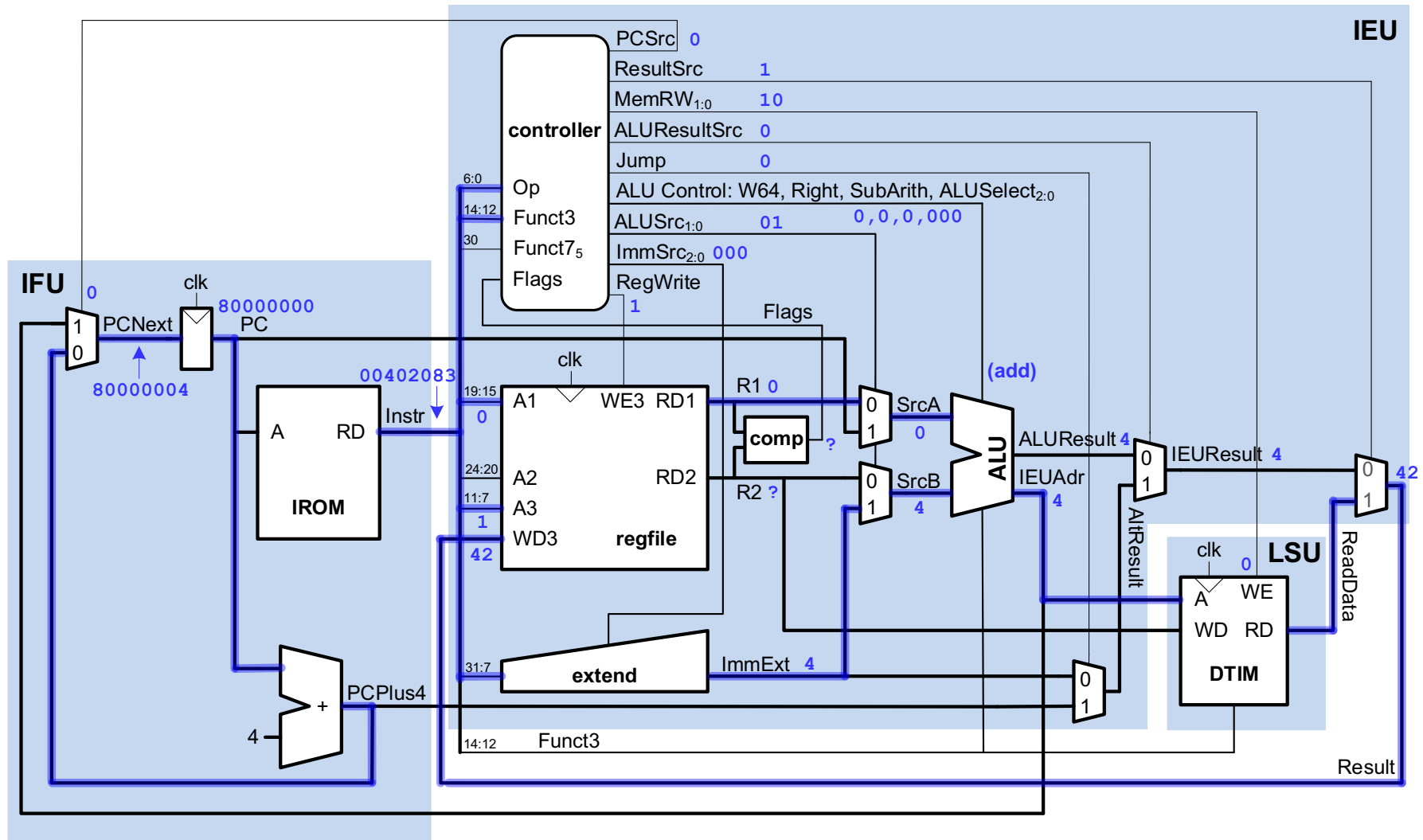


```
// address instruction    machine code
80000000    lw x1, 4(x0)    00402083
```


Chapter 7: Pipelined Core

Pipelined RV32I Core

Pipelined Processor



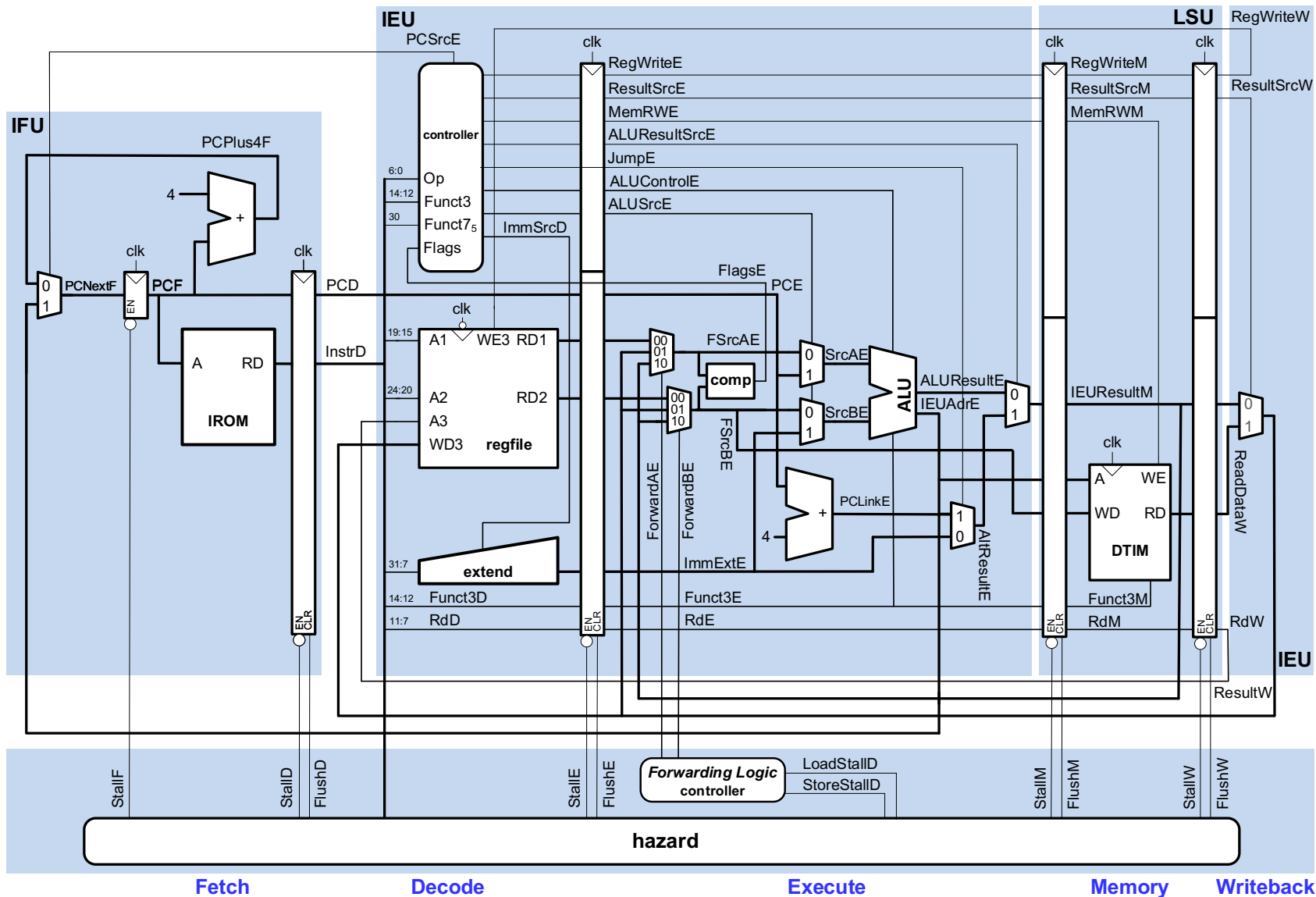


- Pipeline registers
- Hazard unit
- Bypass muxes

Synchronous Memories

- **Read may be synchronous or asynchronous** – memories with asynchronous reads are called “asynchronous memories”
- **Writes are always synchronous** (on rising or falling edge)
- **Synchronous (vs. asynchronous) memories:**
 - Smaller area
 - Higher Performance

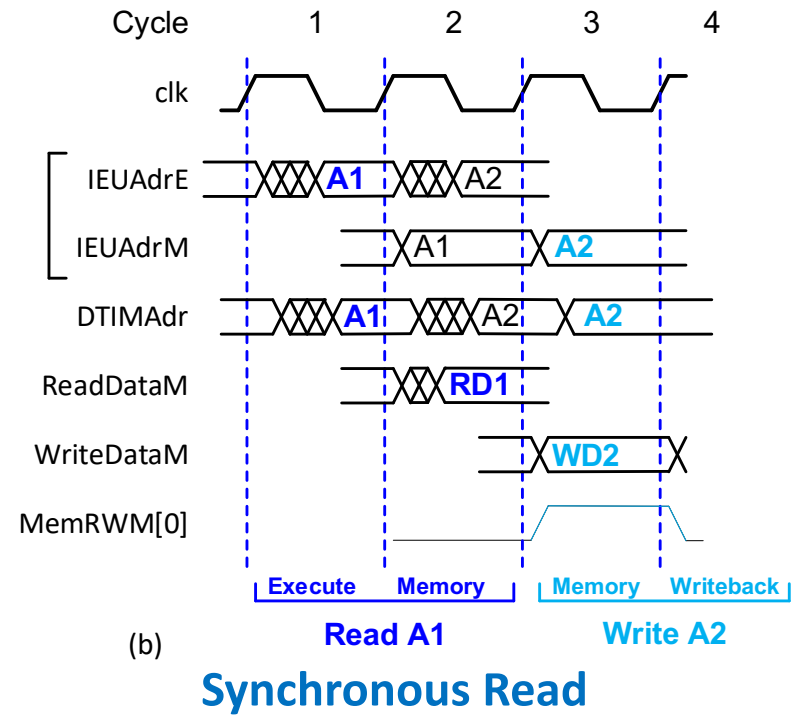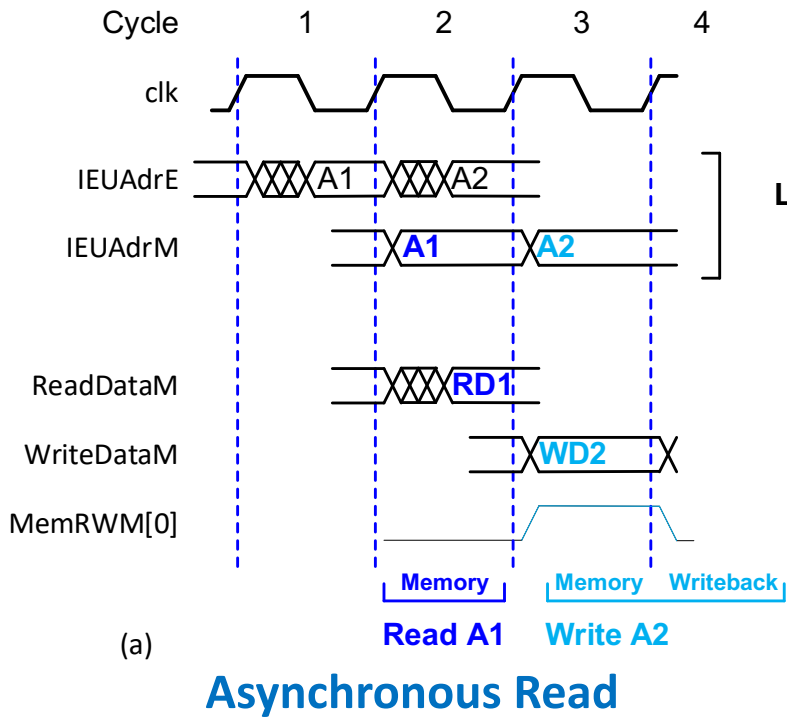 
Synchronous Memories: \downarrow w then SW



Synchronous IROM

- **Similar to DTIM:**
 - Address must set up before rising edge of Fetch stage
 - So IROM uses **PCNextF** (instead of PCNext)

Pipeline with Synch. Memories

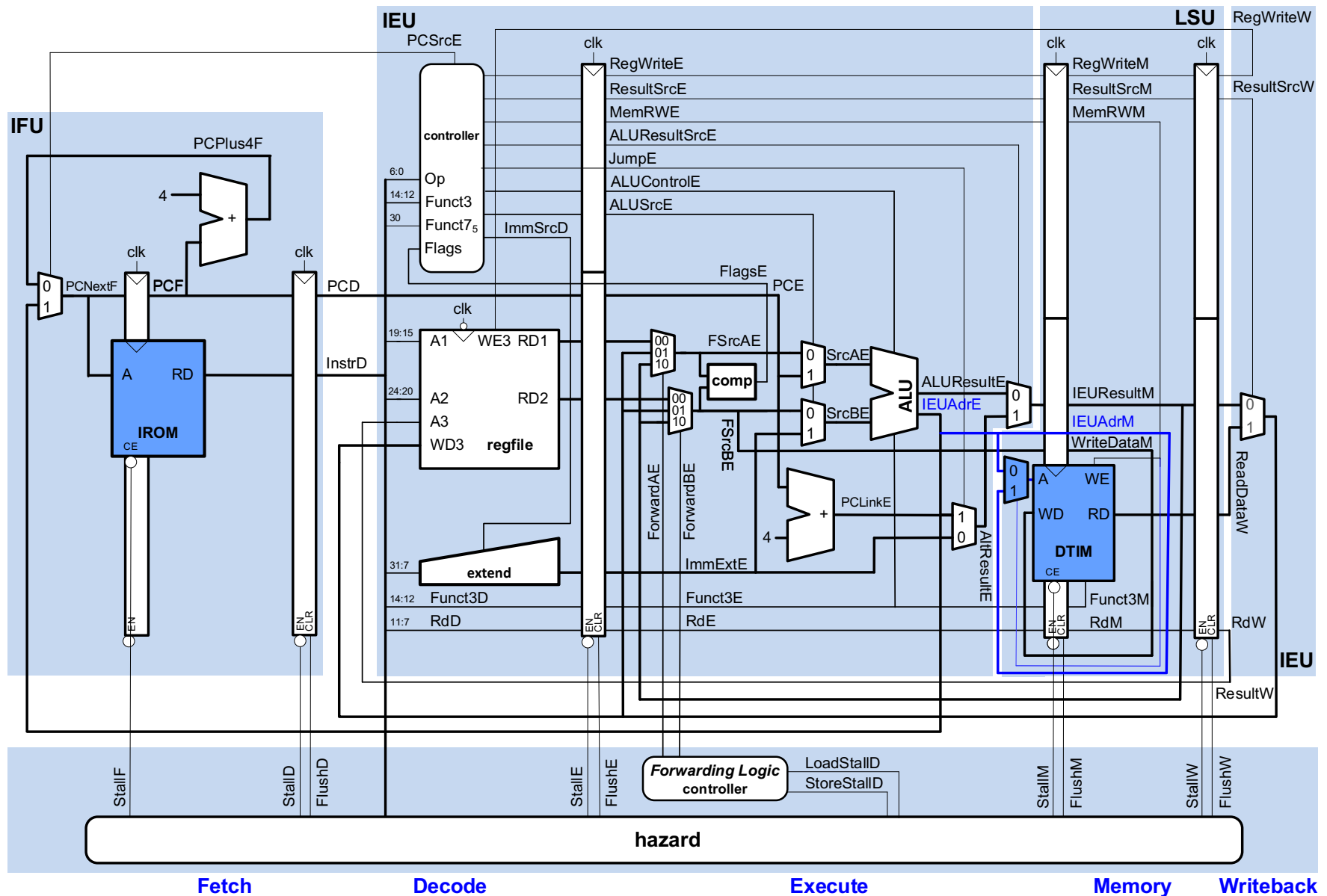

Chapter 7: Pipelined Core

Hazards


Types of Hazards

- **Data hazard:** Instruction needs a result from a previous instruction
- **Control hazard:** Next instruction address has not been calculated yet (because of branch or jump)

Hazard Resolution


- **Forward:** Send result from in-flight instruction
- **Stall:** Stop pipeline
- **Flush:** Discard incorrect instructions from pipeline

Program with Hazards

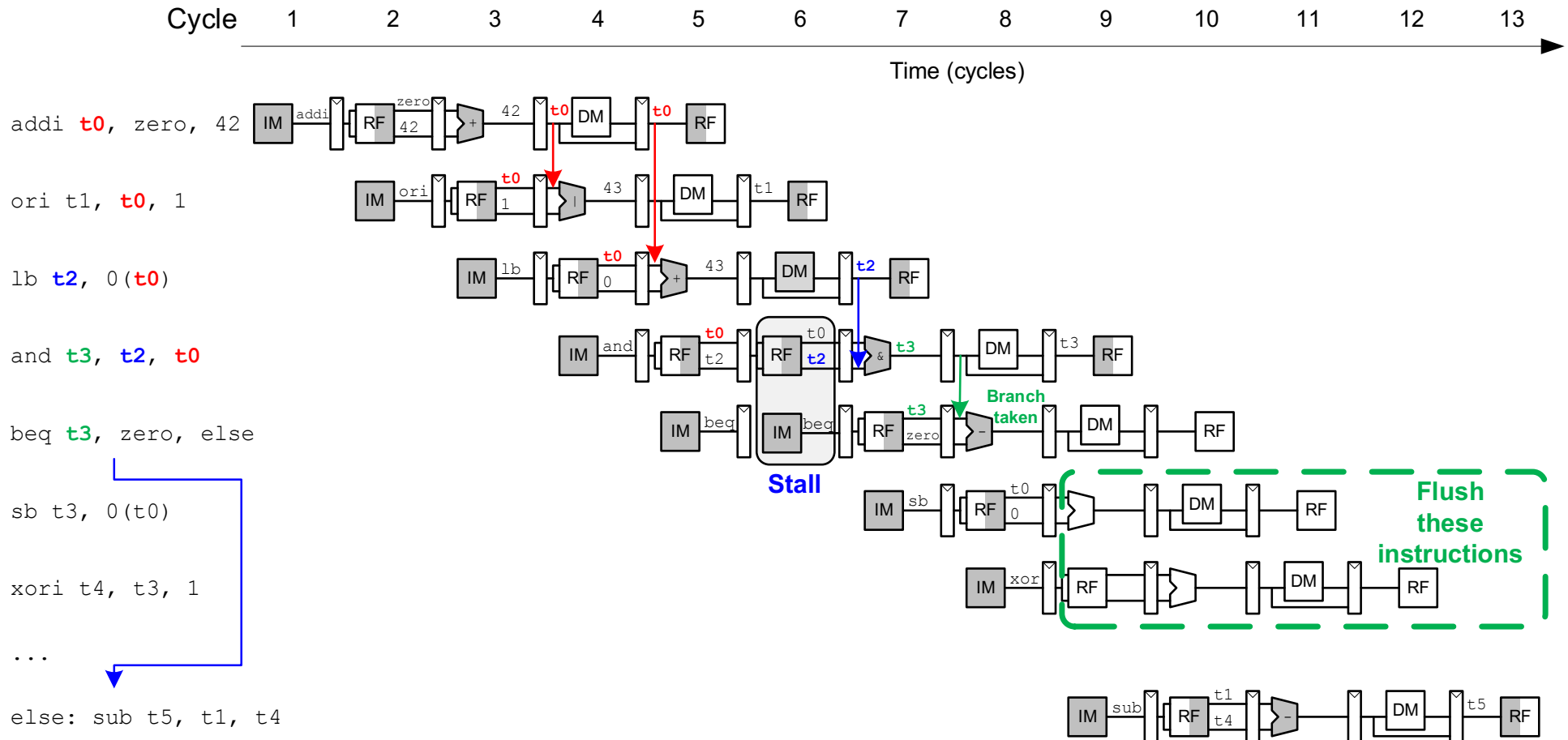

Data hazards: **t0** and **t2** accesses
Control hazard: **beq**

Pipeline Registers

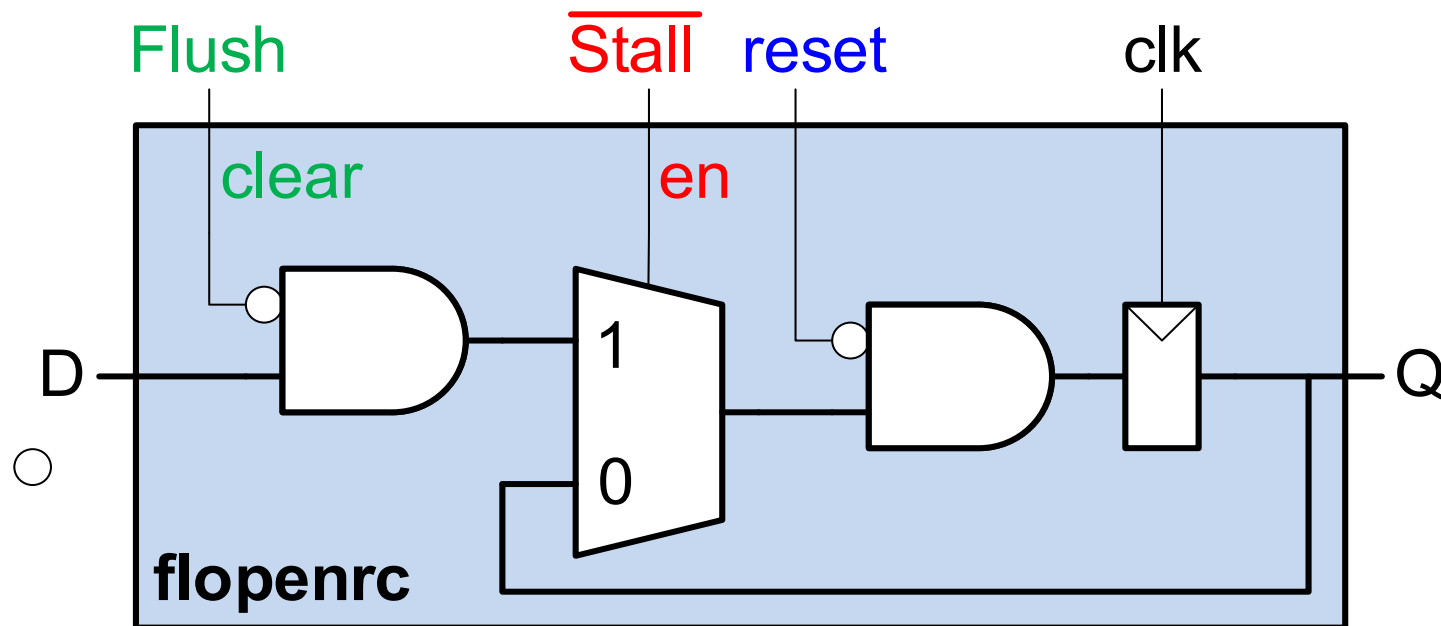

All pipeline registers have:


- **clear** (synchronous): connected to **Flush**
- **en**: connected to **Stall**
- **reset** (asynchronous): global reset

Forwarding Logic

- **Handles:**
 - **Forwards:** When source register in Execute stage same as destination register in Memory or Writeback stage
- The Forwarding Logic is inside the **controller unit**

Forwarding Logic

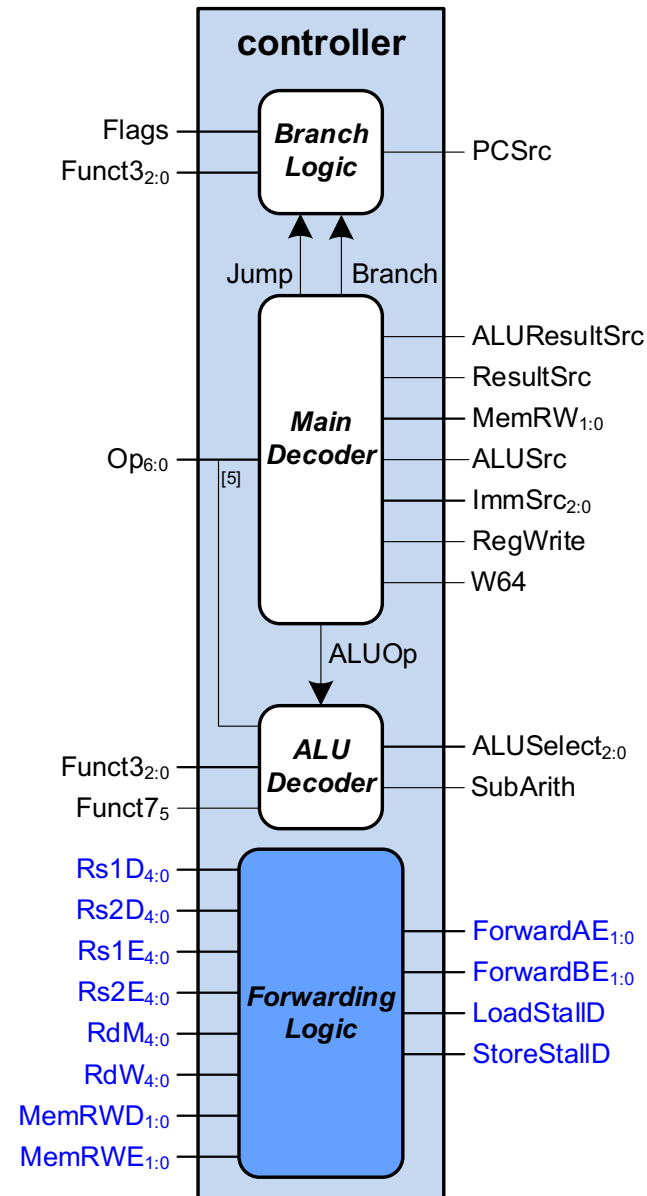- **Handles:**
 - **Forwards:** When source register in Execute stage same as destination register in Memory or Writeback stage
- The Forwarding Logic is inside the **controller unit**



Forwarding Logic

- **Handles:**
 - **Forwards:** Source register in Execute stage same as destination register in Memory or Writeback stage

Example: ForwardAE (for SrcA of ALU):

```
# mem stage
if      ((Rs1E == RdM) & RegWriteM) & (Rs1E != 0) ForwardAE = 10
# writeback stage
else if ((Rs1E == RdW) & RegWriteW) & (Rs1E != 0) ForwardAE = 01
# no forward
else                                          ForwardAE = 00
```

ForwardBE (for SrcB) is similar (replace Rs1E with Rs2E).

Hazard Unit

- **Handles:**
 - **Stalls:**
 - Load followed by use
 - Store followed by a load

Hazard Unit

- **Handles:**

- **Stalls:**

- **Load followed by use:** detected in Decode stage

- Load is in Execute stage:

- $$\text{MemRW}[1] = 1$$

- Either source register in Decode stage is same as Execute's destination register:

- $$\text{MatchDE} = (\text{Rs1D} == \text{RdE} \mid \text{Rs2D} = \text{RdE})$$

- Thus, $\text{LoadStallD} = \text{MemRWE}[1] \ \& \ \text{MatchDE}$

- **Store followed by a load:**

- $$\text{StoreStallD} = \text{MemRWE}[0] \ \& \ \text{MemRWD}[1]$$

Recall:

$\text{MemRW}[1] = 1$ for loads

$\text{MemRW}[0] = 1$ for stores

Hazard Unit

- Also includes flushes for control hazards:
 - PCSrcE = 1 for jumps or taken branches
 - So, when PCSrcE = 1, Decode and Execute stages must be flushed (on next cycle). Thus,

$\text{FlushDCause} = \text{PCSrcE}$ $\text{FlushECause} = \text{PCSrcE}$
--

Summary: Forwarding & Hazards

Forward:

```
if      ((Rs1E == RdM) & RegWriteM) & (Rs1E != 0) ForwardAE = 10
else if ((Rs1E == RdW) & RegWriteW) & (Rs1E != 0) ForwardAE = 01
else                                         ForwardAE = 00
```

```
if      ((Rs2E == RdM) & RegWriteM) & (Rs2E != 0) ForwardBE = 10
else if ((Rs2E == RdW) & RegWriteW) & (Rs2E != 0) ForwardBE = 01
else                                         ForwardBE = 00
```


Stall:

```
MatchDE      = (Rs1D == RdE | Rs2D == RdE) & (RdE != 0)
LoadStallD   = MemRWE[1] & MatchDE
StoreStallD  = MemRWE[0] & MemRWD[1]
```


Flush:

```
FlushDCause = PCSrcE
FlushECause  = PCSrcE
```

Hazard Unit Architecture

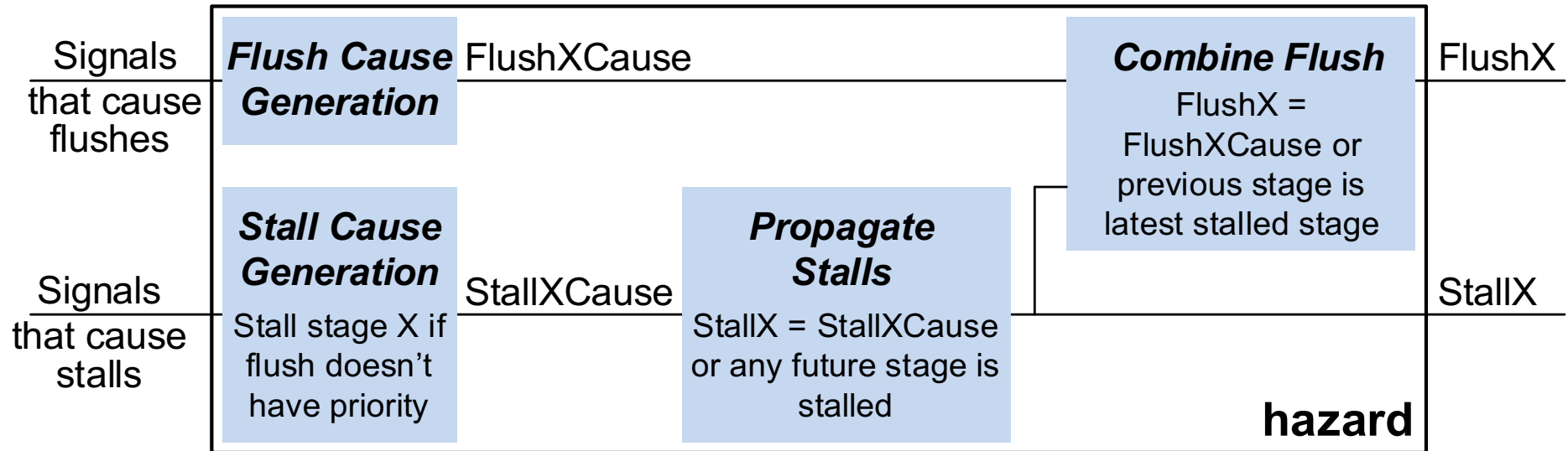

Stall and Flush Logic

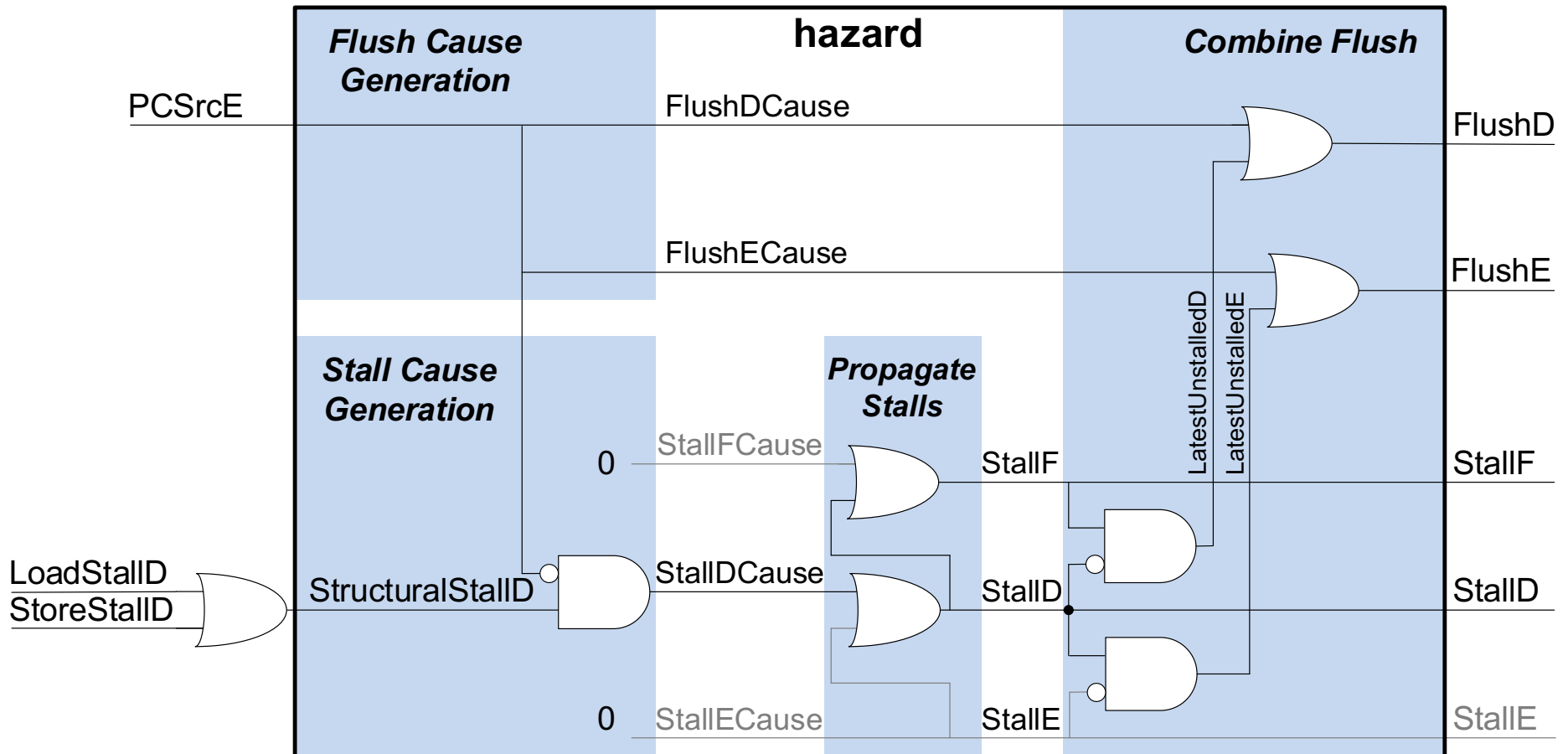

Pipelined Performance

$$\text{Execution Time} = \# \text{ instructions} \times \text{CPI} \times T_C$$

Example: CoreMark Benchmark

Type	# Instructions	% of Total Instructions	CPI
R- or I-type ALU	1,320,259	49.7%	1
Jumps	46,750	1.8%	3
Branches	588,905	22.2%	1.84
Loads/stores	698,738	26.3%	1.41
Total	2,654,652	100%	1.34

- **Branches:** 11% mispredicted (costs 2 more cycles to flush two fetched instructions)
 - So, branch CPI = $1 + 0.11 \times 2 = 1.22$
- **Jumps:** always take 3 cycles (1 to execute, 2 flushed). So, CPI = 3
- **40.1% of loads/stores** cause a stall (either a store followed by load or a load that is immediately used by next instruction)
 - So, load/store CPI = $1 + 0.40 \times 1 = 1.46$
- **Overall CPI:**
 $(0.5 \times 1) + (0.02 \times 3) + (0.222 \times 1.84) + (0.263 \times 1.41) = \mathbf{1.34}$

CoreMark's empirically reported CPI: **1.27**

About these Notes

RISC-V System-on-Chip Design Lecture Notes

© 2025 D. Harris, J. Stine, R. Thompson, and S. Harris

These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.