

Audio Spectrum Analyzer Final Report

Corey O'Connor
Josh Smallman

December 15, 2003

Abstract

Our final project was to build a simple audio spectrum analyzer. The device will take line-level stereo audio input and display the spectrum on a bank of LED arrays. There will be seven frequency bands for both the left and right channels for a total of 14 bands. The first major element of our system is the input processing section. This section is responsible for splitting the audio signal into the 14 bands with 7 parallel bandpass filters for each channel. This section then multiplexes the signals into a PIC through a set of logarithmic converters for sampling. The sampled values are then sent serially to the FPGA which drives a series of multiplexed LED arrays.

We successfully completed the PIC program, the input multiplexing, and the FPGA LED driver. We were unable to complete the bandpass filters for the input processing section. Instead we simplified the hardware to monitor amplitudes of 8 distinct stereo inputs. We also designed and built a custom PC board for our LED display.

Introduction

When working with audio it's important to have good feedback. The frequency spectrum of an audio signal is useful for finding which component frequencies might be too loud or too soft to in order to get a properly equalized and balanced audio source.. Having a stand-alone system to display the spectrum from standard audio sources is a useful tool for anybody working with audio.

Our system is composed of an input processing section, a PIC for sampling, and an FPGA configured as an LED display controller. Our initial plan for the input processing section would take a stereo input and first separate each channel into seven separate bands. Given a stereo signal this would of made a total of 14 bands. Each copy of the signal would have been processed by a set of bandpass filters and then logarithmic converters before being sampled by the PIC. The logarithmic converters would have converted the AC signal into a DC representation of the volume. Each channel would have had the same set of seven bandpass filters which would have been configured with center frequencies approximately equal to: 60 Hz, 120 Hz, 400 Hz, 1 kHz, 2.5 kHz, 6.25 kHz, and 16 kHz.

The system we actually built was designed to handle 8 separate stereo inputs instead of one input split into 7 frequency bands per channel. Instead of using logarithmic conversion to get the volume level we sampled the half-wave rectification to get the amplitude of the signals.

The PIC microcontroller is used to sample from each input 30 times a second. This means the PIC would have sampled at 420 Hz in order to sample 14 inputs at the desired rate. Since we actually built the system to handle 8 stereo inputs this means the PIC must sample at 480 Hz. The PIC is also responsible for controlling the multiplexing IC's since there are not enough physical connectors on the PIC's A-to-D port to handle more than 8 inputs at once. Once a given input has been sampled the value is sent over the serial line to the FPGA. The PIC samples to a 10 bit resolution, but only the top 8 bits are sent since this is more convenient and we only needed the top 4 bits for our bargraph-style display.

The FPGA is continuously multiplexing the LED arrays for the display where each LED array represents a value from the PIC. The LED arrays are driven in groups of two at a time: One array for the left channel, one for the right channel. After 8 FPGA clock cycles the next two LED arrays for the next two inputs are driven. This repeats indefinitely. Each value received over the serial line is written into a register file containing the current values for each input.

New Hardware

The PIC only has 8 analog inputs, and we needed 16. In order to sample from all 16 inputs we used two eight-channel analog multiplexers. These are essentially an SP8T solid state switch. The CS4051 set of chips implement this nicely for a cheap price. For our project we used the MC140551B (Which is equivalent to the CS4051). These worked well, except as side test revealed these are unsuitable for multiplexing the audio input directly. They had a frequency response that attenuated the higher frequencies significantly.

The bandpass filters were to be implemented using a set of active filters. We chose a resistor programmable universal filter IC. These are active filters that can operate as a several different types of filters. Exactly which filters an active filter IC implements depends largely on the manufacturer. There are several varieties available, but we chose the Mixed Signal Integration MSU2F. These are dual filter, switch-capacitor, resistor programmable IC's. They can implement lowpass, highpass, bandpass and allpass among other things. On each IC, both filter's center or cutoff frequency depends on the frequency of the clock input times some multiplier.

The MSU2F promised to be an extremely flexible chip. With a clock programmable center frequency we could use a single IC to implement several different bandpass filters. Simply changing the input clock would change the center frequency. Sadly the datasheet was inconsistent and very unclear. For instance, The symbol f_0 is used to represent a constant, the input for a clock multiplier setting, and the center frequency. In fact the input voltages for the clock were specified as 0 to 2.5 volts for dual supply on the datasheet, but should have been specified as -2.5 to 2.5 volts. Even with tech support from Mixed Signal Interactions we were unable to get the filters operating correctly. A better choice would have been to use the LMF100 from National Semiconductor, or one of the many similar chips from Maxim IC. The datasheets for both IC's are very clear and helpful.

Schematics

Figure 1 shows the schematic for a multiplexing circuit containing 2 channels of 8 LED arrays. Each single LED array consists of 10 LEDs, connected in a common-anode configuration. Each LED is either on or off, depending on which pin is pulled high or low. Pins 1-10 of the standard IDE ribbon cable connector control the value displayed on the left, while pins 31-40 control the right side. Each line is pulled through a 330 Ohm resistor to prevent too much current from flowing through the LEDs. Pins 13-20 receive a one-cold signal that ensures that only one PNP transistor is open, allowing only a single array from each side to be active at any moment in time. The base of each transistor is connected to the FPGA through a 4.7K ohm resistor to limit the amount of current flowing into the base when we drive it low.

Figure 2 details the layout of the PCB we constructed that contains the circuit of Figure 1. We used single-sided copper clad board and the Press-n-Peel resist transfer system in order to construct the board. Since we used single-sided board, the red traces had to be made manually with jumper wires.

Figure 3 shows the schematic of the circuit we breadboarded for the final demonstration. It shows the connection of 8 stereo line-level audio inputs to 2 8-channel analog multiplexers. The select controls of the multiplexers are set by 3 incoming data lines from PortB of the PIC. The outputs of each multiplexer run through a half-wave rectifier circuit in order to convert the AC audio signal into a DC signal representing the amplitude of the signal, therefore giving some indication of the volume level of the audio input. The output of each of the half-wave rectifiers are routed directly into A/D inputs 1 and 2 of the PIC, where they are sampled according to a reference voltage input obtained through a 1k potentiometer connected to A/D input 3. The signal is also routed through a lowpass filter with a cutoff frequency at around 34 kHz. This eliminates any clock or multiplexer noise from the signal. The rest of the figure details the FPGA's pin output connections to the 40-pin ribbon cable that connects the breadboard to the LED Array PCB (Fig. 2)


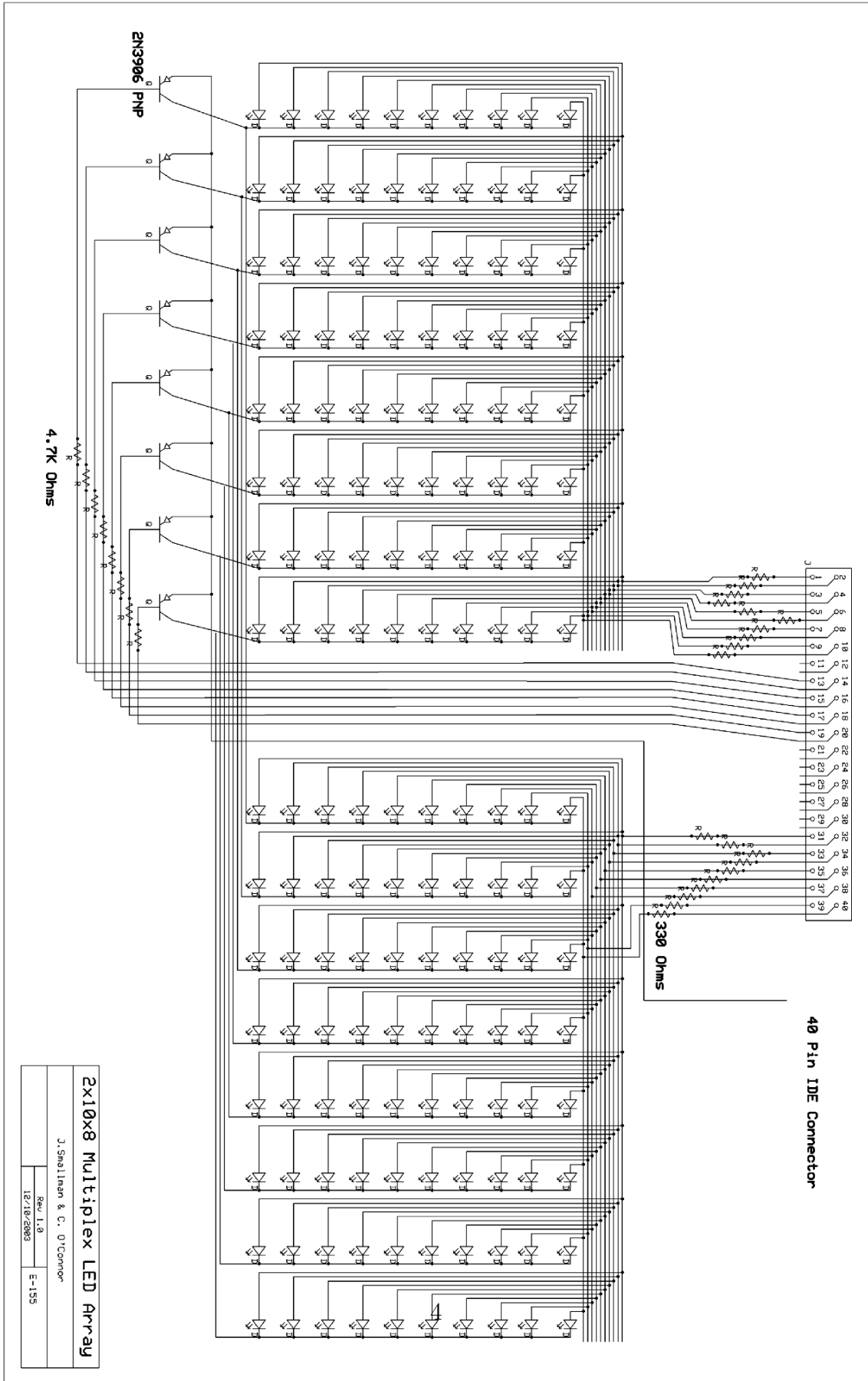


Figure 1: Multiplexing Circuit

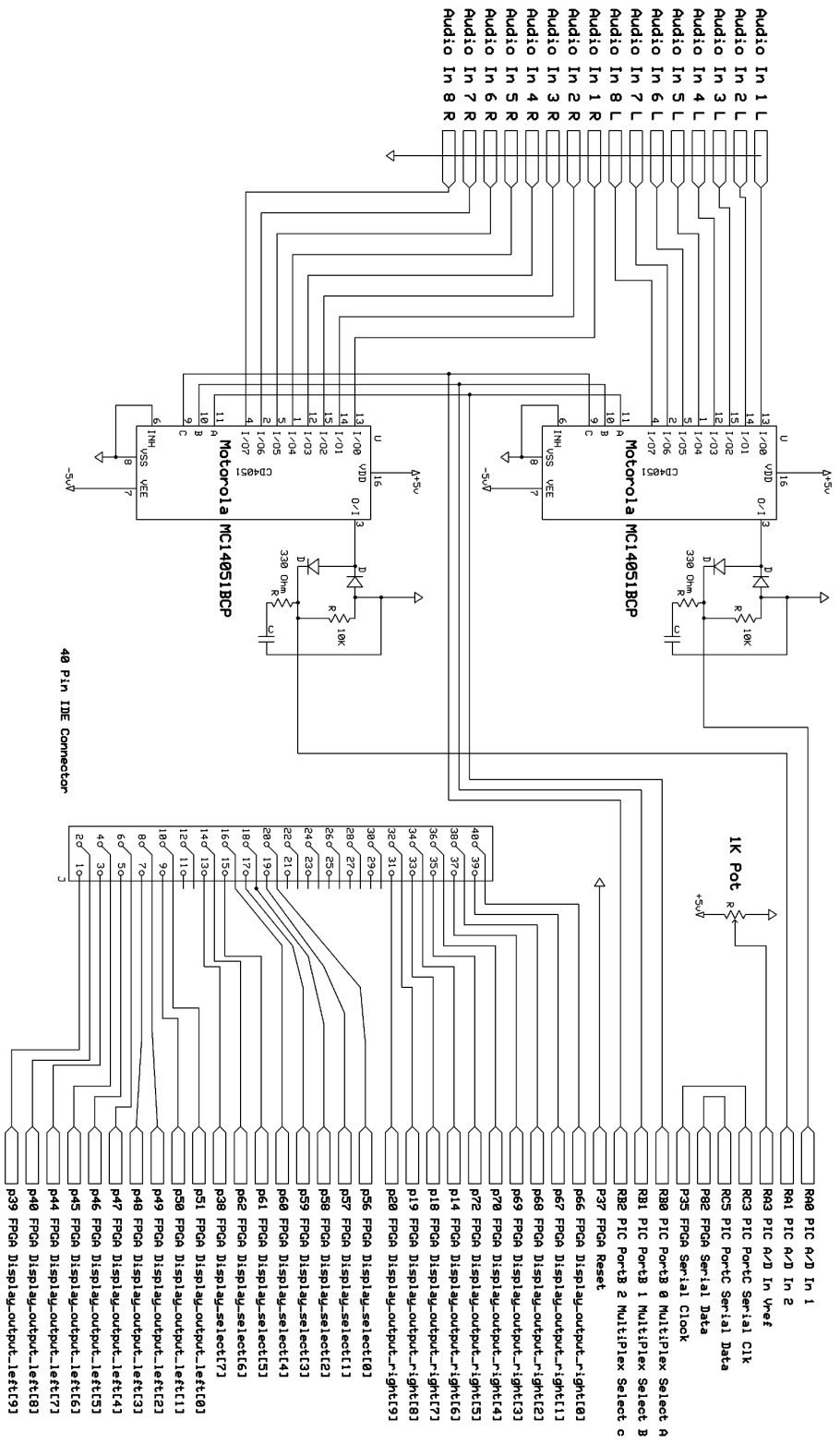

10

8x2 Half Wave Multiplexer	
J. Smallman & C. O'Connor	
Rev 1.0	E155
12/10/2003	

Figure 2: PCB Circuit

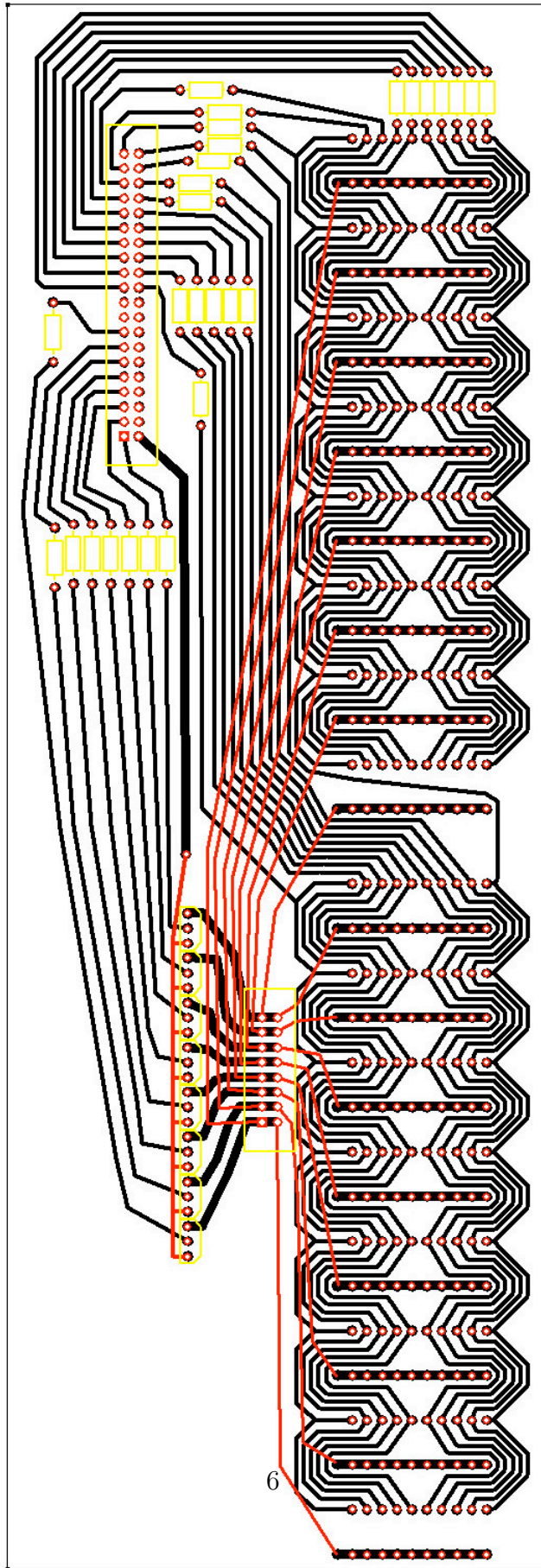


Figure 3: Breadboard Circuit

Microcontroller Design

The PIC is responsible for sampling the input signal and controlling the input multiplexing. Each frequency band is sampled 30 times a second. For 16 bands that requires the PIC to sample from the A/D input port 480 times a second. Running off a 1 MHz clock means the time to sample each band can at most take about 520 instruction cycles.

On startup `InitializeSampleTimer` is called to set up the timer and CCP. The CCP is configured to interrupt whenever Timer 1 reaches a value of 520. Then the A/D module is initialized. Then `InitializeInputControl` is called to set up the input multiplexers to start on the first band of each channel. Once all this has been initialized the interrupts are enabled, the timer is started, then the A/D conversion is started.

The CCP interrupt writes the sampled data to the serial port and changes what pin the A/D samples from. Although our code checks to insure the A/D has completed successfully, the conversion should always be completed by the time the CCP interrupt fires. This way we don't need to use the A/D interrupt also. Every time the PIC is set to sample from the left channel's input the program calls `NextBand` to increment the output that controls the analog multiplexers. Then the timer is reset and the A/D conversion is started again.

FPGA Design

The FPGA has two primary responsibilities in this design. It monitors an incoming serial data line and a serial data clock input, grabbing 8 bit words and storing the top 4 bits into one of 16 allocated registers. Its other function is to write the incoming data values to a multiplexed display consisting of 16 LED arrays.

The driver module consists of several sub-modules which perform its functionality. The main module takes in a serial_clock and serial_data, and has 28 output pins. 10 pins control the the 10 LEDs in a single LED array via display_output_left/right, while an additional 8 pins assigned to display_select control transistors that activate a single pair of LED arrays.

In order to slow down the 1MHz clock to a reasonable refresh rate for the display, the clkDivideBy8 module takes the clk input and outputs a reduced clock signal that is used to drive the multiplexed arrays. It also creates a 3 on 1 off duty cycled display_enable signal, which is used to reduce bleed through that is associated with multiplexed displays. The DisplaySelectGen module takes the divided clock and generates a one-cold 8 bit signal that indicates which of the 8 arrays is currently active.

Our GetSerialData module shifts in bits that come in over the serial_data line as the serial_clk wiggles asynchronously. The top 4 bits of the incoming word are assigned to serial_data_word, and every time 8 bits has been received, the serial_data_rx flag is raised to indicate that serial_data_word contains a valid value.

The synchro module takes the output of GetSerialData and synchronizes its signals before passing them on to the BandRegisters module. BandRegisters contains 2 arrays of 8 4-bit registers, called L and R, which are used to store the 16 most recent data values received over the serial line. As each word comes into the module (after being synchronized) and the serial_data_rxs flag is raised, BandRegisters updates the appropriate register and waits for the next word. Additionally, BandRegisters uses the one-cold display_select signal to determine which pair of LED arrays are currently active, and assigns current_band_out_R and current_band_out_L the appropriate values extracted from the register array.

The two current_band_out_L/R signals generated by BandRegisters are converted by two incarnations of the BandLEDOutput module. The BandLEDOutput module takes the 4 bit input and generates a 10-bit bargraph value, but with the applied 3 on 1 off duty cycle of display_enable. That means that when display_enable is low, BandLEDOutput will output all 1's, which turns off all 10 LED's in an array. When display_enable is high, it will output the converted value as determined by FourBitToBar, a simple module that performs the actual 4 to 10 bit conversion. The outputs of the two BandLedOutput modules directly drive the 20 output pins of the FPGA.

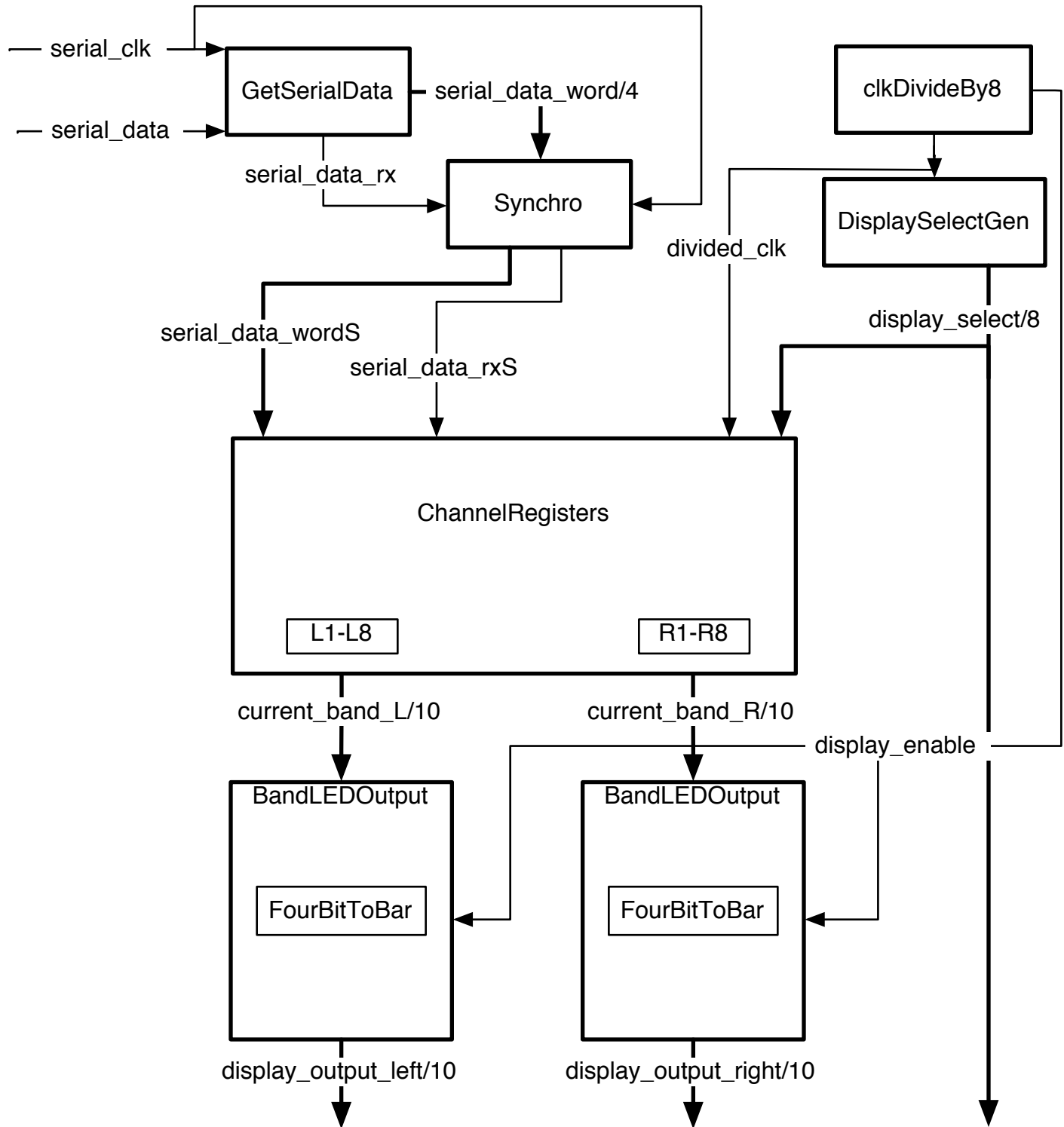


Figure 4: FPGA Block Diagram

Results

Our project resulted in the creation several components, which when put together form a functional 16 channel audio analyzer and display.

Originally, we had planned on the input section composing of bandpass filters that would divide 1 stereo source into 14 signals, send each of the 14 signals through a logarithmic converter to generate a voltage representing sound pressure, and finally multiplex the 14 signals into 2 inputs on the PIC's A/D. The first change we decided on was to increase the width of our analyzer to 8 channels per side instead of 7, since our analog multiplexer had 8 inputs. Additionally, because we were unable to prototype a working bandpass filter circuit, we decided to input 8 distinct stereo signals into the system instead of generating the 16 signals from a single pair. The final change from our original plan was in the use of a half-wave rectifier to convert the AC audio signal into a DC representation of volume. We found that multiplexing the logarithmic converters caused samples to bleed through to each other, because the setup time for the circuit was longer than our sample rate. By switching to a half wave rectifier, our value would vary linearly with the amplitude of the signal, instead of the logarithmic representation of sound pressure.

Our design for the PIC Microcontroller and FPGA remained in line with our original plans, except for the expansion from 7 to 8 channels, since once the input is generated, how it is sampled, communicated, and displayed remains the same regardless of the nature of the data. The PIC controls the analog multiplexers, sampling each of the 8 stereo inputs through 2 of its A/D inputs, and sends the top 8 bits of the sample across the serial data line. The FPGA receives the 8 bit words coming across the serial line, and stores the top 4 bits in a register array. The FPGA also generates outputs to drive our custom made PCB, consisting of 16 multiplexed LED arrays and support resistors/transistors.

The most difficult challenges for this project were introduced by the analog circuits we wanted to use for signal preparation. We invested a significant portion of our effort (and budget) into the bandpass filters, but eventually had to abandon their use as our deadline approached. Although we had identified the analog section as a risk, we took too long to decide that an alternative approach to the problem was necessary. In the future, we should ensure that all serious risks are navigated and handled as soon as possible, and be willing to seek alternatives sooner.

Using the LMF100 active filter IC would have been a better choice than the MSU2F. The LMF100 is a well established chip, and many examples exist how to use the IC. The datasheet is also significantly better with long discussions on exactly how the IC should be configured and connected for best performance. However, a distributor, manufacturer or datasheet for this IC was not located until after the MSU2F's had already been purchased and shipped.

References

1. Horowitz and Hill. *the Art of Electronics* Cambridge, United Kingdom: Cambridge University Press, 1989
2. Mixed Signal Interaction MSU2F Active Filter IC, <http://www.mix-sig.com/MSUF.pdf>
3. National Semiconductor LMF100, <http://www.swarthmore.edu/NatSci/echeeve1/Ref/DataSheet/LMF100.pdf>
4. Motorola MC14051B, <http://www.fe.up.pt/~victorm/DataSheet/CMOS/mc14051brev3.pdf>

Parts List

- 2x [Analog Multiplexer] Motorola MC14051B. from MarVac, <http://www.marvac.com>.
\$3.20
- 8x [Analog Bandpass Filters] MSU2F. From Mixed Signal Interactions, (408)-434-6305
\$34.34

Appendices

PIC Microcontroller program: multi_sampler.asm

```
; Author: Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
; File: multi_sampler.asm
; 11/18/2003
; This program alternates between sampling from two A/D ports.
; The top 8-bits of the samples are then communicated over the serial line.
; Uses bits 0-2 of PortB to control two 8-input analog multiplexers, where the
; output of each is connected to A/D inputs 1 and 2. Vref is provided by I/O 3 of the A/D
; converter.
; Essentially, this program takes 8-bit samples from 16 different analog inputs and outputs
; them in order and repeatedly over the serial line.
```

```
LIST p=18F452
include "p18f452.inc"
```

```
SAMPLE_RATE EQU D'520'
```

```
LEFT_CHANNEL EQU 0
RIGHT_CHANNEL EQU 1
```

```
nextValueToSend RES 1
currentChannel RES 1
currentBand RES 1
```

```
org 0
bra start
```

```
; High priority interrupt vector
org 8
btfsc PIR1, CCP1IF
bra CCPInterrupt
retfie
```

```
CCPInterrupt
; Clear interrupt flag
bcf PIR1, CCP1IF
```

```
; Skip this if the A/D is incomplete
btfsc ADCON0, GO
```

```

bra CCPTimerReset

; Send the current value over the serial port
movff ADRESH, SSPBUF

; noop until the word is sent.
nop
nop
nop
nop
nop
nop
nop
nop
nop
nop
nop

; Set the A/D to sample from the other channel
comf currentChannel
btfsc currentChannel, 0
bra SampleFromRight

; Sample from left channel
bcf ADCON0, CHSO
call NextBand

bra StartSampling

SampleFromRight
; Sample from right channel
bsf ADCON0, CHSO

StartSampling
; Start the sampling
bsf ADCON0, GO

CCPTimerReset
; Restart the timer
movlw high SAMPLE_RATE
movwf TMR1H

```

```

movlw low SAMPLE_RATE
movwf TMR1L

retfie

; start of the main program
start
; Initialize serial line
; Set port C for output
clrf TRISC

; Configure the serial port register
; Set bit 5: Enable
; Clear bit 4: clock idle state is low
; Clear bits 0-3: osc/4 clock
; Clear bits 6,7: Clear overflow and collision flags.
movlw B'00100000'
movwf SSPCON1

; Configure the serial port status
; Set bit 7: Master mode
; Set bit 6: Data transmitted on rising edge of SCK
movlw B'11000000'
movwf SSPSTAT

; Set current channel and band
movlw LEFT_CHANNEL
movwf currentChannel
movlw 0
movwf currentBand

; Initialize multiplexed input control
call InitializeInputControl, 1

; Initialize CCP and a timer to interrupt at the correct sampling rate
call InitializeSamplingTimer, 1

; Initialize A/D port
; Set pins 0 and 1 on porta for input
bsf TRISA, 0
bsf TRISA, 1

```



```

; Configure ADCON0
; clear bits 7-6: Set Tad to Fosc/4
; clear bits 5-3: Sampling AN0 (left channel)
; set bit 0: Turn on A/D module.
movlw B'00000001'
movwf ADCON0

; Configure ADCON1
; clear bit 7: Left justify result
; set bit 6: tad = Fosc/4
; clear bits 3-1: AN0 & AN1 as analog inputs, bit 0 high makes AN3 into VREF+
movlw B'01000001'
movwf ADCON1

; Start sampling
bsf ADCON0, GO

; Start the timer
bsf T1CON, 0

; Enable interrupts
bsf INTCON, GIE
bsf INTCON, PEIE

; Loop
end_loop
bra end_loop

InitializeInputControl
; Set current band of left and right channels to 0
; Reset the filters if necessary

; Set port B for output
bcf TRISB, 0
bcf TRISB, 1
bcf TRISB, 2

movlw 0
movwf PORTB

return 1

```

```

InitializeSamplingTimer
; Initialize Timer 1
; Set bit 7
; Clear bits 4,5: 1:1 prescale
; Clear bit 1: Internal clock
; Don't start the timer yet
movlw B'10000000'
movwf T1CON

; Initialize CCP
; Set bits 3-0 to 1010: Compare mode. Interrupt on match
movlw B'00001010'
movwf CCP1CON

; Set timer 1 as clock source for CCP1
bcf T3CON, 6
bcf T3CON, 3

; Set the compare value so the interrupt fires every 1200 instructions.
movlw high SAMPLE_RATE
movwf CCPR1H
movlw low SAMPLE_RATE
movwf CCPR1L

; Initialize interrupts
; Clear interrupt flag
bcf PIR1, CCP1IF

; Enable CCP compare interrupts
bsf PIE1, CCP1IE

return 1

NextBand
; Add one to currentChannel
incf currentBand
movff currentBand, PORTB

return 1

end

```

Main Verilog module: driver.v

```
// driver.v, a Display Driver for a custom Multiplexed LED Array PCB.
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
// 11/18/2003
// This module is used to receive a repeating series of 16 8-bit words via a serial interface
// It displays the top 4 bits of each word in bargraph mode on one of 16 LED Arrays.

module driver(clk, reset,
             serial_data, serial_clk,
             display_select,
             display_output_left, display_output_right);
    input clk;
input reset;
    input serial_clk;
input serial_data;
    output [7:0] display_select; // one-hot controls which of the 8 pairs of LED Array
    output [9:0] display_output_left; // 10-bit value that is written bitwise to the 10 LEDs
    output [9:0] display_output_right; // Since one array from each side is displayed at a time

wire divided_clk; // slow down the clock for a reasonable refresh rate
wire display_enable; // duty cycle (3 on 1 off) the display to reduce blur between multiplexed words

wire [3:0] current_band_L, current_band_R;
wire [3:0] serial_data_word; // the word that just came in over the serial line
wire serial_data_rx; // indicates a complete word has been received

wire [3:0] serial_data_wordS; // holds synchronized complete word
wire serial_data_rxS; // holds synchronized serial_data_rx flag

/* filterDriver filterDriver(clk, reset, filter_clock);*/

// create the divided clock and display enable signals
clkDivideBy8 clkDivideBy8(clk, reset, divided_clk, display_enable);
// create the display_select signal
DisplaySelectGen DisplaySelectGen(clk, reset, divided_clk, display_select);

// shift in serial data from the serial line and put words into serial_data_word
// Also raises serial_data_rx flag
GetSerialData GetSerialData(serial_clk, reset, serial_data,
                             serial_data_word, serial_data_rx, clk);
```

```

// synchronize the serial data, since the serial_clk input is asynchronous
Synchro Synchro(clk, reset, serial_clk, serial_data_word, serial_data_rx,
    serial_data_wordS, serial_data_rxS);

// stores incoming words in an array of registers, and outputs what 4 bit values should
// displayed on the 2 currently active LED arrays.
BandRegisters ChannelRegisters(clk, reset,
    divided_clk, display_select,
serial_data_rxS, serial_data_wordS,
current_band_L, current_band_R);

// convert the 4-bit output of BandRegisters to the 10-bit value we need for display on
BandLEDOutput leftChannelOutput(current_band_L,
    display_enable,
    display_output_left);
BandLEDOutput rightChannelOutput(current_band_R,
    display_enable,
display_output_right);

endmodule

```

clkDivideBy8.v

```
// clkDivideBy8.v
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
// 11/18/2003
// Standard Clock divider, also creates an enable output with a duty cycle
// of 3 on 1 off.
```

```
module clkDivideBy8(clk,reset,out, enable);
    input clk;
    input reset;
    output out;
    output enable;

    reg [1:0] state;

    always @(posedge clk or posedge reset)
    if (reset) state <= 2'b000;
    //else if (state == 3'b111) state <= 3'b000;
    else state <= state + 1;

    assign out = ~state[1];
    assign enable = state[0] | state[1];
endmodule
```

DisplaySelectGen.v

```
// DisplaySelectGen.v
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
// 11/18/2003
// Creates a one-cold 8 bit output that left shifts on positive edges of the shift input

module DisplaySelectGen(clk,reset, shift, display_select);
    input clk;
    input reset;
    input shift;
    output [7:0] display_select;

    reg [7:0] display_select;

    always @(posedge reset or posedge shift)
    begin
        if(reset)
display_select <= 8'b11111110;
        else if(shift)
display_select <= {display_select[6:0], display_select[7]};
        end

endmodule
```

```

GetSerialData.v
// GetSerialData.v
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
// 11/18/2003
// This module shifts in serial data and stores each 8-bits as a word.
// Outputs top 4 bits of each incoming word.
// Also raises a flag when an entire 8-bit word has been captured.

module GetSerialData(serial_clk,reset,serial_data,serial_data_word,serial_data_rx, clk);
    input clk;
        input serial_clk;
        input reset;
        input serial_data;
        output [3:0] serial_data_word;
        output serial_data_rx;

    reg [2:0] word_size; // counter for how big the word should be
    reg [7:0] shiftreg; // stores each bit as it comes in

    reg started; // ignore the high serial_clk input it goes down first
        // and back up with a rising edge
    always@(posedge reset or posedge serial_clk)
        begin
    if (reset)
        begin
    word_size <= 0;
    shiftreg <= 0;
    started <= 0;
    end
    else
        begin
    shiftreg <= {shiftreg[6:0],serial_data};
    word_size <= word_size + 1;
    started <=1;
    end
    end

    // output the top 4 bits of the incoming word, and create the rx flag.
    assign serial_data_word = shiftreg[7:4],
        serial_data_rx = (word_size == 3'b000) & (started == 1);

endmodule

```

Synchro.v

```
// Synchro.v
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
// 11/18/2003
// Synchronizes the asynchronous serial_data_word and serial_data_rx inputs
// Outputs the synchronized signals.

module Synchro(clk,reset,serial_clk,serial_data_word,serial_data_rx,serial_data_wordS,
               serial_data_rxS);
    input clk;
input reset;
    input serial_clk;
    input [3:0] serial_data_word;
    input serial_data_rx;
    output [3:0] serial_data_wordS;
    output serial_data_rxS;

    reg [3:0] serial_data_wordS;
    reg serial_data_rxS;

    always@(posedge reset or posedge clk)
begin
    if (reset)
begin
serial_data_wordS <= 4'b0;
serial_data_rxS <= 1'b0;
end
    else
begin
if(serial_clk)
begin
serial_data_rxS <= serial_data_rxS ? 0 : serial_data_rx;
serial_data_wordS <= serial_data_word;
end
end
end

endmodule
```


BandRegisters.v

```
// BandRegisters.v
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)
// 11/18/2003
// This module receives repeating loops of 16 4-bit words and stores them in one of
// sixteen 4-bit registers. It also outputs the two 4-bit words according to the
// one-cold encoding of the display_select input.

module BandRegisters(clk,reset,divided_clk,display_select,serial_data_rxS,
                    serial_data_wordS,current_band_out_L,current_band_out_R);

    input clk;
    input reset;
    input divided_clk;
    input [7:0] display_select; // one-cold encoding of which pair of LED arrays are active
    input serial_data_rxS; // synchronized flag indicating complete word received
    input [3:0] serial_data_wordS; // synchronized word received.
    output [3:0] current_band_out_L; // the value to be displayed on the currently active
    output [3:0] current_band_out_R; // the value to be displayed on the currently active

    reg [3:0] R[0:7]; // array of 8 registers, each holding 4 bit value to be displayed on
    reg [3:0] L[0:7]; // array for left side
    reg [1:0] state; // state variable used to ensure proper serial word receipt and processing

    // this points to which register is next to be
    // updated from the incoming word on the serial line
    reg [3:0] current_serial_to_register;

    always @(posedge reset or posedge clk)
    begin
        if(reset)
        begin
            // Set starting values, display ramp on board
            state <= 2'b00;
            current_serial_to_register <= 4'b0;
            L[0] <= 4'b0001;
            L[1] <= 4'b0010;
            L[2] <= 4'b0011;
            L[3] <= 4'b0100;
            L[4] <= 4'b0101;
            L[5] <= 4'b0110;
            L[6] <= 4'b0111;
            L[7] <= 4'b1000;
```

```

R[0] <= 4'b1001;
R[1] <= 4'b1010;
R[2] <= 4'b1011;
R[3] <= 4'b1100;
R[4] <= 4'b1101;
R[5] <= 4'b1110;
R[6] <= 4'b1111;
R[7] <= 4'b0000;
end
else
// this code ensures that each word that comes in over the serial line
// is only received once.
case(state)
2'b00: // starting state
begin
if(serial_data_rxS) // if we've received a word
begin
if(current_serial_to_register[0] == 0) // put the word into the right register
L[current_serial_to_register[3:1]] <= serial_data_wordS;
else
R[current_serial_to_register[3:1]] <= serial_data_wordS;
state <= 2'b01; // increment state
end
end
2'b01: // second state, just put word into register.
begin
// increment the pointer to the next register to be updated
current_serial_to_register <= current_serial_to_register + 1;
state <= 2'b10; // increment state
end
2'b10: // third state, stay in third state until serial_data_rxS flag goes back down.
if(serial_data_rxS)
state <= 2'b10;
else
state <= 2'b00;
endcase
end
// assign the value pointed to by display_select to the current_band_out outputs.
assign current_band_out_R = (display_select[0] == 0) ? R[0] : {4{1'bz}},
current_band_out_R = (display_select[1] == 0) ? R[1] : {4{1'bz}},
current_band_out_R = (display_select[2] == 0) ? R[2] : {4{1'bz}},
current_band_out_R = (display_select[3] == 0) ? R[3] : {4{1'bz}},

```

```
current_band_out_R = (display_select[4] == 0) ? R[4] : {4{1'bz}},
current_band_out_R = (display_select[5] == 0) ? R[5] : {4{1'bz}},
current_band_out_R = (display_select[6] == 0) ? R[6] : {4{1'bz}},
current_band_out_R = (display_select[7] == 0) ? R[7] : {4{1'bz}};
assign current_band_out_L = (display_select[0] == 0) ? L[0] : {4{1'bz}},
current_band_out_L = (display_select[1] == 0) ? L[1] : {4{1'bz}},
current_band_out_L = (display_select[2] == 0) ? L[2] : {4{1'bz}},
current_band_out_L = (display_select[3] == 0) ? L[3] : {4{1'bz}},
current_band_out_L = (display_select[4] == 0) ? L[4] : {4{1'bz}},
current_band_out_L = (display_select[5] == 0) ? L[5] : {4{1'bz}},
current_band_out_L = (display_select[6] == 0) ? L[6] : {4{1'bz}},
current_band_out_L = (display_select[7] == 0) ? L[7] : {4{1'bz}};
endmodule
```

BandLEDOutput.v

```
// BandLEDOutput.v,  
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)  
// 11/18/2003  
// This module takes a 2 4bit inputs and converts them to a 10 bit bargraph value  
// All the work is done by the FourBitToBar module  
  
module BandLEDOutput(current_band,display_enable,display_out);  
    input [3:0] current_band;  
    input display_enable;  
    output [9:0] display_out;  
  
    wire [9:0] converted_value;  
  
    FourBitToBar FourBitToBar(current_band, converted_value);  
  
    assign display_out = display_enable ? converted_value : {10{1'b1}};  
endmodule
```

FourBitToBar.v

```
// FourBitToBar.v, a Display Driver for a custom Multiplexed LED Array PCB.  
// Written by Corey O'Connor (coconnor@hmc.edu) & Josh Smallman (jsmallman@hmc.edu)  
// 11/18/2003  
// Takes a 4 bit input and outputs a bargraph encoded 10-bit value.
```

```
module FourBitToBar(data, bar_out);  
    input [3:0] data;  
    output [9:0] bar_out;
```

```
    reg [9:0] bar_out;
```

```
    parameter ZERO = {10{1'b1}};  
    parameter ONE = 10'b1111111110;  
    parameter TWO = 10'b1111111100;  
    parameter THREE = 10'b11111111000;  
    parameter FOUR = 10'b11111110000;  
    parameter FIVE = 10'b11111100000;  
    parameter SIX = 10'b11111000000;  
    parameter SEVEN = 10'b11100000000;  
    parameter EIGHT = 10'b11000000000;  
    parameter NINE = 10'b10000000000;  
    parameter TEN = 10'b00000000000;
```

```
    always @(data)  
        case(data)  
4'b0000: bar_out <= ZERO;  
4'b0001: bar_out <= ONE;  
4'b0010: bar_out <= ONE;  
4'b0011: bar_out <= TWO;  
4'b0100: bar_out <= THREE;  
4'b0101: bar_out <= THREE;  
4'b0110: bar_out <= FOUR;  
4'b0111: bar_out <= FIVE;  
4'b1000: bar_out <= FIVE;  
4'b1001: bar_out <= SIX;  
4'b1010: bar_out <= SEVEN;  
4'b1011: bar_out <= SEVEN;  
4'b1100: bar_out <= EIGHT;  
4'b1101: bar_out <= NINE;  
4'b1110: bar_out <= NINE;  
4'b1111: bar_out <= TEN;
```

```
default: bar_out <= TEN;  
    endcase  
  
endmodule
```