 


# Introduction to CMOS VLSI Design

## Lecture 16: Circuit Pitfalls

David Harris



Harvey Mudd College  
Spring 2004

# Outline


---

- ❑ Circuit Pitfalls
  - Detective puzzle
  - Given circuit and symptom, diagnose cause and recommend solution
  - All these pitfalls have caused failures in real chips
- ❑ Noise Budgets
- ❑ Reliability

# Bad Circuit 1

## ❑ Circuit

- 2:1 multiplexer

 

## ❑ Principle:

## ❑ Solution:


## ❑ Symptom

- Mux works when selected D is 0 but not 1.
- Or fails at low  $V_{DD}$ .
- Or fails in SF/SF corner.

# Bad Circuit 1

## ❑ Circuit

- 2:1 multiplexer

 

## ❑ Principle: Threshold drop

- $X$  never rises above  $V_{DD} - V_t$
- $V_t$  is raised by the body effect
- The threshold drop is most serious as  $V_t$  becomes a greater fraction of  $V_{DD}$ .

## ❑ Solution:


## ❑ Symptom

- Mux works when selected  $D$  is 0 but not 1.
- Or fails at low  $V_{DD}$ .
- Or fails in SF/SF corner.

# Bad Circuit 1

## ❑ Circuit

- 2:1 multiplexer

 

## ❑ Symptom

- Mux works when selected  $D$  is 0 but not 1.
- Or fails at low  $V_{DD}$ .
- Or fails in SFSF corner.

## ❑ Principle: Threshold drop


- $X$  never rises above  $V_{DD} - V_t$
- $V_t$  is raised by the body effect
- The threshold drop is most serious as  $V_t$  becomes a greater fraction of  $V_{DD}$ .

## ❑ Solution: Use transmission gates, not pass transistors

# Bad Circuit 2

## ❑ Circuit

- Latch

 

## ❑ Principle:

## ❑ Solution:


## ❑ Symptom

- Load a 0 into Q
- Set  $\phi = 0$
- Eventually Q spontaneously flips to 1

# Bad Circuit 2

## ❑ Circuit

- Latch

 

## ❑ Symptom

- Load a 0 into Q
- Set  $\phi = 0$
- Eventually Q spontaneously flips to 1

## ❑ Principle: Leakage


- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge

## ❑ Solution:

# Bad Circuit 2

## ❑ Circuit

- Latch

 

## ❑ Symptom


- Load a 0 into Q
- Set  $\phi = 0$
- Eventually Q spontaneously flips to 1

## ❑ Principle: Leakage

- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge
 
## ❑ Solution: Staticize node with feedback


- Or periodically refresh node (requires fast clock, not practical processes with big leakage)



# Bad Circuit 3

## ❑ Circuit

- Domino AND gate

 

## ❑ Symptom

- Precharge gate ( $Y=0$ )
- Then evaluate
- Eventually Y spontaneously flips to 1


## ❑ Principle:

## ❑ Solution:

# Bad Circuit 3

## ❑ Circuit

- Domino AND gate

 

## ❑ Symptom

- Precharge gate ( $Y=0$ )
- Then evaluate
- Eventually  $Y$  spontaneously flips to 1

## ❑ Principle: Leakage


- $X$  is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge

## ❑ Solution:

# Bad Circuit 3

## ❑ Circuit

- Domino AND gate

 


## ❑ Symptom

- Precharge gate ( $Y=0$ )
- Then evaluate
- Eventually Y spontaneously flips to 1

## ❑ Principle: Leakage

- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge


## ❑ Solution: Keeper

 

# Bad Circuit 4

## ❑ Circuit

- Pseudo-nMOS OR

 

## ❑ Principle:

## ❑ Solution:


## ❑ Symptom

- When only one input is true,  $Y = 0$ .
- Perhaps only happens in SF corner.

# Bad Circuit 4

## ❑ Circuit

- Pseudo-nMOS OR

 

## ❑ Symptom

- When only one input is true,  $Y = 0$ .
- Perhaps only happens in SF corner.

## ❑ Principle: Ratio Failure


- nMOS and pMOS fight each other.
- If the pMOS is too strong, nMOS cannot pull X low enough.

## ❑ Solution:

# Bad Circuit 4

## ❑ Circuit

- Pseudo-nMOS OR

 

## ❑ Symptom

- When only one input is true,  $Y = 0$ .
- Perhaps only happens in SF corner.

## ❑ Principle: Ratio Failure


- nMOS and pMOS fight each other.
- If the pMOS is too strong, nMOS cannot pull X low enough.

## ❑ Solution: Check that ratio is satisfied in all corners

# Bad Circuit 5

## ❑ Circuit

- Latch

 

## ❑ Principle:

## ❑ Solutions:


## ❑ Symptom

- Q stuck at 1.
- May only happen for certain latches where input is driven by a small gate located far away.

# Bad Circuit 5

## ❑ Circuit

- Latch

 


## ❑ Principle: Ratio Failure (again)

- Series resistance of D driver, wire resistance, and  $t_{gate}$  must be much less than weak feedback inverter.

## ❑ Solutions:
 
## ❑ Symptom


- Q stuck at 1.
- May only happen for certain latches where input is driven by a small gate located far away.



# Bad Circuit 5

## ❑ Circuit

- Latch

 

## ❑ Principle: Ratio Failure (again)


- Series resistance of D driver, wire resistance, and  $t_{gate}$  must be much less than weak feedback inverter.

## ❑ Solutions: Check relative strengths

- Avoid unbuffered diffusion inputs where driver is unknown
 
## ❑ Symptom

- Q stuck at 1.
- May only happen for certain latches where input is driven by a small gate located far away.






# Bad Circuit 6

## ❑ Circuit

- Domino AND gate

 


## ❑ Principle: Charge Sharing

- If X was low, it shares charge with Y

## ❑ Solutions:
 
## ❑ Symptom


- Precharge gate while  $A = B = 0$ , so  $Z = 0$
- Set  $\phi = 1$
- A rises
- Z is observed to sometimes rise



# Bad Circuit 6

## ❑ Circuit

- Domino AND gate

 

## ❑ Principle: Charge Sharing

- If X was low, it shares charge with Y


## ❑ Solutions: Limit charge sharing

$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$

- Safe if  $C_Y \gg C_X$
- Or precharge node X too
 
## ❑ Symptom


- Precharge gate while  $A = B = 0$ , so  $Z = 0$
- Set  $\phi = 1$
- A rises
- Z is observed to sometimes rise



# Bad Circuit 7

## ❑ Circuit

- Dynamic gate + latch

 

## ❑ Principle:

## ❑ Solution:


## ❑ Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls

# Bad Circuit 7

## ❑ Circuit

- Dynamic gate + latch

 

## ❑ Principle: Charge Sharing

- If Y was low, it shares charge with X

## ❑ Solution:


## ❑ Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls

# Bad Circuit 7

## ❑ Circuit

- Dynamic gate + latch

 

## ❑ Principle: Charge Sharing

- If Y was low, it shares charge with X

## ❑ Solution: Buffer dynamic nodes before driving transmission gate


## ❑ Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls

# Bad Circuit 8

## ❑ Circuit

- Latch

 

## ❑ Principle:

## ❑ Solution:


## ❑ Symptom

- $Q$  changes while latch is opaque
- Especially if  $D$  comes from a far-away driver

# Bad Circuit 8

## ❑ Circuit

- Latch

 

## ❑ Symptom

- Q changes while latch is opaque
- Especially if D comes from a far-away driver

## ❑ Principle: Diffusion Input Noise Sensitivity


- If  $D < -V_{t}$ , transmission gate turns on
- Most likely because of power supply noise or coupling on D

## ❑ Solution:

# Bad Circuit 8

## ❑ Circuit

- Latch

 


## ❑ Symptom

- Q changes while latch is opaque
- Especially if D comes from a far-away driver

## ❑ Principle: Diffusion Input Noise Sensitivity

- If  $D < -V_t$ , transmission gate turns on
- Most likely because of power supply noise or coupling on D

## ❑ Solution: Buffer D locally


 


# Bad Circuit 9

- ❑ Circuit
  - Anything
- ❑ Symptom
  - Some gates are slower than expected
- ❑ Principle:
  
# Bad Circuit 9

- ❑ Circuit
  - Anything
- ❑ Symptom
  - Some gates are slower than expected
  
- ❑ Principle: Hot Spots and Power Supply Noise



# Noise

## ❑ Sources


- Power supply noise / ground bounce
- Capacitive coupling
- Charge sharing
- Leakage
- Noise feedthrough

## ❑ Consequences

- Increased delay (for noise to settle out)
- Or incorrect computations

# Reliability

- ❑ Hard Errors
- ❑ Soft Errors

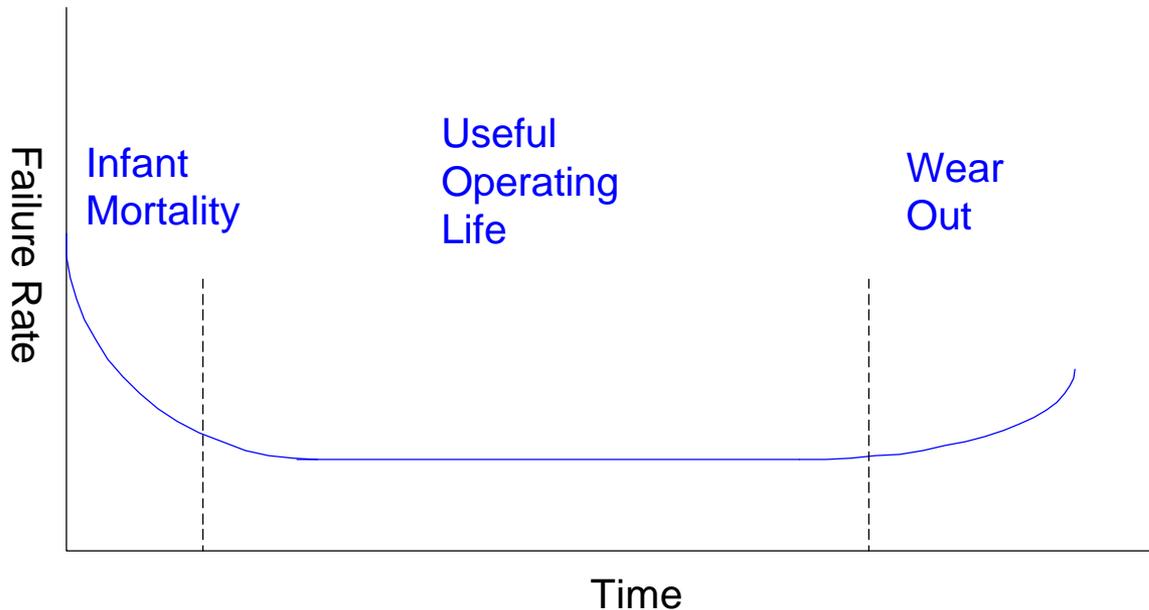

# Electromigration

- ❑ “Electron wind” causes movement of metal atoms along wires
- ❑ Excessive electromigration leads to open circuits
- ❑ Most significant for unidirectional (DC) current
  - Depends on current density  $J_{dc}$  (current / area)
  - Exponential dependence on temperature
  - Black’s Equation:  $MTTF \propto \frac{e^{\frac{E_a}{kT}}}{J_{dc}^n}$
  - Typical limits:  $J_{dc} < 1 - 2 \text{ mA} / \mu\text{m}^2$
- ❑ See videos

# Self-Heating

- ❑ Current through wire resistance generates heat
  - Oxide surrounding wires is a thermal insulator
  - Heat tends to build up in wires
  - Hotter wires are more resistive, slower
- ❑ Self-heating limits AC current densities for reliability

$$I_{rms} = \sqrt{\frac{\int_0^T I(t)^2 dt}{T}}$$



- Typical limits:  $J_{rms} < 15 \text{ mA} / \mu\text{m}^2$

# Hot Carriers

- ❑ Electric fields across channel impart high energies to some carriers
  - These “hot” carriers may be blasted into the gate oxide where they become trapped
  - Accumulation of charge in oxide causes shift in  $V_t$  over time
  - Eventually  $V_t$  shifts too far for devices to operate correctly
- ❑ Choose  $V_{DD}$  to achieve reasonable product lifetime
  - Worst problems for inverters and NORs with slow input risetime and long propagation delays

  
# Latchup

- ❑ Latchup: positive feedback leading to  $V_{DD}$  – GND short
  - Major problem for 1970's CMOS processes before it was well understood
- ❑ Avoid by minimizing resistance of body to GND /  $V_{DD}$ 
  - Use plenty of substrate and well taps


 
# Guard Rings

- ❑ Latchup risk greatest when diffusion-to-substrate diodes could become forward-biased
- ❑ Surround sensitive region with guard ring to collect injected charge



# Overvoltage

- ❑ High voltages can damage transistors
  - Electrostatic discharge
  - Oxide arcing
  - Punchthrough
  - Time-dependent dielectric breakdown (TDDB)
    - Accumulated wear from tunneling currents
- ❑ Requires low  $V_{DD}$  for thin oxides and short channels
- ❑ Use ESD protection structures where chip meets real world

# Summary

---

- ❑ Static CMOS gates are very robust
  - Will settle to correct value if you wait long enough
- ❑ Other circuits suffer from a variety of pitfalls
  - Tradeoff between performance & robustness
- ❑ Very important to check circuits for pitfalls
  - For large chips, you need an automatic checker.
  - Design rules aren't worth the paper they are printed on unless you back them up with a tool.

# Soft Errors

- ❑ In 1970's, DRAMs were observed to occasionally flip bits for no apparent reason
  - Ultimately linked to alpha particles and cosmic rays
- ❑ Collisions with particles create electron-hole pairs in substrate
  - These carriers are collected on dynamic nodes, disturbing the voltage
- ❑ Minimize soft errors by having plenty of charge on dynamic nodes
- ❑ Tolerate errors through ECC, redundancy