

Lecture 22: PLLs and DLLs

Outline

- Clock System Architecture
- Phase-Locked Loops
- Delay-Locked Loops


Clock Generation

- ❑ Low frequency:
 - Buffer input clock and drive to all registers
- ❑ High frequency
 - Buffer delay introduces large skew relative to input clocks
 - Makes it difficult to sample input data
 - Distributing a very fast clock on a PCB is hard

Zero-Delay Buffer


- ❑ If the periodic clock is delayed by T_c , it is indistinguishable from the original clock
- ❑ Build feedback system to guarantee this delay

Phase-Locked Loop (PLL)

 

(a)


Delay-Locked Loop (PLL)

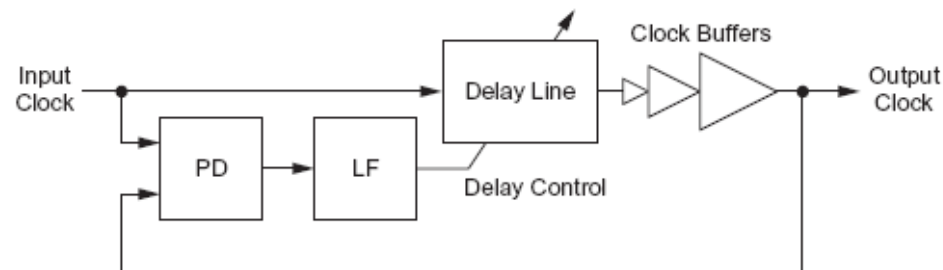

(b)

Frequency Multiplication

- PLLs can multiply the clock frequency

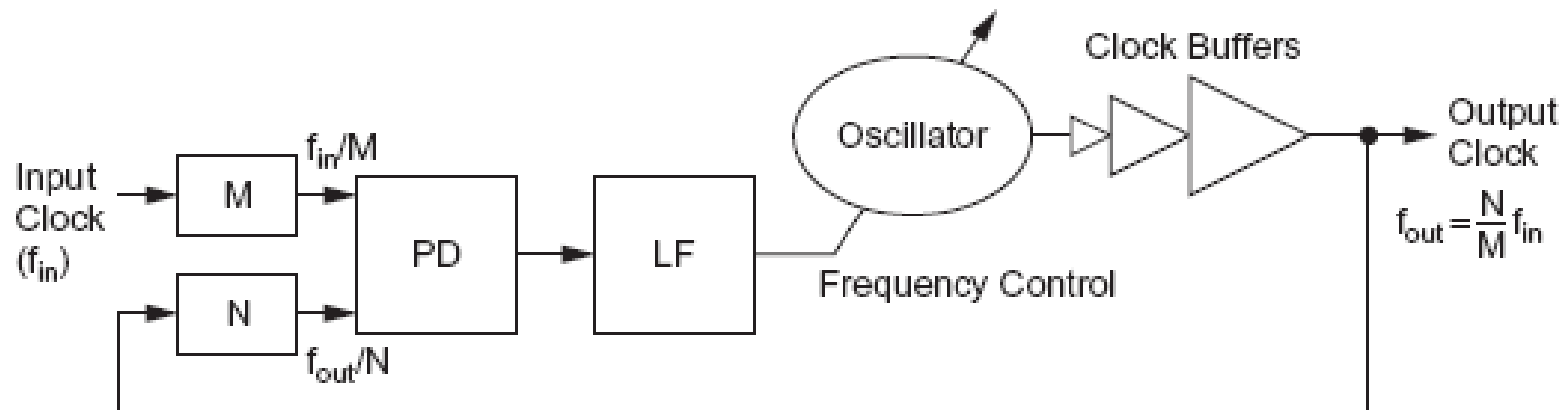


Phase and Frequency

- Analyze PLLs and DLLs in term of phase $\Phi(t)$ rather than voltage $v(t)$

$$\text{clk} = \begin{cases} 1 & \Phi(t) \bmod 2\pi < \pi \\ 0 & \Phi(t) \bmod 2\pi \geq \pi \end{cases}$$

$$\Phi(t) = 2\pi \int_0^t f(t) dt$$

 

- Input and output clocks may deviate from locked phase
 - Small signal analysis

$$\Phi_{\text{in}}(t) = \Phi(t) + \Delta\Phi_{\text{in}}(t)$$


$$\Phi_{\text{out}}(t) = N\Phi(t) + \Delta\Phi_{\text{out}}(t)$$

Linear System Model


- ❑ Treat PLL/DLL as a linear system
 - Compute deviation DF from locked position
 - Assume small deviations from locked
 - Treat system as linear for these small changes
- ❑ Analysis is not valid far from lock
 - e.g. during acquisition at startup
- ❑ Continuous time assumption
 - PLL/DLL is really a discrete time system
 - Updates once per cycle
 - If the bandwidth $\ll 1/10$ clock freq, treat as continuous
- ❑ Use Laplace transforms and standard analysis of linear continuous-time feedback control systems

Phase-Locked Loop (PLL)

System

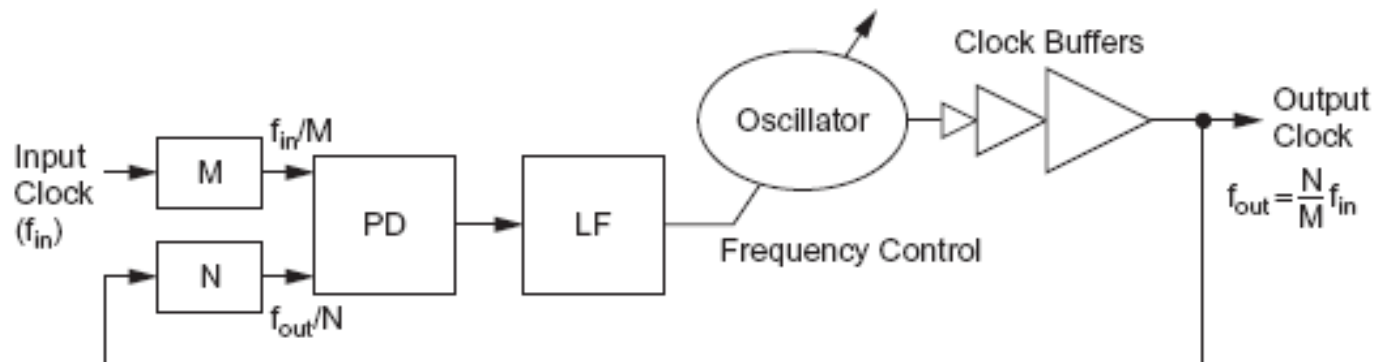


Linear Model

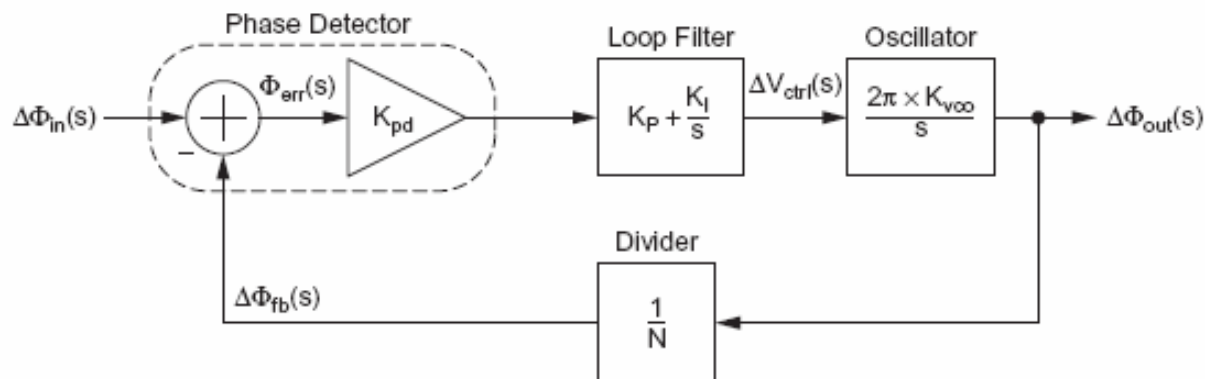

Voltage-Controlled Oscillator



□ VCO

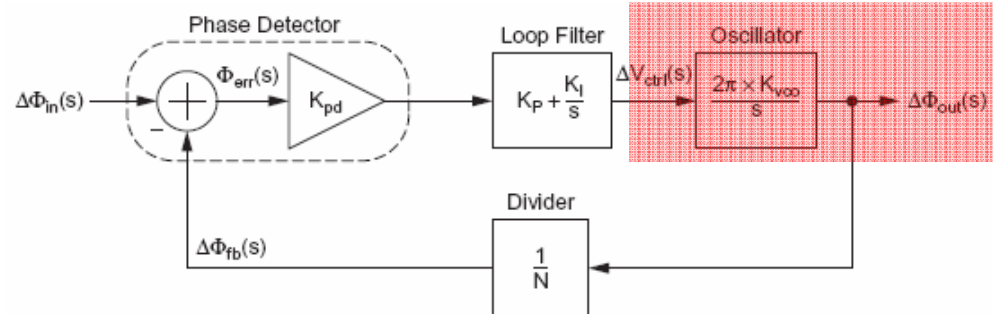


$$V_{ctrl}(t) = V_{ctrl0} + \Delta V_{ctrl}(t)$$

$$\frac{\Delta f_{out}}{\Delta V_{ctrl}} = K_{vco}$$
 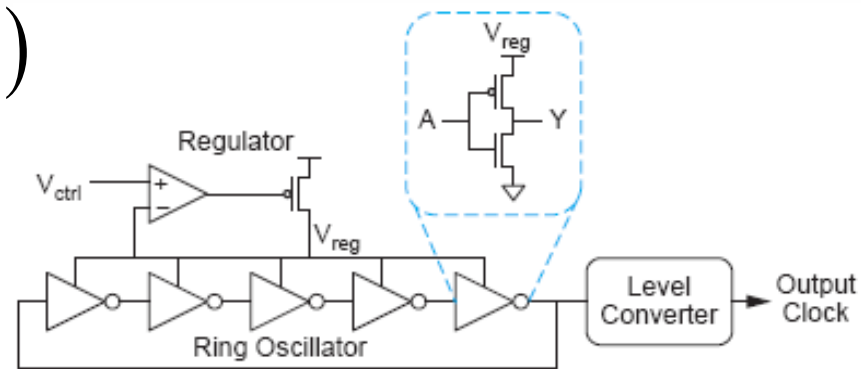
$$\frac{\Delta \Phi_{out}(s)}{\Delta V_{ctrl}(s)} = \frac{2\pi K_{vco}}{s}$$




Alternative Delay Elements

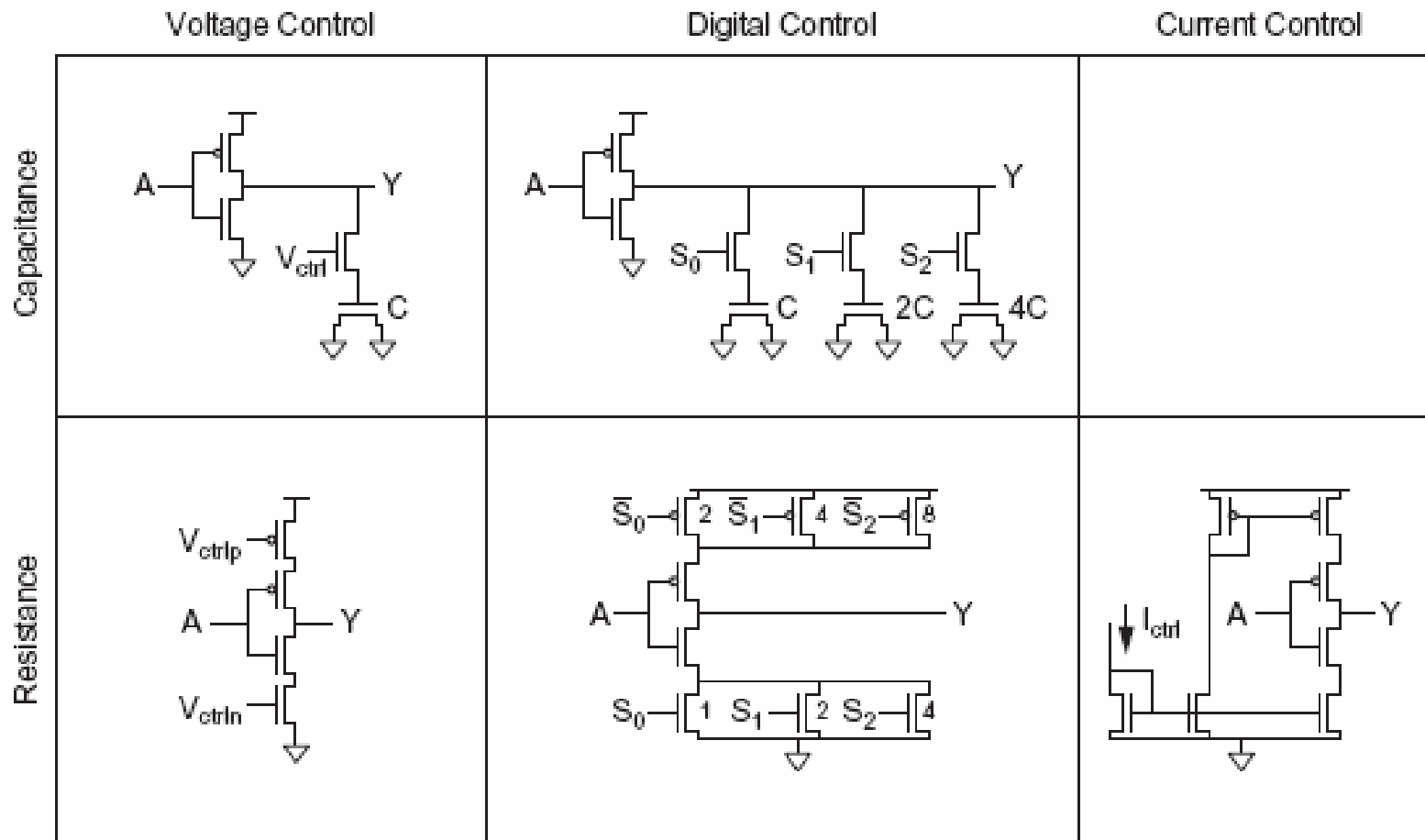

Frequency Divider

- Divide clock by N
 - Use mod-N counter

 


$$\Delta f_{fb} = \frac{\Delta f_{out}}{N}$$




$$\Delta\Phi_{fb} = \frac{\Delta\Phi_{out}}{N}$$

Phase Detector

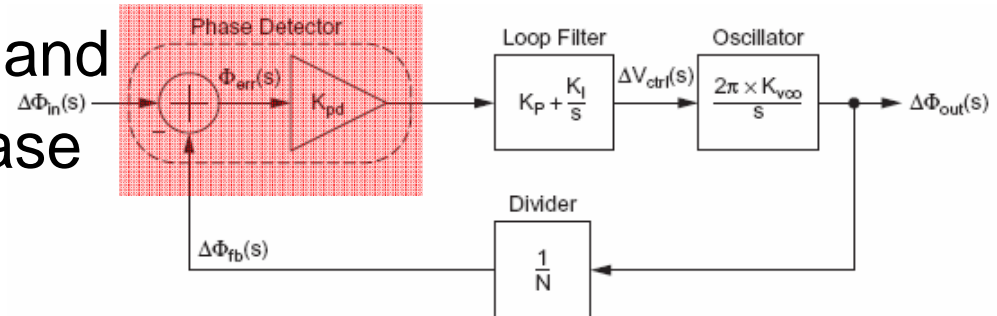- Difference of input and feedback clock phase



  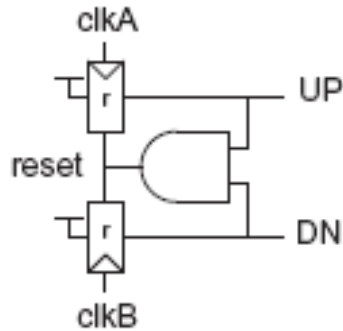
- Often built from phase-frequency detector (PFD)



Phase Detector


- Convert up and down pulses into current proportional to phase error using a charge pump
 
$$\frac{I_{pd}(s)}{\Phi_{err}(s)} = \frac{I_{cp}}{2\pi} = K_{pd}$$




Loop Filter

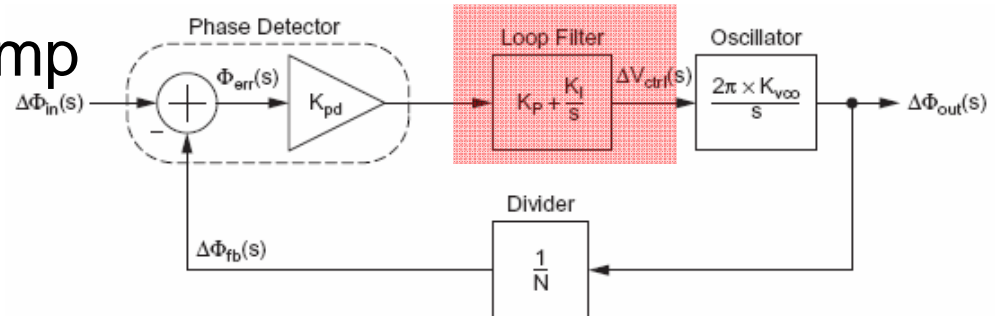- Convert charge pump current into V_{ctrl}



- Use proportional-integral control (PI) to generate a control signal dependent on the error and its integral
 - Drives error to 0
 
$$\frac{V_{ctrl}(s)}{I_{pd}(s)} = \frac{1}{sC} + R$$



PLL Loop Dynamics

- ❑ Closed loop transfer function of PLL

$$H(s) = \frac{\Delta\Phi_{\text{out}}(s)}{\Delta\Phi_{\text{in}}(s)} = \frac{K_{pd} \left(R + \frac{1}{sC} \right) \frac{2\pi K_{\text{vco}}}{s}}{1 + \frac{1}{N} K_{pd} \left(R + \frac{1}{sC} \right) \frac{2\pi K_{\text{vco}}}{s}}$$

- ❑ This is a second order system

$$H(s) = N \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad \omega_n = \sqrt{\frac{I_{cp} K_{\text{vco}}}{NC}}$$
$$\zeta = \frac{\omega_n}{2} RC$$


- ❑ ω_n indicates loop bandwidth
- ❑ ζ indicates damping; choose 0.7 – 1 to avoid ringing

Delay Locked Loop


- ❑ Delays input clock rather than creating a new clock with an oscillator
- ❑ Cannot perform frequency multiplication
- ❑ More stable and easier to design
 - 1st order rather than 2nd
- ❑ State variable is now time (T)
 - Locks when loop delay is exactly T_c
 - Deviations of ΔT from locked value

Delay-Locked Loop (DLL)

System

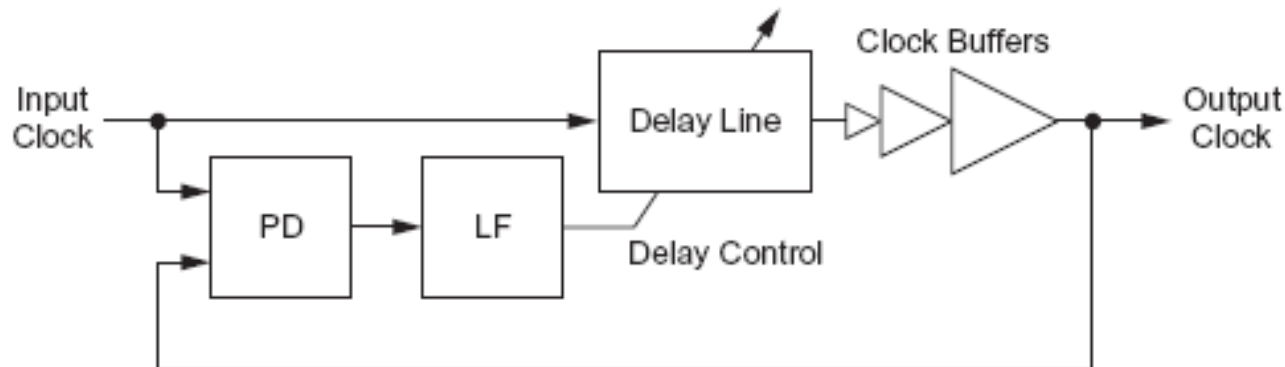


Linear Model

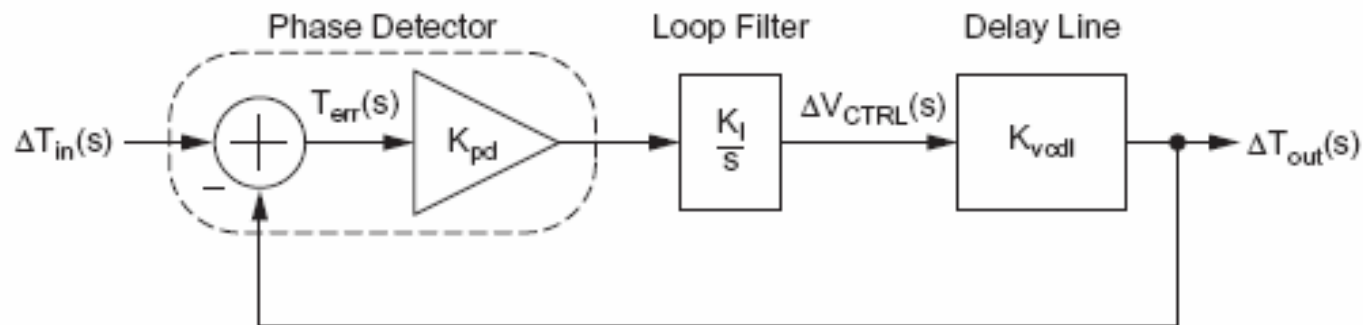



Delay Line

- Delay input clock

 


- Typically use voltage-controlled delay line
  
$$\frac{\Delta T_{\text{out}}(s)}{\Delta V_{\text{ctrl}}(s)} = K_{\text{vcdl}}$$



Phase Detector

- Detect phase error

 


- Typically use PFD and charge pump, as in PLL

$$\frac{I_{pd}(s)}{T_{err}(s)} = \frac{I_{cp}}{T_c}$$


Loop Filter

 - ❑ Convert error current into control voltage



- ❑ Integral control is sufficient
- ❑ Typically use a capacitor as the loop filter
 
$$\frac{\Delta V_{\text{ctrl}}(s)}{I_{\text{pd}}(s)} = \frac{K_I}{s} = \frac{1}{sC}$$



DLL Loop Dynamics

- ❑ Closed loop transfer function of DLL

$$H(s) = \frac{\Delta T_{\text{out}}(s)}{\Delta T_{\text{in}}(s)} = \frac{1}{s\tau + 1}$$

- ❑ This is a first order system

$$\tau = \frac{1}{K_{pd} K_I K_{vc dl}} = \frac{C T_c}{I_{cp} K_{vc dl}}$$

- ❑ τ indicates time constant (inverse of bandwidth)
 - Choose at least $10T_c$ for continuous time approx.