

Lecture 17: Adders

Outline


- Single-bit Addition
- Carry-Ripple Adder
- Carry-Skip Adder
- Carry-Lookahead Adder
- Carry-Select Adder
- Carry-Increment Adder
- Tree Adder

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

PGK


- For a full adder, define what happens to carries (in terms of A and B)
 - Generate: $C_{out} = 1$ independent of C
 - $G =$
 - Propagate: $C_{out} = C$
 - $P =$
 - Kill: $C_{out} = 0$ independent of C
 - $K =$

Full Adder Design I

- ❑ Brute force implementation from eqns


$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

 


Full Adder Design II

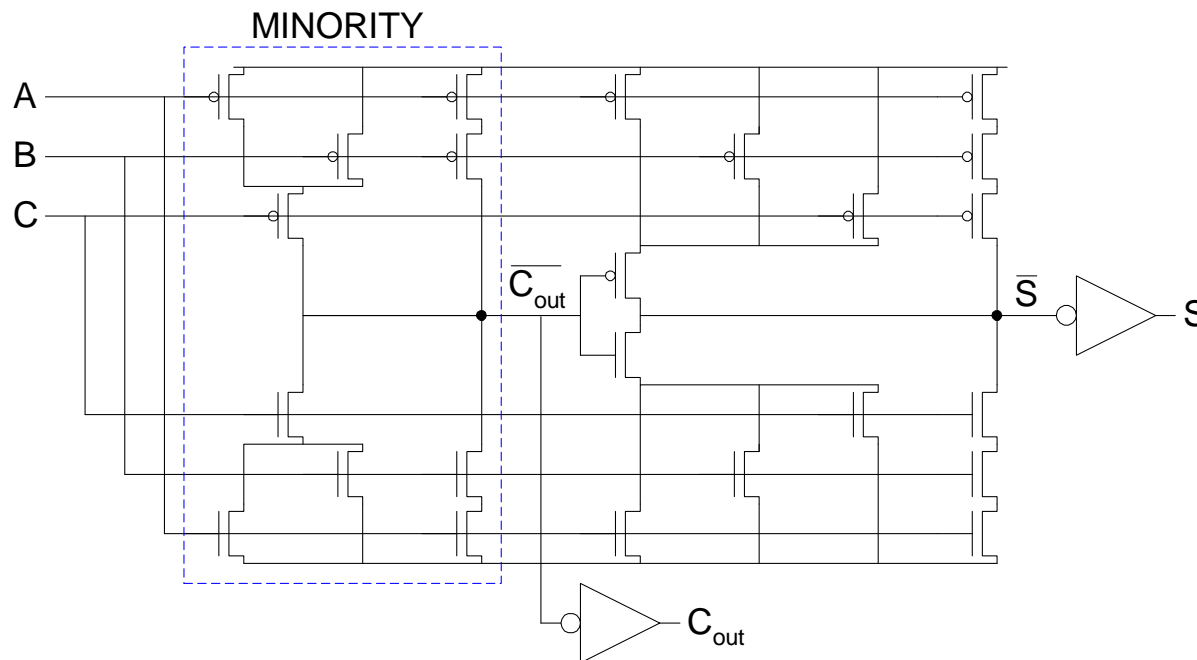- ❑ Factor S in terms of C_{out}
$$S = ABC + (A + B + C)(\sim C_{out})$$
- ❑ Critical path is usually C to C_{out} in ripple adder




Layout

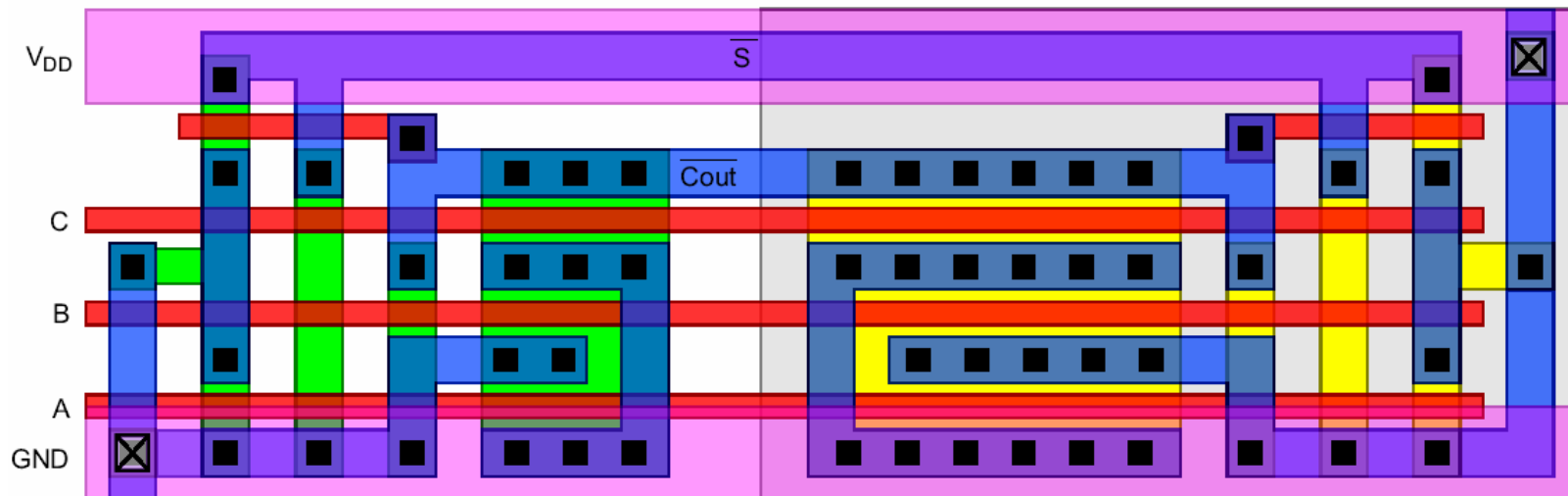- ❑ Clever layout circumvents usual line of diffusion
 - Use wide transistors on critical path
 - Eliminate output inverters



Full Adder Design III

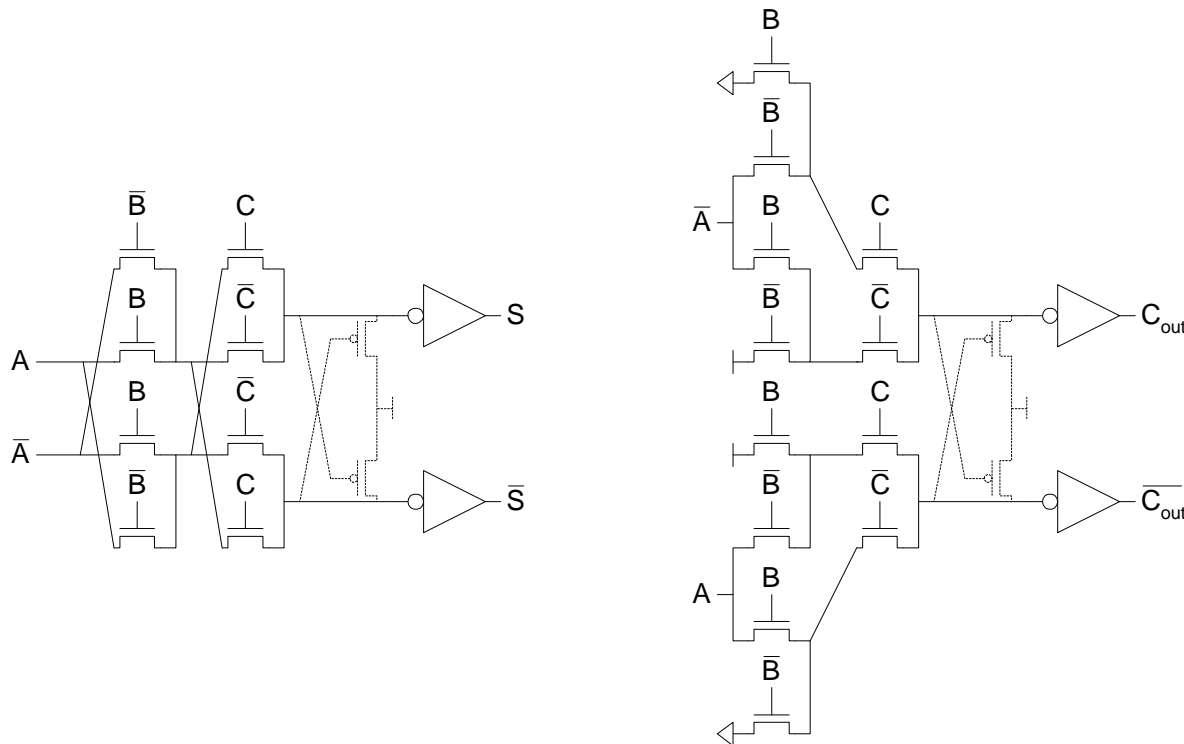
- ❑ Complementary Pass Transistor Logic (CPL)
 - Slightly faster, but more area



Full Adder Design IV


❑ Dual-rail domino

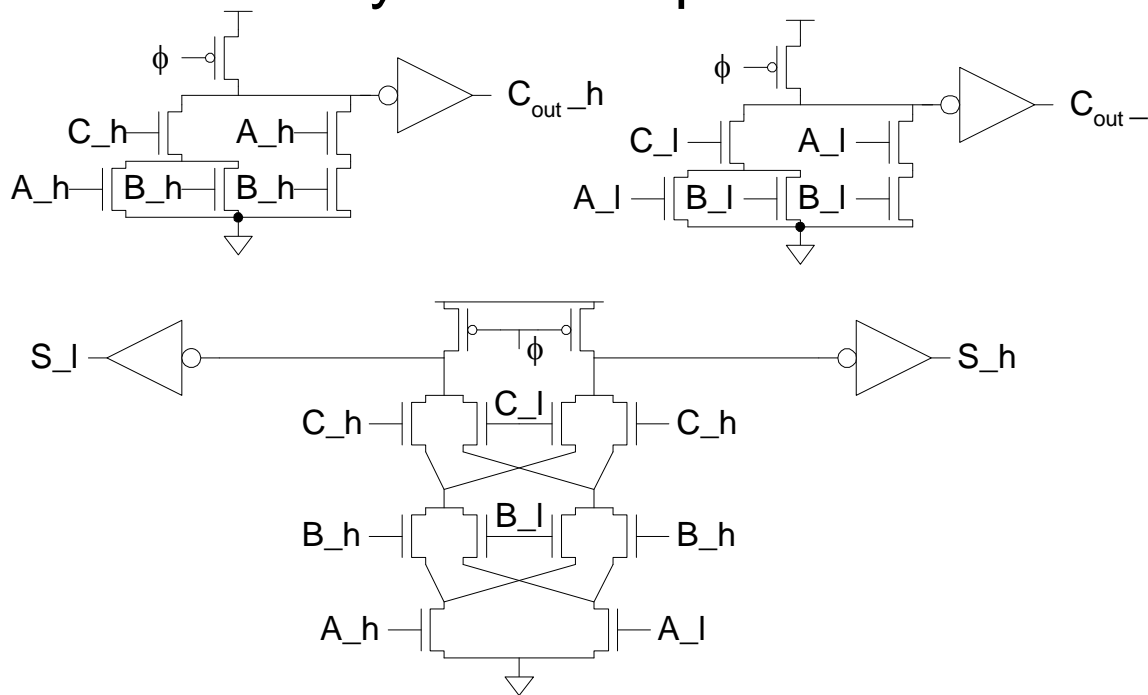- Very fast, but large and power hungry
- Used in very fast multipliers



Carry Propagate Adders

 - ❑ N-bit adder called CPA
 - Each sum bit depends on all previous carries
 - How do we compute all these carries quickly?




$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{0}000\textcircled{0} \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{1}111\textcircled{1} \quad \text{carries} \\ 1111 \quad A_{4...1} \\ +0000 \quad B_{4...1} \\ \hline 0000 \quad S_{4...1} \end{array}$$


Carry-Ripple Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Inversions

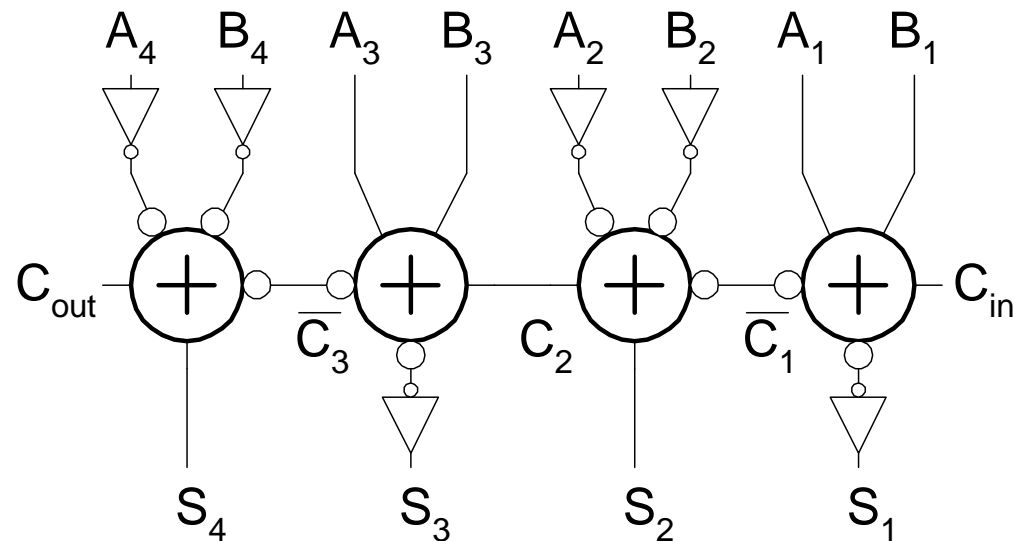- ❑ Critical path passes through majority gate
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



Generate / Propagate

- ❑ Equations often factored into G and P
- ❑ Generate and propagate for groups spanning i:j

$$G_{i:j} =$$

$$P_{i:j} =$$

- ❑ Base case

$$G_{i:i} \equiv$$

$$P_{i:i} \equiv$$


$$G_{0:0} \equiv$$

$$P_{0:0} \equiv$$

- ❑ Sum:


$$S_i =$$

PG Logic

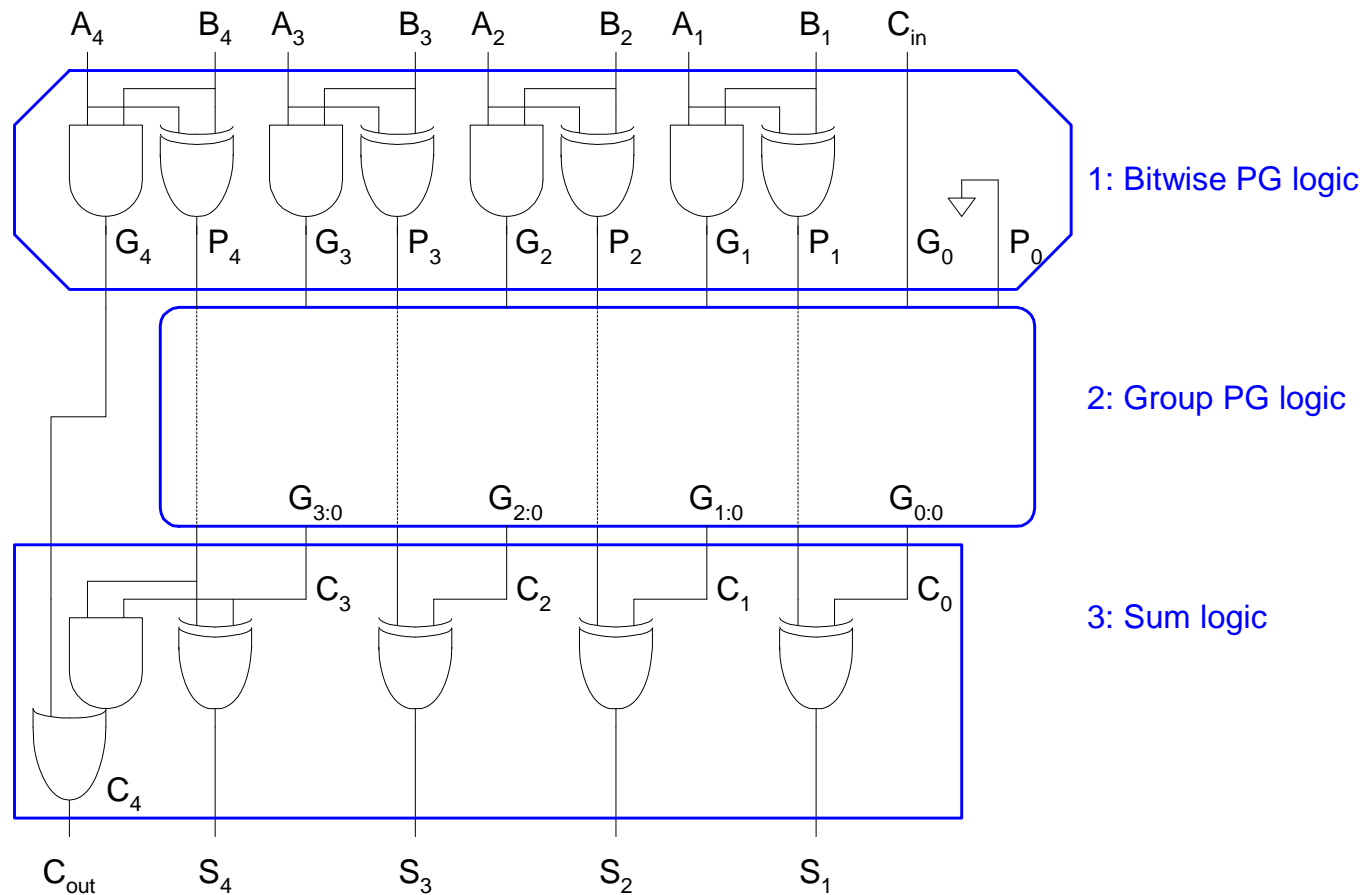


Carry-Ripple Revisited

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

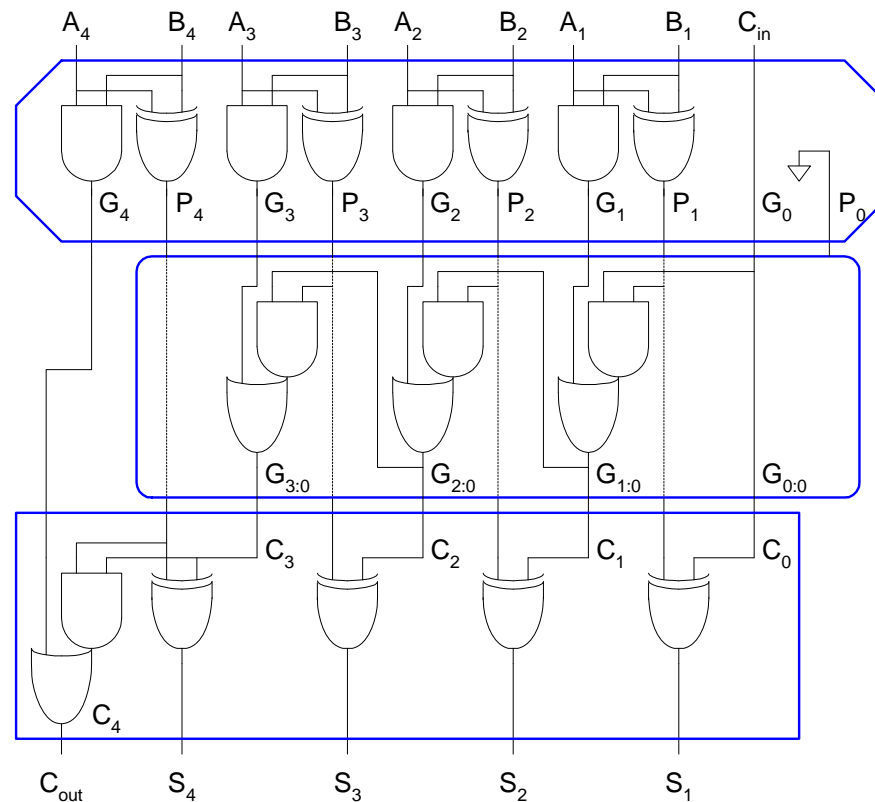


Carry-Ripple PG Diagram

$t_{\text{ripple}} =$

 


PG Diagram Notation





Black cell

 

Gray cell

 


Buffer

    


Carry-Skip Adder

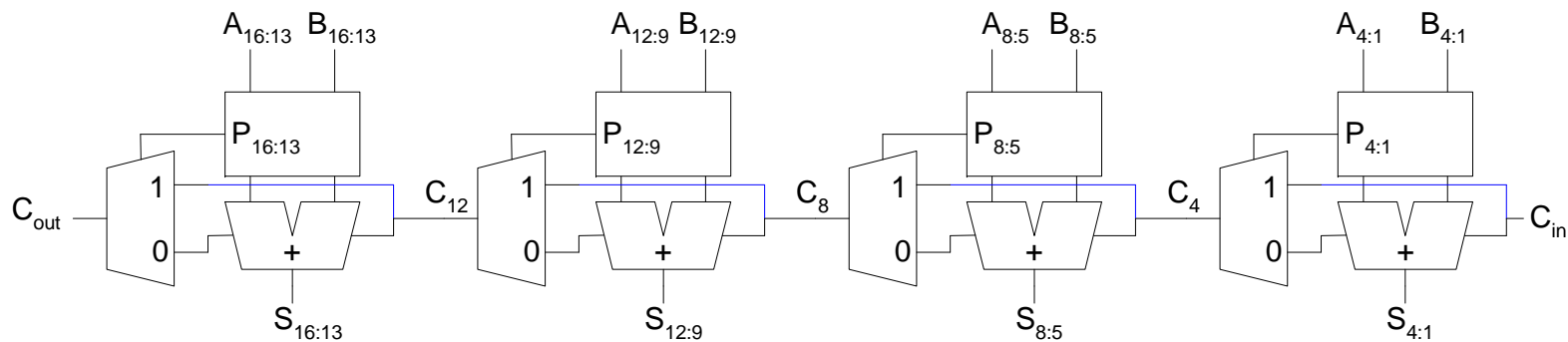- ❑ Carry-ripple is slow through all N stages
- ❑ Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal




Carry-Skip PG Diagram

 

For k n-bit groups ($N = nk$)

$$t_{\text{skip}} =$$


Variable Group Size

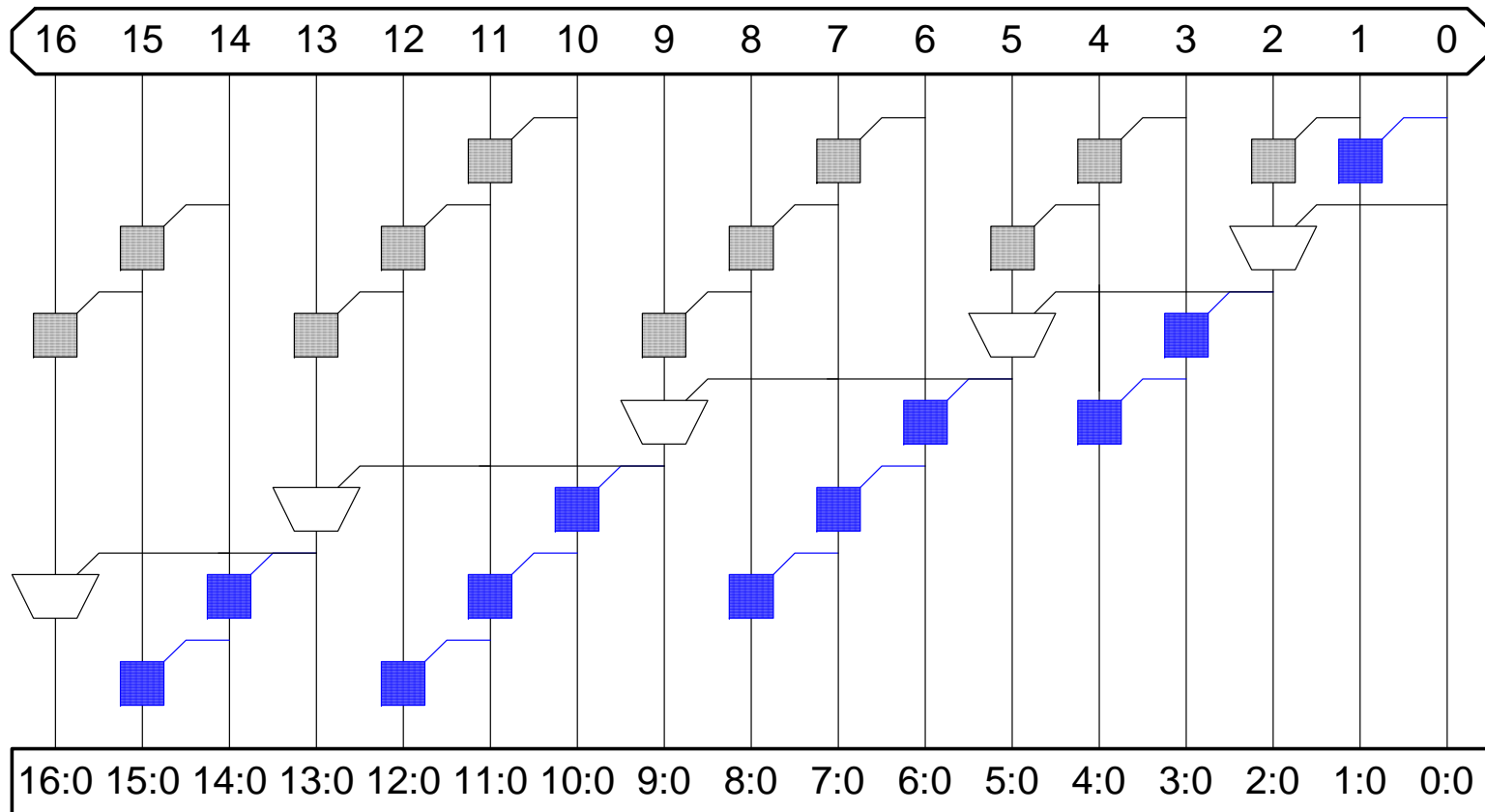


Delay grows as $O(\sqrt{N})$

Carry-Lookahead Adder


 
- ❑ Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel.
- ❑ Uses higher-valency cells with more than two inputs.



CLA PG Diagram

 


Higher-Valency Cells

  


Carry-Select Adder

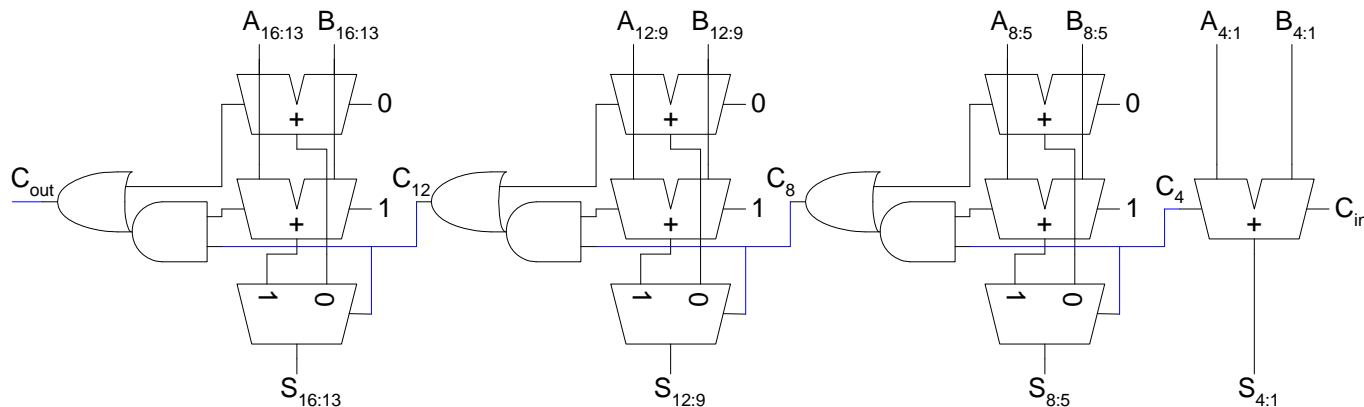- ❑ Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- ❑ Carry-select adder precomputes n -bit sums
 - For both possible carries into n -bit group



Carry-Increment Adder

 
- Factor initial PG and final XOR out of carry-select



$$t_{\text{increment}} =$$

Variable Group Size


- Also buffer noncritical signals

 


Tree Adder

- ❑ If lookahead is good, lookahead across lookahead!
 - Recursive lookahead gives $O(\log N)$ delay
- ❑ Many variations on tree adders


Brent-Kung

 

Sklansky

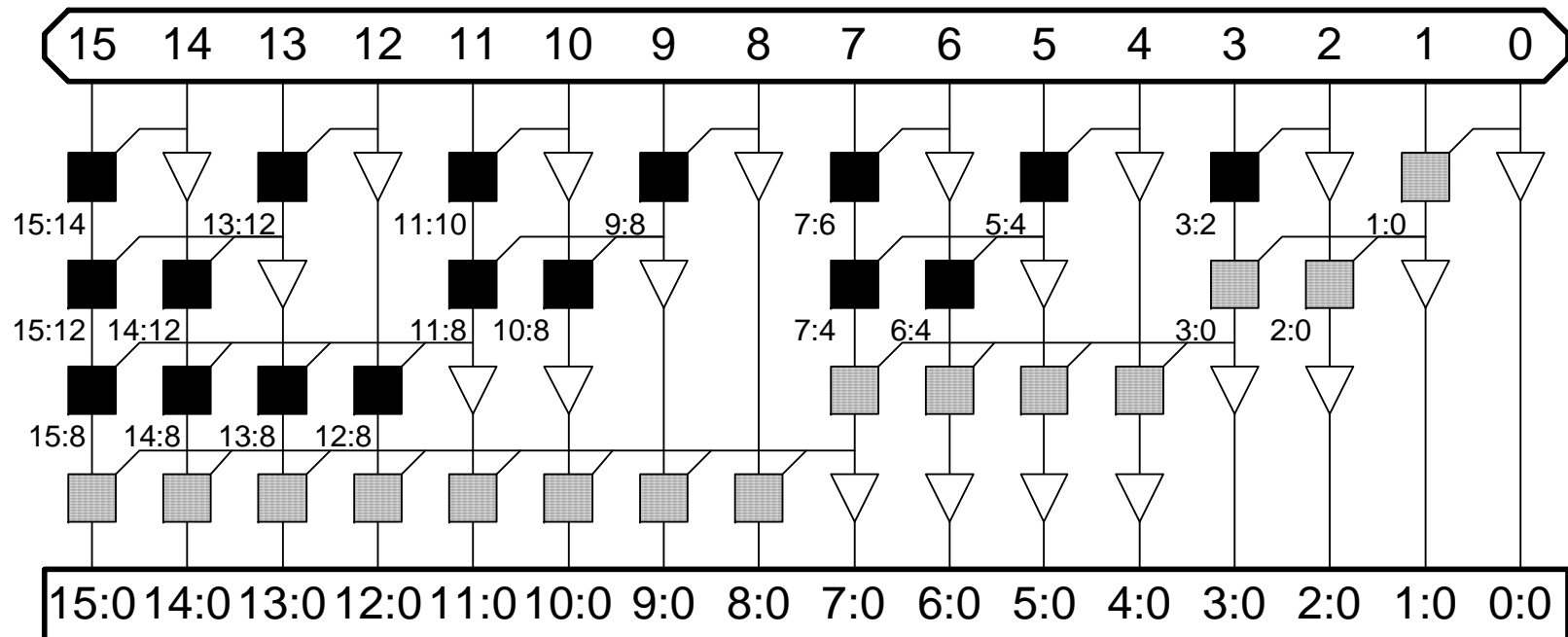


Kogge-Stone

 


Tree Adder Taxonomy

- ❑ Ideal N-bit tree adder would have
 - $L = \log N$ logic levels
 - Fanout never exceeding 2
 - No more than one wiring track between levels
- ❑ Describe adder with 3-D taxonomy (l, f, t)
 - Logic levels: $L + l$
 - Fanout: $2^f + 1$
 - Wiring tracks: 2^t
- ❑ Known tree adders sit on plane defined by
$$l + f + t = L - 1$$


Tree Adder Taxonomy

 


Han-Carlson

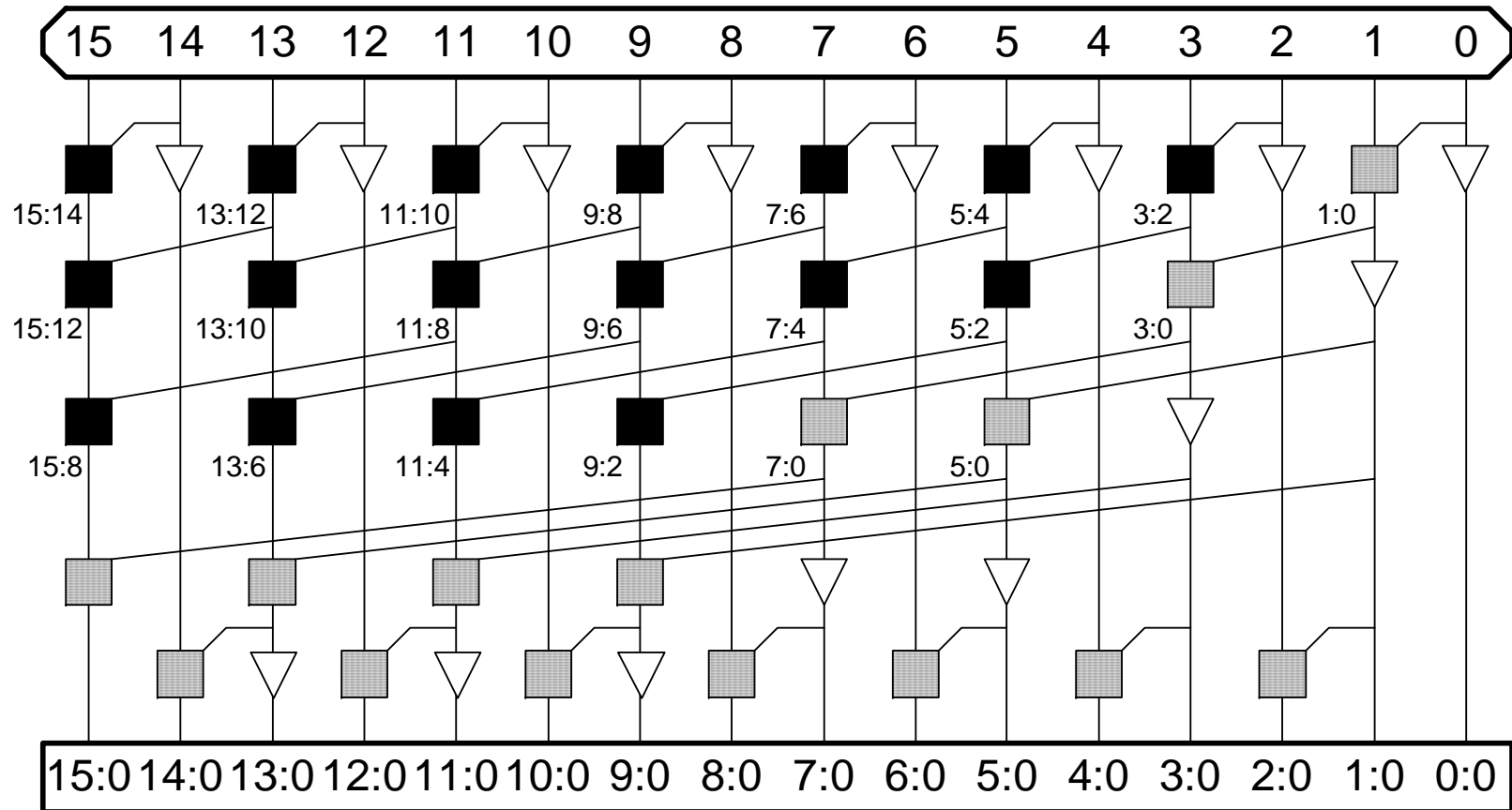

Knowles [2, 1, 1, 1]

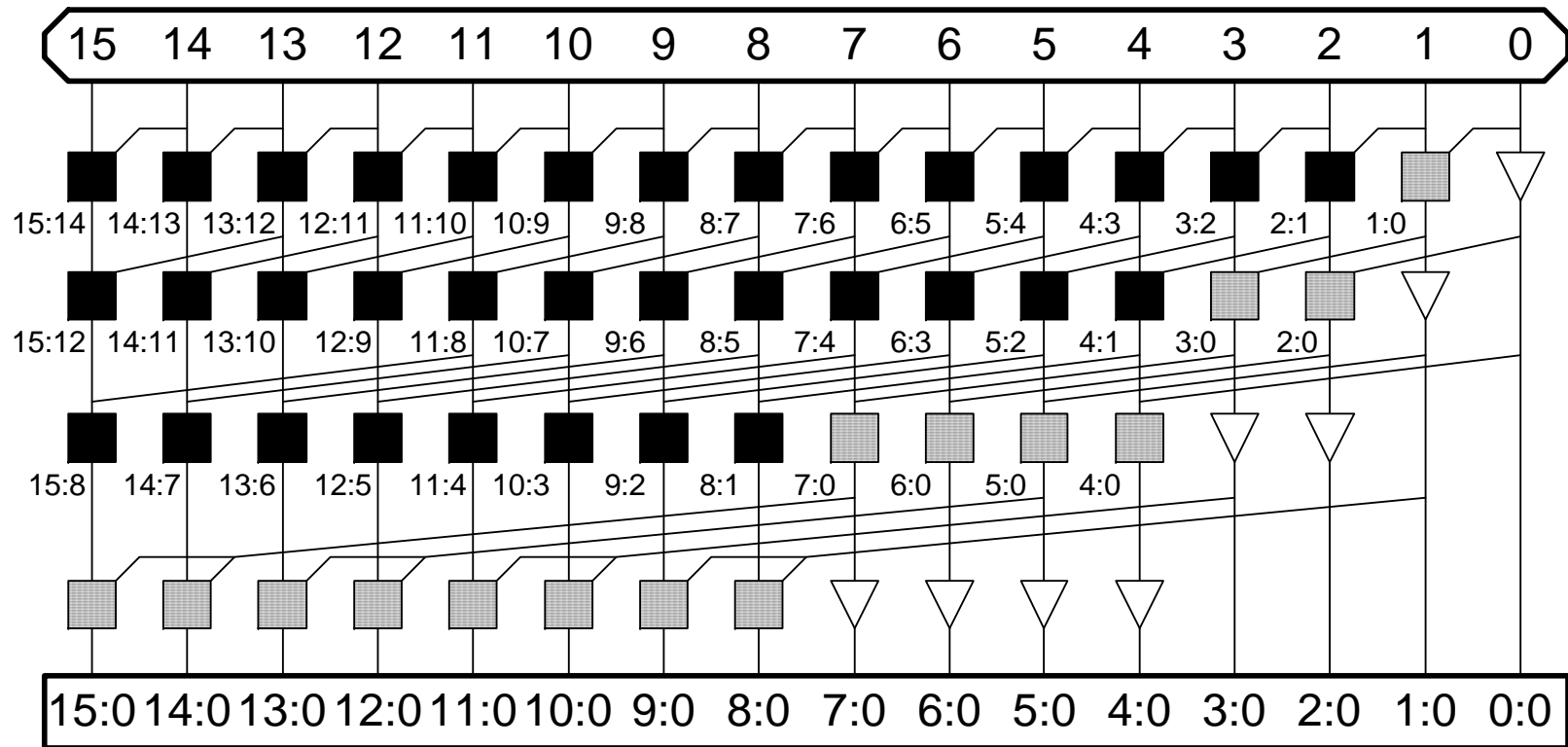


Ladner-Fischer

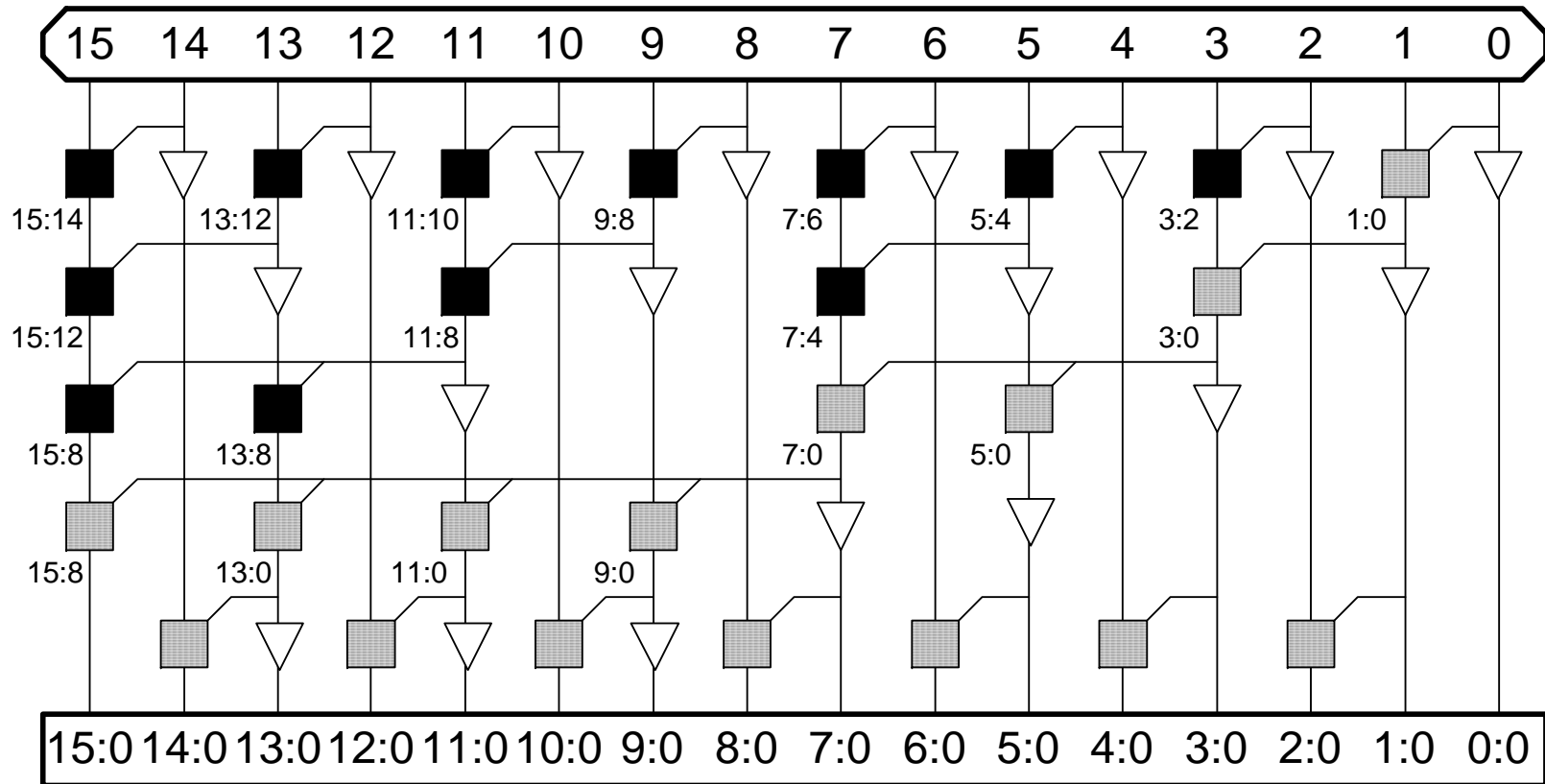


Taxonomy Revisited


(b) Sklansky

 


(e) Knowles [2,1,1,1]

 


(c) Kogge-Stone

 



(f) Ladner-Fischer

 

(a) Brent-Kung

 

(d) Han-Carlson

  

Summary

Adder architectures offer area / power / delay tradeoffs.
Choose the best one for your application.

Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		$N-1$	1	1	N
Carry-Skip $n=4$		$N/4 + 5$	2	1	$1.25N$
Carry-Inc. $n=4$		$N/4 + 2$	4	1	$2N$
Brent-Kung	$(L-1, 0, 0)$	$2\log_2 N - 1$	2	1	$2N$
Sklansky	$(0, L-1, 0)$	$\log_2 N$	$N/2 + 1$	1	$0.5 N \log_2 N$
Kogge-Stone	$(0, 0, L-1)$	$\log_2 N$	2	$N/2$	$N \log_2 N$