

# **Lecture 1: Circuits & Layout**


# Outline

---


- ☐ A Brief History
- ☐ CMOS Gate Design
- ☐ Pass Transistors
- ☐ CMOS Latches & Flip-Flops
- ☐ Standard Cell Layouts
- ☐ Stick Diagrams
 
# A Brief History

- ❑ 1958: First integrated circuit
  - Flip-flop using two transistors
  - Built by Jack Kilby at Texas Instruments
- ❑ 2010
  - Intel Core i7  $\mu$ processor
    - 2.3 billion transistors
  - 64 Gb Flash memory
    - > 16 billion transistors



Courtesy Texas Instruments

 

[Trinh09]  
© 2009 IEEE.

# Growth Rate

- ❑ 53% compound annual growth rate over 50 years
  - No other technology has grown so fast so long
- ❑ Driven by miniaturization of transistors
  - Smaller is cheaper, faster, lower in power!
  - Revolutionary effects on society




[Moore65]

Electronics Magazine

 
# Annual Sales

- ❑  $>10^{19}$  transistors manufactured in 2008
  - 1 billion for every human on the planet


 
# Invention of the Transistor

- ❑ Vacuum tubes ruled in first half of 20<sup>th</sup> century  
Large, expensive, power-hungry, unreliable
- ❑ 1947: first point contact transistor
  - John Bardeen and Walter Brattain at Bell Labs
  - See *Crystal Fire*  
by Riordan, Hodgeson



AT&T Archives.  
Reprinted with  
permission.


# Transistor Types

- ❑ Bipolar transistors
  - npn or pnp silicon structure
  - Small current into very thin base layer controls large currents between emitter and collector
  - Base currents limit integration density
- ❑ Metal Oxide Semiconductor Field Effect Transistors
  - nMOS and pMOS MOSFETS
  - Voltage applied to insulated gate controls current between source and drain
  - Low power allows very high integration




# MOS Integrated Circuits

- ❑ 1970's processes usually had only nMOS transistors
  - Inexpensive, but consume power while idle

 

[Vadasz69]  
© 1969 IEEE.

Intel 1101 256-bit SRAM

 

Intel Museum.  
Reprinted with permission.


Intel 4004 4-bit  $\mu$ Proc

- ❑ 1980s-present: CMOS processes for low idle power



# Moore's Law: Then

- ❑ 1965: Gordon Moore plotted transistor on each chip
  - Fit straight line on semilog scale
  - Transistor counts have doubled every 26 months

 

[Moore65]

Electronics Magazine

## Integration Levels


**SSI:** 10 gates

**MSI:** 1000 gates

**LSI:** 10,000 gates


**VLSI:** > 10k gates

# And Now...

 

 
# Feature Size

- ❑ Minimum feature size shrinking 30% every 2-3 years


 
# Corollaries

- Many other factors grow exponentially
  - Ex: clock frequency, processor performance



# CMOS Gate Design


---

- Activity:
  - Sketch a 4-input CMOS NOR gate


 
# Complementary CMOS


- ❑ Complementary CMOS logic gates
  - nMOS *pull-down network*
  - pMOS *pull-up network*
  - a.k.a. static CMOS



	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

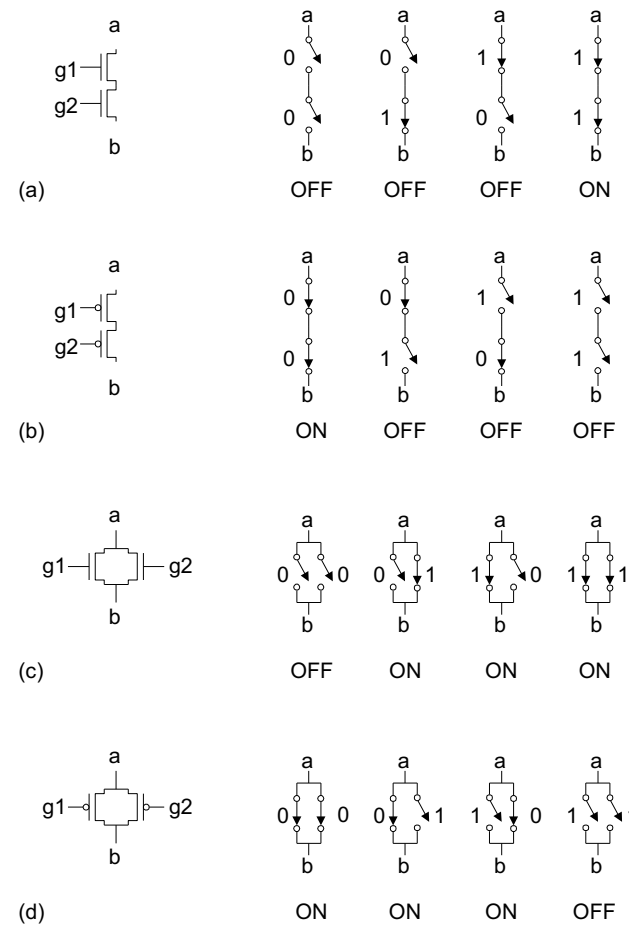
# Series and Parallel

- ❑ nMOS: 1 = ON
- ❑ pMOS: 0 = ON
- ❑ *Series*: both must be ON
- ❑ *Parallel*: either can be ON





 
# Conduction Complement

- ❑ Complementary CMOS gates always produce 0 or 1
- ❑ Ex: NAND gate
  - Series nMOS:  $Y=0$  when both inputs are 1
  - Thus  $Y=1$  when either input is 0
  - Requires parallel pMOS
- ❑ Rule of *Conduction Complements*
  - Pull-up network is complement of pull-down
  - Parallel  $\rightarrow$  series, series  $\rightarrow$  parallel



   
# Compound Gates

- ❑ Compound gates can do any inverting function
- ❑ Ex:  $Y = A \cdot B + C \cdot D$  (AND-AND-OR-INVERT, AOI22)


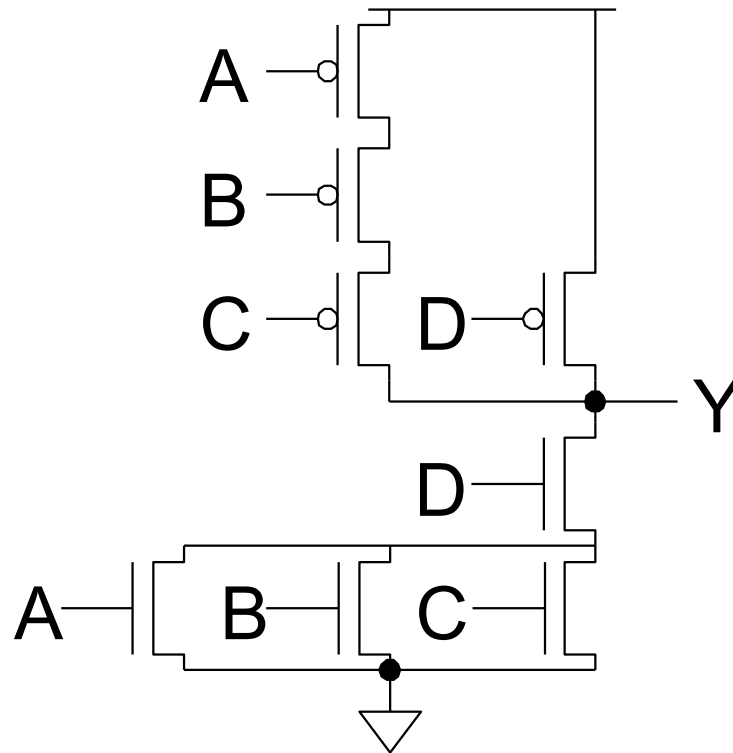
# Example: O3AI

$$\square Y = \overline{(A + B + C) \cdot D}$$














# Signal Strength

- ❑ *Strength* of signal
  - How close it approximates ideal voltage source
- ❑  $V_{DD}$  and GND rails are strongest 1 and 0
- ❑ nMOS pass strong 0
  - But degraded or weak 1
- ❑ pMOS pass strong 1
  - But degraded or weak 0
- ❑ Thus nMOS are best for pull-down network


# Pass Transistors

- Transistors can be used as switches

         

 
# Transmission Gates

- ❑ Pass transistors produce degraded outputs
- ❑ *Transmission gates* pass both 0 and 1 well



$g = 0, gb = 1$

 

$g = 1, gb = 0$



Input




Output

$g = 1, gb = 0$

0 → strong 0

$g = 1, gb = 0$



1 → strong 1

   

# Tristates


- ❑ *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	
0	1	
1	0	
1	1	

  
 
# Nonrestoring Tristate


- ❑ Transmission gate acts as tristate buffer
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y




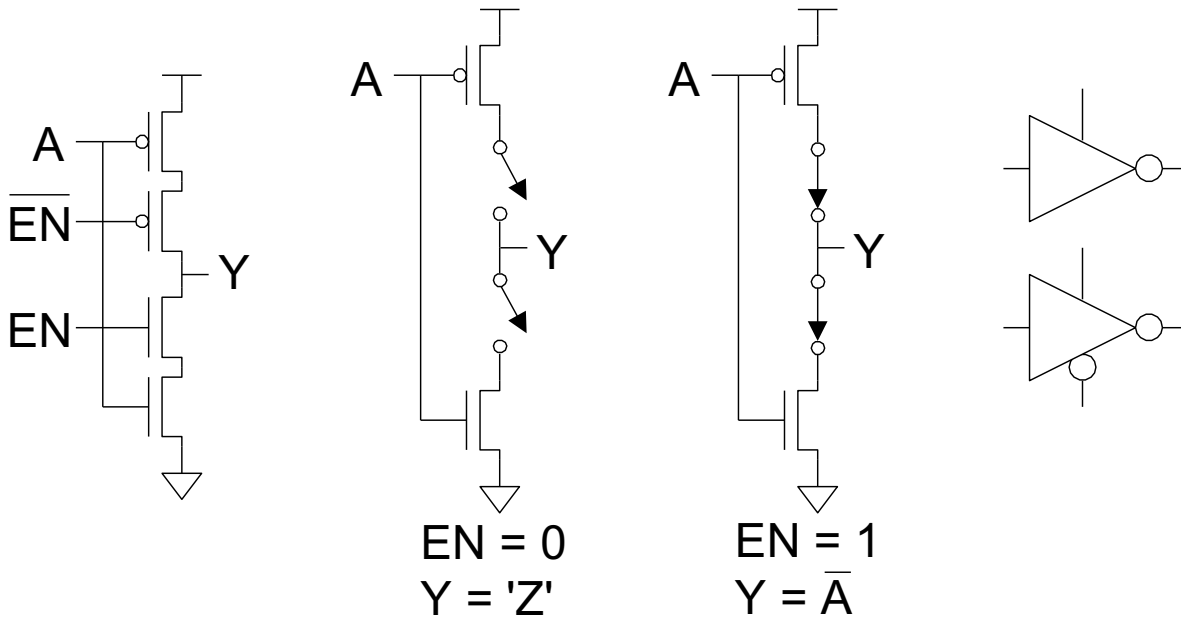
# Tristate Inverter


- ❑ Tristate inverter produces restored output
  - Violates conduction complement rule
  - Because we want a Z output



# Multiplexers

- ❑ 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

 


# Gate-Level Mux Design

- ❑  $Y = SD_1 + \bar{S}D_0$  (too many transistors)
- ❑ How many transistors are needed?



 
# Transmission Gate Mux

- ❑ Nonrestoring mux uses two transmission gates
  - Only 4 transistors


   
# Inverting Mux



- ❑ Inverting multiplexer
  - Use compound AOI22
  - Or pair of tristate inverters
  - Essentially the same thing
- ❑ Noninverting multiplexer adds an inverter





  
# 4:1 Multiplexer

- ❑ 4:1 mux chooses one of 4 inputs using two selects
  - Two levels of 2:1 muxes
  - Or four tristates




 
# D Latch

- ❑ When  $\text{CLK} = 1$ , latch is *transparent*
  - D flows through to Q like a buffer
- ❑ When  $\text{CLK} = 0$ , the latch is *opaque*
  - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or *level-sensitive latch*






# D Latch Design

- ❑ Multiplexer chooses D or old Q

  


# D Latch Operation

   

 
# D Flip-flop

- ❑ When CLK rises, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*




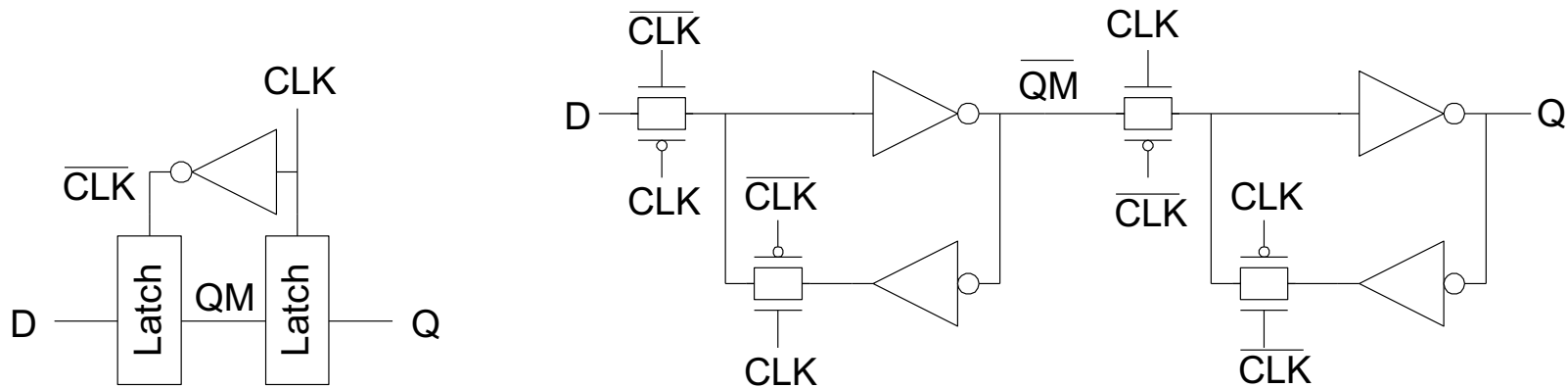
# D Flip-flop Design

- ❑ Built from master and slave D latches




\_\_\_\_\_

  
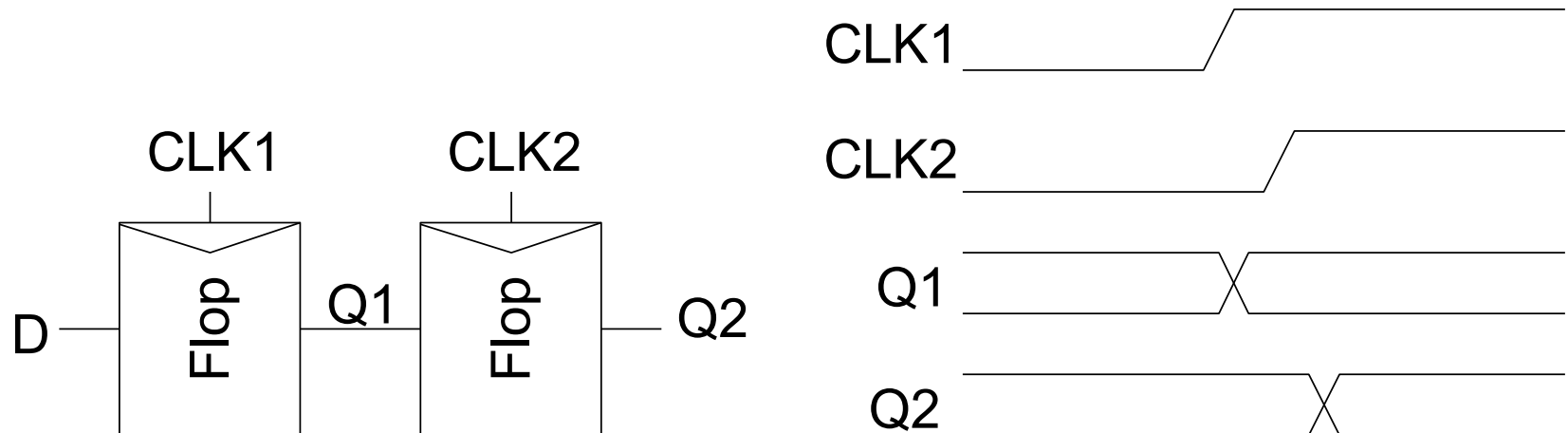
# Race Condition


- ❑ Back-to-back flops can malfunction from clock skew
  - Second flip-flop fires late
  - Sees first flip-flop change and captures its result
  - Called *hold-time failure* or *race condition*




 
# Nonoverlapping Clocks


- ❑ Nonoverlapping clocks can prevent races
  - As long as nonoverlap exceeds clock skew
- ❑ We will use them in this class for safe design
  - Industry manages skew more carefully instead



# Gate Layout


- ❑ Layout can be very time consuming
  - Design gates to fit together nicely
  - Build a library of standard cells
- ❑ Standard cell design methodology
  - $V_{DD}$  and GND should abut (standard height)
  - Adjacent gates should satisfy design rules
  - nMOS at bottom and pMOS at top
  - All gates include well and substrate contacts

# Example: Inverter

 

 
# Example: NAND3

- ❑ Horizontal N-diffusion and p-diffusion strips
- ❑ Vertical polysilicon gates
- ❑ Metal1  $V_{DD}$  rail at top
- ❑ Metal1 GND rail at bottom
- ❑  $32\lambda$  by  $40\lambda$



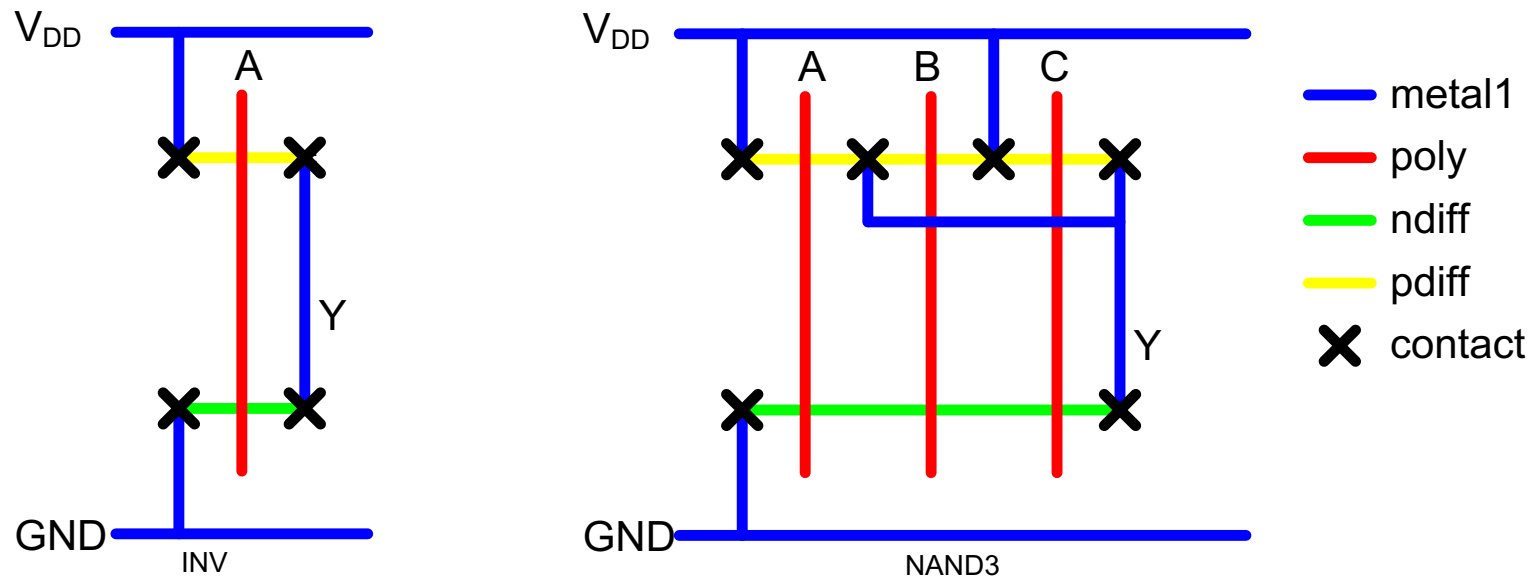
# Stick Diagrams

- ❑ *Stick diagrams* help plan layout quickly
  - Need not be to scale
  - Draw with color pencils or dry-erase markers



 
# Wiring Tracks

- ❑ A *wiring track* is the space required for a wire
  - $4\lambda$  width,  $4\lambda$  spacing from neighbor =  $8\lambda$  pitch
- ❑ Transistors also consume one wiring track



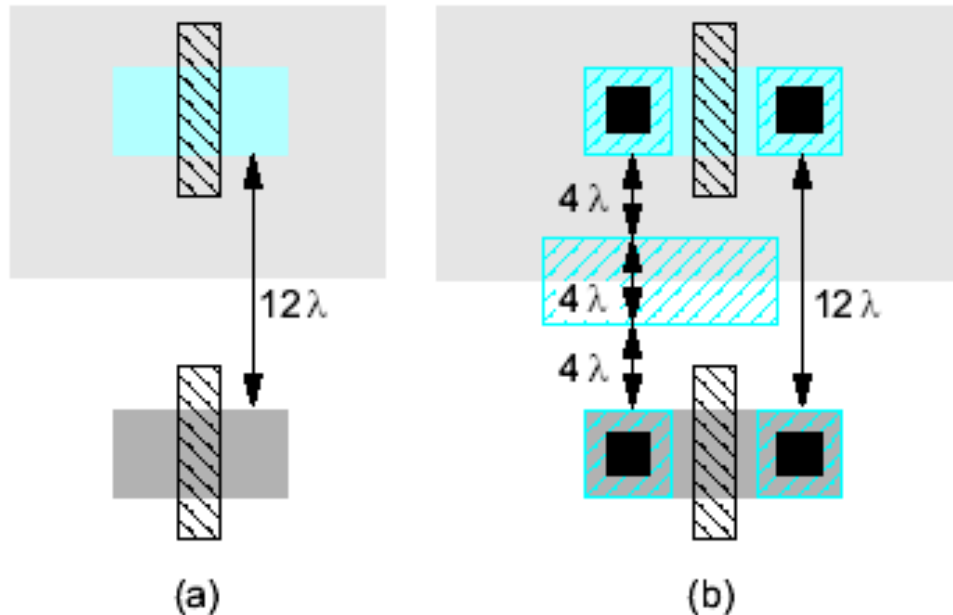
# Well spacing

- ❑ Wells must surround transistors by  $6\lambda$ 
  - Implies  $12\lambda$  between opposite transistor flavors
  - Leaves room for one wire track


 
# Area Estimation

- ❑ Estimate area by counting wiring tracks
  - Multiply by 8 to express in  $\lambda$





# Example: O3AI

- Sketch a stick diagram for O3AI and estimate area

$$Y = \overline{(A + B + C)} \cdot D$$

