

# **Lecture 12: Adders**

# Outline

---


- ☐ Single-bit Addition
- ☐ Carry-Ripple Adder
- ☐ Carry-Skip Adder
- ☐ Carry-Lookahead Adder
- ☐ Carry-Select Adder
- ☐ Carry-Increment Adder
- ☐ Tree Adder

# Single-Bit Addition

## Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	$C_{out}$	S
0	0		
0	1		
1	0		
1	1		

## Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	$C_{out}$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

# PGK


- ❑ For a full adder, define what happens to carries  
(in terms of A and B)
  - Generate:  $C_{out} = 1$  independent of C
    - $G =$
  - Propagate:  $C_{out} = C$ 
    - $P =$
  - Kill:  $C_{out} = 0$  independent of C
    - $K =$

# Full Adder Design I

- ❑ Brute force implementation from eqns


$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

 

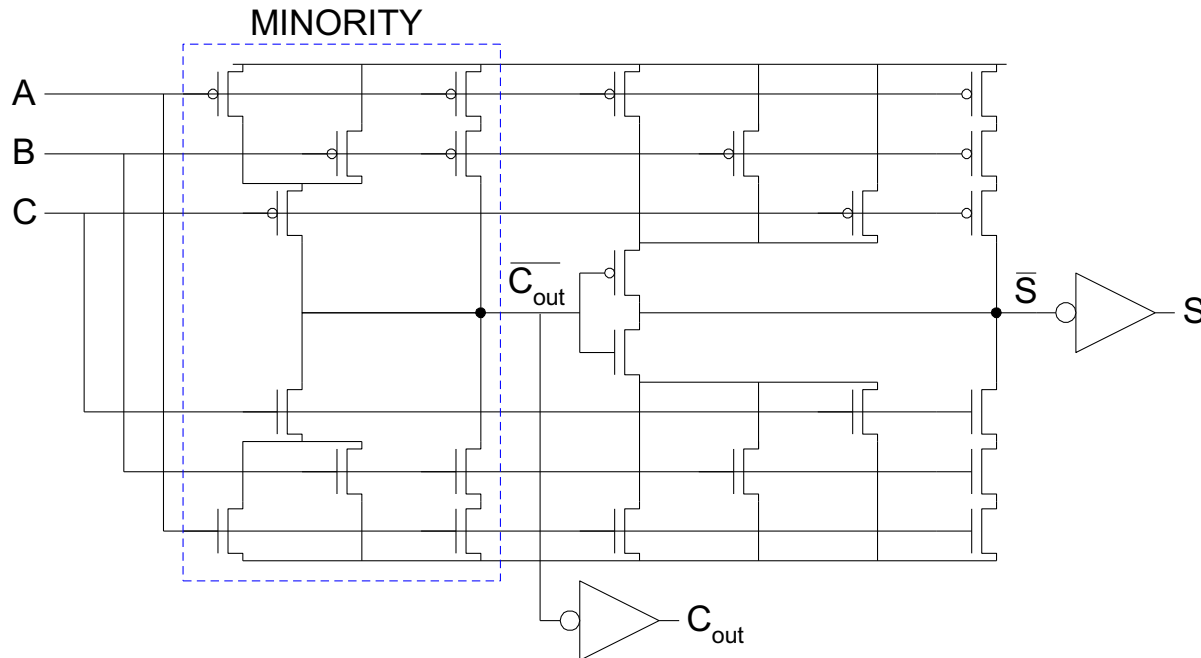
# Full Adder Design II

- ❑ Factor S in terms of  $C_{out}$   
$$S = ABC + (A + B + C)(\sim C_{out})$$
- ❑ Critical path is usually C to  $C_{out}$  in ripple adder



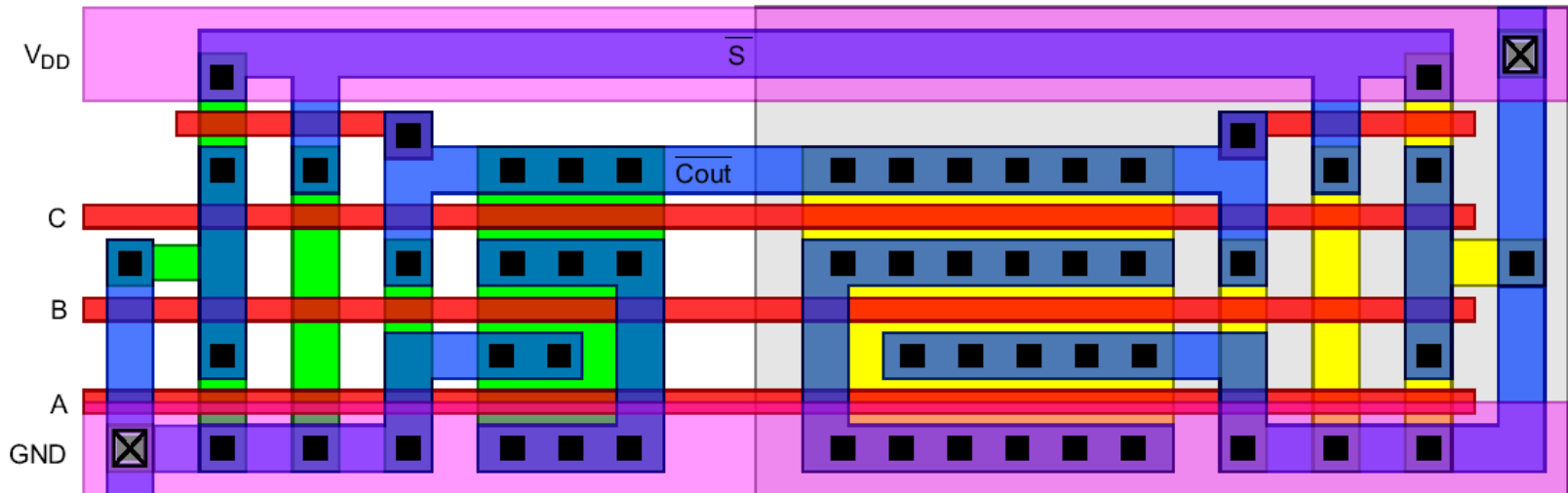
# Layout

- ❑ Clever layout circumvents usual line of diffusion
  - Use wide transistors on critical path
  - Eliminate output inverters


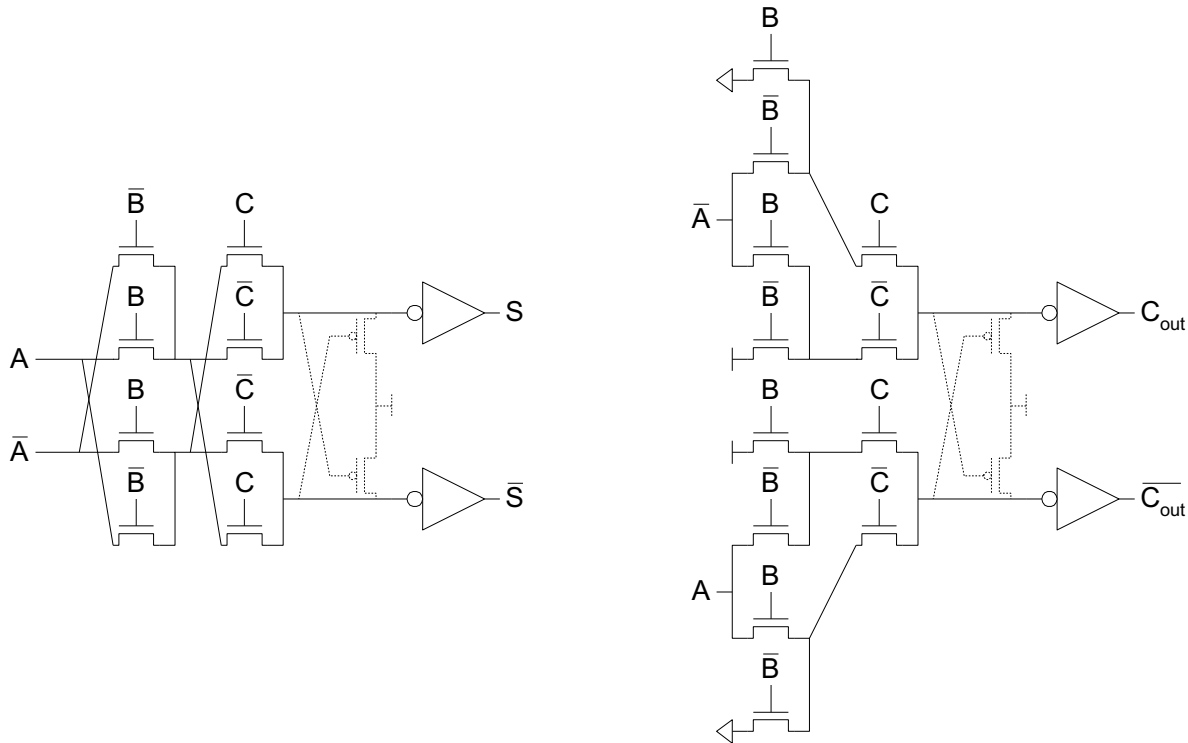
# Full Adder Design III


- ❑ Complementary Pass Transistor Logic (CPL)
  - Slightly faster, but more area





 
# Full Adder Design IV

- ❑ Dual-rail domino
  - Very fast, but large and power hungry
  - Used in very fast multipliers


 
# Carry Propagate Adders

- N-bit adder called CPA
  - Each sum bit depends on all previous carries
  - How do we compute all these carries quickly?




$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{0}000\textcircled{0} \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{1}111\textcircled{1} \\ 1111 \\ +0000 \\ \hline 0000 \end{array} \quad \begin{array}{l} \text{carries} \\ A_{4...1} \\ B_{4...1} \\ S_{4...1} \end{array}$$

 
# Carry-Ripple Adder

- ❑ Simplest design: cascade full adders
  - Critical path goes from  $C_{in}$  to  $C_{out}$
  - Design full adder to have fast carry delay


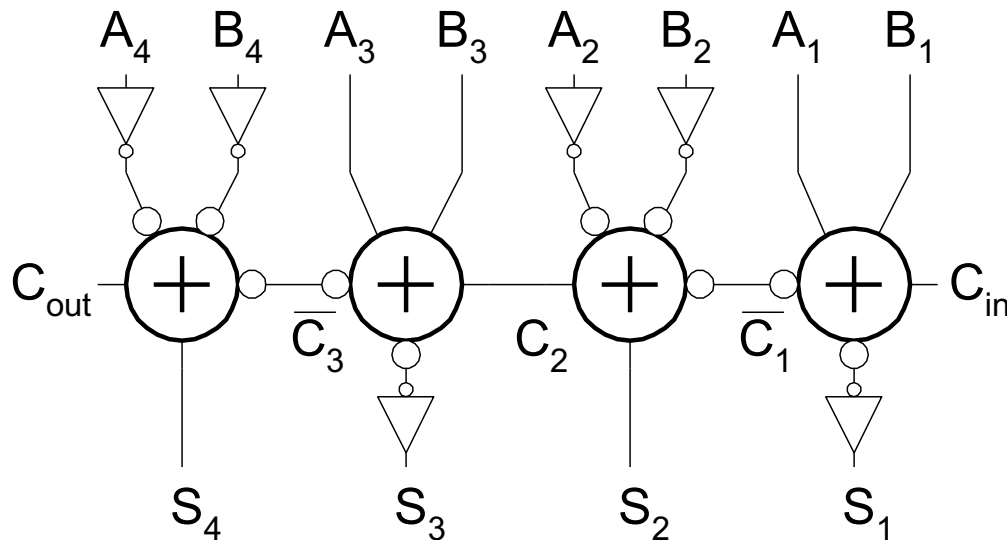
# Inversions

- ❑ Critical path passes through majority gate
  - Built from minority + inverter
  - Eliminate inverter and use inverting full adder



# Generate / Propagate

- ❑ Equations often factored into G and P
- ❑ Generate and propagate for groups spanning i:j

$$G_{i:j} =$$

$$P_{i:j} =$$

- ❑ Base case

$$G_{i:i} \equiv$$

$$P_{i:i} \equiv$$


$$G_{0:0} \equiv$$

$$P_{0:0} \equiv$$

- ❑ Sum:


$$S_i =$$

# PG Logic

 


# Carry-Ripple Revisited

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

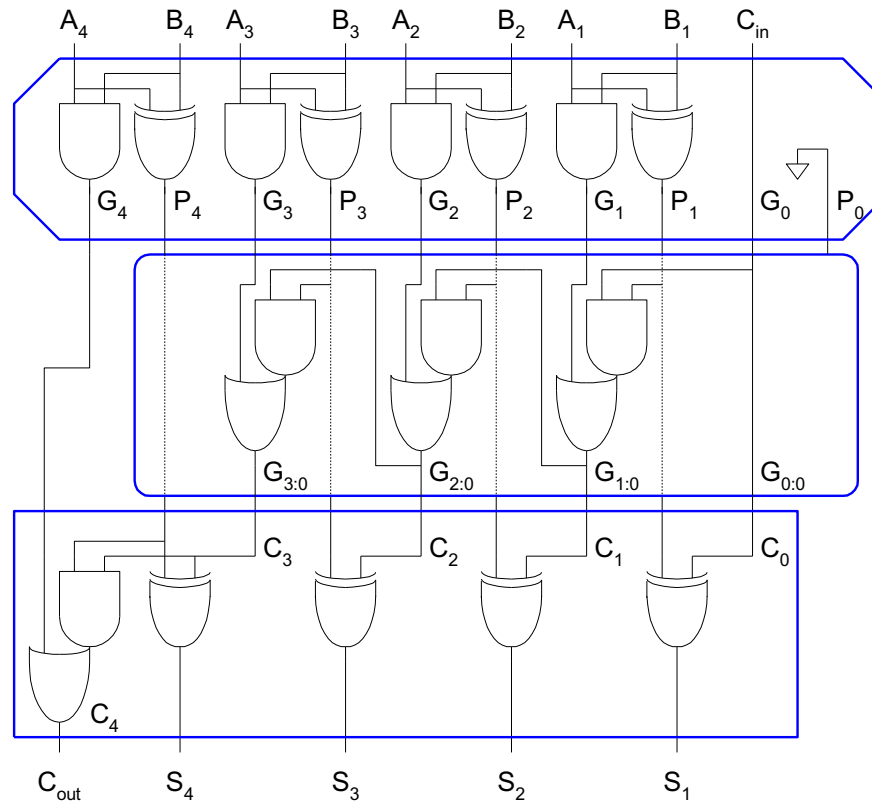

# Carry-Ripple PG Diagram


$t_{\text{ripple}} =$

 




# PG Diagram Notation





Black cell

 

Gray cell

 


Buffer

    

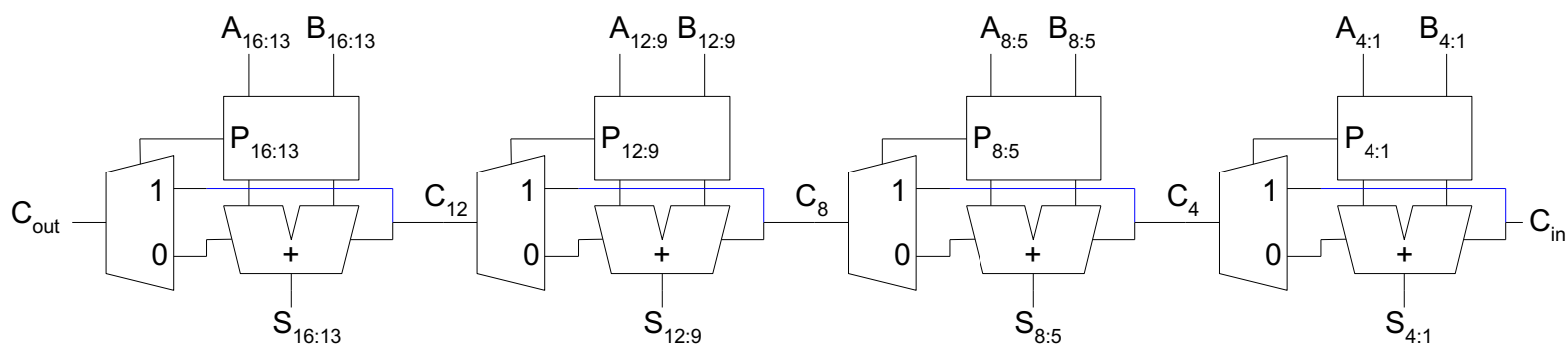
# Carry-Skip Adder

- ❑ Carry-ripple is slow through all N stages
- ❑ Carry-skip allows carry to skip over groups of n bits
  - Decision based on n-bit propagate signal




# Carry-Skip PG Diagram

 

For k n-bit groups ( $N = nk$ )

$$t_{\text{skip}} =$$


# Variable Group Size

 


Delay grows as  $O(\sqrt{N})$
 
# Carry-Lookahead Adder


- ❑ Carry-lookahead adder computes  $G_{i:0}$  for many bits in parallel.
- ❑ Uses higher-valency cells with more than two inputs.



# CLA PG Diagram

 


# Higher-Valency Cells

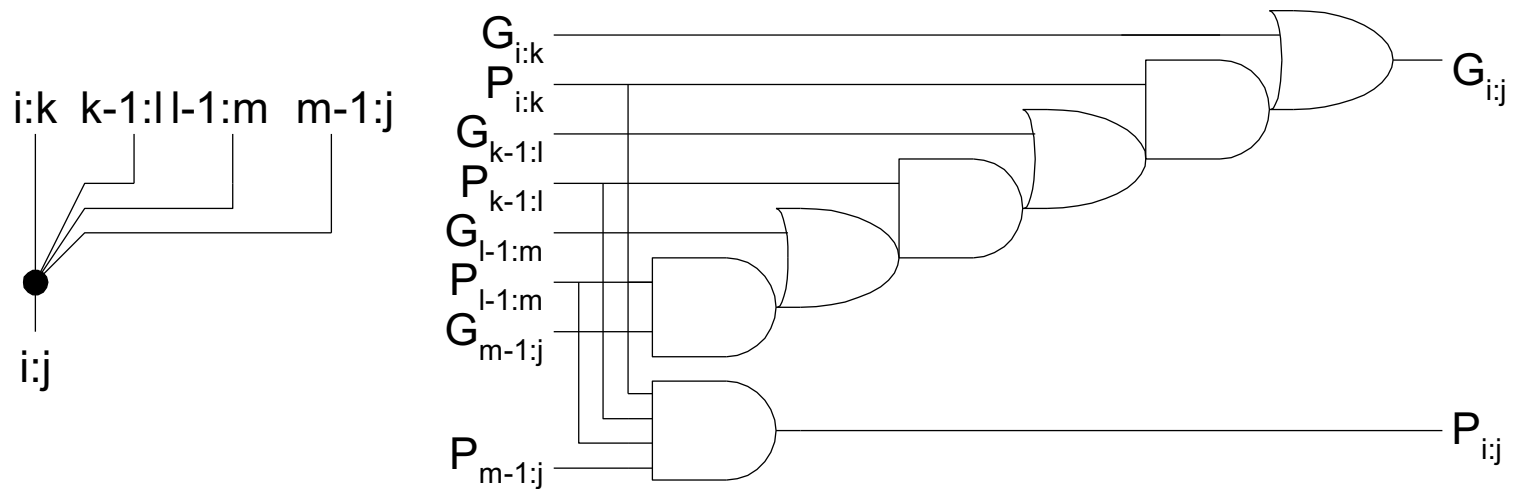
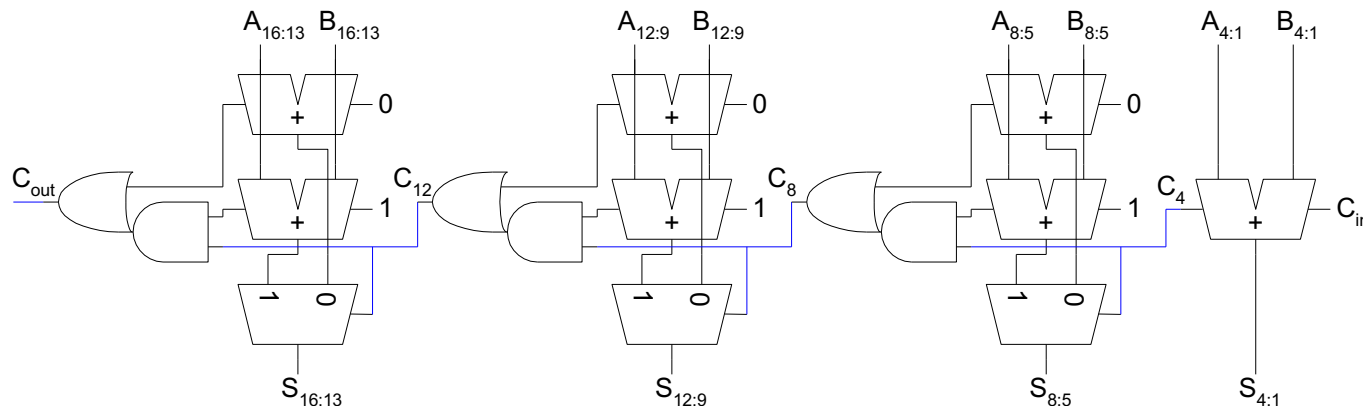
# Carry-Select Adder


- ❑ Trick for critical paths dependent on late input X
  - Precompute two possible outputs for  $X = 0, 1$
  - Select proper output when  $X$  arrives
- ❑ Carry-select adder precomputes n-bit sums
  - For both possible carries into n-bit group




 
# Carry-Increment Adder


- Factor initial PG and final XOR out of carry-select



$$t_{\text{increment}} =$$

# Variable Group Size


- Also buffer noncritical signals

 


# Tree Adder

- ❑ If lookahead is good, lookahead across lookahead!
  - Recursive lookahead gives  $O(\log N)$  delay
- ❑ Many variations on tree adders


# Brent-Kung

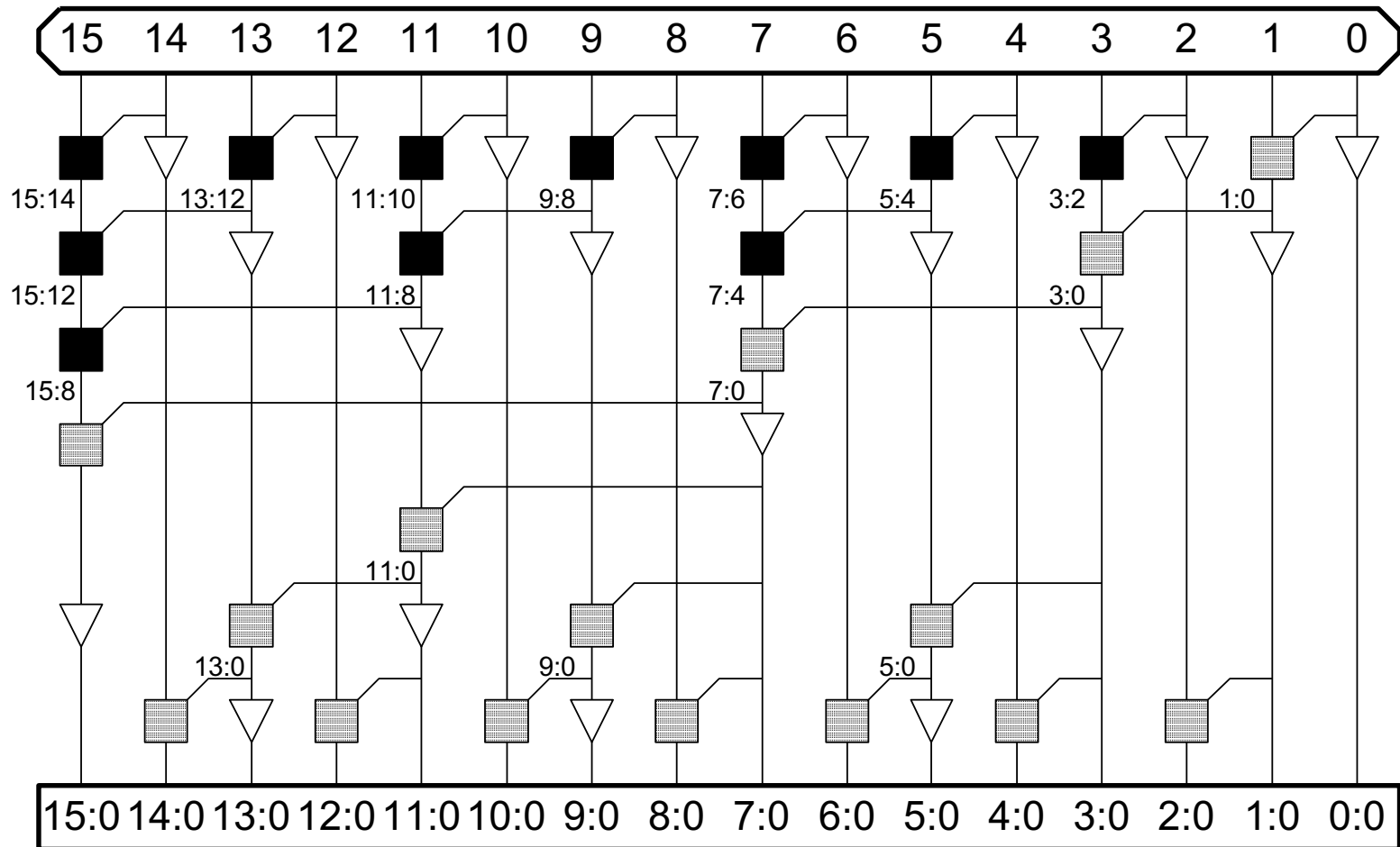

# Sklansky

 


# Kogge-Stone

 

# Tree Adder Taxonomy


- ❑ Ideal N-bit tree adder would have
  - $L = \log N$  logic levels
  - Fanout never exceeding 2
  - No more than one wiring track between levels
- ❑ Describe adder with 3-D taxonomy ( $l, f, t$ )
  - Logic levels:  $L + l$
  - Fanout:  $2^f + 1$
  - Wiring tracks:  $2^t$
- ❑ Known tree adders sit on plane defined by
$$l + f + t = L - 1$$

# Tree Adder Taxonomy

 





# Han-Carlson

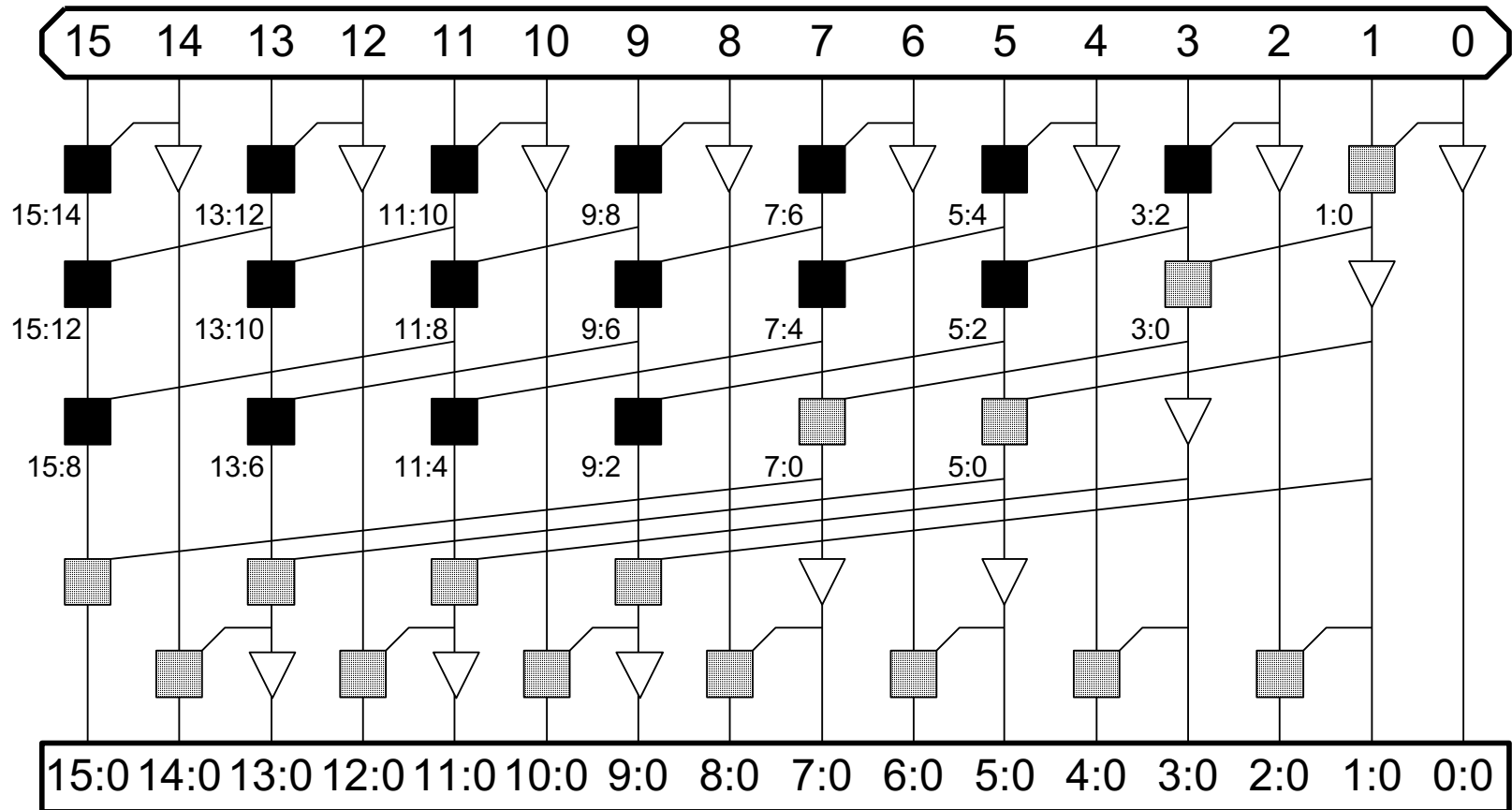


# Knowles [2, 1, 1, 1]

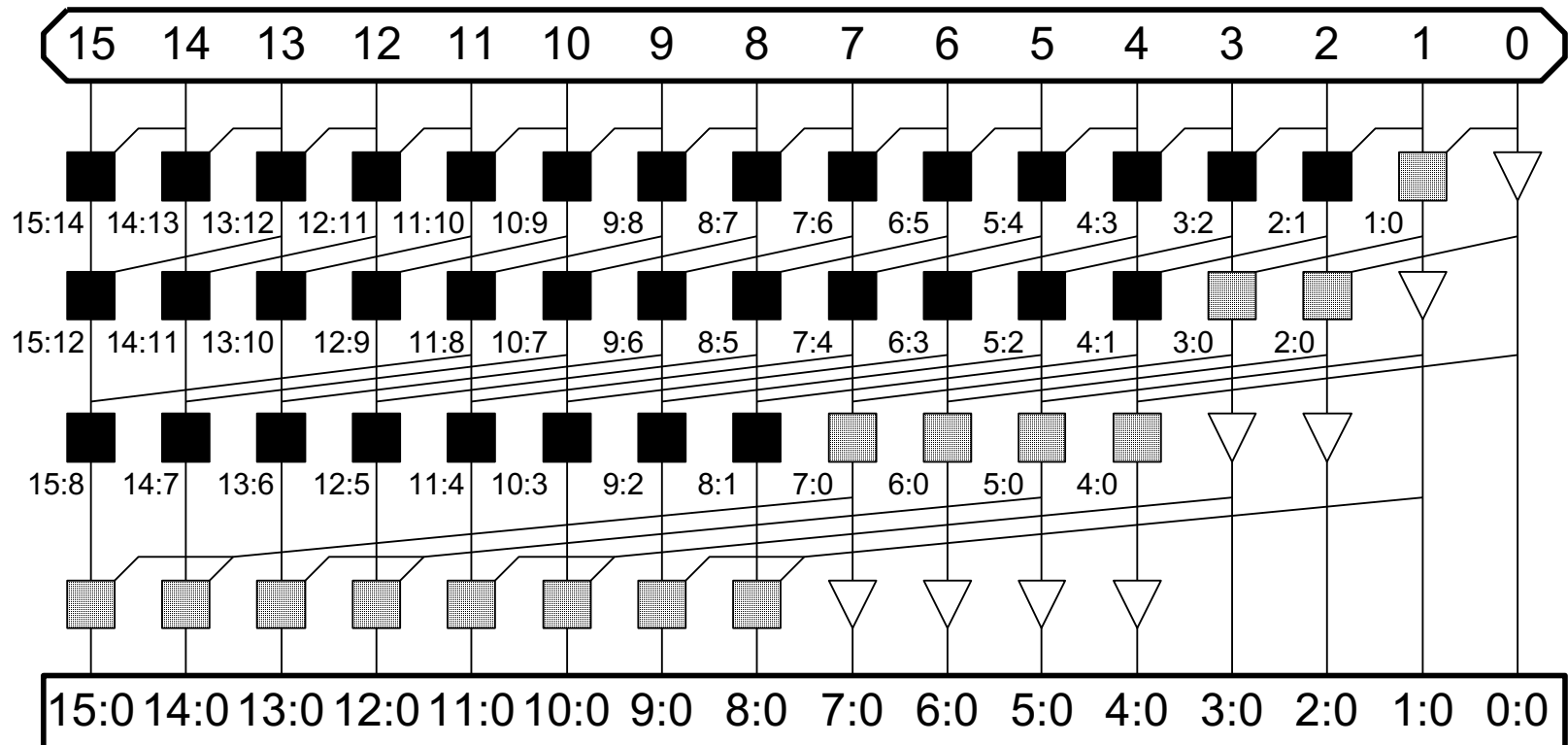

# Ladner-Fischer

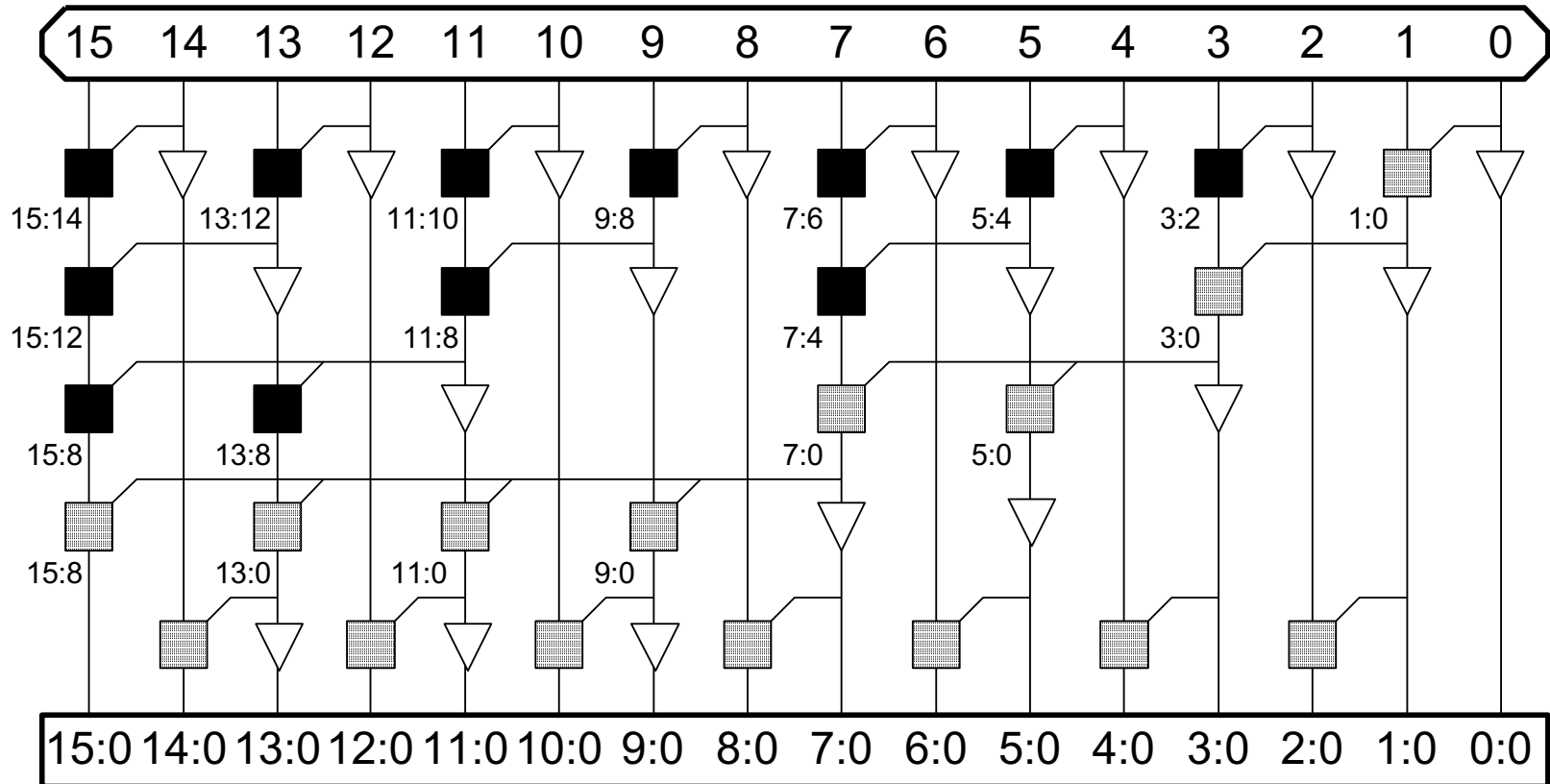

# Taxonomy Revisited

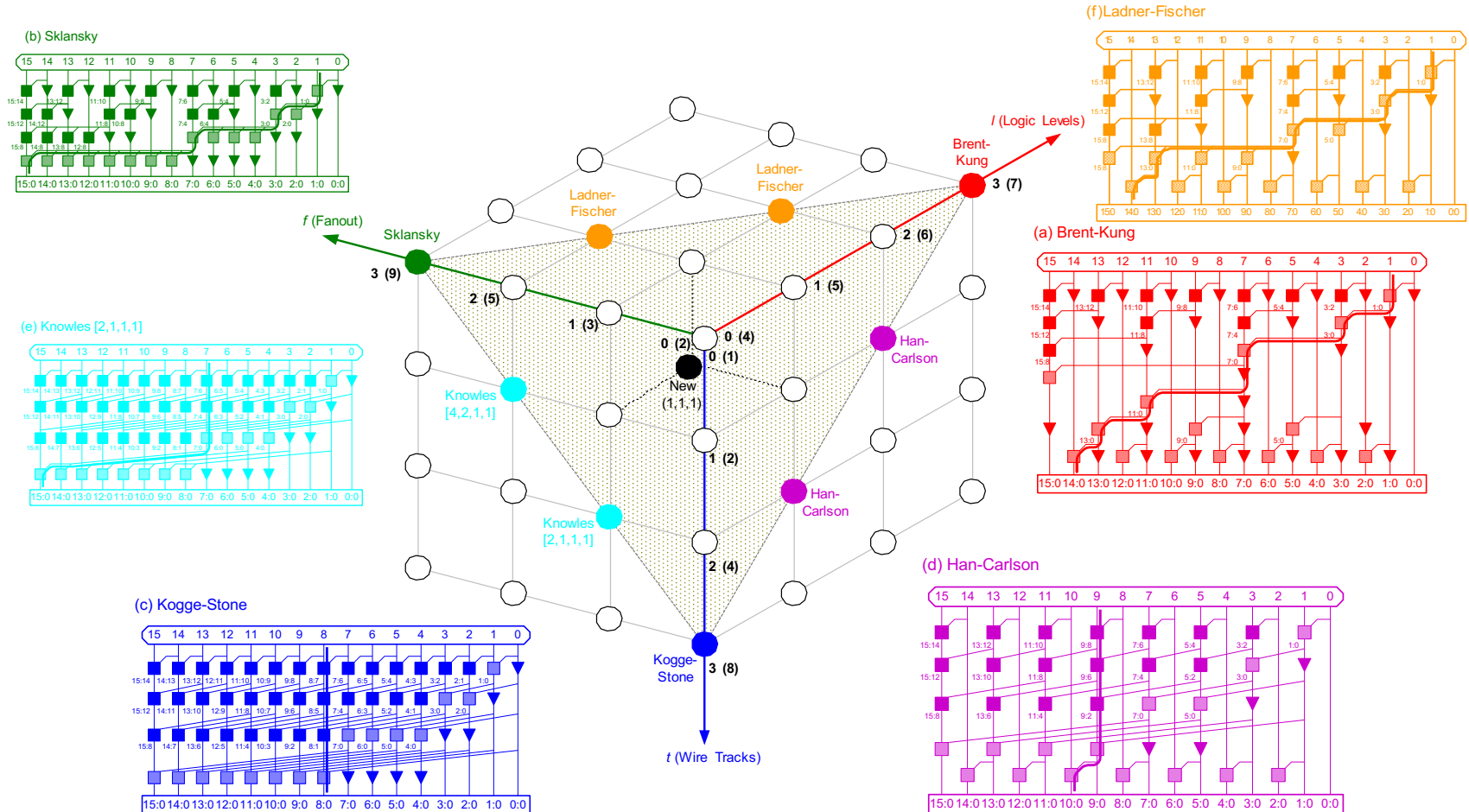

# Summary

Adder architectures offer area / power / delay tradeoffs.

Choose the best one for your application.

Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		$N-1$	1	1	$N$
Carry-Skip $n=4$		$N/4 + 5$	2	1	$1.25N$
Carry-Inc. $n=4$		$N/4 + 2$	4	1	$2N$
Brent-Kung	$(L-1, 0, 0)$	$2\log_2 N - 1$	2	1	$2N$
Sklansky	$(0, L-1, 0)$	$\log_2 N$	$N/2 + 1$	1	$0.5 N \log_2 N$
Kogge-Stone	$(0, 0, L-1)$	$\log_2 N$	2	$N/2$	$N \log_2 N$