

Lecture 18: Circuit Pitfalls

Outline

- ☐ Variation
- ☐ Noise Budgets
- ☐ Reliability
- ☐ Circuit Pitfalls

Variation


- ❑ Process
 - Threshold
 - Channel length
 - Interconnect dimensions
- ❑ Environment
 - Voltage
 - Temperature
- ❑ Aging / Wearout

Process Variation

❑ Threshold Voltage

- Depends on placement of dopants in channel
- Standard deviation inversely proportional to channel area

$$\sigma_{V_t} = \frac{t_{\text{ox}}}{\epsilon_{\text{ox}}} \frac{\sqrt[4]{q^3 \epsilon_{\text{si}} \phi_b N_a}}{\sqrt{2LW}} = \frac{A_{V_t}}{\sqrt{LW}}$$

 

[Bernstein06]

❑ Channel Length


- Systematic *across-chip linewidth variation* (ACLV)
- Random line edge roughness (LER)



Courtesy Texas Instruments

❑ Interconnect

- Etching variations affect w, s, h

 


Courtesy Larry Pileggi

Spatial Distribution

☐ Variations show spatial correlation

- *Lot-to-lot* (L2L)
- *Wafer-to-wafer* (W2W)
- *Die-to-die* (D2D) / *inter-die*
- *Within-die* (WID) / *intradie*

☐ Closer transistors match better

 


Courtesy M. Pelgrom

Environmental Variation

□ Voltage

 - V_{DD} is usually designed +/- 10%
- Regulator error
- On-chip droop from switching activity




Courtesy IBM

□ Temperature

- Ambient temperature ranges
- On-die temperature elevated by chip power consumption

Standard	Minimum	Maximum
Commercial	0 °C	70 °C
Industrial	-40 °C	85 °C
Military	-55 °C	125 °C

 


[Harris01b]

Aging

- ❑ Transistors change over time as they wear out
 - Hot carriers
 - Negative bias temperature instability
 - Time-dependent dielectric breakdown
- ❑ Causes threshold voltage changes
- ❑ More on this later...

Process Corners

 - ❑ Model extremes of process variations in simulation
- ❑ Corners
 - Typical (T)
 - Fast (F)
 - Slow (S)
- ❑ Factors
 - nMOS speed
 - pMOS speed
 - Wire
 - Voltage
 - Temperature



Corner	Voltage	Temperature
F	1.98	0 °C
T	1.8	70 °C
S	1.62	125 °C


Corner Checks

- ❑ Circuits are simulated in different corners to verify different performance and correctness specifications

Corner					Purpose
nMOS	pMOS	Wire	V_{DD}	Temp	
T	T	T	S	S	Timing specifications (binned parts)
S	S	S	S	S	Timing specifications (conservative)
F	F	F	F	F	Race conditions, hold time constraints, pulse collapse, noise
S	S	?	F	S	Dynamic power
F	F	F	F	S	Subthreshold leakage noise and power, overall noise analysis
S	S	F	S	S	Races of gates against wires
F	F	S	F	F	Races of wires against gates
S	F	T	F	F	Pseudo-nMOS and ratioed circuits noise margins, memory read/write, race of pMOS against nMOS
F	S	T	F	F	Ratioed circuits, memory read/write, race of nMOS against pMOS

Monte Carlo Simulation

 - ❑ As process variation increases, the worst-case corners become too pessimistic for practical design
- ❑ Monte Carlo: repeated simulations with parameters randomly varied each time
- ❑ Look at scatter plot of results to predict yield
- ❑ Ex: impact of V_t variation
 - ON-current
 - leakage



Noise

❑ Sources

- Power supply noise / ground bounce
- Capacitive coupling
- Charge sharing
- Leakage
- Noise feedthrough

❑ Consequences

- Increased delay (for noise to settle out)
- Or incorrect computations

Reliability


❑ Hard Errors

- Oxide wearout
- Interconnect wearout
- Overvoltage failure
- Latchup

❑ Soft Errors


❑ Characterizing reliability

 - Mean time between failures (MTBF)
 - # of devices × hours of operation / number of failures
- Failures in time (FIT)
 - # of failures / thousand hours / million devices



Accelerated Lifetime Testing

 - ❑ Expected reliability typically exceeds 10 years
- ❑ But products come to market in 1-2 years
- ❑ Accelerated lifetime testing required to predict adequate long-term reliability



Hot Carriers

- ❑ Electric fields across channel impart high energies to some carriers
 - These “hot” carriers may be blasted into the gate oxide where they become trapped
 - Accumulation of charge in oxide causes shift in V_t over time
 - Eventually V_t shifts too far for devices to operate correctly
- ❑ Choose V_{DD} to achieve reasonable product lifetime
 - Worst problems for inverters and NORs with slow input risetime and long propagation delays

NBTI

- ❑ *Negative bias temperature instability*
- ❑ Electric field applied across oxide forms dangling bonds called traps at Si-SiO₂ interface
- ❑ Accumulation of traps causes V_t shift
- ❑ Most pronounced for pMOS transistors with strong negative bias ($V_g = 0$, $V_s = V_{DD}$) at high temperature

$$\Delta V_t = k e^{\frac{E_{ox}}{E_0}} t^{0.25}$$

$$E_{ox} = V_{DD}/t_{ox}$$

TDDDB


- ❑ *Time-dependent dielectric breakdown*
 - Gradual increase in gate leakage when an electric field is applied across an oxide
 - a.k.a *stress-induced leakage current*
- ❑ For 10-year life at 125 C, keep E_{ox} below ~ 0.7 V/nm

Electromigration

- ❑ “Electron wind” causes movement of metal atoms along wires
- ❑ Excessive electromigration leads to open circuits
- ❑ Most significant for unidirectional (DC) current
 - Depends on current density J_{dc} (current / area)
 - Exponential dependence on temperature


- Black’ s Equation: $MTTF \propto \frac{e^{\frac{E_a}{kT}}}{J_{dc}^n}$

- Typical limits: $J_{dc} < 1 - 2 \text{ mA} / \mu\text{m}^2$

 

[Christiansen06]

Electromigration Video

 

Electromigration Video 2

In-situ Observation of Electromigration via HVSEM

J. Doan, S. Lee J. Bravman, P. Flinn, *T. Marieb

Dept. of Materials Science & Engineering, Stanford University

*Components Research, Intel Corporation - Santa Clara

Aluminum Alloy Study: Alscnt01
1/19/97

Copyright © 1997 by J. C. Doan

Self-Heating

- ❑ Current through wire resistance generates heat
 - Oxide surrounding wires is a thermal insulator
 - Heat tends to build up in wires
 - Hotter wires are more resistive, slower
- ❑ Self-heating limits AC current densities for reliability

$$I_{rms} = \sqrt{\frac{\int_0^T I(t)^2 dt}{T}}$$



- Typical limits: $J_{rms} < 15 \text{ mA} / \mu\text{m}^2$

Overvoltage Failure

- ❑ High voltages can blow out tiny transistors
- ❑ *Electrostatic discharge (ESD)*
 - kilovolts from static electricity when the package pins are handled
- ❑ *Oxide breakdown*
 - In a 65 nm process, $V_g \approx 3 \text{ V}$ causes *arcing* through thin gate oxides
- ❑ *Punchthrough*
 - High V_{ds} causes depletion region between source and drain to touch, leading to high current flow and destructive overheating


Latchup

  - ❑ Latchup: positive feedback leading to V_{DD} – GND short
 - Major problem for 1970's CMOS processes before it was well understood
- ❑ Avoid by minimizing resistance of body to GND / V_{DD}
 - Use plenty of substrate and well taps




Guard Rings

 - ❑ Latchup risk greatest when diffusion-to-substrate diodes could become forward-biased
- ❑ Surround sensitive region with guard ring to collect injected charge




Soft Errors

 - ❑ In 1970's, DRAMs were observed to randomly flip bits
 - Ultimately linked to alpha particles and cosmic ray neutrons
- ❑ Collisions with atoms create electron-hole pairs in substrate
 - These carriers are collected on p-n junctions, disturbing the voltage



Radiation Hardening

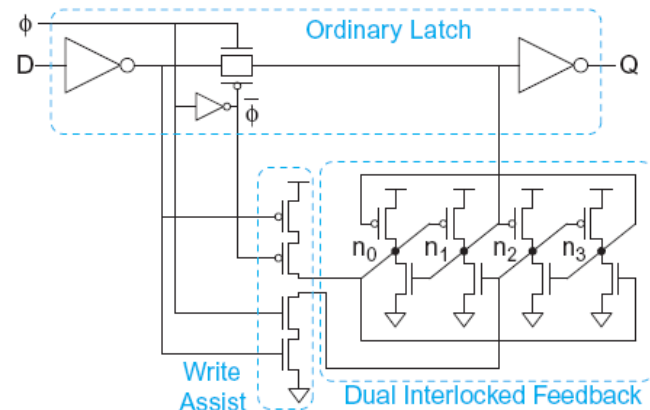- ❑ Radiation hardening reduces soft errors
 - Increase node capacitance to minimize impact of collected charge
 - Or use redundancy
 - E.g. *dual-interlocked cell*
- ❑ Error-correcting codes
 - Correct for soft errors that do occur




Circuit Pitfalls

- ❑ Detective puzzle
 - Given circuit and symptom, diagnose cause and recommend solution
 - All these pitfalls have caused failures in real chips

Bad Circuit 1

❑ Circuit

- 2:1 multiplexer

 

❑ Symptom

- Mux works when selected D is 0 but not 1.
- Or fails at low V_{DD} .
- Or fails in SF/SF corner.

❑ Principle:


-
-
-

❑ Solution:

Bad Circuit 2

❑ Circuit

- Latch

 

❑ Symptom

- Load a 0 into Q
- Set $\phi = 0$
- Eventually Q spontaneously flips to 1

❑ Principle:


-
-

❑ Solution:

Bad Circuit 3

❑ Circuit

- Domino AND gate

 

❑ Symptom

- Precharge gate ($Y=0$)
- Then evaluate
- Eventually Y spontaneously flips to 1

❑ Principle:


-
-

❑ Solution:

Bad Circuit 4

❑ Circuit

- Pseudo-nMOS OR

 

❑ Symptom

- When only one input is true, $Y = 0$.
- Perhaps only happens in SF corner.

❑ Principle:


–
–

❑ Solution:

Bad Circuit 5

❑ Circuit

- Latch

 

❑ Principle:

–

❑ Solutions:


❑ Symptom

- Q stuck at 1.
- May only happen for certain latches where input is driven by a small gate located far away.

Bad Circuit 6

□ Circuit

- Domino AND gate

 

❏ Principle:

Solutions:


☐ Symptom

- Precharge gate while $A = B = 0$, so $Z = 0$
- Set $\phi = 1$
- A rises
- Z is observed to sometimes rise

Bad Circuit 7

❑ Circuit

- Dynamic gate + latch

 

❑ Principle:

–

❑ Solution:


❑ Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls

Bad Circuit 8

❑ Circuit

- Latch

 

❑ Symptom

- Q changes while latch is opaque
- Especially if D comes from a far-away driver

❑ Principle:

-
-

❑ Solution:

Summary

- ❑ Static CMOS gates are very robust
 - Will settle to correct value if you wait long enough
- ❑ Other circuits suffer from a variety of pitfalls
 - Tradeoff between performance & robustness
- ❑ Essential to check circuits for pitfalls
 - For large chips, you need an automatic checker.
 - Design rules aren't worth the paper they are printed on unless you back them up with a tool.