

Lecture 2: ARM Processor Example

Outline

- ❑ Design Partitioning
- ❑ ARM Processor Example
 - Architecture
 - Microarchitecture
 - Logic Design
 - Circuit Design
 - Physical Design
- ❑ Fabrication, Packaging, Testing

Activity 2

- Sketch a stick diagram for a 4-input NOR gate

Coping with Complexity

- ❑ How to design System-on-Chip?
 - Many millions (even billions!) of transistors
 - Tens to hundreds of engineers
- ❑ Structured Design
- ❑ Design Partitioning


Structured Design

- ❑ **Hierarchy:** Divide and Conquer
 - Recursively system into modules
- ❑ **Regularity**
 - Reuse modules wherever possible
 - Ex: Standard cell library
- ❑ **Modularity:** well-formed interfaces
 - Allows modules to be treated as black boxes
- ❑ **Locality**
 - Physical and temporal

Design Partitioning

- ❑ **Architecture:** User's perspective, what does it do?
 - Instruction set, registers
 - ARM, MIPS, x86, Alpha, PIC, RISC-V, ...
- ❑ **Microarchitecture**
 - Single cycle, multicycle, pipelined, superscalar?
- ❑ **Logic:** how are functional blocks constructed
 - Ripple carry, carry lookahead, carry select adders
- ❑ **Circuit:** how are transistors used
 - Complementary CMOS, pass transistors, domino
- ❑ **Physical:** chip layout
 - Datapaths, memories, random logic

Gajski Y-Chart

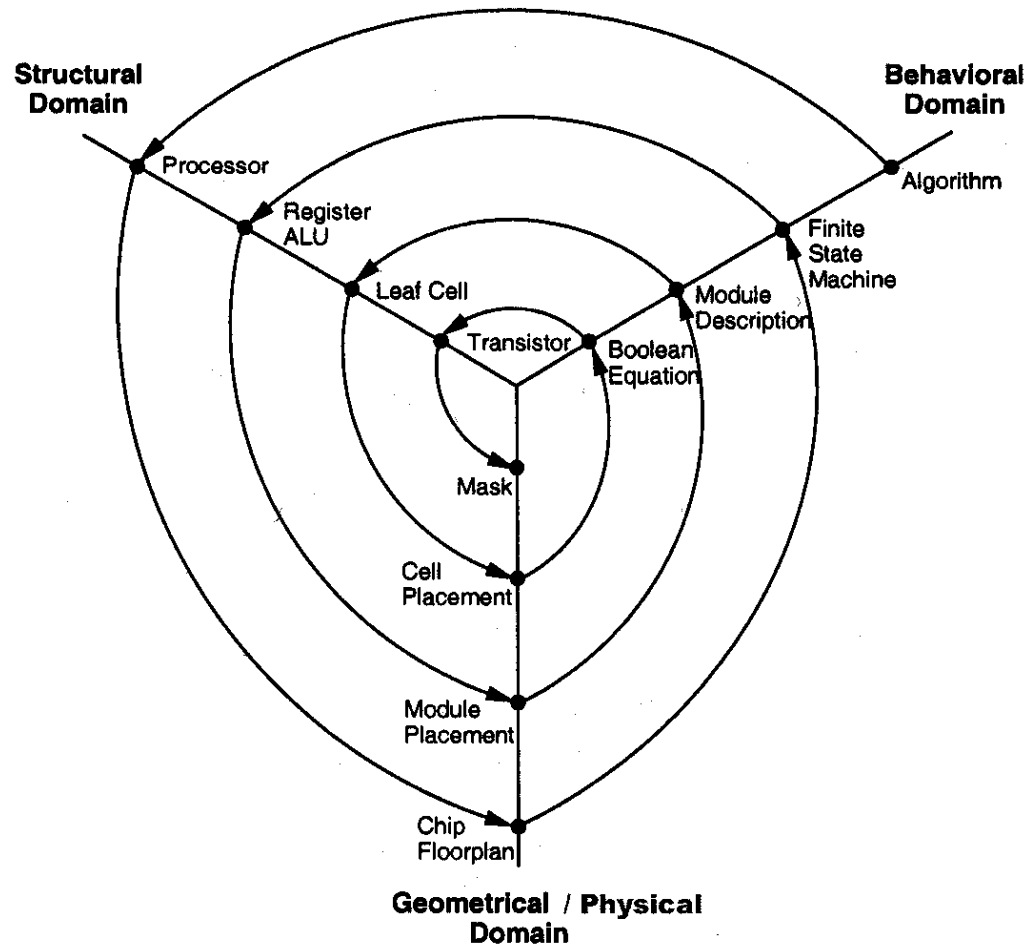

ARM Architecture


- ❑ Example: subset of ARM processor architecture
 - Drawn from DDCA ARM Ed. (Harris & Harris)
- ❑ ARM is a 32-bit architecture with 16 registers
 - Consider 8-bit subset using 8-bit datapath
 - Only implement 8 registers (R0 - R7)
 - 8-bit program counter in R7
- ❑ You' ll build this processor in the labs
 - Illustrate the key concepts in VLSI design

Instruction Set

- ❑ Data Processing
 - ADD, SUB, AND, OR
 - Each accepts register / immediate 2nd sources
- ❑ Memory
 - LDR, STR
 - Positive immediate offset
- ❑ Branch
 - B

Instruction Encoding

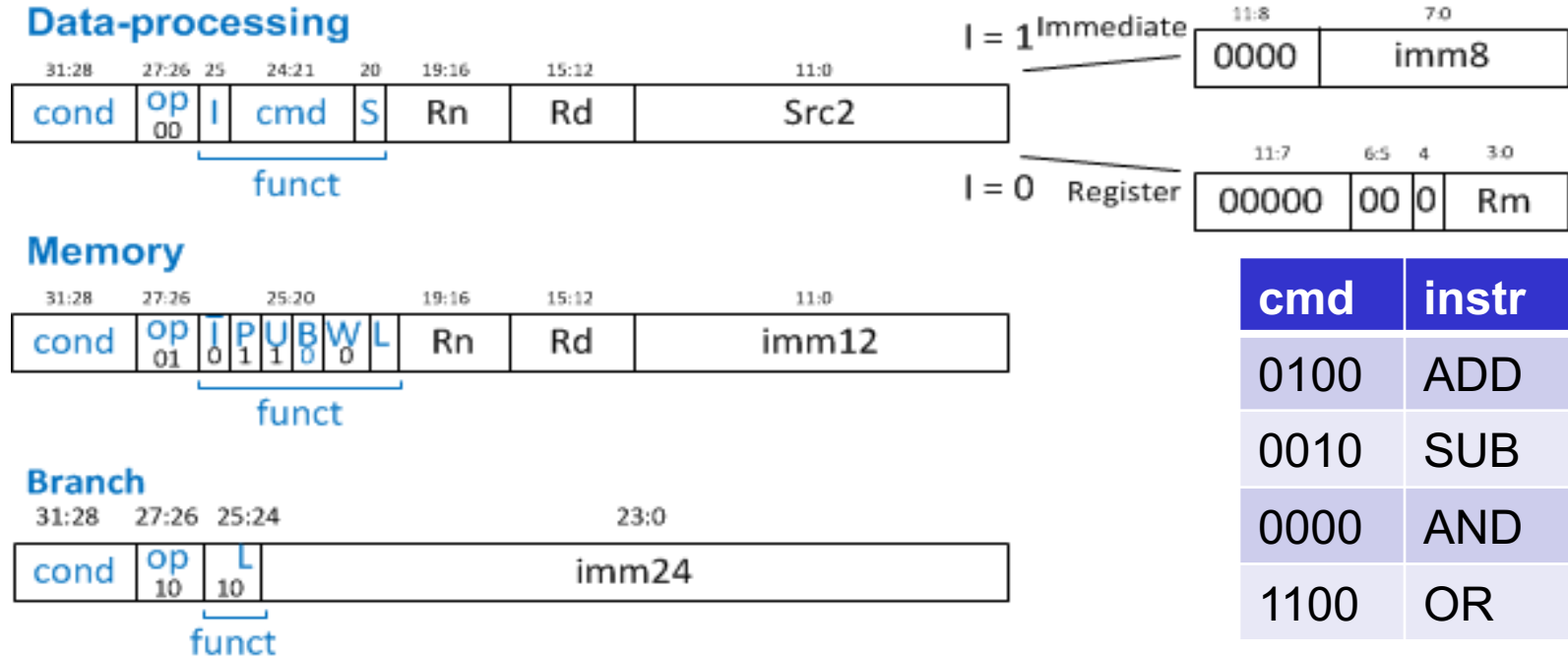- ❑ 32-bit instruction encoding
 - Requires four cycles to fetch on 8-bit datapath



Fibonacci (C)

$$f_0 = 1; f_{-1} = -1$$

$$f_n = f_{n-1} + f_{n-2}$$

$f = 1, 1, 2, 3, 5, 8, 13, \dots$

```
int fib(void)
{
    int n = 8;           /* compute nth Fibonacci number */
    int f1 = 1, f2 = -1; /* last two Fibonacci numbers */

    while (n != 0) {      /* count down to n = 0 */
        f1 = f1 + f2;
        f2 = f1 - f2;
        n = n - 1;
    }
    return f1;
}
```


Fibonacci (Assembly)

fib.asm


Register usage: R0 = 0, R3 = n, R4 = f1, R5 = f2

Put result in address 255




fib	add R3, R0, #8	# initialize n = 8
	add R4, R0, #1	# initialize f1 = 1
	add R5, R0, #-1	# initialize f2 = -1
loop	subs R3, R0, end	# n = 0?
	beq done	# then done
	add R4, R4, R5	# f1 = f1 + f2
	sub R5, R4, R5	# f2 = f1 - f2
	add R3, R3, #-1	# n = n-1
	b loop	# repeat until done
done	str R4, [R0, #255]	# store result in adr 255

ARM Microarchitecture

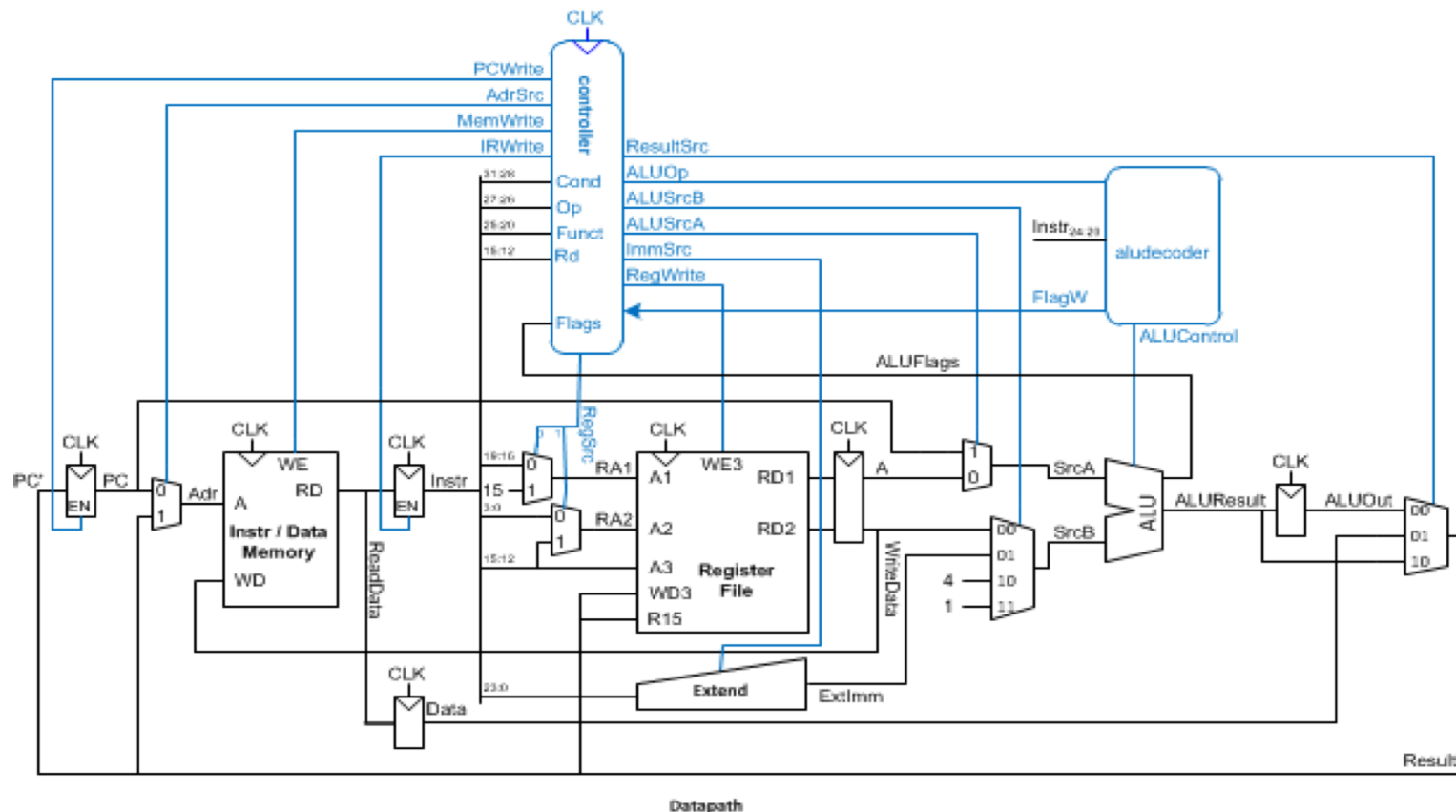
- ❑ Multicycle μ architecture (Harris DDCA ARM Ed.)



Multicycle Controller

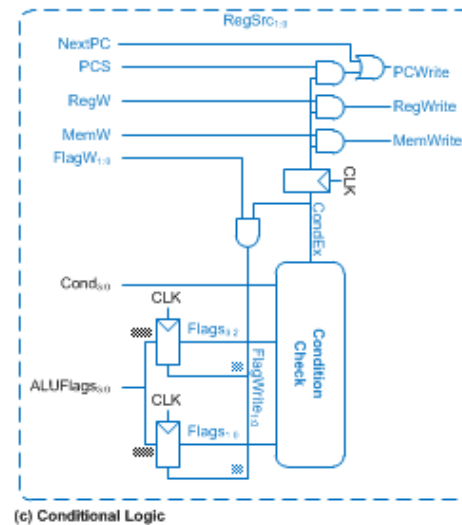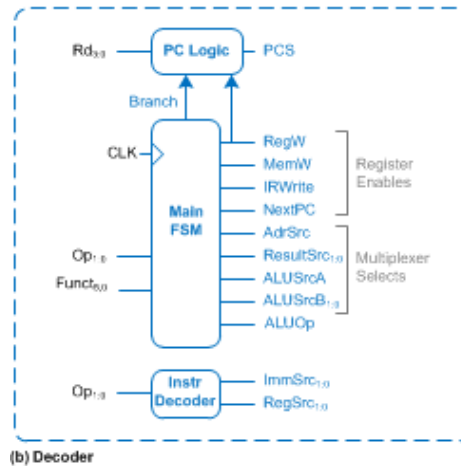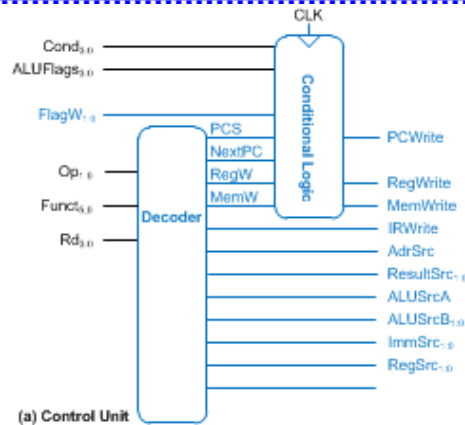


Multicycle FSM

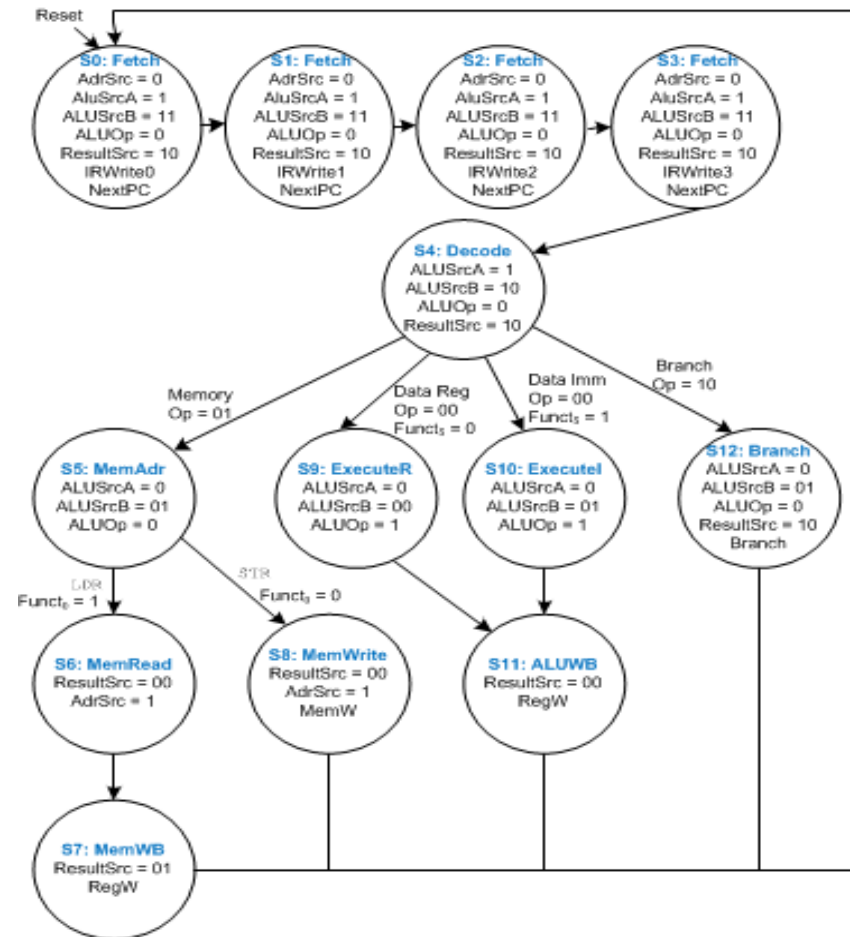


Logic Design

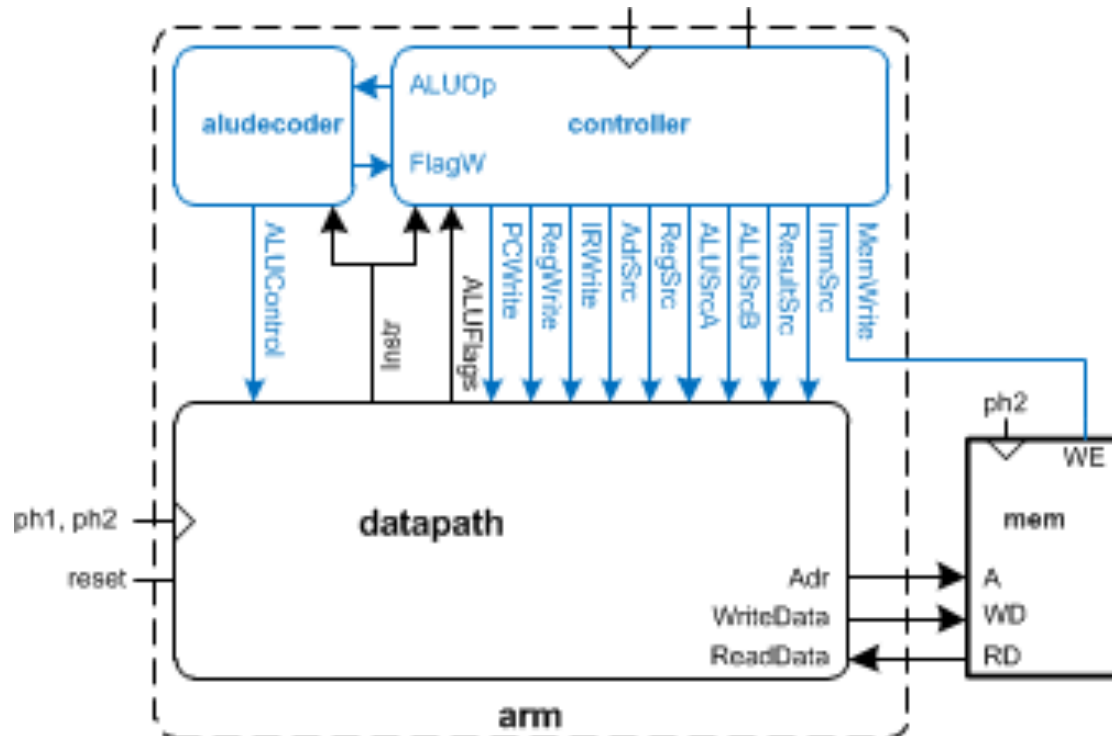- ❑ Start at top level
 - Hierarchically decompose ARM into units



Hierarchical Design

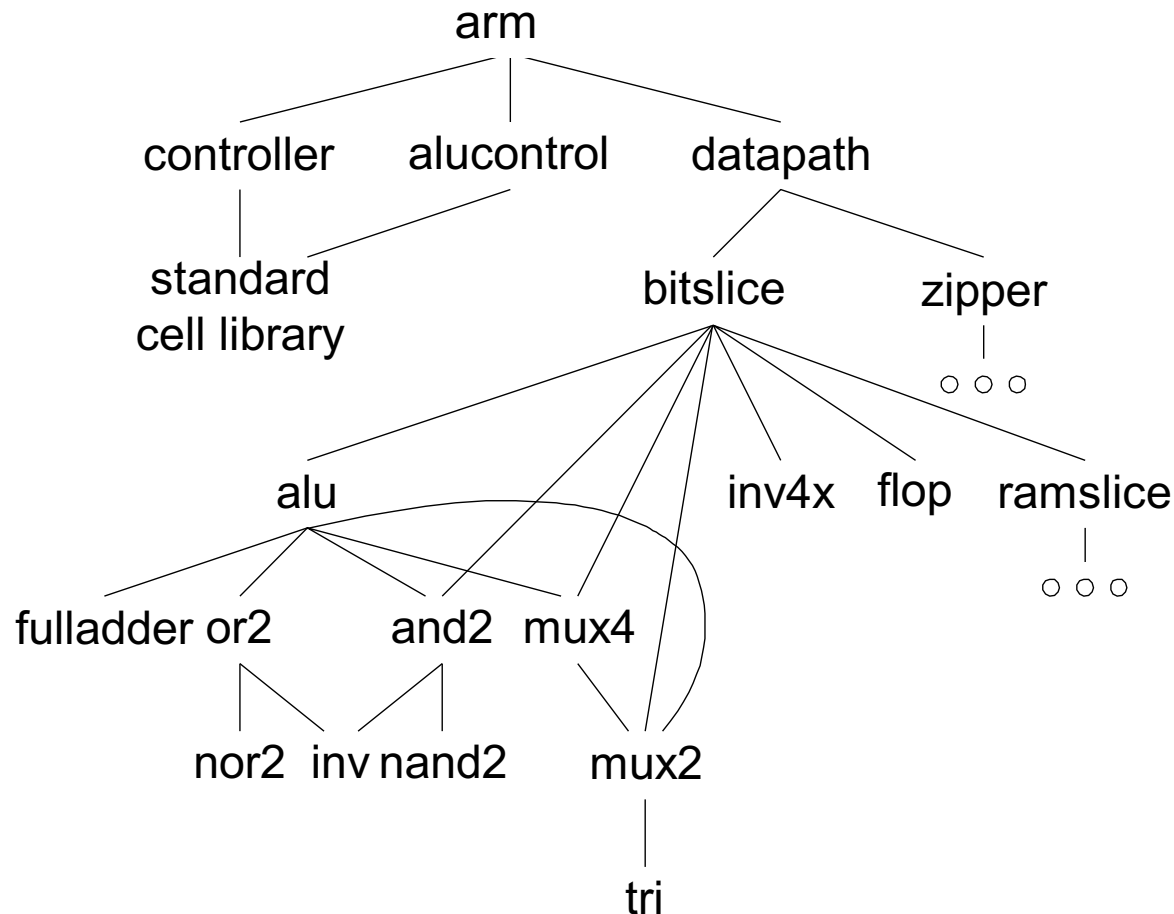

HDLs

- ❑ Hardware Description Languages
 - Widely used in logic design
 - Verilog and VHDL
- ❑ Describe hardware using code
 - Document logic functions
 - Simulate logic before building
 - Synthesize code into gates and layout
 - Requires a library of standard cells

Verilog Example

```
module fulladder(input  a, b, c,  
                 output s, cout);
```

```
    sum          s1(a, b, c, s);
```


```
    carry        c1(a, b, c, cout);
```

```
endmodule
```

```
module carry(input  a, b, c,  
              output cout)
```

```
    assign cout = (a&b) | (a&c) | (b&c);
```

```
endmodule
```


 


Circuit Design

- ❑ How should logic be implemented?
 - NANDs and NORs vs. ANDs and ORs?
 - Fan-in and fan-out?
 - How wide should transistors be?
- ❑ These choices affect speed, area, power
- ❑ Logic synthesis makes these choices for you
 - Good enough for many applications
 - Hand-crafted circuits are still better

Example: Carry Logic

□ **assign** cout = (a&b) | (a&c) | (b&c);

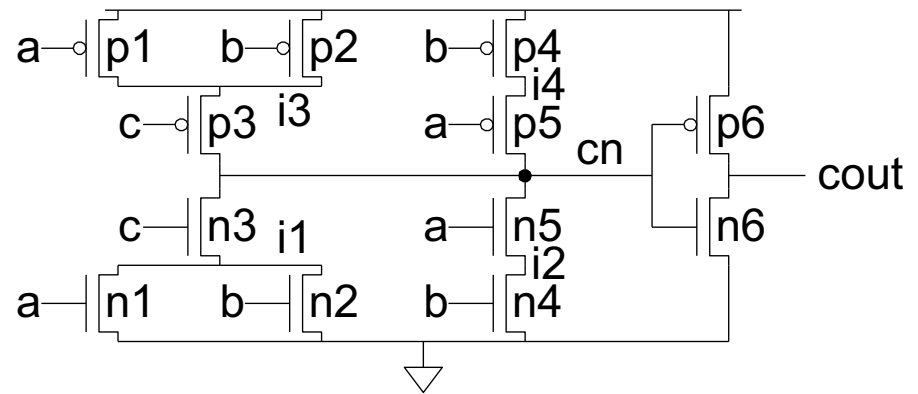 

Transistors? Gate Delays?

Gate-level Netlist

```
module carry(input  a, b, c,  
              output cout)
```

```
    wire      x, y, z;
```


```
    and g1(x, a, b);
```

```
    and g2(y, a, c);
```

```
    and g3(z, b, c);
```

```
    or  g4(cout, x, y, z);
```

```
endmodule
```

 


Transistor-Level Netlist

```
module carry(input  a, b, c,
              output cout)

    wire      i1, i2, i3, i4, cn;

    tranif1 n1(i1, 0, a);
    tranif1 n2(i1, 0, b);
    tranif1 n3(cn, i1, c);
    tranif1 n4(i2, 0, b);
    tranif1 n5(cn, i2, a);
    tranif0 p1(i3, 1, a);
    tranif0 p2(i3, 1, b);
    tranif0 p3(cn, i3, c);
    tranif0 p4(i4, 1, b);
    tranif0 p5(cn, i4, a);
    tranif1 n6(cout, 0, cn);
    tranif0 p6(cout, 1, cn);

endmodule
```

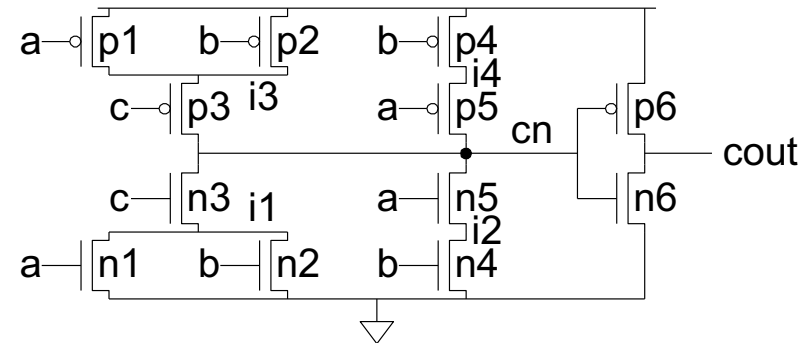


SPICE Netlist

```
.SUBCKT CARRY A B C COUT VDD GND
MN1 I1 A GND GND NMOS W=1U L=0.18U AD=0.3P AS=0.5P
MN2 I1 B GND GND NMOS W=1U L=0.18U AD=0.3P AS=0.5P
MN3 CN C I1 GND NMOS W=1U L=0.18U AD=0.5P AS=0.5P
MN4 I2 B GND GND NMOS W=1U L=0.18U AD=0.15P AS=0.5P
MN5 CN A I2 GND NMOS W=1U L=0.18U AD=0.5P AS=0.15P
MP1 I3 A VDD VDD PMOS W=2U L=0.18U AD=0.6P AS=1 P
MP2 I3 B VDD VDD PMOS W=2U L=0.18U AD=0.6P AS=1P
MP3 CN C I3 VDD PMOS W=2U L=0.18U AD=1P AS=1P
MP4 I4 B VDD VDD PMOS W=2U L=0.18U AD=0.3P AS=1P
MP5 CN A I4 VDD PMOS W=2U L=0.18U AD=1P AS=0.3P
MN6 COUT CN GND GND NMOS W=2U L=0.18U AD=1P AS=1P
MP6 COUT CN VDD VDD PMOS W=4U L=0.18U AD=2P AS=2P
CI1 I1 GND 2FF
CI3 I3 GND 3FF
CA A GND 4FF
CB B GND 4FF
CC C GND 2FF
CCN CN GND 4FF
CCOUT COUT GND 2FF
.ENDS
```


Physical Design

- ☐ Floorplan
- ☐ Standard cells
 - Place & route
- ☐ Datapaths
 - Slice planning
- ☐ Area estimation

ARM Floorplan

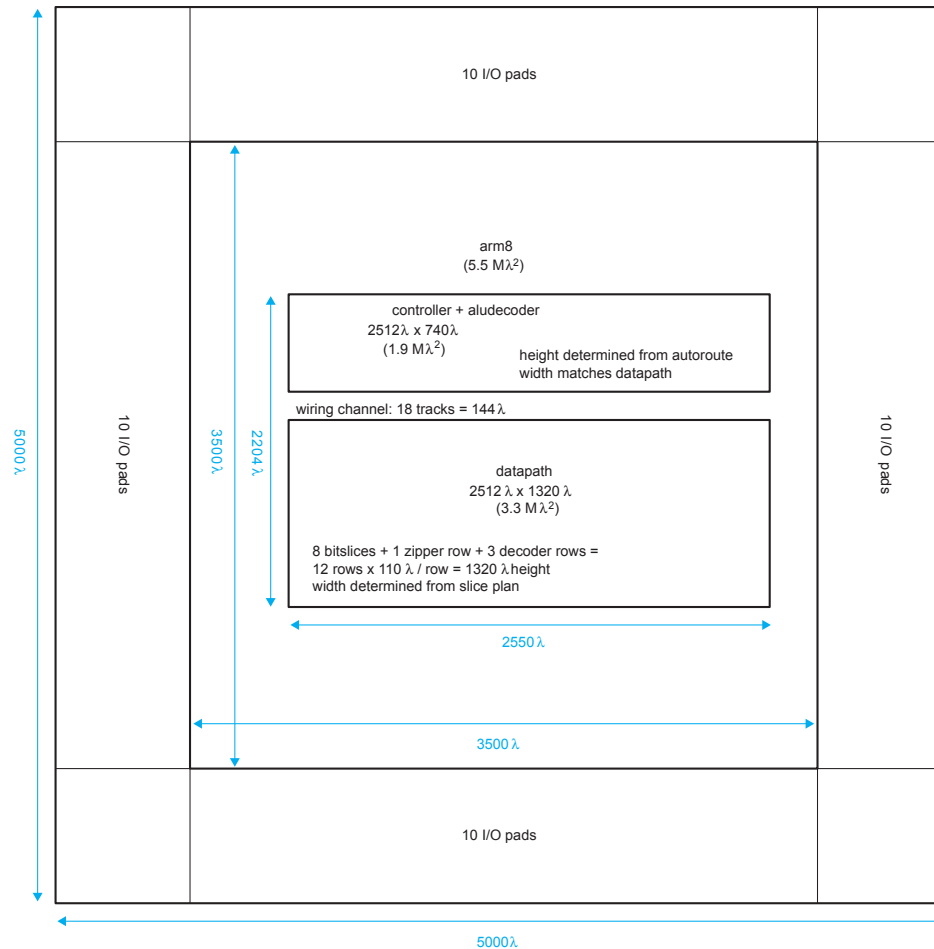


ARM Layout

 


Standard Cells

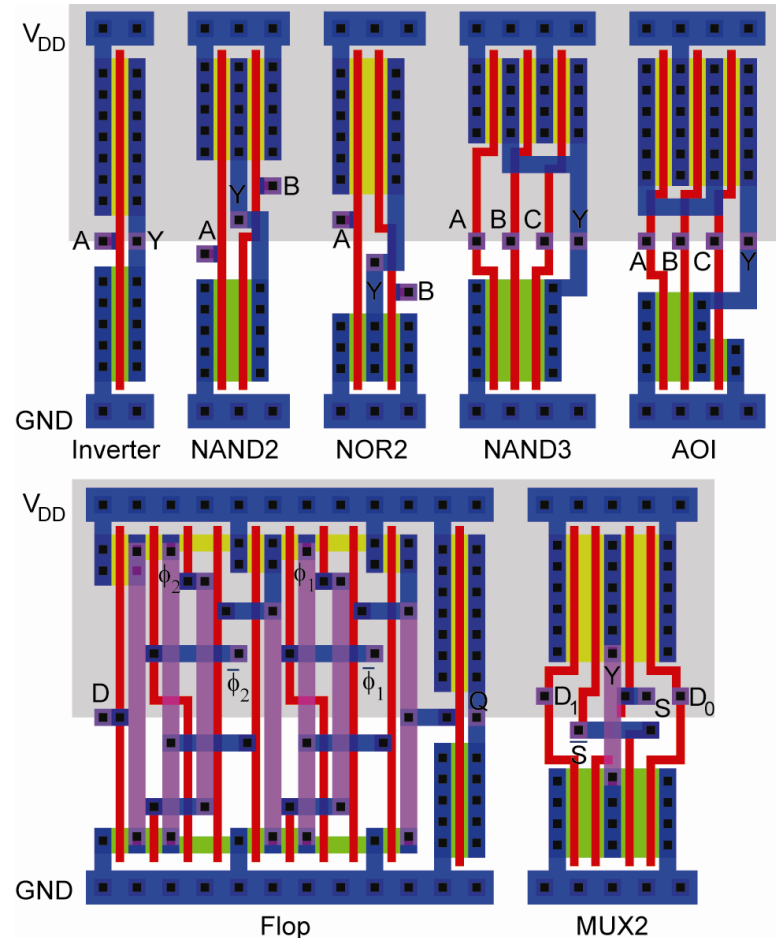- ❑ Uniform cell height
- ❑ Uniform well height
- ❑ M1 V_{DD} and GND rails
- ❑ M2 Access to I/Os
- ❑ Well / substrate taps
- ❑ Exploits regularity



Synthesized Controller

 - ❑ Synthesize HDL into gate-level netlist
- ❑ Place & Route using standard cell library




Pitch Matching

- ❑ Synthesized controller area is mostly wires
 - Design is smaller if wires run through/over cells
 - Smaller = faster, lower power as well!
- ❑ Design snap-together cells for datapaths and arrays
 - Plan wires into cells
 - Connect by abutment
 - Exploits locality
 - Takes lots of effort

A	A	A	A	B
A	A	A	A	B
A	A	A	A	B
A	A	A	A	B
C		C		D


ARM Datapath

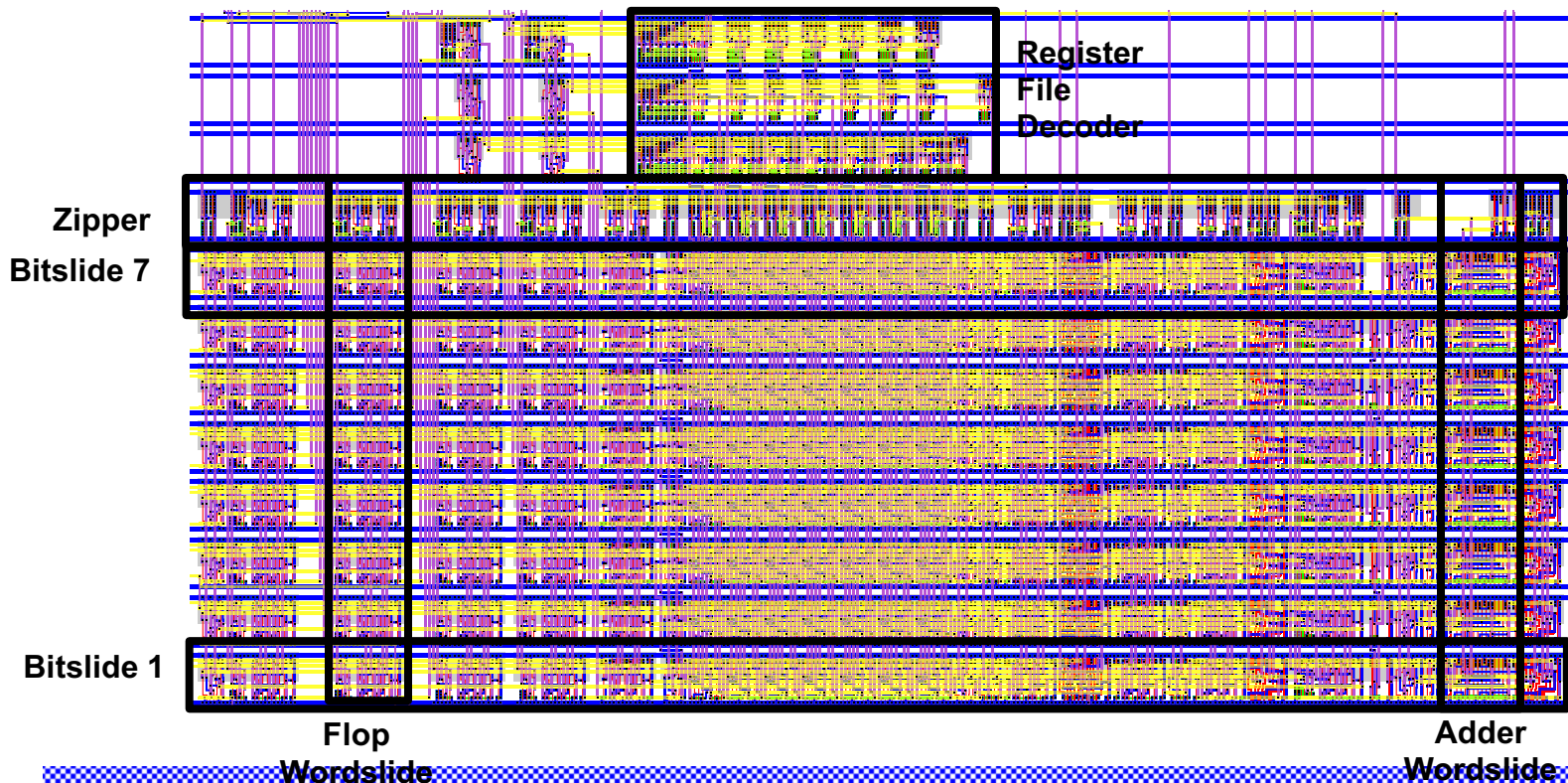- ❑ 8-bit datapath built from wordlices
- ❑ Zipper at top drives control signals to datapath



Slice Plans

 - ❑ Slice plan for bitslice
 - Cell ordering, dimensions, wiring tracks
 - Arrange cells for wiring locality



Area Estimation


- ❑ Need area estimates to make floorplan
 - Compare to another block you already designed
 - Or estimate from transistor counts
 - Budget room for large wiring tracks
 - Your mileage may vary; derate by 2x for class.

Table 1.10 Typical layout densities

Element	Area
random logic (2-level metal process)	1000 – 1500 λ^2 / transistor
datapath	250 – 750 λ^2 / transistor or 6 WL + 360 λ^2 / transistor
SRAM	1000 λ^2 / bit
DRAM (in a DRAM process)	100 λ^2 / bit
ROM	100 λ^2 / bit



Design Verification

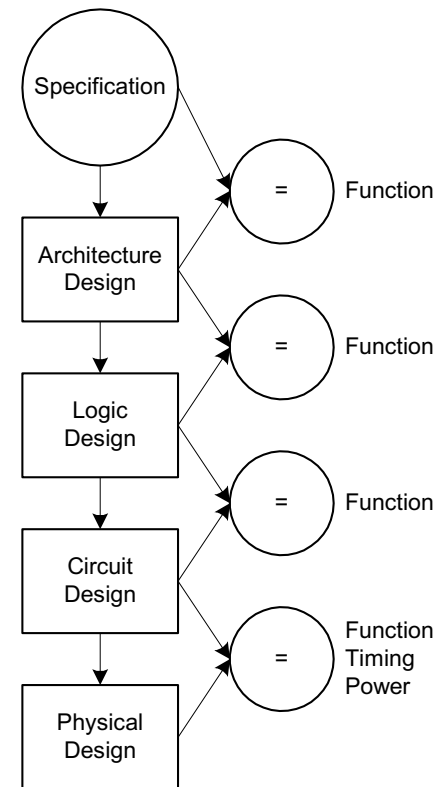- ❑ Fabrication is slow & expensive
 - MOSIS 0.6 μ m: \$1000, 3 months
 - 65 nm: \$3M, 1 month
- ❑ Debugging chips is very hard
 - Limited visibility into operation
- ❑ Prove design is right before building!
 - Logic simulation
 - Ckt. simulation / formal verification
 - Layout vs. schematic comparison
 - Design & electrical rule checks
- ❑ Verification is > 50% of effort on most chips!



Fabrication & Packaging

  - ❑ Tapeout final layout
- ❑ Fabrication
 - 6, 8, 12" wafers
 - Optimized for throughput, not latency (10 weeks!)
 - Cut into individual dice
- ❑ Packaging
 - Bond gold wires from die I/O pads to package





Testing

- ❑ Test that chip operates
 - Design errors
 - Manufacturing errors
- ❑ A single dust particle or wafer defect kills a die
 - Yields from 90% to $< 10\%$
 - Depends on die size, maturity of process
 - Test each part before shipping to customer


Custom vs. Synthesis

❑ 8-bit Implementations

  

ARM1 Processor

 - ❑ 1st generation ARM chip (1985)
- ❑ 24,800 transistors
- ❑ 3-stage pipeline
- ❑ 8 MHz
- ❑ 3 μm process
- ❑ 49 mm²
- ❑ 82-pin PLCC package
- ❑ Average power = 0.1 W
- ❑ 2-phase nonoverlapping clocks
- ❑ Built for Acorn Computer



© 1985 ARM Ltd.