

# **Lecture 20: PLLs and DLLs**

# Outline

---

- ☐ Clock System Architecture
- ☐ Phase-Locked Loops
- ☐ Delay-Locked Loops

# Clock Generation


---

- ❑ Low frequency:
  - Buffer input clock and drive to all registers
- ❑ High frequency
  - Buffer delay introduces large skew relative to input clocks
    - Makes it difficult to sample input data
  - Distributing a very fast clock on a PCB is hard


# Zero-Delay Buffer

- ❑ If the periodic clock is delayed by  $T_c$ , it is indistinguishable from the original clock
- ❑ Build feedback system to guarantee this delay

## Phase-Locked Loop (PLL)

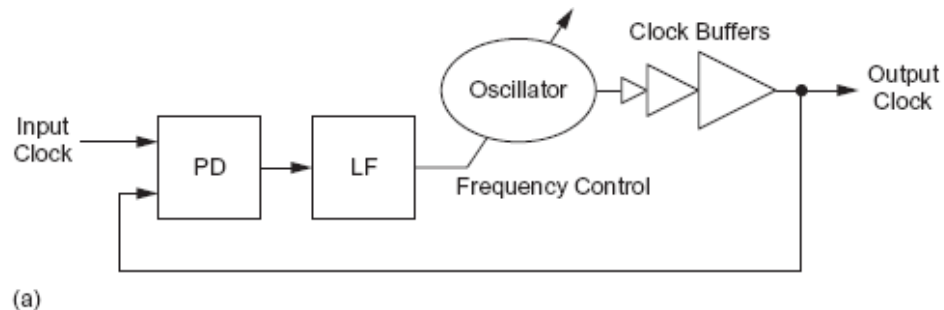


## Delay-Locked Loop (PLL)

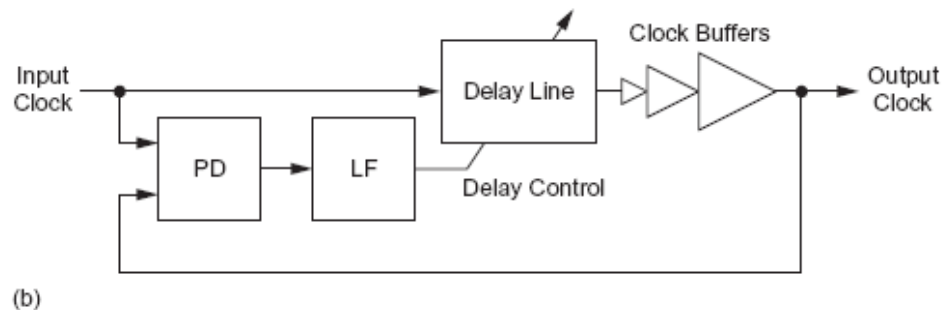
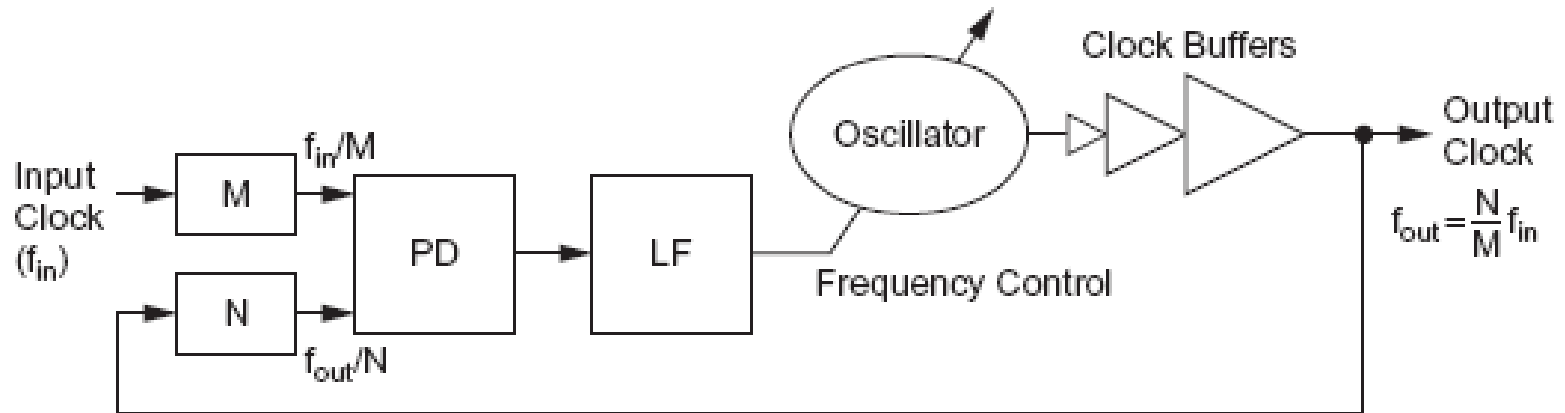
# Frequency Multiplication

- ❑ PLLs can multiply the clock frequency




# Phase and Frequency

- Analyze PLLs and DLLs in term of phase  $\Phi(t)$  rather than voltage  $v(t)$

$$\text{clk} = \begin{cases} 1 & \Phi(t) \bmod 2\pi < \pi \\ 0 & \Phi(t) \bmod 2\pi \geq \pi \end{cases}$$

$$\Phi(t) = 2\pi \int_0^t f(t) dt$$

 

- Input and output clocks may deviate from locked phase
  - Small signal analysis

$$\Phi_{\text{in}}(t) = \Phi(t) + \Delta\Phi_{\text{in}}(t)$$


$$\Phi_{\text{out}}(t) = N\Phi(t) + \Delta\Phi_{\text{out}}(t)$$

# Linear System Model


- ❑ Treat PLL/DLL as a linear system
  - Compute deviation DF from locked position
  - Assume small deviations from locked
  - Treat system as linear for these small changes
- ❑ Analysis is not valid far from lock
  - e.g. during acquisition at startup
- ❑ Continuous time assumption
  - PLL/DLL is really a discrete time system
    - Updates once per cycle
  - If the bandwidth  $\ll 1/10$  clock freq, treat as continuous
- ❑ Use Laplace transforms and standard analysis of linear continuous-time feedback control systems

# Phase-Locked Loop (PLL)

## □ System

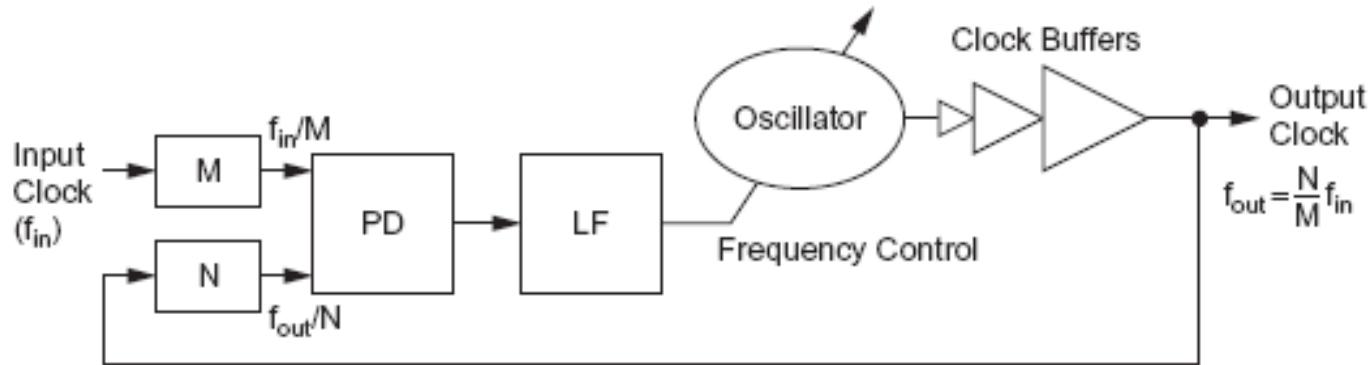


## □ Linear Model

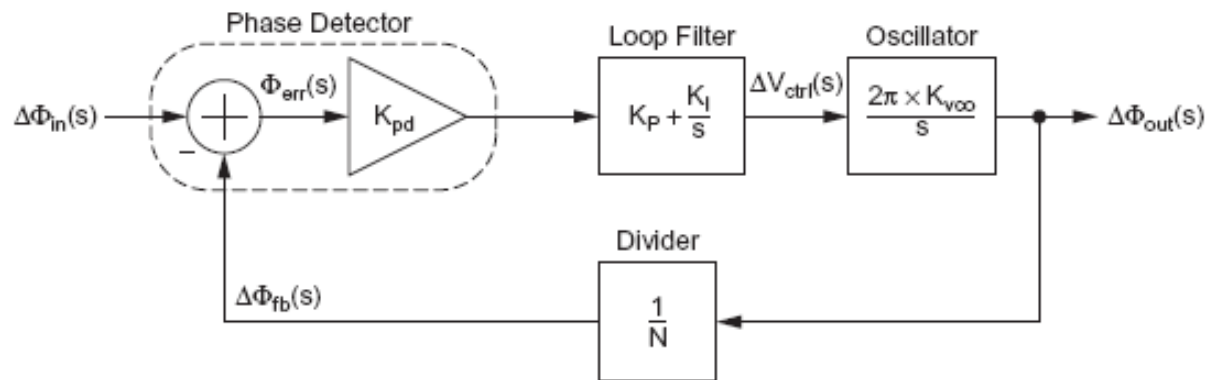



# Voltage-Controlled Oscillator



□ VCO

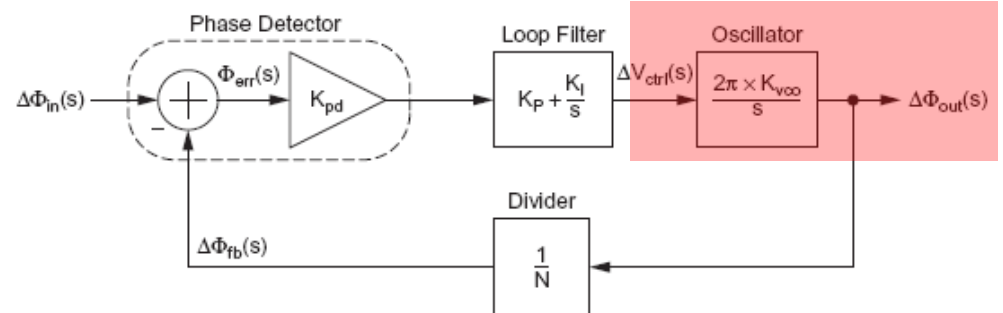


$$V_{ctrl}(t) = V_{ctrl0} + \Delta V_{ctrl}(t)$$

$$\frac{\Delta f_{out}}{\Delta V_{ctrl}} = K_{vco}$$
  
$$\frac{\Delta \Phi_{out}(s)}{\Delta V_{ctrl}(s)} = \frac{2\pi K_{vco}}{s}$$




# Alternative Delay Elements

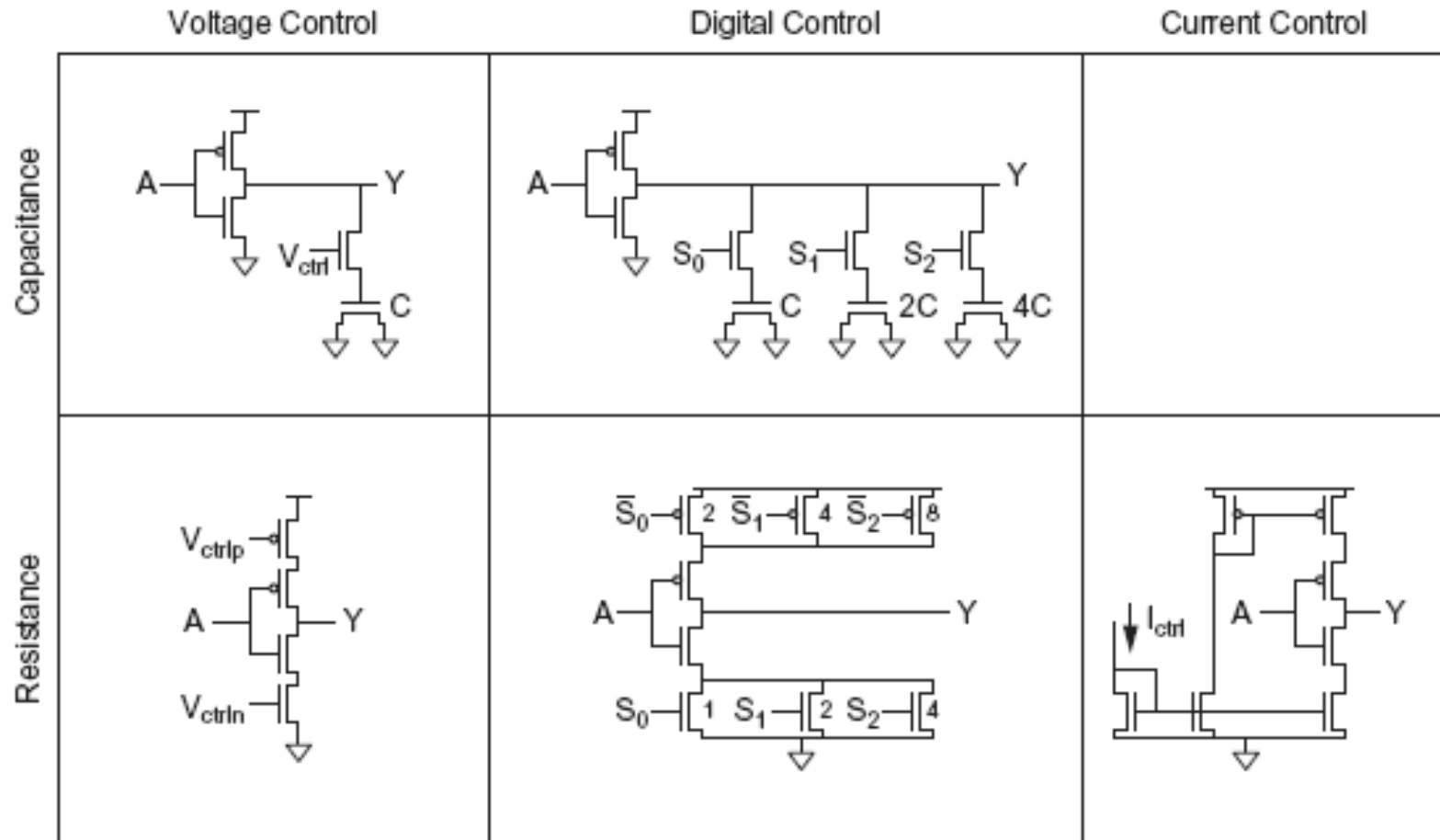
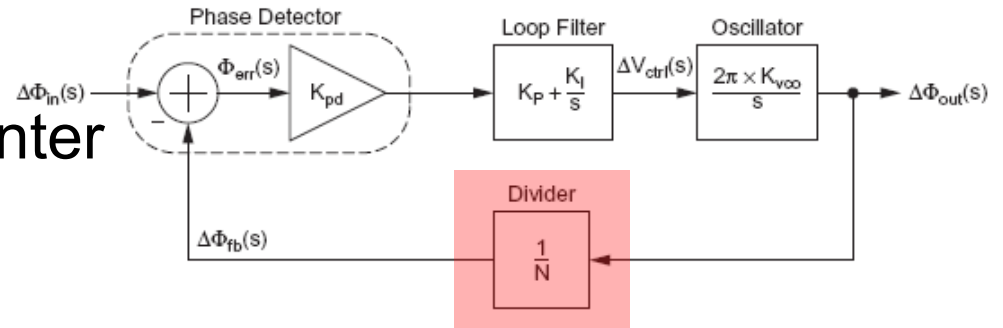
# Frequency Divider

- Divide clock by N
  - Use mod-N counter




$$\Delta f_{fb} = \frac{\Delta f_{out}}{N}$$




$$\Delta\Phi_{fb} = \frac{\Delta\Phi_{out}}{N}$$
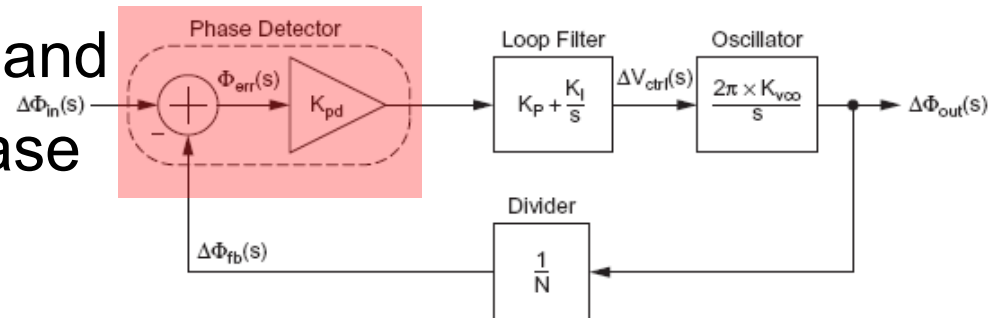
# Phase Detector

- ❑ Difference of input and feedback clock phase



   
- ❑ Often built from phase-frequency detector (PFD)


 
# Phase Detector


- ❑ Convert up and down pulses into current proportional to phase error using a charge pump

$$\frac{I_{pd}(s)}{\Phi_{err}(s)} = \frac{I_{cp}}{2\pi} = K_{pd}$$



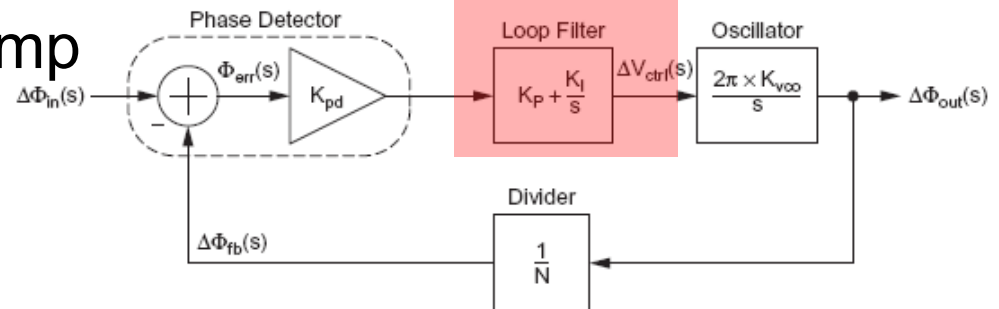
# Loop Filter

- ❑ Convert charge pump current into  $V_{ctrl}$



- ❑ Use proportional-integral control (PI) to generate a control signal dependent on the error and its integral
  - Drives error to 0
 
$$\frac{V_{ctrl}(s)}{I_{pd}(s)} = \frac{1}{sC} + R$$



# PLL Loop Dynamics

- ❑ Closed loop transfer function of PLL

$$H(s) = \frac{\Delta\Phi_{\text{out}}(s)}{\Delta\Phi_{\text{in}}(s)} = \frac{K_{pd} \left( R + \frac{1}{sC} \right) \frac{2\pi K_{\text{vco}}}{s}}{1 + \frac{1}{N} K_{pd} \left( R + \frac{1}{sC} \right) \frac{2\pi K_{\text{vco}}}{s}}$$

- ❑ This is a second order system

$$H(s) = N \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad \omega_n = \sqrt{\frac{I_{cp} K_{\text{vco}}}{NC}}$$
$$\zeta = \frac{\omega_n}{2} RC$$

- ❑  $\omega_n$  indicates loop bandwidth
- ❑  $\zeta$  indicates damping; choose 0.7 – 1 to avoid ringing


# Delay Locked Loop

- ❑ Delays input clock rather than creating a new clock with an oscillator
- ❑ Cannot perform frequency multiplication
- ❑ More stable and easier to design
  - 1<sup>st</sup> order rather than 2<sup>nd</sup>
- ❑ State variable is now time (T)
  - Locks when loop delay is exactly  $T_c$
  - Deviations of  $\Delta T$  from locked value




# Delay-Locked Loop (DLL)

## □ System

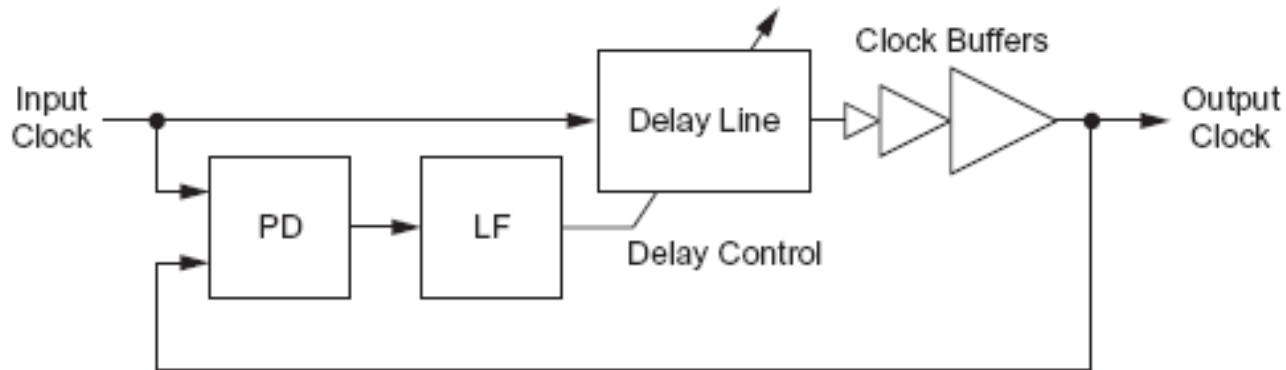


## □ Linear Model

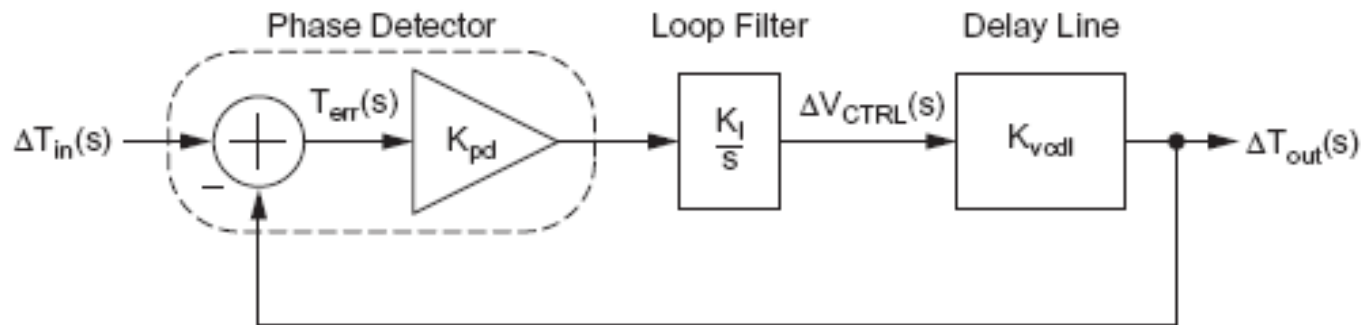


# Delay Line

- ❑ Delay input clock

 


- ❑ Typically use voltage-controlled delay line
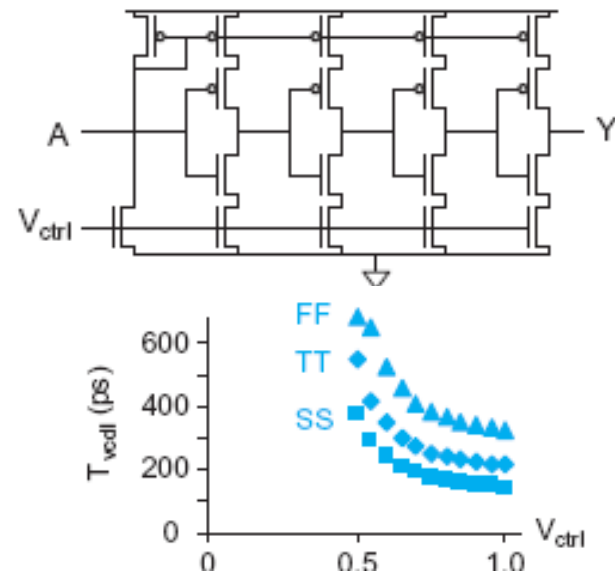
$$\frac{\Delta T_{out}(s)}{\Delta V_{ctrl}(s)} = K_{vcdl}$$



# Phase Detector

- ❑ Detect phase error

 


- ❑ Typically use PFD and charge pump, as in PLL

$$\frac{I_{pd}(s)}{T_{err}(s)} = \frac{I_{cp}}{T_c}$$

 
# Loop Filter

- ❑ Convert error current into control voltage



- ❑ Integral control is sufficient
- ❑ Typically use a capacitor as the loop filter
 
$$\frac{\Delta V_{ctrl}(s)}{I_{pd}(s)} = \frac{K_I}{s} = \frac{1}{sC}$$



# DLL Loop Dynamics

- ❑ Closed loop transfer function of DLL

$$H(s) = \frac{\Delta T_{\text{out}}(s)}{\Delta T_{\text{in}}(s)} = \frac{1}{s\tau + 1}$$

- ❑ This is a first order system

$$\tau = \frac{1}{K_{pd}K_IK_{vc dl}} = \frac{CT_c}{I_{cp}K_{vc dl}}$$

- ❑  $\tau$  indicates time constant (inverse of bandwidth)
  - Choose at least  $10T_c$  for continuous time approx.