

# Digital Electronics & Computer Engineering (E85)

Harris & Brake

Spring 2020

## Final Exam

This is a closed-book take-home exam. Electronic devices including calculators are not allowed. You are permitted one side of two  $8.5 \times 11$ " sheets of paper with notes.

You are bound by the HMC Honor Code while taking this exam.

There is no time limit for this exam. You do not need to work on the exam in one contiguous block of time. However, you should record each of your start and stop times and the total time spent on the exam in the table below.

Return the exam as a single scanned or digitally filled PDF uploaded to Sakai no later than **12 pm on May 14<sup>th</sup>, 2020**. If you scan your exam, please ensure that your answers are legible. If possible, we encourage you to use a scanner or a smartphone scanning app with the flash enabled.

Alongside each question, the number of points is written in brackets. All work and answers should be written directly on this exam. Insert additional pages of work in your PDF submission as necessary. The work for each problem should appear with its respective problem, not at the end of your PDF. Show your work for partial credit.


Name: \_\_\_\_\_

Page	Score	Total Available
2		3
3		4
4		3
5		4
6		6
7		5
8		3
9		6
10		4
11		7
<b>Total</b>		<b>45</b>


Date	Start Time	Stop Time

**Total Time:** \_\_\_\_\_ hrs

 Consider the following finite state machine.



 [3] Sketch a state transition diagram for the FSM.




Assume the following component delays and ignore timing issues related to P and W to answer the following questions. The FSM schematic is repeated here for your convenience.

Cell	Propagation Delay (ps)	Contamination Delay (ps)	Setup Time (ps)	Hold Time (ps)
2-input gate	20	10		
Flip-flop	40	25	30	17

[2] If the clock skew is 15 ps, what is the minimum clock period for which the system will work reliably?

 [2] How much clock skew may the system experience before it becomes unreliable at low frequencies?



[3] Write a simplified behavioral Verilog description of the FSM (repeated here for your convenience).

```

module fsm(input  logic clk, reset,
           input  logic P,
           output logic W);


```

```


endmodule

```

 [4] Design a  $2048 \times 8$  Read Only Memory (ROM) with input terminals  $A[10:0]$  and output terminals  $RD[7:0]$  using  $256 \times 32$  ROMs (input terminals  $A[7:0]$  and output terminals  $RD[31:0]$ ) and N-bit 2:1 multiplexers. Draw a schematic of your design. Use no more hardware than necessary. Blocks for your design are shown below.



(a) N-bit, 2:1 multiplexer

 

(b)  $256 \times 32$  ROM

Block diagram elements

What is the minimum number of logic elements required to build each of the following circuits on the Cyclone IV FPGA that we used in lab and class? A block diagram of a single logic element is attached at the end of the exam for your reference.

---

```
module mux2(input  logic [31:0] d0, d1,          ELEMENTS: _____ [2]
            input  logic          s,
            output logic [31:0] y);

    assign y = s ? d0 : d1;
endmodule
```

---

```
module gates(input  logic a, b, c, d,          ELEMENTS: _____ [2]
              output logic y);

    assign y = ((a & b) ^ (c | d)) & ~b;
endmodule
```

---

```
module fsm(input  logic          clk, reset,    ELEMENTS: _____ [2]
            input  logic          a,
            output logic [1:0] q);

    logic [1:0] nextq;

    always_ff @(posedge clk, posedge reset)
        if (~reset) q <= 2'b00;
        else q <= nextq;

    always_comb
        case(q)
            2'b00: if (a) nextq <= 2'b01;
                   else  nextq <= 2'b00;
            2'b01: if (a) nextq <= 2'b10;
                   else  nextq <= 2'b01;
            2'b10: if (a) nextq <= 2'b11;
                   else  nextq <= 2'b10;
            2'b11: if (a) nextq <= 2'b11;
                   else  nextq <= 2'b00;
        endcase
endmodule
```

[2] Express the IEEE 754 floating point number C1BE0000 in base 10.

[3] Assume the array `c` is initialized at a base memory address of `0x2000_0000` and is running on a 32-bit architecture to answer the following questions.

(a) What is the value of `carSize`?

(b) What is the value of `y`?

```
typedef struct car {
    char make[56];
    char model[16];
    unsigned int year;
    unsigned long num_seats;
} car;

car myCar;
unsigned long carSize = sizeof(myCar);

car c[10];
unsigned long *y = &c[5].year;
```

[3] Translate the following RISC-V instruction from machine code to its corresponding assembly instruction. You may refer to registers by index rather than by name (e.g., `x9` instead of `s1`). Selected tables from Appendix B are attached to the end of this exam for your reference.

`0x012E1A93`



[6] Write RISC-V assembly code to implement the following function, which performs matrix-vector multiplication. The code snippet computes the product of a  $3 \times 3$  matrix  $A$  and a  $3 \times 1$  vector  $x$ . The result is stored in a  $3 \times 1$  vector  $y$ .

Use  $s0$  for  $i$ ,  $s1$  for  $j$ , and  $s2$  for  $temp$ . The base address of  $A$  is stored in  $s3$ , the base address of  $x$  is stored in  $s4$ , and the base address of  $y$  is stored in  $s5$ .

```
int A[3][3];

int x[3];
int y[3];
int i, j, temp;

for(i = 0; i < 3; i++)
{
    temp = 0;
    for(j = 0; j < 3; j++)
    {
        temp += A[i][j]*x[j];
    }
    y[i] = temp;
}
```

Consider the 5-stage pipelined RISC-V processor with hazard unit from Chapter 7 running the following program. The first addi instruction is issued on cycle 1.

```

addi t0, zero, 42
addi t1, zero, 12
and t2, t0, t1
lw t4, 0(t1)
add t5, t4, t4
beq ZERO, ZERO, else
if: or t3, t0, t1
sub t3, t3, t0
beq zero, zero, done
else: sw t2, 0(t1)
done:


```

[1] On which cycle is t2 written?

[1] What value is written to t2?

[1] On which cycle is t5 written?

[1] On which cycle is MemWrite asserted?

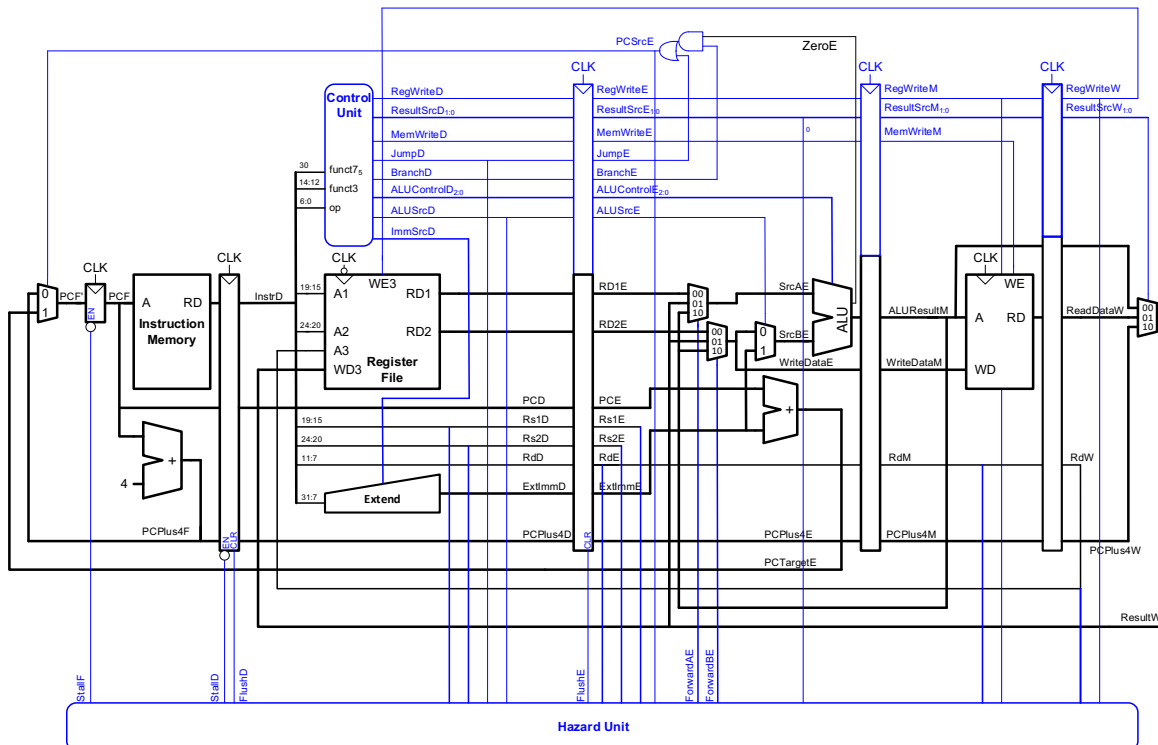


Consider modifying the single-cycle RISC-V processor to support the `lhu` (load halfword unsigned) instruction. `lhu rd, imm(rs1)` reads a 16-bit half-word from memory address  $(rs1 + imm)$  and places it in the bottom 16 bits of register `rd`. The upper 16 bits of register `rd` are filled with zeros. The address must be even. `lhu` has `op = 3` and `funct3 = 5`. In comparison, `lw` also has `op = 3` but `funct3 = 2`. A table of the instruction formats is included in the material attached to the end of the exam for your reference.

Recall that our memory reads out a 32-bit word on `RD` from the address specified by `A[31:2]`.


[2] Write `lhu x5, 28(x3)` in machine language. Express your answer in hexadecimal.

[5] Modify the attached single-cycle processor datapath and controller to support `lhu`. Feel free to add new hardware blocks, but keep your design as simple as possible.

## Single Cycle Processor

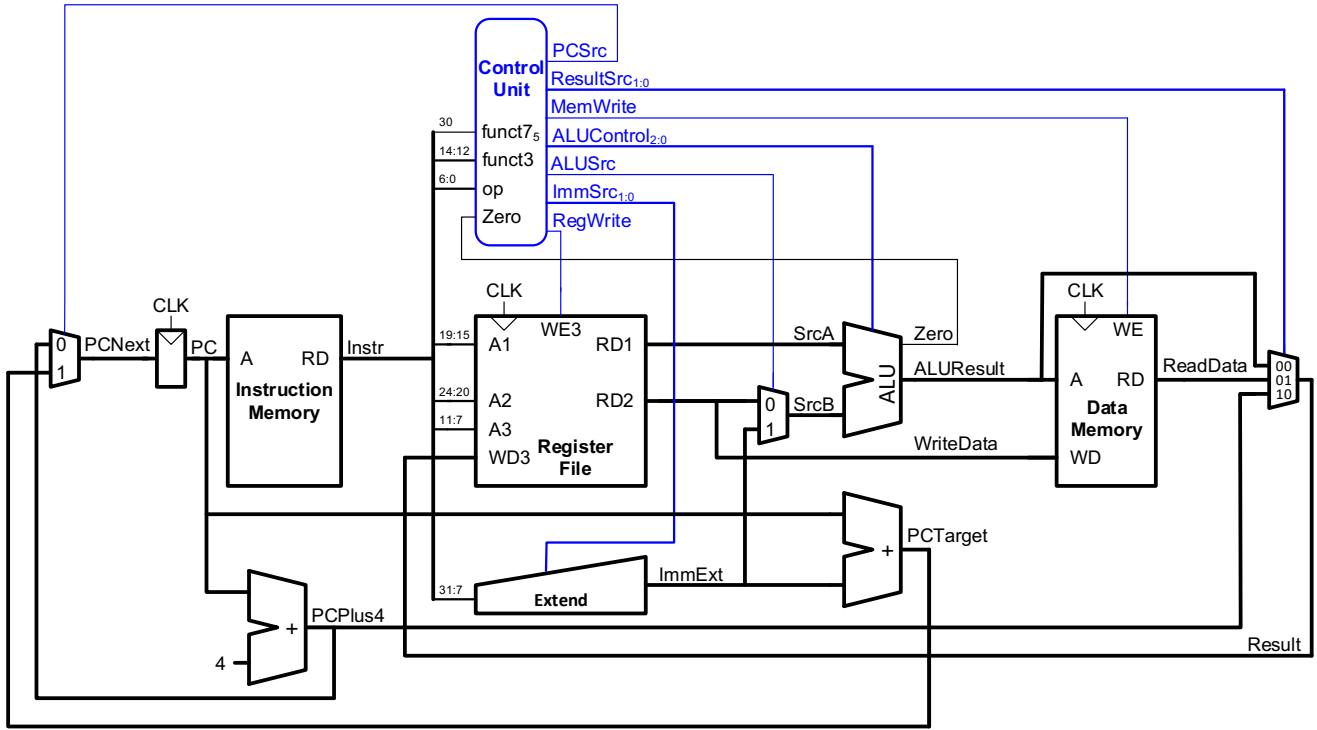

## Single Cycle Controller

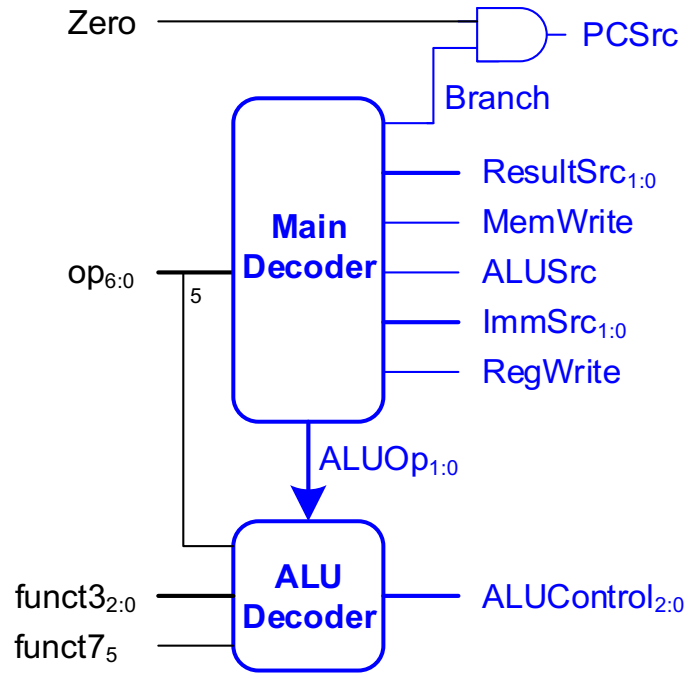

**Main Decoder truth table**

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	00	1	0	01	0	00	0
sw	0100011	0	01	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	00	0	10	0
beq	1100011	0	10	0	0	xx	1	01	0
addi	0010011	1	00	0	0	00	0	10	0
jal	1101111	1	11	x	0	10	0	xx	1

**ALU Decoder truth table**

ALUOp	funct3	ops, funct7s	ALUControl	Instruction
00	xxx	xx	010 (add)	lw, sw
01	xxx	xx	110 (subtract)	beq
10	000	00, 01, 10	010 (add)	add
10	000	11	110 (subtract)	sub
10	010	xx	111 (set less than)	slt
10	110	xx	001 (or)	or
10	111	xx	000 (and)	and

**ImmSrc encoding**

ImmSrc	ImmExt	Type	Description
00	{{20{Instr[31]}}, Instr[31:20]}	I	12-bit signed immediate
01	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}	S	12-bit signed immediate
10	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}	B	13-bit signed immediate
11	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}	J	21-bit signed immediate

**Immediate encodings**

Type	Bits Encoded	Immediate	Field Width
I	imm <sub>11:0</sub>	{20{imm <sub>11</sub> }, imm <sub>11:0</sub> }	12 bits
S	imm <sub>11:0</sub>	{20{imm <sub>11</sub> }, imm <sub>11:0</sub> }	12 bits
B	imm <sub>12:1</sub>	{19{imm <sub>12</sub> }, imm <sub>12:0</sub> , 1'b0}	12 bits
J	imm <sub>20:1</sub>	{11{imm <sub>20</sub> }, imm <sub>20:1</sub> , 1'b0}	20 bits
U	imm <sub>31:12</sub>	{imm <sub>31:12</sub> , 12'b0}	20 bits
R	rs <sub>24:0</sub>	shamt <sub>4:0</sub>	5 bits

## RISC-V instruction formats

7 bits	5 bits	5 bits	3 bits	5 bits	7 bits	
funct7	rs2	rs1	funct3	rd	op	<b>R-Type</b>
imm <sub>11:0</sub>		rs1	funct3	rd	op	<b>I-Type</b>
imm <sub>11:5</sub>	rs2	rs1	funct3	imm <sub>4:0</sub>	op	<b>S-Type</b>
imm <sub>12,10:5</sub>	rs2	rs1	funct3	imm <sub>4:1,11</sub>	op	<b>B-Type</b>
imm <sub>31:12</sub>				rd	op	<b>U-Type</b>
imm <sub>20,10:1,11,19:12</sub>				rd	op	<b>J-Type</b>
20 bits				5 bits	7 bits	

### RV32I instructions – sorted by opcode, then funct3

op	f3	f7	Type	Instruction	Description	Operation
3	0	-	I	lb rd, imm(rs1)	load byte	rd = SignExt([Address] <sub>7:0</sub> )
3	1	-	I	lh rd, imm(rs1)	load half	rd = SignExt([Address] <sub>15:0</sub> )
3	2	-	I	lw rd, imm(rs1)	load word	rd = [Address]
3	4	-	I	lbu rd, imm(rs1)	load byte unsigned	rd = ZeroExt([Address] <sub>7:0</sub> )
3	5	-	I	lhu rd, imm(rs1)	load half unsigned	rd = ZeroExt([Address] <sub>15:0</sub> )
19	0	-	I	addi rd, rs1, imm	add immediate	rd = rs1 + SignExt(imm)
19	1	0	R	slli rd, rs1, shamt	shift left logical immediate	rd = rs1 << shamt
19	2	-	I	slti rd, rs1, imm	set less than immediate	rd = (rs1 < SignExt(imm))
19	3	-	I	sltiu rd, rs1, imm	set less than immediate unsigned	rd = (rs1 < SignExt(imm))
19	4	-	I	xori rd, rs1, imm	xor immediate	rd = rs1 ^ SignExt(imm)
19	5	0	R	srlr rd, rs1, shamt	shift right logical immediate	rd = rs1 >> shamt
19	5	32	R	srair rd, rs1, shamt	shift right arithmetic immediate	rd = rs1 >>> shamt
19	6	-	I	ori rd, rs1, imm	or immediate	rd = rs1   SignExt(imm)
19	7	-	I	andi rd, rs1, imm	and immediate	rd = rs1 & SignExt(imm)
23	-	-	U	auipc rd, imm	add upper immediate to PC	rd = {imm <sub>31:12</sub> , 12'b0} + PC
35	0	-	S	sb rs2, imm(rs1)	store byte	[Address] <sub>7:0</sub> = rs2 <sub>7:0</sub>
35	1	-	S	sh rs2, imm(rs1)	store half	[Address] <sub>15:0</sub> = rs2 <sub>15:0</sub>
35	2	-	S	sw rs2, imm(rs1)	store word	[Address] = rs2
51	0	0	R	add rd, rs1, rs2	add	rd = rs1 + rs2
51	0	32	R	sub rd, rs1, rs2	sub	rd = rs1 - rs2
51	1	0	R	sll rd, rs1, rs2	shift left logical	rd = rs1 << rs2 <sub>4:0</sub>
51	2	0	R	slt rd, rs1, rs2	set less than	rd = (rs1 < rs2)
51	3	0	R	sltu rd, rs1, rs2	set less than unsigned	rd = (rs1 < rs2)
51	4	0	R	xor rd, rs1, rs2	xor	rd = rs1 ^ rs2
51	5	0	R	srl rd, rs1, rs2	shift right logical	rd = rs1 >> rs2
51	5	32	R	sra rd, rs1, rs2	shift right arithmetic	rd = rs1 >>> rs2
51	6	0	R	or rd, rs1, rs2	or	rd = rs1   rs2
51	7	0	R	and rd, rs1, rs2	and	rd = rs1 & rs2
55	-	-	U	lui rd, imm	load upper immediate	rd = {imm <sub>31:12</sub> , 12'b0}
99	0	-	B	beq rs1, rs2, label	branch if =	if (rs1==rs2) PC = BTA
99	1	-	B	bne rs1, rs2, label	branch if !=	if (rs1!=rs2) PC = BTA
99	4	-	B	blt rs1, rs2, label	branch if <	if (rs1< rs2) PC = BTA
99	5	-	B	bge rs1, rs2, label	branch if ≥	if (rs1>=rs2) PC = BTA
99	6	-	B	bltu rs1, rs2, label	branch if < unsigned	if (rs1< rs2) PC = BTA
99	7	-	B	bgeu rs1, rs2, label	branch if ≥ unsigned	if (rs1>=rs2) PC = BTA
103	0	-	I	jalr rd, rs1, imm	jump and link register	rd = PC + 4, PC = rs1 + SignExt(imm)
111	-	-	J	jal rd, label	jump and link	rd = PC + 4, PC = JTA

### RISC-V multiply and divide instructions (RVM extension)

op	f3	f7	Type	Instruction	Description	Operation
51	0	1	R	mul rd, rs1, rs2	multiply	$rd = \{rs1 \times rs2\}_{31:0}$
51	1	1	R	mulh rd, rs1, rs2	multiply high (signed signed)	$rd = \{rs1 \times rs2\}_{63:32}$
51	2	1	R	mulhsu rd, rs1, rs2	multiply high signed unsigned	$rd = \{rs1 \times rs2\}_{63:32}$
51	3	1	R	mulhu rd, rs1, rs2	multiply high unsigned	$rd = \{rs1 \times rs2\}_{63:32}$
51	4	1	R	div rd, rs1, rs2	divide (signed)	$rd = rs1 / rs2$
51	5	1	R	divu rd, rs1, rs2	divide unsigned	$rd = rs1 / rs2$
51	6	1	R	rem rd, rs1, rs2	remainder (signed)	$rd = rs1 \% rs2$
51	7	1	R	remu rd, rs1, rs2	remainder unsigned	$rd = rs1 \% rs2$

## Diagram of a single Logic Element (LE) in a Cyclone IV FPGA

**Figure 2-1. Cyclone IV Device LEs**

