 


# E85 Digital Design & Computer Engineering



## Lecture 01011: Midterm Review

**HARVEY  
MUDD  
COLLEGE**

# Midterm Review

- **Logic Levels**
- **Number Systems**
- **CMOS Transistors**
- **Power Consumption**
- **Combinational Logic Design**
- **Finite State Machines**
- **Timing**
- **Verilog**
- **Arithmetic Circuits**



# Logic Levels

- Assign  $V_{IH}$ ,  $V_{IL}$ ,  $V_{OH}$ ,  $V_{OL}$  to maximize noise margins  
 $|V_{OH} - V_{IH}|$ ,  $|V_{OL} - V_{IL}|$
- Normally at the unity gain points
- If the curve has many bends, pick the ones to maximize noise margins



# Logic Levels: Example

- What is the logic function?

- What are the logic levels?

$$V_{IL} =$$

$$V_{IH} =$$


$$V_{OL} =$$

$$V_{OH} =$$

- What are the noise margins?

$$NM_L =$$

$$NM_H =$$

 

# Logic Levels: Compatibility

- Consider two logic families

$$A: V_{IL} = 1, V_{IH} = 2.3, V_{OL} = 0.4, V_{OH} = 2.9$$

$$B: V_{IL} = 2, V_{IH} = 3, V_{OL} = 1.1, V_{OH} = 3.2$$

Can A drive itself?

Can B drive itself?

Can A drive B?

Can B drive A?



# Number Systems: Signed and Unsigned

Find decimal value of  $101_2$  interpreted as:

Unsigned:

Sign/Magnitude:

Two's Complement:



# Number Systems: Negative Numbers

Write 19 as a 6-bit binary number:

19 =

Write -19 as a 6-bit binary number

Two's complement

Invert the bits and add 1

Sign/Magnitude



# Number Systems: Bases

Write  $37_{10}$  in other bases

Hexadecimal:

Binary:





# CMOS Transistors

- Design nMOS pull-down network
  - Series for AND, parallel for OR
- pMOS pull-up network is complement
- CMOS gates are inherently inverting
- Add another stage to get non-inverting



# CMOS Transistors: OR3

- Sketch a 3-input OR gate
  - Use NOR3 + inverter
  - NOR3: nMOS in parallel, hence pMOS in series



# CMOS Transistors: AOI

- Sketch an AND-OR-INVERT gate  $Y = \sim(AB+C)$ 
  - nMOS network
    - A and B in series. This stack in parallel with C
  - pMOS network is complement
    - A and B in parallel. This stack in series with C





# Switches and LEDs

- Switch:

- Choose R big enough to limit power, small enough to keep a good logic level if  $I_{load}$  is leakage current.
- $P = V_{DD}^2/R$
- $V_{out} = I_{load} * R < V_{IL}$

- Light Emitting Diode

 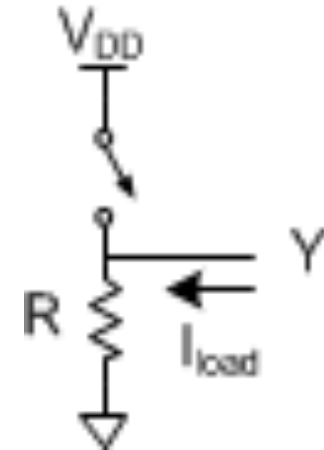- Choose R small enough to make the LED bright, large enough to not overstress  $I_{OH}$  of the gate driving  $V_{in}$ .
- $I_D \sim (V_{in} - 2) / R$
- 5 mA is visible in room lighting and near max  $I_{OH}$  of many gates



# Power Consumption

- $P = P_{\text{dynamic}} + P_{\text{static}} = \alpha C V_{\text{DD}}^2 f + I_{\text{static}} V_{\text{DD}}$ 
  - $\alpha$  = activity factor:
    - 1 for clocks rising and falling each cycle
    - 0.5 for data signal switching once per cycle
    - 0.5p for data signal switching with probability p
- Know your units
  - K =  $10^3$ , M =  $10^6$ , G =  $10^9$ , T =  $10^{12}$
  - m =  $10^{-3}$ ,  $\mu$  =  $10^{-6}$ , n =  $10^{-9}$ , p =  $10^{-12}$ , f =  $10^{-15}$



# Power Consumption: Example

- $V_{DD} = 0.707 \text{ V}$
- 1000 flip-flops clocked at 1 GHz. For each:
  - 100 nA leakage
  - 5 fF of clock capacitance
  - 20 fF capacitance on Q
  - 10% of inputs change on any given cycle
- Idle power =  $P_{\text{static}} =$
- Running power =  $P_{\text{static}} + P_{\text{dynamic}} = 70.7 \mu\text{W} +$




# Combinational Logic Design

- Output depends on current inputs
- Write truth table
- Circle 1's to find sum of products
- Simplify with Boolean algebra or inspection



# Combinational Logic: Example

- Write a truth table & eqn for

 

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Y =





# Combinational Logic: K-Map

- Write inputs in Gray code order 00 01 11 10
- Populate grid
- Circle 1's in boxes 1, 2, or 4 on a side
- Optionally circle Xs if it simplifies

		AB			
		00	01	11	10
CD	00	0	1	X	1
	01	0	1	1	0
	11	0	0	0	0
	10	X	0	0	1

$Y =$




# Sequential Circuits

- Sequential circuits: output depends on previous as well as current inputs
- Flip-flops
  - On the rising edge of CLK, Q gets D.
  - Enables
  - Reset: synchronous or asynchronous
- Synchronous sequential design: every element is combinational or a flip-flop, and all flops share the same clock. Easy to analyze.




 
# Finite State Machines

- State transition diagram
  - State encodings
  - Next state and output tables
  - Derive and simplify Boolean equations
  - Sketch circuit
- 
- Inverse problems: derive diagram from circuit




  
# Moore Vs. Mealy Machines

- Moore:
  - output depends only on state.
  - labeled in bubbles




  - Mealy:
  - output depends on state and inputs
  - labeled on arcs




 
# Inverse FSM Problems

- Derive FSM state transition diagram from circuit
- Trace FSM
  - Start in reset state
  - For each state being explored
    - Determine next state for each input pattern
    - Determine output



# Timing

  

$$T_c \geq$$



# Metastability

For each sample, probability of failure is:

$$P(\text{failure}) = (T_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$


$$P(\text{failure})/\text{second} =$$

$$(NT_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$

$$\text{MTBF} =$$

$$1/[P(\text{failure})/\text{second}] =$$
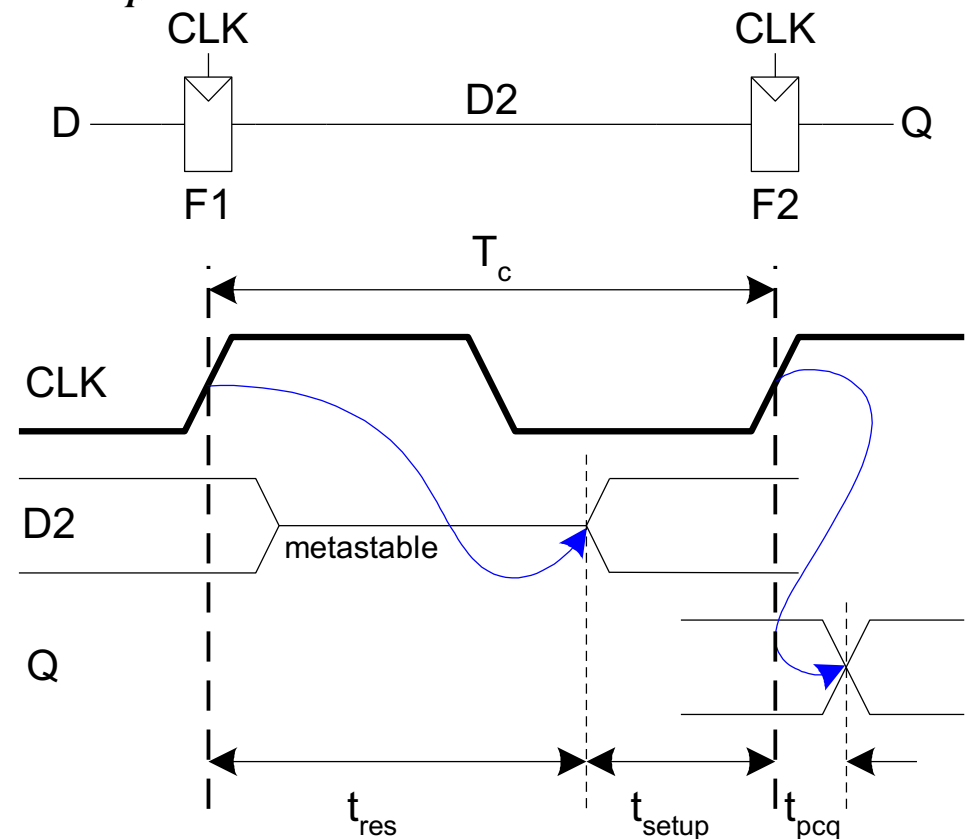
$$(T_c/NT_0) e^{(T_c - t_{\text{setup}})/\tau}$$



# Verilog

- Think of the logic you want first
- Use Verilog as shorthand for logic
- Pick the appropriate idiom for each element





# Verilog Idioms: Combinational Logic

## Combinational Logic with Boolean Eqns.

```
assign y = (a & b) ^ (c | ~d);
```

## Multiplexers

```
assign y = s ? d1 : d0;
```


## Comb logic with truth tables

```
always_comb
    casez (in)
        3'b1xx: y <= 2'b11;
        3'b01x: y <= 2'b10;
        3'b001: y <= 2'b01;
        default: y <= 2'b00;
    endcase
```


 
# Verilog Idioms: FSMs

```
module fsmWithInputs(input logic clk,  
                    input logic reset,  
                    input logic a,  
                    output logic q);  
  
typedef enum logic [1:0] {S0, S1, S2} statetype;  
statetype state, nextstate;  
  
// state register  
always_ff @(posedge clk, posedge reset)  
    if (reset) state <= S0;  
    else      state <= nextstate;  
  
// next state logic  
always_comb  
    case (state)  
        S0:      if (a) nextstate = S1;  
                else nextstate = S0;  
        S1:      nextstate = S2;  
        S2:      if (a) nextstate = S2;  
                else nextstate = S0;  
        default: nextstate = S0;  
    endcase  
  
// output logic  
assign q = (state == S2);  
endmodule
```



# Verilog Idioms: Structural

```
module mux2(input  logic [3:0] d0, d1,  
            input  logic      s,  
            output logic [3:0] y);
```

```
    assign y = s ? d1 : d0;  
endmodule
```


```
module mux2_8(input  logic [7:0] d0, d1,  
              input  logic      s,  
              output logic [7:0] y);
```

```
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```




# Adders

## Ripple Carry

 

## Carry Lookahead

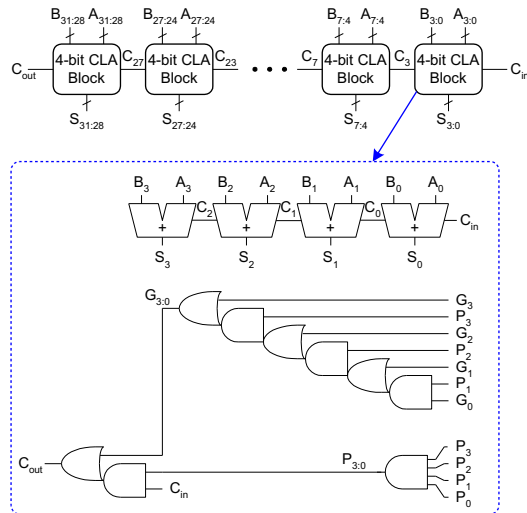

## Parallel Prefix

