


**Digital Design &
Computer Architecture**

Sarah Harris & David Harris

**Chapter 2:
Combinational Logic
Design**

Chapter 2 :: Topics

- **Combinational Circuits**
- **Boolean Equations**
- **Boolean Algebra**
- **From Logic to Gates**
- **X's and Z's, Oh My**
- **Karnaugh Maps**
- **Combinational Building Blocks**
- **Timing**

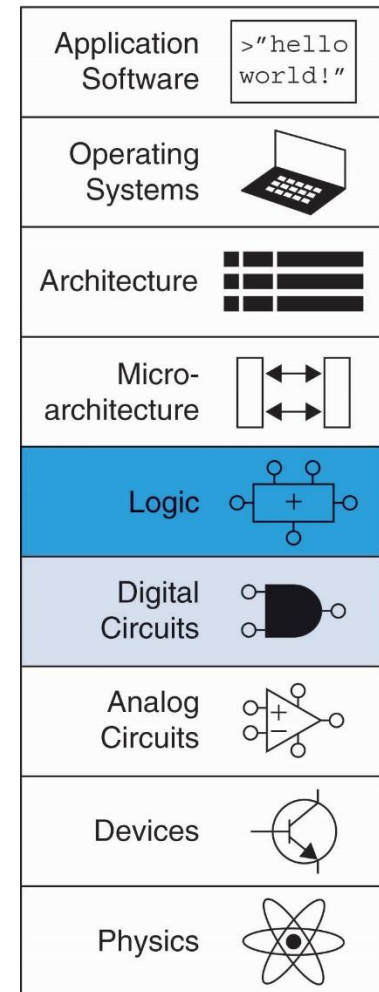


Chapter 2: Combinational Logic

Combinational Circuits

Introduction

A logic circuit is composed of:

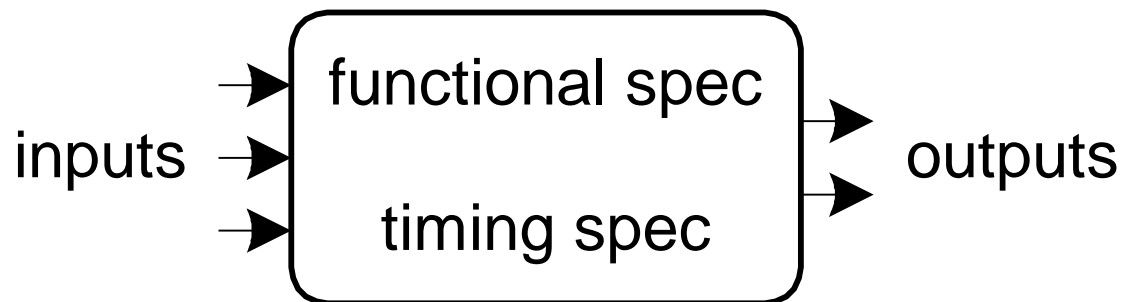- Inputs
- Outputs
- Functional specification
- Timing specification




Circuits

- **Nodes**

- Inputs: A, B, C
- Outputs: Y, Z
- Internal: $n1$

- **Circuit elements**

- $E1, E2, E3$
- Each a circuit

 


Types of Logic Circuits

- **Combinational Logic**

- Memoryless
- Outputs determined by current values of inputs


- **Sequential Logic**

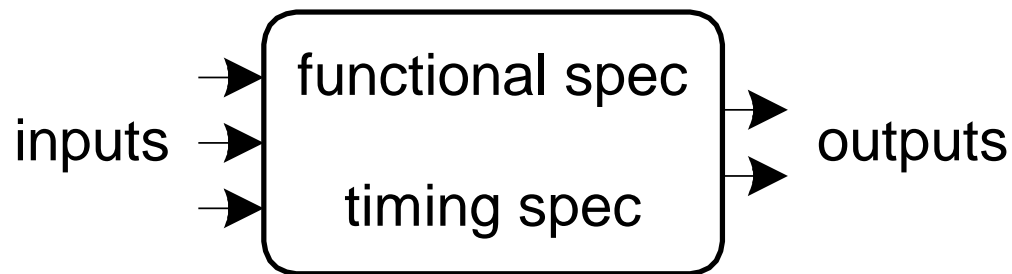- Has memory
- Outputs determined by previous and current values of inputs



Rules of Combinational Composition

- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- **Example:**

 


Chapter 2: Combinational Logic

Boolean Equations

Boolean Equations

- Functional specification of outputs in terms of inputs

 - **Example:** $S = F(A, B, C_{in})$
 $C_{out} = F(A, B, C_{in})$



$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Some Definitions

- **Complement:** variable with a bar over it

$\bar{A}, \bar{B}, \bar{C}$

- **Literal:** variable or its complement

$A, \bar{A}, B, \bar{B}, C, \bar{C}$

- **Implicant:** product of literals

$AB\bar{C}, \bar{A}C, BC$

- **Minterm:** product that includes all input variables

$AB\bar{C}, \bar{A}\bar{B}\bar{C}, ABC$

- **Maxterm:** sum that includes all input variables

$(A+\bar{B}+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$

Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing minterms** where output is **1**
- Thus, a **sum** (OR) of **products** (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) =$$

Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing minterms** where output is **1**
- Thus, a **sum** (OR) of **products** (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	m_0
0	1	1	$\bar{A} B$	m_1
1	0	0	$A \bar{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \bar{A}B + AB = \Sigma(1, 3)$$

Long-hand Short-hand

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a **sum** (OR) of literals
- Each maxterm is **FALSE** for that row (and only that row)
- Form function by **ANDing maxterms** where output is **0**
- Thus, a **product** (AND) of **sums** (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B) = (A + B) \bullet (\overline{A} + B) = \Pi(\mathbf{0}, \mathbf{2})$$

Long-hand

Short-hand

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch ($E = 0$)
 - If it's not clean ($C = 0$) or
 - If they only serve meatloaf ($M = 1$)
- Write a truth table for determining if you will eat lunch (E).

C	M	E
0	0	
0	1	
1	0	
1	1	

SOP & POS Form

SOP – sum-of-products

C	M	E	minterm
0	0	0	$\overline{C} \overline{M}$
0	1	0	$\overline{C} M$
1	0	1	$C \overline{M}$
1	1	0	$C M$

POS – product-of-sums

C	M	E	maxterm
0	0	0	$C + M$
0	1	0	$C + \overline{M}$
1	0	1	$\overline{C} + M$
1	1	0	$\overline{C} + \overline{M}$

SOP & POS Form

SOP – sum-of-products

C	M	E	minterm
0	0	0	$\bar{C} \bar{M}$
0	1	0	$\bar{C} M$
1	0	1	$C \bar{M}$
1	1	0	$C M$

$$\begin{aligned} E &= C\bar{M} \\ &= \Sigma(2) \end{aligned}$$

POS – product-of-sums

C	M	E	maxterm
0	0	0	$C + M$
0	1	0	$C + \bar{M}$
1	0	1	$\bar{C} + M$
1	1	0	$\bar{C} + \bar{M}$

$$\begin{aligned} E &= (C + M)(C + \bar{M})(\bar{C} + \bar{M}) \\ &= \Pi(0, 1, 3) \end{aligned}$$

Forming Boolean Expressions

Example 1:

We will go to the Park (P is the output) if it's not Raining (\overline{R}) and we have Sandwiches (S).

Boolean Equation:

Forming Boolean Expressions

Example 2:

You will be considered a Winner (**W** is the output) if we send you a Million dollars (**M**) or a small Notepad (**N**).

Boolean Equation:

Forming Boolean Expressions

Example 3:

You can Eat delicious food (E is the output) if you Make it yourself (M) or you have a personal Chef (C) and she/he is talented (T) but not eXpensive (\bar{X}).

Boolean Equation:

Forming Boolean Expressions

Example 4:

You can Enter the building if you have a Hat and Shoes on or if you have a Hat on.

Boolean Equation:

Forming Boolean Expressions

Example 5:

You can Enter the building if you have a Hat and Shoes on or if you have a Hat and no Shoes on.

Boolean Equation:

Chapter 2: Combinational Logic

Boolean Algebra: Axioms

Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
 - ANDs and ORs, 0's and 1's interchanged

Boolean Axioms

Number	Axiom	Name
A1	$B = 0 \text{ if } B \neq 1$	Binary Field
A2	$\bar{0} = 1$	NOT
A3	$0 \bullet 0 = 0$	AND/OR
A4	$1 \bullet 1 = 1$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	AND/OR

Boolean Axioms

Number	Axiom	Dual	Name
A1	$B = 0 \text{ if } B \neq 1$	$B = 1 \text{ if } B \neq 0$	Binary Field
A2	$\bar{0} = 1$	$\bar{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	$1 + 0 = 0 + 1 = 1$	AND/OR

Dual: Replace: \bullet with $+$
 0 with 1

Chapter 2: Combinational Logic

Boolean Algebra: Theorems of One Variable

Boolean Theorems of One Variable

Number	Theorem	Name
T1	$B \bullet 1 = B$	Identity
T2	$B \bullet 0 = 0$	Null Element
T3	$B \bullet B = B$	Idempotency
T4	$\overline{\overline{B}} = B$	Involution
T5	$B \bullet \overline{B} = 0$	Complements

Dual: Replace: \bullet with $+$
 0 with 1

Boolean Theorems of One Variable

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	$B + \overline{B} = 1$	Complements

Dual: Replace: \bullet with $+$
 0 with 1

T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

T4: Involution Theorem

- $\overline{\overline{B}} = B$

T5: Complement Theorem

- $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$

Recap: Basic Boolean Theorems

Number	Theorem	Dual	Name
T1	$B \cdot 1 = B$	$B + 0 = B$	Identity
T2	$B \cdot 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \cdot B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \cdot \overline{B} = 0$	$B + \overline{B} = 1$	Complements

Chapter 2: Combinational Logic

Boolean Algebra: Theorems of Several Variables

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

Warning: T8' differs from traditional algebra:
OR (+) distributes over AND (•)

How to Prove

- **Method 1:** Perfect induction
- **Method 2:** Use other theorems and axioms to simplify the equation
 - Make one side of the equation look like the other

Proof by Perfect Induction

- Also called: **proof by exhaustion**
- Check every possible input value
- If the two expressions produce the same value for every possible input combination, the expressions are equal

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Prove true by:

- **Method 1:** Perfect induction
- **Method 2:** Using other theorems and axioms

T9: Covering

Number	Theorem	Name
T9	$B \cdot (B+C) = B$	Covering

Method 1: Perfect Induction

<i>B</i>	<i>C</i>	<i>(B+C)</i>	<i>B(B+C)</i>
0	0		
0	1		
1	0		
1	1		

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 2: Prove true using other axioms and theorems.

T10: Combining

Number	Theorem	Name
T10	$(B \cdot C) + (B \cdot \overline{C}) = B$	Combining

Prove true using other axioms and theorems:

De Morgan's Theorem: Dual

#	Theorem	Dual	Name
T12	$\overline{B \cdot C \cdot D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B + C + D \dots} = \bar{B} \cdot \bar{C} \cdot \bar{D} \dots$	De Morgan's Theorem

The **complement** of the **product** is the **sum** of the **complements**.

Recap: Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus
T12	$\overline{B \bullet C \bullet D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B + C + D \dots} = \bar{B} \bullet \bar{C} \bullet \bar{D} \dots$	De Morgan's

Chapter 2: Combinational Logic

Boolean Algebra: Simplifying Equations

Simplifying an Equation

Simplifying may mean minimal sum of products form:

- SOP form that has the **fewest number of implicants**, where each implicant has the **fewest literals**

- **Implicant:** product of literals

$$ABC, A\bar{C}, B\bar{C}$$

- **Literal:** variable or its complement

$$A, \bar{A}, B, \bar{B}, C, \bar{C}$$

Simplifying could also mean fewest number of gates, lowest cost, lowest power, etc. For example, $Y \equiv A \text{ xor } B$ is likely simpler than minimal Sum of Products $Y = AB + \bar{A}\bar{B}$. These depend on details of the technology.

Simplifying Boolean Equations

Example 1:

$$Y = \bar{A}B + AB$$

$$Y = B$$

T10: Combining

or

$$Y = B(A + \bar{A})$$

T8: Distributivity

$$= B(1)$$

T5': Complements

$$= B$$

T1: Identity

Simplifying Boolean Equations

Example 2:

$$Y = \bar{A}\bar{B}C + ABC + \bar{A}BC$$

$$= \bar{A}\bar{B}C + \color{red}{ABC} + \color{red}{ABC} + \bar{A}BC \quad \text{T3': Idempotency}$$

$$= (\color{red}{\bar{A}\bar{B}C+ABC}) + (\color{blue}{ABC+\bar{A}BC}) \quad \text{T7': Associativity}$$

$$= \color{red}{AC} + \color{blue}{BC} \quad \text{T10: Combining}$$

Chapter 2: Combinational Logic

Extra Examples

**Boolean Algebra:
Simplifying Equations**

Simplification methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{PA} + PA = P$
- **Expansion**
 $P = \overline{PA} + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Proving the “Simplification” Theorem

“Simplification” theorem

$$A + \overline{A}P = A + P$$

Method 1:

Method 2:

T11: Consensus

Number	Theorem	Name
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) =$ $(B \bullet C) + (\bar{B} \bullet D)$	Consensus

Prove using other theorems and axioms:

Simplification methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{PA} + PA = P$
- **Expansion**
 $P = \overline{PA} + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Simplification methods

- **Distributivity (T8, T8')** $B(C+D) = BC + BD$
 $B + CD = (B+ C)(B+D)$
- **Covering (T9')** $A + AP = A$
- **Combining (T10)** $\overline{PA} + PA = P$
- **Expansion** $P = \overline{PA} + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem** $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Simplifying Boolean Equations

Example 3:

$$Y = A(AB + ABC)$$

Simplification methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{PA} + PA = P$
- **Expansion**
 $P = \overline{PA} + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Simplifying Boolean Equations

Example 4:

$$Y = A'BC + A'$$

Recall: $A' = \bar{A}$

Simplifying Boolean Equations

Example 4:

$$Y = A'BC + A'$$

Recall: $A' = \bar{A}$

or

Multiplying Out: SOP Form

An expression is in **sum-of-products (SOP)** form when all products contain literals only.

- **SOP form:** $Y = AB + BC' + DE$
- **NOT SOP form:** $Y = DF + E(A' + B)$
- **SOP form:** $Z = A + BC + DE'F$

Multiplying Out: SOP Form

Example 5:

$$Y = (A + C + D + E)(A + B)$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

or

Simplifying Boolean Equations

Example 6:

$$Y = AB + BC + B'D' + AC'D'$$

Method 1:

Method 2:

Literal and implicant ordering

- Variables within an implicant should be in alphabetical order.
- The order of implicants doesn't matter.

Simplifying Boolean Equations

Example 7:

$$Y = (A + BC)(A + DE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

or

Review: Canonical SOP & POS Forms

SOP – sum-of-products $E = \boxed{C\bar{M}}$

C	M	E	minterm
0	0	0	$\bar{C}\bar{M}$
0	1	0	$\bar{C}M$
1	0	1	$C\bar{M}$
1	1	0	CM

same

POS – product-of-sums $E = (C + M)(C + \bar{M})(\bar{C} + \bar{M})$

C	M	E	maxterm
0	0	0	$C + M$
0	1	0	$C + \bar{M}$
1	0	1	$\bar{C} + M$
1	1	0	$\bar{C} + \bar{M}$

Factoring: POS Form

An expression is in **product-of-sums (POS)** form when all sums contain literals only.

- **POS form:** $Y = (A+B)(C+D)(E'+F)$
- **NOT POS form:** $Y = (D+E)(F'+GH)$
- **POS form:** $Z = A(B+C)(D+E')$

Factoring: POS Form

Example 8:

$$Y = (A + B' CDE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Factoring: POS Form

Example 9:

$$Y = AB + C'DE + F$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

De Morgan's Theorem

Example 10:

$$Y = \overline{(A+BD)C}$$

- Work from the **outside in** (i.e., top bar, then down)
- Use **involution** when possible

De Morgan's Theorem

Example 11:

$$Y = \overline{\overline{ACE} + \overline{D}} + B$$

Chapter 2: Combinational Logic

Common Errors

Boolean Algebra: Simplifying Equations

Common Errors

- Using ticks ' instead of **bars** over variables when writing equations by hand – ticks are easy to lose
- **Not** keeping terms **aligned** from step to step
 - Alignment helps you see what changed from step-to-step.
 - It helps in both solving and double-checking the problem.
- Applying **multiple theorems** to the same term in one step
- Applying **your own personal theorems** – don't do it 😊
- And, on a related note: **almost** applying the correct theorem
- **Not** looking for opportunities to use combining, covering, and distributivity (especially the dual form).

Common Errors

- **Losing bars** (alignment will help you avoid this)
- **Losing terms** (alignment will help you avoid this)
- **Trying to do multiple steps at once** – this is prone to errors!
- **Applying theorems incorrectly**, for example:
 - **Wrong:** $ABC + \overline{ABC} = B$ **Correct:** $ABC + \overline{ABC} = AC$. Products may only **differ in a single term** when using the combining theorem.
 - **Wrong:** $(A + \overline{A}) = 0$ **Correct:** $A + \overline{A} = 1$
 - **Wrong:** $(A \cdot \overline{A}) = 1$ **Correct:** $A \cdot \overline{A} = 0$
 - **Wrong:** $ABC = B$ **Correct:** $B + ABC = B$. In order to use the covering theorem, you must have a term that covers the other terms.
 - **Wrong:** $\overline{AC} = \overline{A}\overline{C}$ **Correct:** $\overline{AC} = \overline{A} + \overline{C}$ (De Morgan's)
 - **Wrong:** $\overline{A + C} = \overline{A} + \overline{C}$ **Correct:** $\overline{A + C} = \overline{A}\overline{C}$ (De Morgan's)

Common Errors with De Morgan's

- Not starting from the outside parentheses and working in: this often causes additional steps.
- Trying to apply De Morgan's theorem to an entire **complex operation** (instead of just to terms ANDed under a bar or terms ORed under a bar)
- **Losing bars.** Remember that applying the De Morgan's Theorem is a 3 step process. For a product term under a bar:
 1. Change ANDs to ORs (or vice versa for a sum term under a bar)
 2. Bring down the terms
 3. Put bars over the individual terms
- Not keeping terms associated (i.e., **losing parentheses**)
 - For example, $\overline{ABC} = \overline{A+B+C}$
 - Example error:
 - **Wrong:** $(ABC)'C+D' = A'+B'+C'C + D' = A' + B' + D'$
 - **Correct:** $(ABC)'C + D' = (A'+B'+C')C + D' = A'C+B'C + D'$

Chapter 2: Combinational Logic

From Logic to Gates


From Logic to Gates

Build the following equation using logic gates:

$$Y = A\bar{B} + \bar{C}DE$$

Circuit Schematics Rules

 
- Inputs on the left (or top)
- Outputs on right (or bottom)
- Gates flow from left to right
- Straight wires are best




Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction

 

wires connect
at a dot

 

 wires crossing
without a dot do
not connect





Two-Level Logic

- Two-level logic: **ANDs** followed by **ORs**
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$

Multilevel Logic

  
- Complex logic is often built from many stages of simpler gates.



Multiple-Output Circuits

 - Example: Priority Circuit**

Output asserted
corresponding to most
significant TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0				
0	0	0	1				1
0	0	1	0			1	
0	0	1	1			1	
0	1	0	0		1		
0	1	0	1		1		
0	1	1	0		1		
0	1	1	1		1		
1	0	0	0	1			
1	0	0	1	1			
1	0	1	0	1			
1	0	1	1	1			
1	1	0	0	1			
1	1	0	1	1			
1	1	1	0	1			
1	1	1	0	1			
1	1	1	1	1			
1	1	1	1	1			

Priority Circuit Hardware

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

Don't Cares

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

$$Y_3 = A_3$$

$$Y_2 = \overline{A_3} A_2$$

$$Y_1 = \overline{A_3} \overline{A_2} A_1$$

$$Y_0 = \overline{A_3} \overline{A_2} \overline{A_1} A_0$$

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

Chapter 2: Combinational Logic

Two-Level Logic Forms

Two-Level Logic Variations

- **ANDs** followed by **ORs**: **SOP** form
- **ORs** followed by **ANDs**: **POS** form
- Only **NAND** gates: **SOP** form
- Only **NOR** gates: **POS** form


Most common form of two-level logic

Two-Level Logic Variation

- Two-level logic variation: **ORs** followed by **ANDs**
- Example: $Y = (\bar{A} + \bar{B})(A + B + \bar{C})$


Two-Level Logic

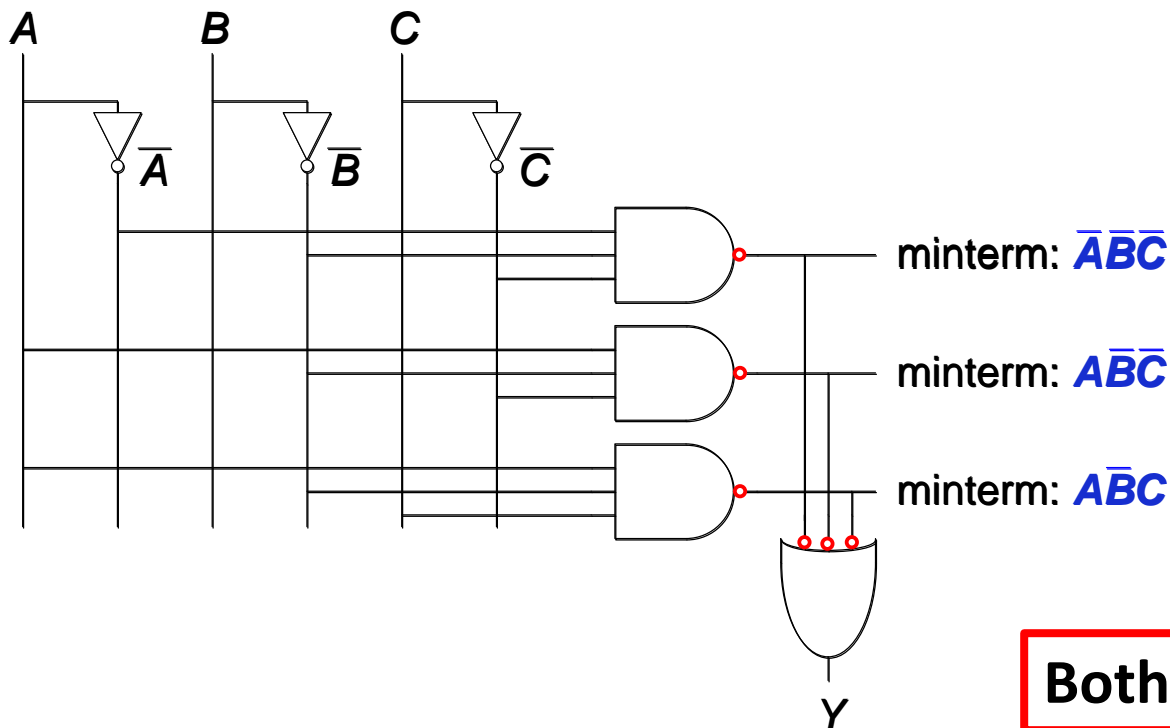- Two-level logic: **ANDs** followed by **ORs** → **NANDs**
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$



Two-Level Logic Variation

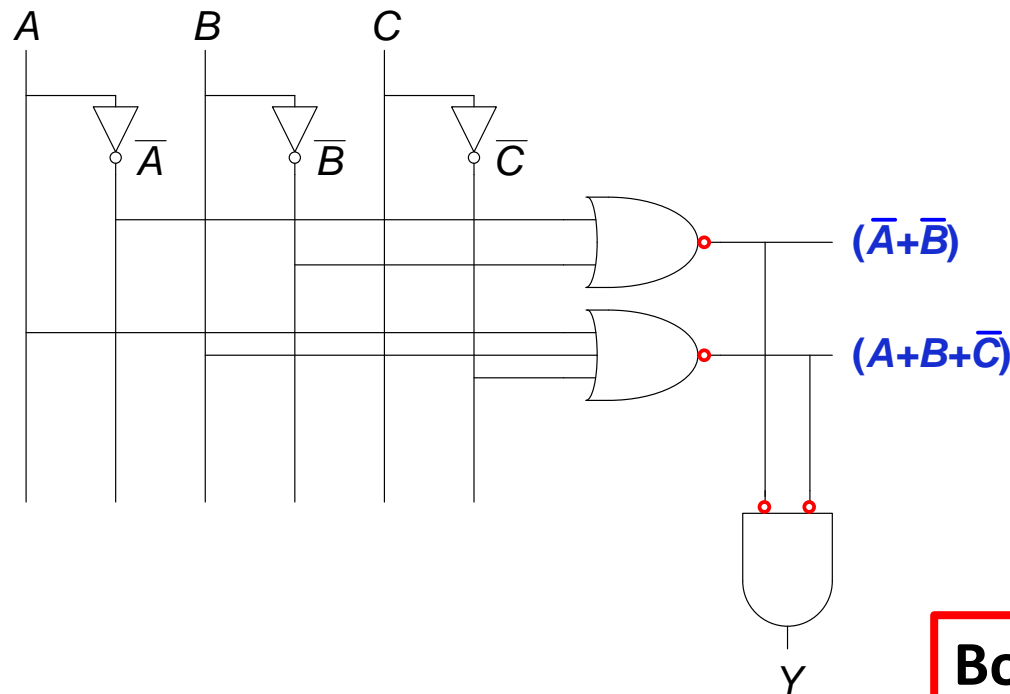- Two-level logic: **ORs** followed by **ANDs** → **NORs**
- Example: $Y = (\bar{A} + \bar{B})(A + B + \bar{C})$



Both: **POS** form

Chapter 2: Combinational Logic

Bubble Pushing

De Morgan's Theorem

#	Theorem	Dual	Name
T12	$\overline{B \cdot C \cdot D \dots} = \overline{B} + \overline{C} + \overline{D} \dots$	$\overline{B + C + D \dots} = \overline{B} \cdot \overline{C} \cdot \overline{D} \dots$	De Morgan's Theorem

De Morgan's Theorem

Example D1:

$$\begin{aligned} Y &= \overline{A+BC} \\ &= \overline{A} \cdot \overline{BC} \\ &= \overline{A} \cdot BC \\ &= \overline{A}BC \end{aligned}$$

- Work from the **outside in** (i.e., top bar, then down)
- Use **involution** when possible

DeMorgan's Theorem

Example D2:

$$\begin{aligned} Y &= \overline{A+BC+\overline{A}\overline{B}} \\ &= \overline{A} \cdot \overline{\overline{BC}} \cdot \overline{\overline{A}\overline{B}} \\ &= \overline{A} \cdot BC \cdot (\overline{\overline{A}} + \overline{\overline{B}}) \\ &= \overline{A}BC \cdot (A + B) \\ &= \overline{A}BCA + \overline{A}BCB \\ &= \overline{A}BC \end{aligned}$$

- De Morgan **applies to**:
 - **Products** under a bar
 - **Sums** under a bar
- **Do not** try to apply DeMorgan's to a **mix of operations**

De Morgan's Theorem

Example D2:

$$\begin{aligned} Y &= \overline{A+BC+\overline{A}\overline{B}} \\ &= \overline{A} \cdot \overline{\overline{BC}} \cdot \overline{\overline{A}\overline{B}} \\ &= \overline{A} \cdot BC \cdot (\overline{\overline{A}} + \overline{\overline{B}}) \\ &= \overline{A}BC \cdot (A + B) \\ &= \overline{A}BCA + \overline{A}BCB \\ &= \overline{A}BC \end{aligned}$$


Don't forget these parentheses!

Remember:


$$\overline{\overline{A}\overline{B}} = (A + B)$$

De Morgan's Theorem: Gates

 
- $Y = \overline{AB} = \overline{A} + \overline{B}$




NAND gate
two forms

 

 - $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



NOR gate
two forms

 

Bubble Pushing


- **Backward:**

- Body changes
- Adds bubbles to inputs




Bubble Pushing

 - What is the Boolean expression for this circuit?




Bubble Pushing Rules

 - Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel



Bubble Pushing Example

 


Chapter 2: Combinational Logic

X's and Z's, Oh My

Contention: X

 - **Contention:** circuit tries to drive output to 1 and 0
 - Actual value somewhere in between
 - Could be 0, 1, or in forbidden zone
 - Might change with voltage, temperature, time, noise
 - Often causes excessive power dissipation




- **X is also used for:**
 - Uninitialized values
 - Don't Care
- **Warnings:**
 - Contention or uninitialized outputs usually indicate a **bug**.
 - Look at the context to tell meaning

Floating: Z

- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
 - A voltmeter **won't** indicate whether a node is floating
 - But if you touch the node or your instructor walks over for a checkoff, it may change randomly

Tristate Buffer

 


E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

Tristate Busses

Floating nodes are used in tristate busses

- Many different drivers
- Exactly one is active at once

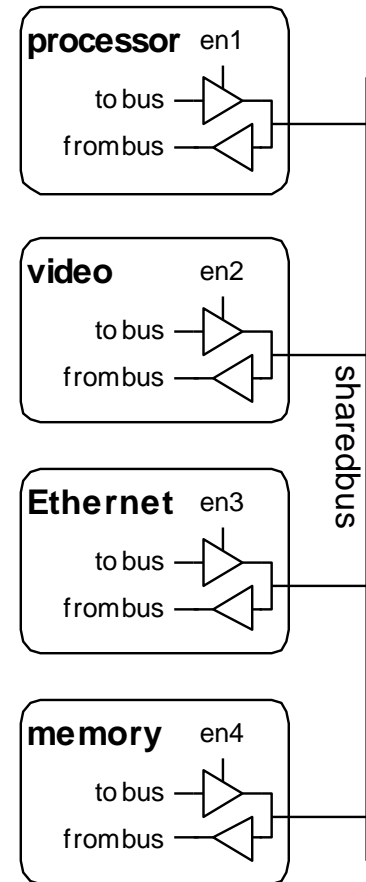



Chapter 2: Combinational Logic

Karnaugh Maps

Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
 - $PA + \overline{PA} = P$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

  

K-Map

- Circle 1's in adjacent squares
- In Boolean expression: include only literals whose true **and** complement form are **not** in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y	AB			
	00	01	11	10
0	1	0	0	0
1	1	0	0	0

Y	AB			
	00	01	11	10
0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C = \bar{A}\bar{B}$$

3-Input K-Map

- Circle 1's in adjacent squares
- In Boolean expression: include only literals whose true **and** complement form are **not** in the circle

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

		AB			
		00	01	11	10
C	0				
	1				

Y =

Some Definitions

- **Complement:** variable with a bar over it

$\bar{A}, \bar{B}, \bar{C}$

- **Literal:** variable or its complement

$A, \bar{A}, B, \bar{B}, C, \bar{C}$

- **Implicant:** product of literals

$ABC, \bar{A}C, BC$

- **Prime implicant:** implicant corresponding to the **largest circle** in a K-map

K-Map Rules

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**


4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

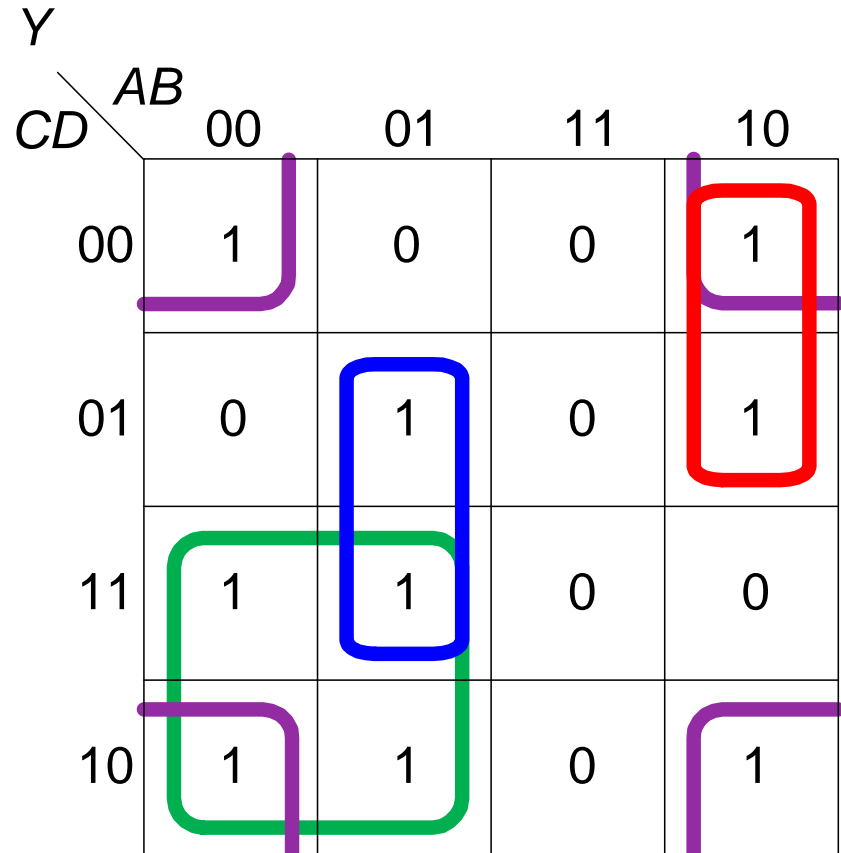

Y =

Chapter 2: Combinational Logic

Karnaugh Maps with Don't Cares

K-Map Rules

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**
- Circle a “**don't care**” (X) **only if it helps** minimize the equation


K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Y	AB	00	01	11	10
CD	00				
01					
11					
10					

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

 


Chapter 2: Combinational Logic

Combinational Building Blocks: Multiplexers

Multiplexer (Mux)

- Selects between one of N inputs to connect to output
- **Select** input is $\log_2 N$ bits – control input
- **Example:**

2:1 Mux

 

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


2:1 Multiplexer Implementations

- **Logic gates**

- Sum-of-products form


Y S	D_0D_1			
	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Y = D_0\bar{S} + D_1S$$

 


- **Tristates**

 - Two tristates
- Turn on exactly one to select the appropriate input




4:1 Multiplexer Implementations


2-Level Logic

 


Tristates

 

4:1 Mux Symbol

 

Hierarchical

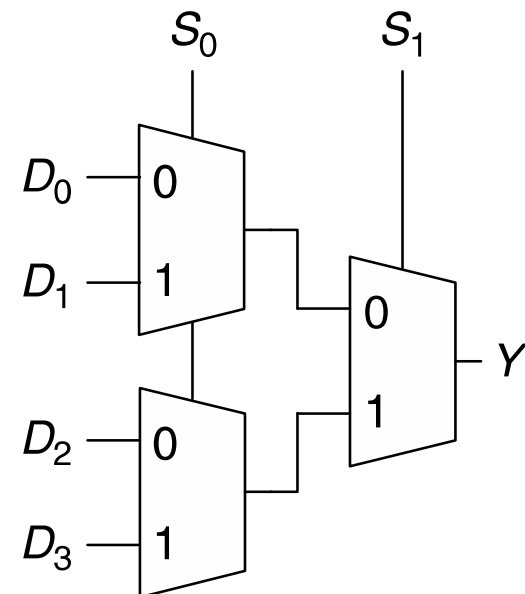


Logic using Multiplexers

Using mux as a **lookup table**

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	0
1	1	0

$$Y = \overline{A}B$$

 


Chapter 2: Combinational Logic

Combinational Building Blocks: Decoders


Decoders

 - N inputs, 2^N outputs
- **One-hot outputs:** only one output **HIGH** at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder Implementation

 

Logic Using Decoders

OR the minterms:

 


Chapter 2: Combinational Logic

Timing


Timing

 - **Delay:** time between input change and output changing
- How to build fast circuits?



Propagation & Contamination Delay

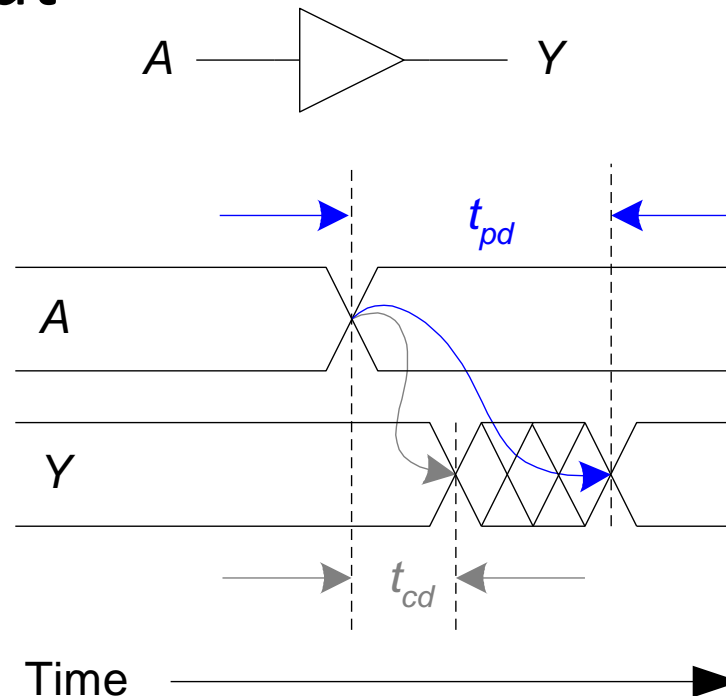
- **Propagation delay:** $t_{pd} = \mathbf{max}$ delay from input to output
- **Contamination delay:** $t_{cd} = \mathbf{min}$ delay from input to output



Propagation & Contamination Delay

- **Delay is caused by**
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- **Reasons why t_{pd} and t_{cd} may be different:**
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold

Critical (Long) & Short Paths

 

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$ (max delay)


Short Path: $t_{cd} = t_{cd_AND}$ (min delay)

Glitches

When a single input change causes an output to change multiple times

Glitch Example


 
What happens when $A = 0$, $C = 1$, B falls?



		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$


Glitch Example (cont.)

  

Fixing the Glitch

Y		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

 

Why Understand Glitches?

- Because of **synchronous design** conventions (see Chapter 3), glitches don't cause problems.
- It's important to **recognize** a glitch: in simulations or on oscilloscope.
- We **can't get rid of all glitches** – simultaneous transitions on multiple inputs can also cause glitches.

About these Notes

Digital Design and Computer Architecture Lecture Notes

© 2021 Sarah Harris and David Harris

These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.