



## 2. Generating Tones

Design a digital system with four inputs from KEY<sub>3:0</sub> and one output to GPIO D0. When a key is pressed, a square wave of the corresponding frequency as given below should be generated. Set the output frequencies within 1% of the desired frequencies.

To generate tones, you may want to use one of the DE0 board's clock signals. There are buffered 50MHz clock signals connected to PIN\_M9, PIN\_H13, PIN\_E10, and PIN\_V15. If you are using a reset signal, you can assign reset to a toggle switch, e.g., SW0, PIN\_U13.

Remember that the keys are wired active low, i.e. they produce a 1 when not pressed and a 0 when pressed.

- Sketch a schematic at the level of registers, adders, multiplexers, and gates.
- Write behavioral SystemVerilog to implement your design.
- Program it onto the DE2 board and test it.
- Measure the output frequency for each key pressed with an oscilloscope.
- Fill out the following table. If more than one key is pressed, you can choose what should happen.

Key	Note	Desired Frequency (Hz)	Actual Frequency (Hz)
KEY3	C	261.6	
KEY2	E	329.6	
KEY1	G	392	
KEY0	A	440	

## 3. A Happy Song (if you enjoy the Bubonic Plague)

- Play a tune by tapping the following keys.

1120 12 1120 12 12 12 11 3

Can you name the tune?

## 4. Extra Credit

- Invent another song for your keyboard or modify the hardware to create another interesting feature, such as the ability to add more notes, change octaves, play more than one note at a time, or play a tune automatically.
- Test your invention.

## What to Turn In

1. Please indicate how many hours you spent on this lab. This will be helpful for calibrating the workload for next time the course is taught.
2. Schematic
3. Behavioral SystemVerilog code
4. Table of actual output frequencies

Key	Note	Desired Frequency (Hz)	Actual Frequency (Hz)
KEY3	C	261.6	
KEY2	E	329.6	
KEY1	G	392	
KEY0	A	440	

5. Does your system play music? Can you name the tune? (it's ok if you don't recognize it)
6. Extra credit, if applicable

Please indicate any bugs you found in this lab manual, or any suggestions you would have to improve the lab.