

Introduction to Computer Engineering (E114)

Harris

Spring 1999

Problem Set 8

Due: Friday, March 26

Reading: Chapter 5.5, 5.7-5.10, Appendix C4-C6

1) Cycle Time of Single-Cycle Implementation

Do problem 5.14 from the text.


2) Performance Comparison of Single and Multi-Cycle Processors

In this problem, we'll compare the performance of single and multi-cycle MIPS processor implementations. The multi-cycle processor has a shorter cycle time because each cycle contains less logic; however, multiple cycles are required to complete an instruction. Overall, is it worthwhile? Hint: many of the answers to parts of this question are given in the book or are very simple. Don't confuse yourself by thinking this problem is harder than it really is.


- Using the function unit timing from page 373, what is the required clock period for the single-cycle processor? What is the clock frequency (in MHz)?
- Using the same timing, what is the required clock period of the multi-cycle processor? What is the clock frequency (in MHz)?
- Assuming the instruction mix given on page 397, what is the average number of cycles per instruction (CPI) required by the multi-cycle processor?
- What is the average CPI of the single-cycle processor? Hint: if you understand what CPI means, you don't need to look at Chapter 5 to answer this part.
- What is the average MIPS rating of the single-cycle processor? Of the multi-cycle processor? Which is better?

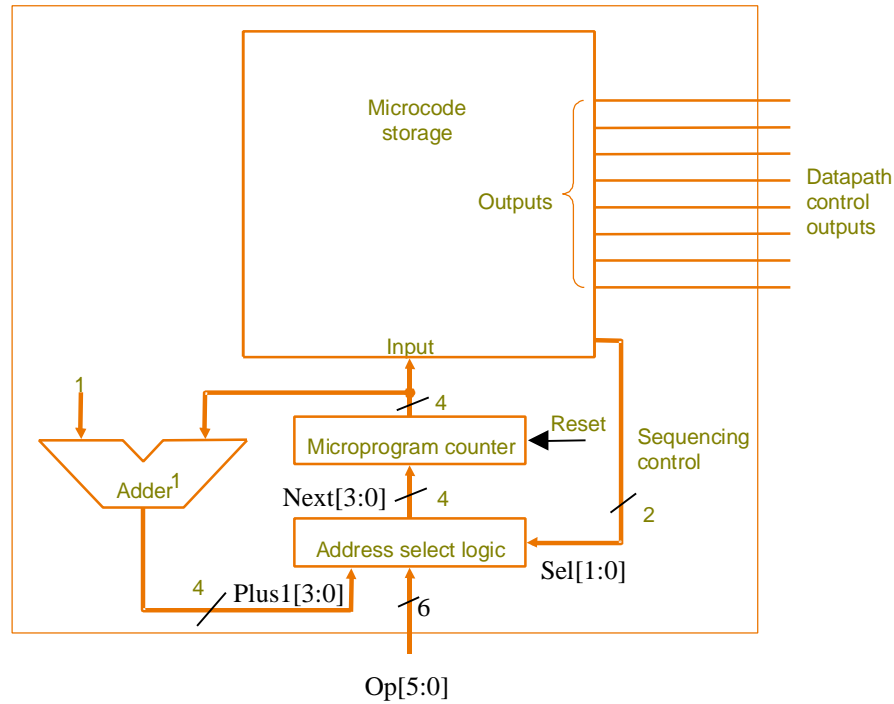3) A Microprogrammed Controller

Ben Bitdiddle is building a multi-cycle MIPS processor. He's decided to build his cbox control unit with microprogramming, as described in Section 5.5. Just as in Lab 7, the cbox receives Reset and Op[5:0] and is responsible for producing all of the control signals to the datapath. The overall architecture is shown below:




The microprogram counter is just a 4-bit register with reset. The microcode storage is a 16 word x 18 bit ROM producing 16 bits of control signals for the datapath and 2 bits of sequencing control used by the Address Select Logic. The Address Select Logic, shown below, is responsible for computing the next value of the microprogram counter. This next value may be Seq, Fetch, Dispatch1, or Dispatch2, as listed in Figure 5.46. Depending on the sequencing control lines Sel[1:0], the next address is chosen from the old microprogram counter plus 1, zero (to go back to fetch), or the outputs of two PLAs containing the dispatch logic.

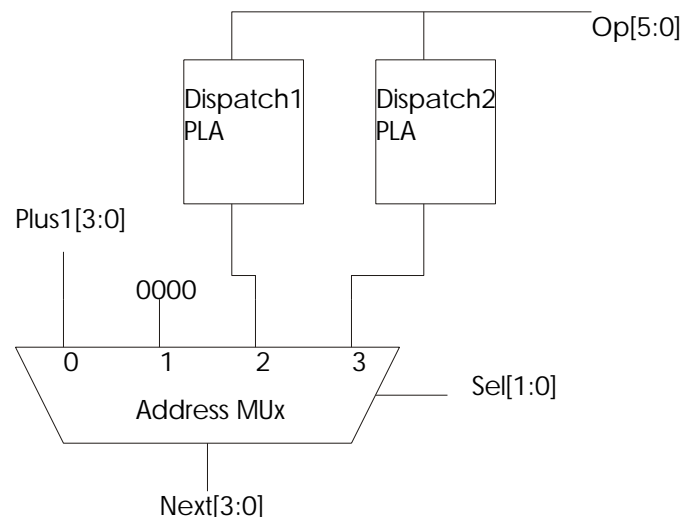

Help Ben by designing the ROM and two DISPATCH PLAs.

 
a) Microcode ROM

Refer to Figures 5.42 and 5.46 to complete the Microcode ROM below. Place an dot on the entries where the ROM should contain 1's. The dotted rows have been completed for you. Since the microcode program is fewer than 16 words long, the last six rows will be empty. A copy of the ROM is on the last page for your convenience.



 b) Dispatch1 PLA

The Dispatch1 PLA uses the 6 bits of the Op field to jump to the appropriate line in the microcode program. The dispatch could be constructed as a 64 word by 4 bit ROM. The six bits of Op could choose one word of the ROM containing the 4-bit destination in the microcode program for that Op. However, this would be wasteful of space because very few instructions are actually implemented, so most of the words in the ROM would be blank. A more efficient approach is to use a PLA. The AND plane of the PLA decodes the instruction. The OR plane produces the microcode address given the instruction. Since we handle five types of instructions (LW, SW, R-format, BEQ, and JUMP), the PLA only requires five minterms. Complete the PLA below. The first minterm for LW (Op = 100011) has been done for you; the Dispatch1 table jumps to MEM1 (address 0010) to process LW. A copy of the PLA is on the last page for your convenience.





c) Dispatch2 PLA

Finally, the Dispatch2 PLA also uses 6 bits of Op to jump to either LW2 or SW2. Again, it could be constructed as a ROM, but the PLA is more efficient. Sketch a circuit for the Dispatch2 PLA.

  4) Time

Please indicate how many hours you spent on this problem set. This will not affect your grade, but will be helpful for calibrating the workload for next semester's class.



Copies of ROM and PLA for your convenience. Tear off and hand in.