

## 1 Lab Introduction

In this lab you will build and characterize a common-source amplifier (loaded resistively and actively) and a current mirror using MOSFETs. The learning goals are listed below:

- Get some practice with MOSFET equations and amplifiers.
- Observe the difference between actively and passively loaded amplifiers

## 2 Resistively Loaded Common Source Amplifier

Build the common source amplifier picture in Figure 1 using the TN2106 N-channel MOSFET. Use the small signal input and XY mode on your scope (find it in the "horiz" menu) to vary  $V_G$  and plot the large-signal transfer characteristic ( $V_O$  vs.  $V_B$ ) for this amplifier. Use the transfer characteristic to pick a value of  $V_B$  that will maximize your gain and swing. Measure  $a_v$  and  $V_{SW}$  in XY mode and save your transfer characteristic. After that, switch back to time domain measurements to measure  $I_D$ ,  $r_{in}$ ,  $r_{out}$ ,  $a_v$ , and  $V_{SW}$  for this design with your  $V_B$  value. Use your results to extract  $g_m$  and  $V_T$  for this device, and compare your  $V_T$  value to the datasheet. Compare your XY  $a_v$  and your time-domain  $a_v$ .

**Required Data:** Transfer characteristic. Descriptions of how to measure  $I_D$ ,  $r_{in}$ ,  $r_{out}$ ,  $g_m$ ,  $a_v$  in XY,  $a_v$  in time domain,  $V_{SW}$  in XY,  $V_{SW}$  in time domain and  $V_T$ . Equation relating some large signal parameters to  $g_m$  and comparison between equation and measurement. Values for all of these parameters.

## 3 Current Mirror

Build the current mirror pictured in Figure 2 using two 2P2104 MOSFETs. Verify that the current in the source and load branches match as you vary the bias current and the load resistance.

**Required Data:** Plot of  $I_{LOAD}$  vs.  $I_{SRC}$ . Plot of  $I_{LOAD}$  vs.  $R_{LOAD}$

## 4 Current Mirror Loaded Common Source Amplifier

Build the common source amplifier picture in Figure 3 by combining your circuits from the first two sections. Biasing this amplifier is going to be a little bit tricky, but XY mode can help. Use the small signal input and the XY mode on your oscilloscope to trace out the transfer characteristic by varying  $V_G$ , then tune your mirror potentiometer until you maximize your gain and swing. Measure  $a_v$  and  $V_{SW}$  in XY mode and save your transfer characteristic. After that, switch back to time domain measurements to measure  $I_D$ ,  $r_{in}$ ,  $r_{out}$ ,  $a_v$ , and  $V_{SW}$  for this design. As before, extract  $g_m$  and  $V_T$  and compare them to your datasheet. Comment on differences in your results as compared to the resistively loaded common source amplifier. Compare your transfer function  $a_v$  to your time-domain  $a_v$ .

**Required Data:** Transfer characteristic. Descriptions of how to measure  $I_D$ ,  $r_{in}$ ,  $r_{out}$ ,  $a_v$  in XY,  $a_v$  in time domain,  $V_{SW}$  in XY,  $V_{SW}$  in time domain and  $V_T$ . Equation relating some large signal parameters to  $g_m$  and comparison between equation and measurement. Values for all of these parameters. Commentary on differences between active load and resistive load.

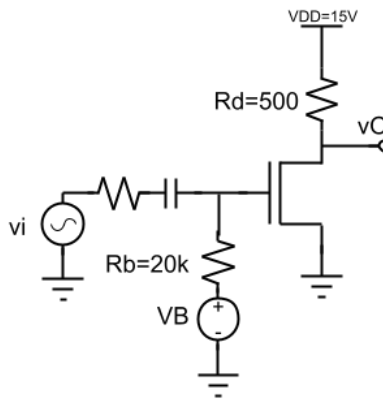


Figure 1: A sample design for a resistively loaded common source amplifier.

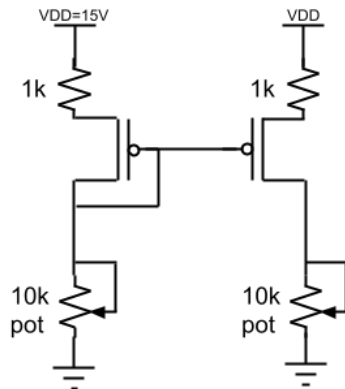


Figure 2: A sample design for a PMOS current mirror.

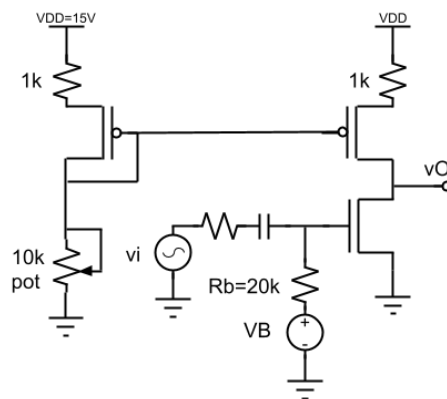


Figure 3: A sample design for an actively loaded common source amplifier.