

# Small Signal Patterns and CE with Degeneration Resistor

Matthew Spencer  
Harvey Mudd College  
E151 – Analog Circuit Design

1

In this video series we're going to take a brief sidetrack to work through some common small signal circuits that show up often. Knowing the solutions to these circuits should help you solve many BJT small signal problems quickly. We're then going to derive the amplifier parameters of another new type of amplifier called the common emitter with resistor degeneration so that we can use it in our multistage designs.

# Small Signal Patterns

Matthew Spencer


Harvey Mudd College

E151 – Analog Circuit Design

2

In this video we're going to look at some common small signal circuits and find their Thevenin resistances. This practice will be handy for finding amplifier parameters. I'm going to offer you the chance to work through these examples as I go through this video and doing so is great practice.

## The $R_E$ Boosting Pattern

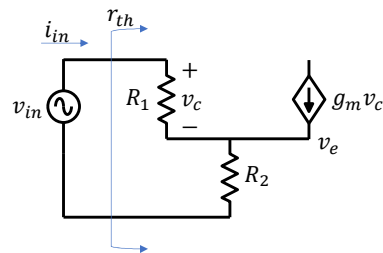

$$v_e = i_{in}(g_m R_1 + 1)R_E$$

$$v_c = i_{in}R_1$$

$$v_{in} = v_e + v_c$$

$$r_{th} = R_1 + (g_m R_1 + 1)R_2$$

3

The first small signal circuit we're going to look at is called the RE boosting small signal pattern. It is pictured above. You'll note that we leave the far side of the current source floating, and that's because current sources have infinite differential impedance, so they perfectly hide impedances or voltages on the other side of them. Also, note that we're using a generic  $v_c$  to describe the control voltage of the  $g_m$  generator, though it will be some variation on  $v_{be}$  in most circuits you analyze.

Pause the video and try to find  $r_{th}$ .


CLICK We solve this circuit by noticing that the emitter voltage is just  $R_2$  times the current running through  $R_2$ , and that the current running through  $R_2$  is the  $R_1$  current plus the  $g_m$  current. We're taking a shortcut here by noting that the  $g_m$  branch is indirectly controlled by  $i_{in}$  because  $v_c$  is equal to  $g_m R_1 i_{in}$ .

We then note that  $v_c$  is equal to  $i_{in} R_1$  and that our total input voltage is  $v_e + v_c$ . Subbing into that equation and dividing off  $i_{in}$  reveals that  $r_{th}$  for this structure is  $R_1 + (g_m R_1 + 1)R_2$ . We saw exactly this result for the input resistance of the emitter follower, where  $R_1$  was  $r_{pi}$  and  $R_2$  was a parallel combination of a bunch of stuff including  $R_E$ . The fact  $R_1$  was equal to  $r_{pi}$  caused the second term to be  $\beta + 1$ .

This structure has the effect of boosting the apparent impedance of  $R_2$ , which sits in series with  $R_1$ . That  $R_2$  boosting effect is because the  $g_m$  generator supplies much of the current to  $R_2$  that is needed to set its voltage to the right level. That means the  $v_{in}$  source doesn't need to send as much current as if the  $g_m$  generator weren't there. That reduction in current sent from the  $v_{in}$  source turns into a boosted resistance as seen from the port. This resistance boosting comes from a type of feedback: raising  $v_{in}$  raises  $v_c$ , which raises  $i_{g_m}$ , which raises  $v_e$ , which reduces  $v_c$ . So the  $g_m$  generator is kind of fighting to keep  $v_c$  small.

That's all interesting, but the main takeaway is that if you see a pattern that looks like a generator driving into a node shared with a resistor with a control voltage, then you can use this Thevenin resistance.

## The Left-Right Pattern

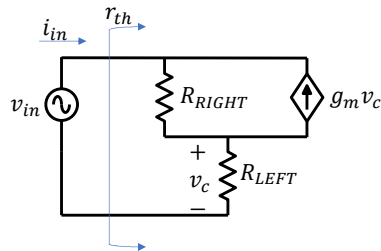

$$v_c = i_{in}R_{LEFT}$$

$$\frac{v_{in} - v_c}{R_{RIGHT}} = i_{in} + g_m v_c$$

$$v_{in} = i_{in}R_{RIGHT} + g_m v_c + v_c$$

$$v_{in} = i_{in}(R_{RIGHT} + R_{LEFT} + g_m R_{RIGHT}R_{LEFT})$$

$$r_{th} = R_{RIGHT} + R_{LEFT} + g_m R_{RIGHT}R_{LEFT}$$

4

The second small signal circuit we're going to look at is called the left-right circuit, and that name is going to seem weird for a bit because it's named after a circuit we'll see much later in the course.


Pause the video and try to find  $r_{th}$ .

CLICK We solve it by first noting that all the current that flows into the top two branches must also flow out of them, so  $i_{in}$  has to be flowing in  $R_{LEFT}$ . That means  $v_c$  is equal to  $i_{in}R_{LEFT}$ . Then we write KVL at the top node of the circuit, observing that the current in  $R_{RIGHT}$  has to be equal to the sum of  $i_{in}$  and  $g_m v_c$ . Rearranging then subbing in  $v_c$  reveals that  $r_{th}$  for this structure is  $R_{RIGHT} + R_{LEFT} + g_m R_{RIGHT}R_{LEFT}$ . We haven't seen this one in any circuits yet, but it's coming right up. You can imagine that  $R_{RIGHT}$  might be a  $r_o$  value from a BJT, because that falls in parallel with  $g_m$  generators in our BJT model. With that hint, be sure to look for this pattern in the output impedance of cascode amplifiers.

The third term, which is the product of  $R_{RIGHT}$  and  $R_{LEFT}$  can be quite large. As is the case with the RE booster, that boosted impedance comes from feedback. Increasing  $v_{in}$  should increase  $i_{in}$ , but the total current seen by  $R_{RIGHT}$  is reduced by the current supplied by the  $g_m$  generator, which means  $i_{in}$  is smaller for a given change in  $v_{in}$  than it would be without

the gm generator.

## The $1/g_m$ Pattern

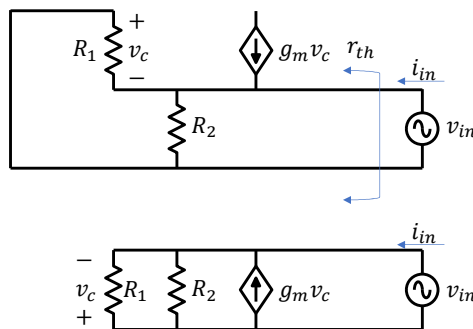

$$i_{in} = -g_m(-v_{in}) + \frac{v_{in}}{R_1} + \frac{v_{in}}{R_2}$$

$$\frac{v_{in}}{i_{in}} = \left( g_m + \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$r_{th} = R_1 || R_2 || \frac{1}{g_m} \approx \frac{1}{g_m}$$

5

The final small signal pattern we're going to look at is called the  $1/g_m$  pattern. I've drawn it in a "BJT way" on top and a "cleaned up way" on the bottom. These circuits are the same if you assume the  $g_m$  generator attaches to ground on the other side, and we're free to pick that because it makes no difference to how much current the generator produces.

Pause the video and try to find  $r_{th}$ .

CLICK In this circuit we're apply a voltage source directly to the control resistor  $R_1$ , so the  $g_m$  generator is producing a current that's proportional to  $v_{in}$ . We note this when we write a KCL equation to express  $i_{in}$  as the current through each branch of this circuit. The  $g_m$  generator is producing a current in the opposite direction of  $i_{in}$ , so we're subtracting it from the KCL equation, but  $v_{in}$  is also negative, which will cancel out that behavior. The other currents are just  $v_{in}$  over resistances.

You can rearrange this equation to find that  $v_{in}/i_{in}$ , which is  $r_{th}$ , is one over the sum of some conductances. That is the same form as a parallel combination, so we can rewrite  $r_{th}$  as  $R_1$  in parallel with  $R_2$  in parallel with  $1/g_m$ .  $1/g_m$  is usually quite small, so this equation is often approximated as  $1/g_m$ .


We saw this in the emitter follower circuit almost exactly, though there was a minor

difference in the emitter follower result that we'll explain in the next video. In general, you should expect this any time you change a gm generator's control voltage by wiggling the node the gm generator feeds. Making that more concrete for our class, you should expect to see an impedance that looks like  $1/g_m$  any time you wiggle an emitter.



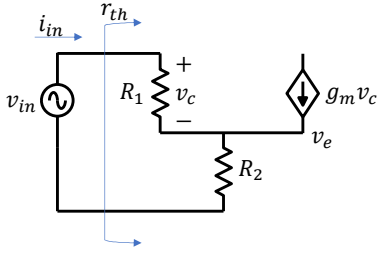
# Summary


- We saw three small signal patterns that appear in many BJT circuits:



$$r_{th} = R_1 + (g_m R_1 + 1)R_2$$

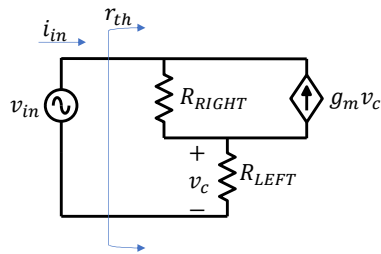
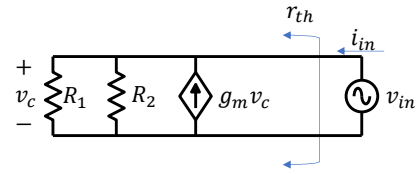
$$r_{th} = R_{RIGHT} + R_{LEFT} + g_m R_{RIGHT} R_{LEFT}$$




$$r_{th} = R_1 || R_2 || \frac{1}{g_m} \approx \frac{1}{g_m}$$

# Small Signal Pattern Transforms

Matthew Spencer  
Harvey Mudd College  
E151 – Analog Circuit Design

In this video we're going to add a handful of transforms to our toolbox that will enable us to recognize our small signal patterns in even more circuits.
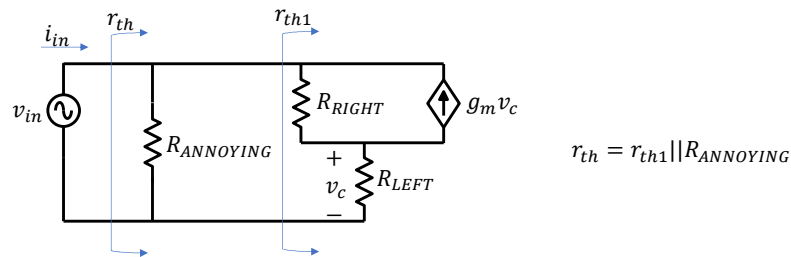
## The “There’s some Stuff in Parallel” Transform




8

OK, the first transform we’re going to talk about is useful when an annoying element is in parallel with an otherwise appealing small signal model. I’ve drawn a circuit above that looks like an annoying resistor in parallel with a great left-right pattern. If the annoying resistor weren’t there, we could just use our earlier left-right result, but we derived that result assuming all of  $i_{in}$  passed through  $R_{LEFT}$ , and that’s not true because the annoying resistor will steal some of  $i_{in}$ .

CLICK So we’re going to analyze this by changing the circuit we’re looking at. First we’re going to find  $r_{th1}$  looking only into the left-right branch, then we’ll just note that the annoying resistor is in parallel with  $r_{th1}$ . The takeaway is that you can peel off parallel elements to look at just a branch of interest just as long as you add them back at the end.

# The Effective gm Transform

- Including gm reversal

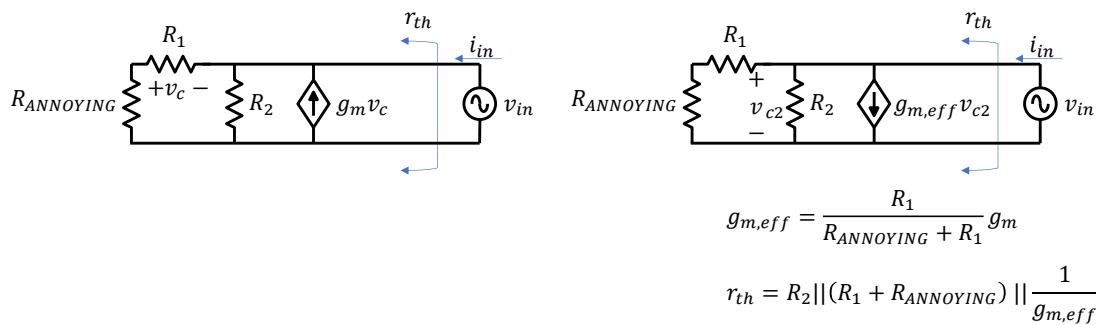

The second transform we're going to see has to do with gm generators with inconvenient control variables. The circuit on the left looks almost like our 1/gm pattern, but the annoying resistor means our control voltage isn't between  $v_{in}$  and ground. We can fix that by redefining our control voltage, which we see on the right. I've made two changes in that circuit: first, the control voltage now runs from  $v_{in}$  to ground, but I've made sure we wind up with the same current in the gm generator by defining an effective gm that is a resistor divided version of gm. Second, I've reversed the direction of the current source by reversing the polarity of the control voltage. By redefining our control voltage we've made our math a little bit easier and given ourselves leeway to eliminate the node between R1 and the annoying resistor by combining those two in series.

In addition to making our life easier, redefining the control voltage like this gives us a bit of physical insight. The divider is reducing the voltage that's applied across the control resistor, so thinking of it as reducing the effect of gm is an apt summary of its effect.

This is a super common transform. We've already seen it at work in our emitter follower output resistance, where R1 was  $r_{pi}$  and RANNNOYING was the source resistance. This effect is why we add  $R_S/\beta$  to  $1/g_m$  in the emitter follower rout.

## Summary

- Take inconvenient parallel elements off of your analysis and add them back in parallel at the end.
- Redefine the value of  $g_m$  in order to use more convenient control variables.

# Common Emitter with Degeneration Resistor


Matthew Spencer  
Harvey Mudd College  
E151 – Analog Circuit Design

11

In this video we're going to find the small signal parameters of an amplifier called the common emitter with degeneration. Like the emitter follower, this is going to be a lot of ground even though the slides will go quick. Also like the emitter follower, you need to remember both the analysis and the results on these slides. Take it slow and work the math when you are asked. Fortunately, we'll see some of our small signal patterns in the common emitter with degeneration, which will hopefully lighten our mental load.
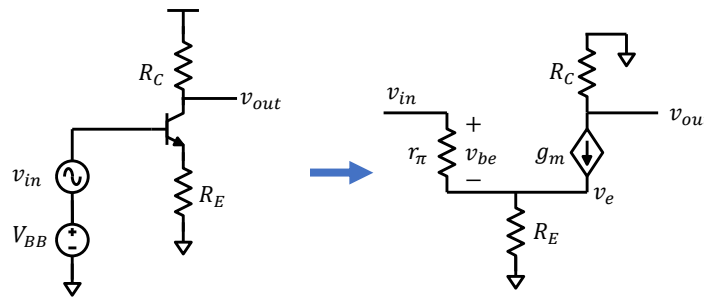
## CE w/ Degen is CE w/ Non-Grounded Emitter

- Will find they have high  $r_{in}$ , high-ish  $r_{out}$ ,  $a_v \approx -R_C/R_E$ .
- Good for precise voltage gains, linearity. ( $a_v$  doesn't depend on  $g_m$ !)
- Assuming  $r_o = \infty$  to simplify math.



12

The common emitter with degeneration is a common emitter with the bypass cap on the emitter node removed. That means the emitter is no longer grounded. We'll find that common emitters with degeneration have high  $r_{in}$ , fairly high  $r_{out}$  and an  $a_v$  that is the ratio of the collector resistor to the emitter resistor. That's exciting because it's easy to find resistors with fairly precise relationships in their ratios, and also because our gain doesn't depend on  $g_m$ ! We expect that to dramatically enhance the linearity of this amplifier. However,  $R_C/R_E$  is often smaller than  $g_m R_C$ , which is why  $R_E$  is often referred to as a degeneration resistor. The gain is degenerated relative to  $g_m R_C$  because of  $R_E$ .


We're going to assume  $r_o$  is infinite throughout our analyses to simplify our math. Including  $r_o$  doesn't change our results much, but it makes the math much harder. You'll be examining the effect of  $r_o$  on common emitters with degeneration on your homework. That's going to be a slog, but being comfortable wrestling with a tough small signal model is a skill that I want you to practice.

The first step in finding amplifier parameters is to draw a small signal model for the common emitter with degeneration. Pause the video and try drawing one now.

CLICK This is my version!

## CE w/ Degen $r_{in}$

- Set  $R_S = 0$ ,  $R_L$  proper value
- R from  $v_{out}$  to ground is  $R_E || r_o || R_L$
- Use  $i_{in}$  as test source: easier than  $v_{in}$

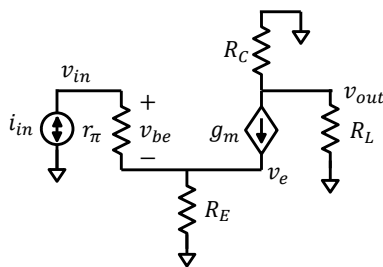

$$v_{be} = i_{in}r_{\pi}$$

$$v_e = (i_{in} + i_{gm})R_E$$

$$= i_{in}(1 + g_m r_{\pi})R_E$$

$$v_{in} = v_e + v_{be}$$

$$= i_{in}(1 + g_m r_{\pi})R_E + i_{in}r_{\pi}$$

$$r_{in} = r_{\pi} + (\beta + 1)R_E \approx \beta R_E$$

13

We set up our analysis to find  $r_{in}$  by remembering the test conditions we use for  $r_{in}$ . We set  $R_S$  to zero so it doesn't add to the  $r_{in}$  that we calculate, and we set  $R_L$  to an appropriate value so that any feedback effects in our amplifier get captured by  $r_{in}$ . I'm applying a test current source to find the input resistance.


Given this setup, I'd like you to pause the video and try to find  $r_{in}$ . Feel free to use our small signal patterns if any are relevant.

CLICK I've included my solution on the right. You'll recognize this math from two places: the emitter follower input and the RE boost small signal pattern. We find the emitter voltage by noting the input current and the  $g_m$  current flow in  $R_E$ , then we relate the  $g_m$  current to the input current, and finally we add the  $v_{be}$  voltage to the  $v_e$  voltage to find  $v_{in}$ . Because this math is identical to the emitter follower and the RE boost pattern, we wind up with the same  $r_{in}$  expression. That's  $r_{\pi} + (\beta + 1)R_E$ , or approximately  $\beta R_E$ .


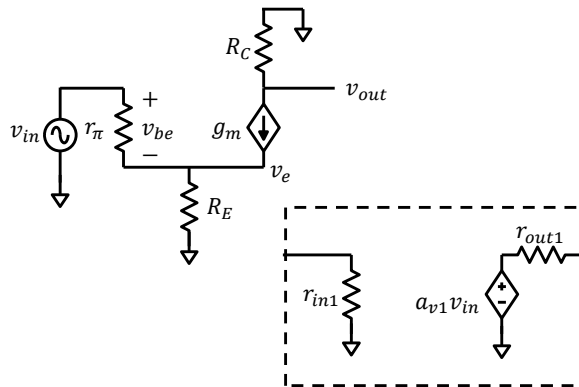
## CE w/ Degen $a_v$

- Set  $R_S = 0, R_L = \infty$
- Must use test voltage



$$\begin{aligned}
 v_{out} &= -i_{gm}R_C \\
 &= -i_{in}\beta R_C \\
 &= -\frac{v_{in}}{r_{in}}\beta R_C \\
 a_v &= \frac{-\beta R_C}{r_{\pi} + (\beta + 1)R_E} \approx -\frac{R_C}{R_E}
 \end{aligned}$$

This doesn't depend on  $g_m$ !

Now we're going to find the voltage gain of the emitter follower. We recall that we calculate voltage gain as small signal  $v_{out}$  over small signal  $v_{in}$  with zero source resistance and infinite load resistance. We set the resistances that way so that we're not measuring either the source or load divider by accident. I've set that up in the small signal model below, note that the resistor from  $v_{out}$  to ground has gone back to  $r_o || R_E$  because we removed the load. Pause the video and try to find the gain of this amplifier.

CLICK This is a somewhat new derivation, so I'm going to show it step-by-step. I started by finding that  $v_{out}$  is given by the  $g_m$  generator current passing through  $R_C$ .  $v_{out}$  is negative because the  $g_m$  generator current runs up through  $R_C$  from ground.

CLICK We note that  $i_{gm}$  is  $\beta$  times  $i_{in}$ , but we're stuck because we don't know  $i_{in}$ .


CLICK So we play the same trick we played with the emitter follower, where we replace this detailed transistor level schematic with the amplifier model for just a second, because the  $r_{in}$  we found on the previous page relates  $v_{in}$  and the  $i_{in}$  that flows into the base. That's exactly what we want, so we know the current flowing into here is  $v_{in}/r_{in}$ .

CLICK Substituting that expression in gives us the gain, which is  $\beta R_C / (r_{\pi} + (\beta + 1)R_E)$ . Because  $\beta$  is big and  $R_C$  and  $R_E$  are often of a similar order to  $r_{\pi}$ , we can

make a super quick lab version of this equation:  $a_v$  is equal to  $-RC/RE$ . I find this super quick lab version to be easy to remember, which is great, and it also doesn't depend on  $g_m$ , which is double great because it eliminates our  $g_m$  nonlinearity. That nonlinearity can sneak back into our expression through  $r_{pi}$ , which you'll recall is  $\beta/g_m$ , but adding degeneration seems to have greatly improved our linearity.
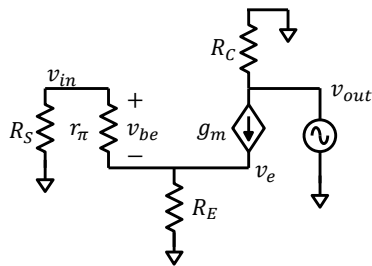
## CE w/ Degen $r_{out}$

- Set  $R_L = \infty$ ,  $R_S$  to proper value
- Test  $v_{out}$  happens to be easier than  $i_{out}$



$$r_{out} = R_C$$

$g_m$  source is shut off because  $v_{be}$  has ground on both sides of it.

Adding  $r_o$  makes a great problem for small signal patterns.

Finally, we're going to find  $r_{out}$  of the emitter follower. Our  $r_{out}$  test conditions are an infinite load resistance, so it doesn't steal any current from our output, and an  $R_S$  that is normal for the amplifier. We're choosing to use a test voltage source for this analysis because it makes our life easier. Pause the video and try to find  $r_{out}$ .

CLICK  $r_{out}$  is just  $R_C$ . That's true because the  $g_m$  generator is shut off when we ground  $v_{in}$  through the source resistance.

There's a little bit of chicken and egg reasoning going on in my assertion that the  $g_m$  generator is off. I'm asserting that  $v_{be}$  is zero since the  $g_m$  generator is off, and the  $g_m$  generator is off because  $v_{be}$  is zero. I confront that reasoning by asserting that if everything on the left side of the circuit is attached to ground, there's no reason for non-ground values in the middle.

If you add  $r_o$  to this problem, then  $v_{be}$  is no longer zero and you have to do more analysis to find an expression for  $r_{out}$ . However, that analysis is a classic example where our small signal models pay off. I won't go over that solution in these videos, but encourage you to try finding  $r_{out}$  with  $r_o$  included and small signal patterns in mind.

## Summary

- CEs w/ Degeneration are amplifiers with high  $r_{in}$  and linear gain.
- CE w/ Degeneration amplifier parameters

$$r_{in} = r_{\pi} + (\beta + 1)R_E \approx \beta R_E$$

$$r_{out} = R_C$$

$$a_v = \frac{-\beta R_C}{r_{\pi} + (\beta + 1)R_E} \approx -\frac{R_C}{R_E}$$