

E157 Lecture 3 Day Plan

Any questions before quiz

Quiz + Team Quiz + Talk through solution

Reminder to submit quiz grades!

Reflection from a

- short
 - Zero voltage, double current
 - Mirror, Mirror → Current doubled b/c mirror universe sucks in current w/ -1V wave.
- capacitor
 - Iload is an RC response, sets reflection boundary condition
 - Intro TDR
 - Parasitic caps can come from fringing fields, corners in traces
- 100Ω load and 25Ω source on 50Ω line, emphasize driving point impedance
 - $V_{in} = 1V$
 - $V_{init} = 50/(25+50) = 2/3 V$,
 -
 - $\Gamma_{load} = (100-50)/(100+50) = +1/3$,
 - $V_{reflect,load} = \Gamma_{load} * V_{init} = 2/9 V$,
 - $V_{load} = V_{init} + V_{reflect,load} = 8/9 V$
 -
 - $\Gamma_{src} = (25-50)/(25+50) = -1/3$,
 - $V_{reflect,source} = \Gamma_{src} * V_{reflect,load} = -2/27 V$
 - $V_{source} = V_{load} + V_{reflect,source} = 22/27 V$
 -
 - $Z_{dp,src,init} = 50$ (used to find V_{init})
 - $Z_{dp,load,reflect1}$
 - $Z_l / (Z_{dp} + Z_l) = V_{load} / V_{in}$
 - $100 / (Z_{dp} + 100) = 8/9$
 - $Z_{dp} = 12.5$
 - $Z_{dp,src,reflect1}$
 - $Z_{dp} / (Z_{dp} + Z_s) = V_{source}$
 - $Z_{dp} / (Z_{dp} + 25) = 22/27$
 - $Z_{dp} = 110$
- spot discontinuity, looks like shunt resistor

Edge rate and reflections

- you only bounce off of things that are big compared to λ ,
- 10-90 rise time is t_r . Size of 10-90 edge calculated w/ velocity
- Appropriate analysis frequency for given t_r is $f_a \sim 0.5/t_r$

Falstad simulator code below:

```
$ 1 0.000005 10.20027730826997 50 5 50 5e-11
R 0 80 0 128 0 2 10 0.5 0.5 0 0.5
r 32 80 112 80 0 25
171 144 80 352 80 0 0.005 50 16 0
r 416 80 416 144 0 100
w 352 80 416 80 0
w 352 96 352 144 0
w 352 144 416 144 0
g 144 96 144 128 0 0
w 144 80 112 80 0
w 0 80 32 80 0
o 9 64 0 4102 1.25 0.025 0 2 9 3
o 8 64 0 4102 1.25 0.025 0 2 8 3
o 4 64 0 4102 1.25 0.0125 0 2 4 3
```

