

E157 Lecture 7 Day Plan

Any questions before quiz

Quiz + Team Quiz + Talk through solution

Design a L-match checking against

<https://www.analog.com/en/design-center/interactive-design-tools/rf-impedance-matching-calculator.html>

- $5\text{Grad/s}=795\text{MHz}$, $Rl=10\text{ ohm}$
- $Q_{\text{desired}} = \sqrt{50/10-1}=2$
- $L_{\text{series}} = 4\text{nH}$, $C_{\text{shunt}} = 8\text{pF}$ OR $L_{\text{shunt}}=5\text{nH}$, $C_{\text{series}}=10\text{pF}$

Lab practice discussion – designing while using a live Smith Chart,

- start w/ 0 Ohm in all positions you intend to populate so you can see load
- Pick next component after each soldering job, accounting for existing parasitics.
- Watch where you land on the Smith Chart after each solder job.
- Really helpful for matching networks, harder for filters where everything needs to be right.

Parasitics discussion –

- Pads have parasitic C to ground
- Amplifiers have shunt C b/c of transistors,
- Vias have series L b/c they close current loops