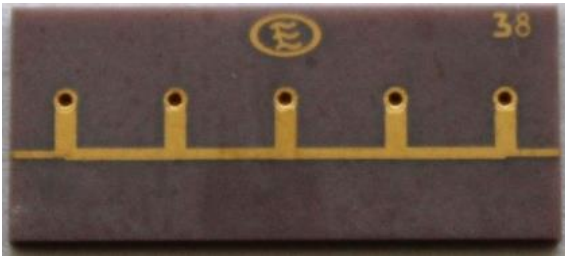


E157 Lecture 8 Day Plan

No quiz! Any questions?


Matching networks with transmission lines – impedance cancellation, single stub

- $\lambda/4$ turns opens to shorts
- Draw a stub
- Imply existence of filters



Tapped Capacitors, Tapped Inductors and Transformers

- Tapped L/C transformer

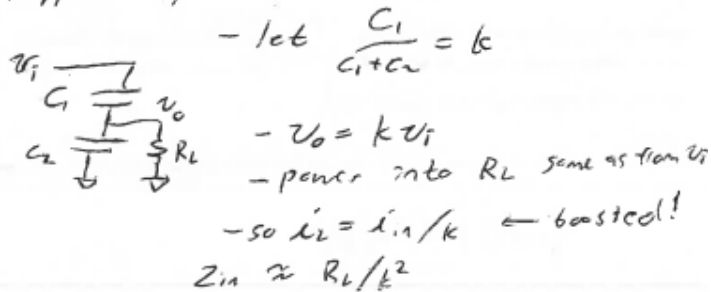

-
- For transformer – same but voltage boosted! $v_o = k \cdot v_i$, $k \gg 1$

Run the VNA sim, work through it as a class, get everyone up and running with s1p import.

- Everyone do the VNA sim from lab 3
- Export in proper format.
 - Simulate
 - Right click in sim pane
 - File -> Export Data as text -> Format Dropdown is Cartesian Re,Im
 - Name must have .s1p suffix
 - Edit file in text editor, add
 - Import as Network using skrf, or use Matlab

Make a spreadsheet/script to design a T-match from 200 Ohms, $2 \cdot \pi \cdot 100$ MHz, $Q=3$

- Check vs. <https://home.sandiego.edu/~ekim/e194rfs01/jwmatcher/matcher2.html>
- $Q_{overall} \rightarrow R_i$, $2Q_{overall} = \sqrt{R_i/Z_0-1} + \sqrt{R_p/Z_0-1}$
- R_i and $\omega_0 \rightarrow C_1$ and C_2 through component Q_s , $Q_{des1} = 1/(\omega_0 \cdot R_i \cdot C_1s)$
- Use ω_0 to find L , and come out from series-parallel or parallel-series

Check-in, office hours for lab 3