

## E157 Lecture 6 Day Plan

Any questions before quiz

Quiz + Team Quiz + Talk through solution

Sociotechnical minute: where do resistors/capacitors/inductors come from?

- <https://eprints.whiterose.ac.uk/130419/1/LCA%20and%20EnvProfile%20Evaluations%20of%20Capacitors%20Manuscript%20-%20CLEAN.pdf>
- Caps: Nickel paste for interlayer,
- Caps: Tantalum (Australia, Brazil, China, DRC, Rwanda, Nigeria, Colombia)
- Resistors: Carbon film
- Inductors: Just wire, ferric cores → iron
- All: Cu electrodes

Q roundup

- Bandpass fractional bandwidth =  $1/Q$
- RLC ring down in step/impulse response ~ number of peaks to 5% =  $Q$
- Series RLC  $Q = \sqrt{L/C} / R$
- Parallel RLC  $Q = R / \sqrt{L/C}$
- Series component  $Q = X/R$  ← This is frequency dependent! Not a full tank!
- Parallel component  $Q = B/G$
- Can find a compound  $Q$  by mixing components  
→ Parallel LC where both cap and inductor have ESR  
→ draw schematic and do series-parallel drawing

Calculating Compound  $Q$  from components

- Same circuit as above
- $X_S = X_P * Q^2 / (Q^2 + 1)$ ,  $R_S = R_P / (Q^2 + 1)$ ,
- $Q$  here is from each element, but we know  $\omega_0$  will be  $1/\sqrt{LC}$ .
  - $Q_1 = 1/\omega_0 R_C = \sqrt{L/C} / R$  ← still  $IM/RE$  because series elements
  - $Q_2 = \omega_0 L / R = \sqrt{L/C} / R$
- Transform, then overall is  $(R_S R_C P || R_S R_L P) / \sqrt{L/C}$
- NOTE that  $X_s$  is always  $< X_p$  and  $R_s$  is always  $< R_p$

Practice ringing out in shunt – 50 ohm || 10pF || 100nH @ 1Grad/s – see below

- You are designing a matching network for a 10pF capacitor in shunt with a 50 Ohm resistor driven by a 1Grad/s signal sent through a 50 Ohm transmission line.
- $B_n = \omega C / (1/Z_0) = Z_0 * \omega * C = 0.5$
- Need negative susceptance, so shunt L
- $B_n = 1/\omega L / (1/50) = 50/\omega L \rightarrow 100\text{nH}$
- $Q = R / \sqrt{L/C} = 50/\sqrt{100\text{e-}9/10\text{e-}12} = 50/\sqrt{1\text{e}4} = 5$
- $\sqrt{1/LC} = 1\text{Grad/s} \rightarrow L * 1\text{e-}11 = 1\text{e-}18 \rightarrow L = 100\text{nH}$

Some practical stuff

- Emphasize that networks of bypass caps exist to manage ESR and ESL.
- Also mention winding resistance for inductors