

Lecture 10: S Parameters

Matthew Spencer

Harvey Mudd College

E157 – Radio Frequency Circuit Design

Two-Port Networks


Matthew Spencer

Harvey Mudd College

E157 – Radio Frequency Circuit Design

In this video we're going to start developing a theory for understanding linear circuits that have two ports, which is a departure from the networks we've looked at up until this point.

Match Networks and Filters have 2 Ports

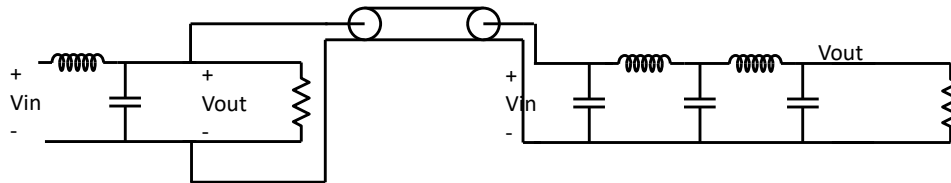


3

As a reminder, a port is a place where we measure circuits, and in this class we've been pretending we only measure 1 port circuits. Everything we've looked at thus far has been some combination of inductors, capacitors and transmission lines that terminates in a load. But we're straining under that idea, because we spent a lot of time talking about how much power went through a filter into a load. We don't really have numerical tools that describe how much of a signal goes through our circuits, and that's because treating everything as a 1 port network is a deceptive because many circuit really have two ports. CLKICK We can see that really clearly if we take off the loads from the matching network and filter pictured here: which reveals that they have both an input and an output, CLICK and if we were feeling really crazy we could hook one output to another input to make a filter that is matched to a different impedance.


That poses a problem for us, because even though we've analyzed matching networks and filters separately, we have no systematic way to combine the two analyses. We could probably figure something out -- the filter will look like some impedance in its pass band, and we could say that's the load on our matching network -- but in this set of videos we're going to describe a more mathematically rigorous way to talk about linear two port networks.

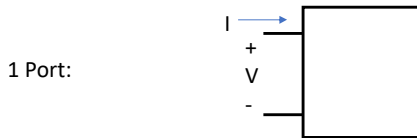Linearity: Each Port IV Set by Weighted Sum



Defined (equivalently) by:
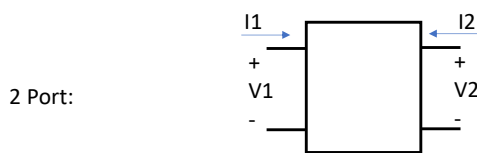
$$V = Z_{th}I \quad \text{OR} \quad \Gamma = \frac{Z_{th} - Z_0}{Z_{th} + Z_0}$$



Each port can affect each other port, so the network is defined by 4 numbers:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{OR} \quad \text{Four } \Gamma\text{-like numbers w/ arbitrary } Z_0 \text{ values}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Typically write as Z matrix:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \text{or} \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

We'll start making our formalism for two port networks by looking closely at one port networks. I've drawn an example one port here, and it has a pair of port variables V and I, and I is defined as positive going into the port. As long as the circuit inside the one port is linear and passive, we can describe the relation between V and I using a Thevenin impedance. Or, equivalently, we could specify a reflection coefficient for the port, which is a one-to-one function of the impedance.

We had to add a bit of extra information to our definition when we defined the reflection coefficient, which was the idea of Z_0 . While we know that we mean Z_0 to refer to the characteristic impedance of the driving transmission line, the one port model doesn't know anything about what it's connected to, so Z_0 seems like some arbitrary constant the designer picks from the one-port's point of view.

CLICK A linear, passive two port network extends this idea. Instead of having one port, it has two, and those two each have names. Creatively, we call them port 1 and port 2. Each port has a port voltage and a port current associated with it, and the port current always points into the port.

Instead of describing the relation between port voltages and currents with one number, like the Thevenin impedance above, we need four numbers. That's because each port can

affect both itself and every other port depending on what circuit is inside the two-port box. I'm being a little fuzzy about what it means for a port to affect another port, and we'll get into it in another video. However, we know that everything in the two-port box is linear, so ports affecting one another has to result in a weighted sum of port variables, which is what the equations I'm showing here indicate.

The weights in this type of equation are called Z parameters, and they are written as a letter with two subscripts, the first is the port being affected, the second is the port doing the affecting. So Z_{12} describes the effect of port 2 on port 1. There are other types of parameters that can describe a two-port network, including a two port version of reflection coefficient called S parameters, so stay tuned. Just like with one ports, we'll probably have to pick a Z_0 to use S parameters.

CLICK Finally, we usually write these equations as a matrix to make them more compact. I'm going to try to indicate vectors with bold font to help you identify matrix equation, but sometimes I might just ask you to pick things up from context. For instance, the Z in this matrix equation represents a matrix, even though I don't use any special notation for it.

Summary

- We care about two port theory because we have been making two port networks. eg: filters, matching networks.
- Two port theory lets us describe “through” behavior in addition to “loading / reflection” behavior.
- Each port has an associated I (into the port) and V
- All the port I and V quantities are related by matrix equations.

Z Parameters


Matthew Spencer

Harvey Mudd College

E157 – Radio Frequency Circuit Design


In this video we're going to look at a specific set of numbers you can use to describe two port networks called Z parameters. These are similar to Thevenin impedances, and they'll serve as an example of two-port analysis to make the idea more concrete.

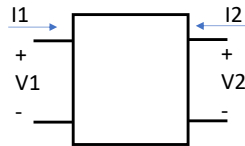Dividers are Common Examples of Two-Ports



$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

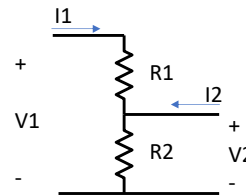

The left side of this slide shows a generic two port while the right side shows a divider, which is a specific example of a two port network. I've drawn ports 1 and 2 on the divider so that we can make a comparison to the generic two port throughout this video. Note that we define all the currents in a two port as pointing into the network for consistency, and we see that in both the generic two port and the divider.

By way of review: I've promised that the voltages of a two port can be described by a weighted sum of the port currents, and I've shown that in a pair of equations here. We called the coefficients of these weighted sums Z parameters.

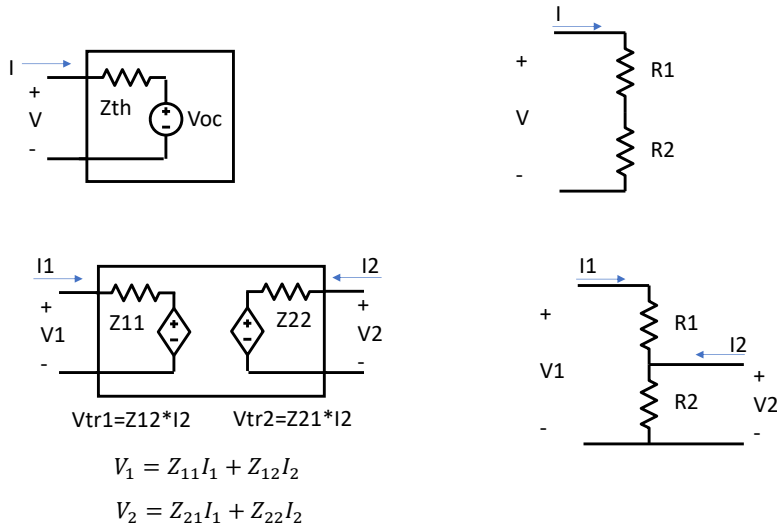There's a Thevenin-like Circuit for the Z Matrix




Any one-port linear network can be described by a Thevenin equivalent circuit. And I've drawn a generic Thevenin equivalent on this slide. Once we find the one-port representation of a linear network, then we can draw either the circuit or its Thevenin equivalent in any schematic we make because the two are electrically identical. So, for instance, the Thevenin impedance of the one-port version of our divider, shown on the right, is $R_1 + R_2$, and the open circuit voltage, V_{oc} , is zero. (We know V_{oc} is zero because the circuit on the right is passive, and you only get non-zero V_{oc} in active circuits.) That means we can put Z_{th} in place of $R_1 + R_2$ anywhere and get the exact same I-V behavior.

OK, maybe not so impressive – that's just the definition of series resistors after all – but this is an important analogy for two port networks.

CLICK Two port networks have their own Thevenin-like circuit that you can drop into a circuit in place of a two port. That equivalent circuit is electrically indistinguishable from the resistor divider on the right of the slide, and the heart of two-port analysis is substituting two port models with well defined interaction and loading rules in place of complex circuits. The two port equivalent circuit consists of two resistors, Z_{11} and Z_{22} , and two current-dependent voltage sources -- V_{tr1} and V_{tr2} , so named after the archaic term "transresistance" -- that carry port currents across to the other port. The Z_{12} and Z_{21} are the control coefficients for these current dependent voltage sources.

CLICK This circuit may seem a little opaque, but it just directly implements the Z-parameter equations we saw on the last slide. It says V_1 is a weighted sum of I_1 and I_2 , because the value of the V_{tr1} is equal to the $Z_{12} \cdot I_2$ term, and the voltage across Z_{11} will be $Z_{11} \cdot I_1$.

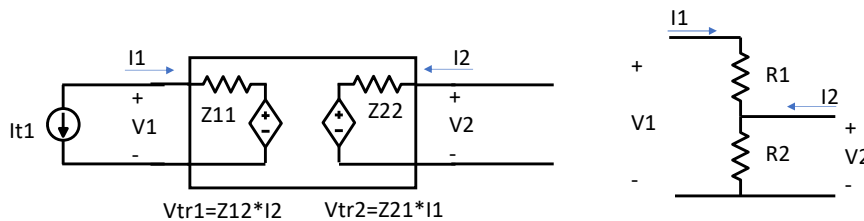Measure Z Params w/ Test Current + Open Ckt



$$\begin{aligned} I_1 &= I_{t1} \\ I_2 &= 0 \\ V_1 &= Z_{11}I_{t1} \\ V_2 &= Z_{21}I_{t1} \end{aligned}$$

$$\begin{aligned} I_1 &= I_{t1} \\ I_2 &= 0 \\ V_1 &= (R_1 + R_2)I_{t1} \\ V_2 &= R_2I_{t1} \end{aligned} \quad \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

9

Now that we have an equivalent circuit, we can think about how to measure or calculate the Z parameters for it.

CLICK The most straightforward way is to drive a current into one port while leaving the other port open circuited. That means we've set the value of I_1 to our test current I_{t1} , and we've set the value of I_2 to zero, because no current flows in an open circuit. We then measure the voltage on port 1, which is all created by the voltage drop on Z_{11} because I_2 is zero, which makes V_{tr1} 0V accordingly. Using that voltage, we can find Z_{11} . Similarly, if we measure the voltage across port 2, we know that it is all created by V_{tr2} because I_2 is zero, and there can't be any voltage drop across Z_{22} .


CLICK If we apply this to our resistor divider, we can find its Z-parameters. If I_1 is I_{t1} , then we can see V_1 will be R_1+R_2 times I_{t1} and V_2 will be R_2 times I_{t1} . That tells us the value of Z_{11} is R_1+R_2 and the value of Z_{21} is R_2 .

CLICK we can repeat that test on the other port to find the values of Z_{22} and Z_{12} , and I've summarized them all in the Z-parameter matrix here. We can verify these Z-parameters are right by showing that this matrix gives rise to standard divider behavior: if I_2 is zero, which would make this circuit act like a normal voltage divider, then V_2 would be $I_1 \cdot R_2$, V_1 would be $I_1 \cdot (R_1+R_2)$, and the ratio of V_2/V_1 would be $R_2/(R_1+R_2)$.


Finally, notice that Z parameters have units of impedance, which is why they're given the symbol Z.

Y Parameters are a 2 Port Version of Norton
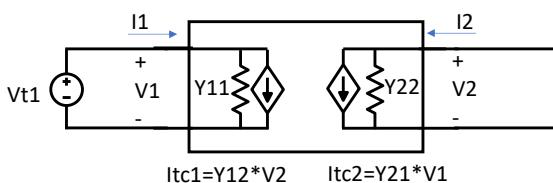
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


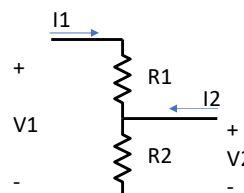
$$\begin{aligned} V_1 &= V_{t1} \\ V_2 &= 0 \\ I_1 &= Y_{11} V_{t1} \\ I_2 &= Y_{21} V_{t1} \end{aligned}$$



$$\begin{aligned} V_1 &= V_{t1} \\ V_2 &= 0 \\ I_1 &= V_{t1}/R_1 \\ I_2 &= V_{t1}/R_1 \end{aligned} \quad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 1/R_1 & 1/R_1 \\ 1/R_1 & 1/(R_1 || R_2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- To measure: Probe with voltage source, observe with short circuit.

There are lots of other types of parameters, for instance Y parameters are an important analog to Z parameters. In a Y parameter representation, we represent the port currents as a weighted sum of port voltages, so the Y values are each like conductances. That behavior is captured by a Norton-like equivalent circuit, and we probe its behavior by applying a voltage source to one port and shorting the other port to prevent it from having a voltage value. I encourage you to pause the video and try to find the Y parameters for this divider.

CLICK I've included the answers here.

Other Parameters

- H parameters – “hybrid” parameters, show up on BJT datasheets

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

- G parameters – “inverse hybrid” parameters

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$


- All equivalent representations, transforms exist between them.

Y parameters are popular enough that they deserved special attention, but there are still other sets of parameters that we'll just skim over. H parameters are useful for describing the output current of bipolar junction transistors, so much so that you still see evidence of them on many BJT datasheets. Often the gain parameter on the BJT datasheet is labeled h_{FE} , which stands for “forward emitter h parameter”. G parameters also exist, and they are like backwards versions of H parameters that can be used to invert H parameter networks.

One take away from these many transformations is that they are all ways of representing the same circuit. At heart, these are all linear summations of port variables that represent a linear, passive circuit.

Summary

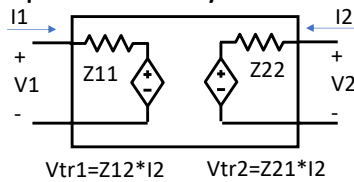- Z-parameters are represented by a Thevenin-like model



- You can measure Z parameters with a test current on one port and open circuit loads on all other ports.
- Many other types of parameters exist, notably Y parameters

S Parameters


Matthew Spencer

Harvey Mudd College

E157 – Radio Frequency Circuit Design

In this video we're going to learn about yet another set of linear parameters called S parameters, where the S is short for scattering. Though we've already got two perfectly good sets of linear network parameters – Y and Z parameters – S parameters are important because they're easy to measure at high frequency. Accordingly, many types of test equipment report S parameter values as their outputs.

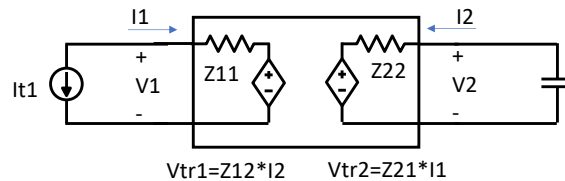We Can't Measure Z Parameters at High Freq.




- Parasitic capacitances (and antennas) ruin high frequency opens.
- This model neglects transmission line phenomena, fixturing.

We need S parameters because we can't measure Z parameters at high frequency. We established that we measure Z parameters by driving a current source into one port and then measuring voltages. Unfortunately, making a high frequency current source is really tough, and making a high frequency open circuit is almost impossible. CLICK That's because any open circuit we make will look like two pieces of metal sticking out into space, and all pieces of metal have some capacitance between them. Pieces of metal in space also look like antennas, which can cause us trouble too.

Further, this model doesn't account for the transmission lines that we need to hook our equipment up to this two-port circuit, so it doesn't help us understand reflections off of our ports.

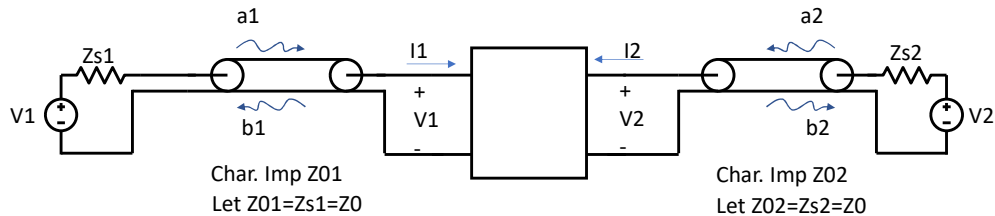Measuring High-f 2 Ports Requires T Lines



$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

- Could technically have different Z_0 on every port.
- S-parameters relate incident and reflected waves a and b.


S parameters fix these problems by bolting a pair of transmission lines to the ports of the two port. These transmission lines could technically each have different characteristic impedances, and they could each be driven by different source impedances, but we're going to assume that everything is matched to a value Z_0 for now.

We're going to assume that each of these transmission lines has a sinusoidal incident wave on it, and we'll say the wave incident on port 1 has amplitude a_1 , while the wave incident on port 2 has amplitude a_2 . We'll call the amplitudes of the reflections of these waves b_1 and b_2 . All of these a and b values could be complex in the general case.

The S parameter matrix relates the a and b waves in this model such that the b vector is equal to the S matrix times the a vector. These parameters are called Scattering parameters because they indicate how waves scatter when they hit a network.

This seems like a promising model: S parameters incorporate transmission lines, and we can make pretty good 50 ohm terminations, even at high frequency

a and b Waves Defined to Calculate Power

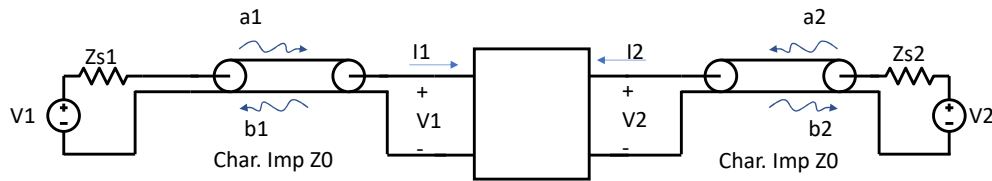

$$V_{+1}(x, t) = V_{+1} e^{j(kx - \omega t)}$$

$$P_+(x, t) = \text{Re}\{V_{+1} I_{+1}^*\} = \frac{|V_{+1}|^2}{Z_0} \text{Re}\{e^{2j(kx - \omega t)}\}$$

Analytic representation of power, "complex power"
(Presuming Z_0 is purely real here)

$$\langle P_+ \rangle = \frac{|V_{+1}|^2}{2Z_0}$$

Average over sinusoid squared is 1/2

$$a_1 = \frac{|V_+|}{\sqrt{Z_0}} \rightarrow \langle P_+ \rangle = \frac{|a_1|^2}{2}$$

Pick a definition of a that makes P easy to calculate

The a and b amplitudes are defined in a special way that makes the calculation of power flow in the system easier.

CLICK So we'll start to figure out a good value for a by calculating the power carried in our right travelling wave on port 1, V_+ . I've included our complex exponential representation of V_+ here.

CLICK We can find the power dissipated at point x of a transmission line by taking voltage times the complex conjugate of current. Because we're using an analytical representation of voltage, we need to multiply by the complex conjugate of current to make sure our power result turns into a real number. That means our real power will be set a coefficient -- the magnitude of the right-travelling wave squared divided by the characteristic impedance -- which I'm assuming is purely real for now -- multiplied by a sinusoid.


CLICK If we average the power over time and space to find the average power delivered to the right traveling wave, we get half of that coefficient, because we're averaging over a sinusoid squared.

CLICK We pick the size of the a wave to easily calculate this coefficient. We set it to the magnitude of the right travelling wave divided by the square root of characteristic

impedance. That means the power carried by the wave is given by the magnitude of a^2 divided by 2. We'll circle back to power flow soon, and this calculation will be handy. Note that a can be complex in the general case where Z_0 is complex, but its real under our current assumptions.

While we're here, I want to make a note about real and imaginary power. Real power is the this we're used to, electrical energy that gets dissipated as heat. Real power comes from voltage and current that are in phase, and multiplying voltage by the complex conjugate of current is one way to calculate the phase relation between voltage and current. We're going to mostly ignore the imaginary part of the power, but it has an interpretation too: it comes from voltage and current that are out of phase, which means that it corresponds to current and voltage getting stored in inductors and capacitors, then released again during each cycle.

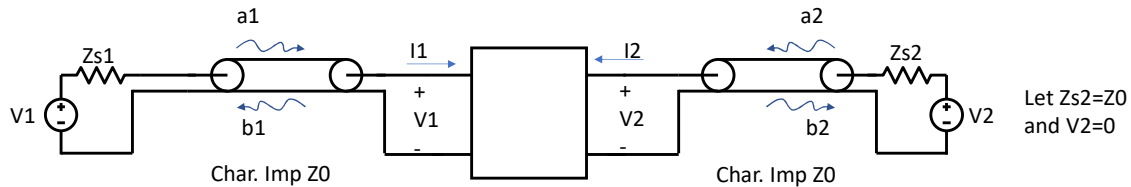Measure S-Params by Terminating Ports in Z0



Let $Z_{s2}=Z_0$
and $V_2=0$

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$b_1 = S_{11}a_1 + S_{12} \cdot 0$$

$$b_2 = S_{21}a_1 + S_{22} \cdot 0$$

$$S_{11} = b_1/a_1 = \Gamma_1 \Big|_{2 \text{ terminated}}$$

$$S_{21} = b_2/a_1 = \text{forward gain}$$

$$S_{12} = b_1/a_2 = \text{reverse isolation}$$

$$S_{22} = b_2/a_2 = \Gamma_2 \Big|_{1 \text{ terminated}}$$

17

We measure S parameters by terminating one port in Z_0 and turning off the wave going into that port. In other words, CLICK we let $Z_{s2}=Z_0$ and $V_2=0$. That means there will be no a_2 wave incident on port 2, so we know reflections b_1 and b_2 both have to be caused by a_1 . CLICK this is that statement in equation form: the a_2 terms in both of our linear S-parameter equations have been set to zero. CLICK this lets us observe some interesting things about S parameters. S_{11} is the ratio of b_1/a_1 , which is the ratio of the reflected wave over the incident wave. We already have a name for that, and it's the reflection coefficient. So S_{11} is the reflection coefficient when port 2 is terminated. S_{22} is similar: it's the reflection coefficient off of port 2 when port 1 is terminated. S_{21} and S_{12} measure types of gain in our system: S_{21} measures how much of an incident wave crosses from port 1 to port 2, and the often undesirable S_{12} discusses how much of a wave incident on port 2 makes it back to port 1.

Summary

- We need S-parameters because they're easy to measure at high f
- S-parameters are ratios of incident and reflected waves

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

- a and b waves are sized to make power calculation easy: $a_1 = \frac{|V_+|}{\sqrt{Z_0}}$
- S11 is the reflection coefficient (if port 2 is terminated)

Calculating S-Parameters in Circuits

Matthew Spencer

Harvey Mudd College


E157 – Radio Frequency Circuit Design

In this video we're going to try to find the S-parameters of a simple circuit.

S-Parameters Don't Map Cleanly to Circuits

$$S_{11} = \Gamma_1 \Big|_{2 \text{ terminated}} = \frac{(R_1 + R_2 || Z_0) - Z_0}{(R_1 + R_2 || Z_0) + Z_0}$$


$$S_{21} = \frac{b_2}{a_1} = \dots$$

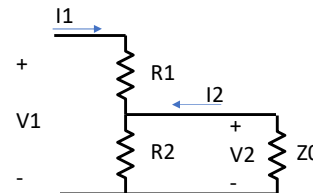

While S-parameters are easy to measure, we're going to find they are tough to analyze. If I was trying to find the S-parameters of our divider, I could start by attaching \$Z_0\$ to port 2. Making that connection ignores the transmission line connecting port 2 to the termination, but this is OK because the driving point impedance of a transmission line with a matched load is always \$Z_0\$ anyway. So we can find reflection coefficient of this structure from the Thevenin impedance of the load.

That was fine, but when we have to find \$S_{21}\$, we're kind of stumped. \$S_{21}\$ is defined in terms of wave amplitudes, but all we have in this model are port voltages and currents, which aren't the same as the amplitudes of incident and reflected waves.

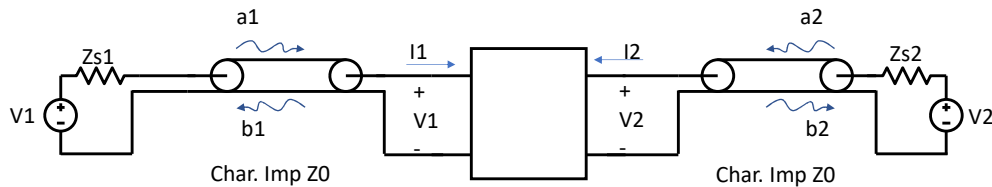a and b Waves Can Be Related to Port I and V



$$V_1 = V_+ + V_- = \sqrt{Z_0}(a_1 + b_1)$$

$$I_1 = \frac{V_+}{Z_0} - \frac{V_-}{Z_0} = \frac{(a_1 - b_1)}{\sqrt{Z_0}}$$

$$a_1 = \frac{V_1 + Z_0 I_1}{2\sqrt{Z_0}}, \quad b_1 = \frac{V_1 - Z_0 I_1}{2\sqrt{Z_0}}$$


21

However, we know the port voltages and currents are given by sums of voltage waves and differences of current waves from our earlier study of transmission lines. CLICK That means we can write a_1 and b_1 in terms of V_1 and I_1 by adding and subtracting the V_1 and I_1 equations in the first two lines.

As an aside: I found these definitions baffling when I first studied S parameters, because they're often the first definitions given for a_1 and b_1 , with no mention of transmission lines. I mentioned earlier that you can think of S parameters without a transmission line around, and pick Z_0 to be some arbitrary value, and many texts opt to do so. However, now that I have the picture of S-parameters as describing a two-port with transmission lines bolted on the side, I make sense of these definitions as mathematical tricks to relate the incident and reflected waves to voltage and current in the load.

S-Parameters Don't Map Cleanly to Circuits

$$S_{11} = \Gamma_1 \Big|_{2 \text{ terminated}} = \frac{(R_1 + R_2 || Z_0) - Z_0}{(R_1 + R_2 || Z_0) + Z_0}$$

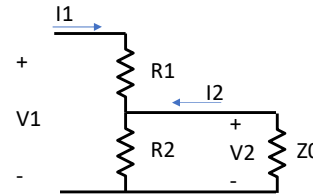

$$S_{21} = \frac{b_2}{a_1} = \frac{V_2 - Z_0 I_2}{V_1 + Z_0 I_1} = \frac{\overbrace{2V_2}^{Z_0 * I_2 = V_2, \text{ see schematic}}}{V_1 \left(1 + \underbrace{\frac{1 - S_{11}}{1 + S_{11}}}_{\text{Independent of network, useful takeaway!}} \right)} = \frac{V_2}{V_1} (1 + S_{11}) = \frac{R_2}{R_2 + R_1} (1 + S_{11})$$

Z_0 / Z_l , so that $V_1 = I_1 * Z_l$

- Tricky to compute with S-parameters ... but doable now.

So, now that we're armed with these port identities we can get one step farther with finding S21. CLICK the step after requires some fancy circuit footwork. First, we can see from the schematic that $I_2 * Z_0$ is going to be equal to $-V_2$ because I_2 flows into the negative terminal of Z_0 . So that means we can substitute $-V_2$ for $Z_0 * I_2$ in the numerator, which means we wind up with a total of $2V_2$ on top of the expression. The bottom of the expression requires even more tortured reasoning, where we express the normalized load impedance in terms of S_{11} . CLICK However, simplifying this, we get a nice expression that relates the voltage gain of the network to S_{21} , and because we haven't put in any details of this particular divider yet, this expression is good for any two-port network. It's a handy tool, keep track of it.

CLICK Finally, we substitute in the resistor divider equation for V_2/V_1 , in order to find the S_{21} of this divider.

Another Option is S-to-Z Conversion Formulas

$$S = (Z - Z_0 I)(Z + Z_0 I)^{-1}$$

$$Z = (I - S)^{-1}(I + S)Z_0$$

$$S_{21} = \frac{2Z_0 Z_{21}}{(Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12} Z_{21}}$$

- Easy to find Z parameters, and all linear representations equivalent

If that all seems like a bit much, there's another option. Z parameters were pretty easy to calculate for the divider, and there's a conversion between S and Z parameters. I've included it on this slide. It's a bunch of matrix math, but it lets you do easy circuit analysis to build intuition, and then let a computer do the hard matrix calculations for you. This is a reasonable approach if you don't need to calculate S parameters in your head right now. I've included the specific calculation that relates S₂₁ to Z parameters on this slide to give some context for how annoying these calculations would be to do by hand.

Before we leave the slide, I find it cute that the matrix versions of these equations kind of look like the scalar equations relating reflection coefficient and load impedance: you can see a Z_l-Z₀ divided by Z_l+Z₀ in the first equation if you squint.