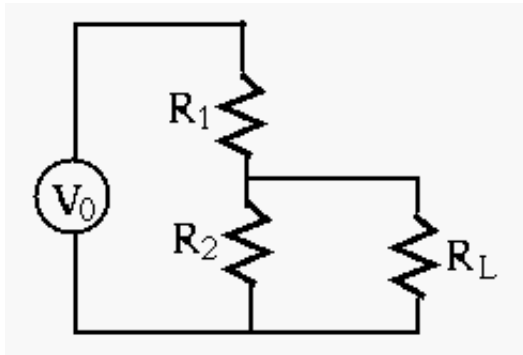


[Next](#)
[Up](#)
[Previous](#)

Next: [About this document ...](#)

## E84 Homework 4


1. In the voltage divider circuit below,  $V_0 = 20V$ ,  $R_1 = R_2 = 500\Omega$ . Use Thevenin's theorem to find the current through and voltage across the load resistor  $R_L$  when it is  $100\Omega$ ,  $200\Omega$ ,  $300\Omega$ , respectively.



**Solution:**

- $R_T = 250$ ,  $V_T = 10V$
- When  $R_L = 100$ ,  $I_L = V_T / (R_T + R_L) = 1/35$ ,  $V_L = I_L R_L = 20/7$
- When  $R_L = 200$ ,  $I_L = V_T / (R_T + R_L) = 1/45$ ,  $V_L = I_L R_L = 40/9$
- When  $R_L = 300$ ,  $I_L = V_T / (R_T + R_L) = 1/55$ ,  $V_L = I_L R_L = 60/11$

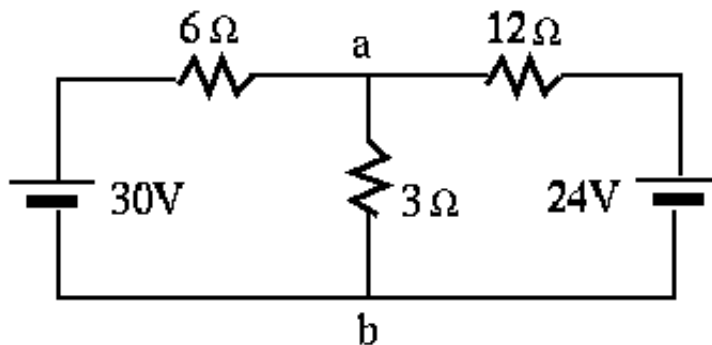2. Use Thevenin's and Norton's theorems to determine the current in the  $3\Omega$  resistor of the following figure.



**Solution:** move two voltage sources to left, and  $3\Omega$  resistor to the right as load find equivalent voltage  $V_o$  and internal resistance and  $R_o$ .

- Use Thevenin's theorem:

The current going clockwise around the loop (without load) is  $(30 - 24)/(6 + 12) = 1/3$ , the voltages across the  $6\Omega$  resistor and  $12\Omega$  resistor are  $-2V$  and  $4V$ , respectively.

$$V_T = 30 - 6/3 = 24 + 12/3 = 28 V, \quad R_T = 6//12 = 4\Omega$$


The current through the load resistor is

$$I_L = \frac{V_T}{R_T + R_L} = \frac{28}{4 + 3} = 4 A$$

- Use Norton's theorem: Turn the two voltage sources to current sources  $I_1 = 30/6 = 5 A$ ,  $I_2 = 24/12 = 2 A$ . These two current sources are in parallel to form a total current source of  $I_N = I_1 + I_2 = 7 A$ . The two internal resistances are also in parallel  $R_N = R_1//R_2 = 6//12 = 4\Omega$ . The current through the load resistor is obtained by current divider:

$$I_L = I_N \frac{R_N}{R_N + R_L} = 7 \frac{4}{4 + 3} = 4 A$$

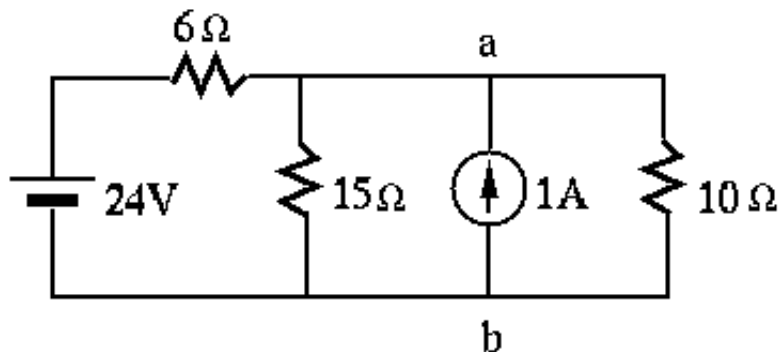3. Find voltage across and the current through the  $10\Omega$  resistor.



**Solution:**

- Use superposition principle. When  $24V$  is acting alone with  $1A$  open, parallel resistors  $15$  and  $10$  become  $15//10 = 6$ ,  $V'_{ab} = 24 \times 6/(6 + 6) = 12V$ ,  
 $I' = 12/10 = 1.2A$ . When  $1A$  is acting alone with  $24V$  closed, parallel resistors  $6$  and  $15$  become  $90/21 = 30/7$ ,  $I'' = (30/7)/(10 + 30/7) = 3/10 = 0.3A$ ,  
 $V''_{ab} = I'' \times 10 = 3V$ , overall  $V = V' + V'' = 12 + 3 = 15$ ,


$$I = I' + I'' = 1.2 + 0.3 = 1.5A.$$

- Use Norton's theorem. Turn the voltage source to a current source with  $I = 24/6 = 4A$  and  $R = 6\Omega$ . Then the two current sources in parallel form a total current source of  $I_N = 5A$  with internal resistance  $R_N = 15//6 = 30/7$ . By current divider, we get

$$I_L = 5 \frac{30/7}{10 + 30/7} = 1.5, \quad V_L = 1.5 \times 10 = 15V$$

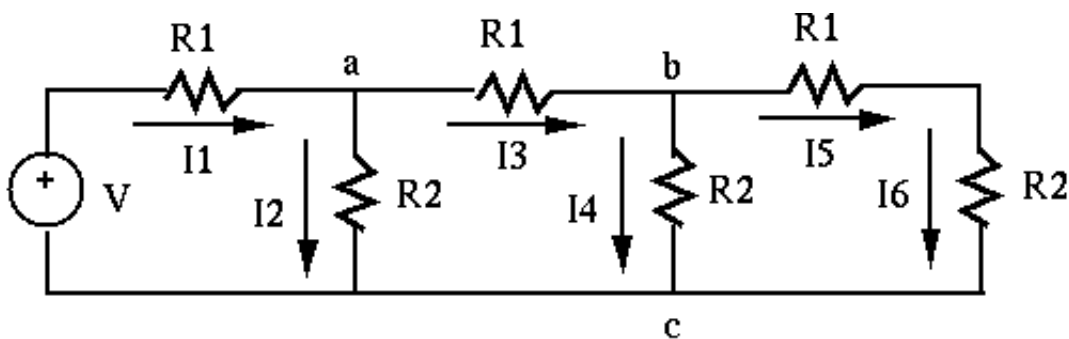4. Find all currents in the diagram in which  $V = 120V$ ,  $R_1 = 2\Omega$ ,  $R_2 = 20\Omega$ .

**Hint:** It is very hard to solve the problem by finding the currents in the order of  $I_1, I_3, I_5$ , as computing the resistances of the resistor network is tedious. However, it is much more straight forward to find the currents in the order of  $I_5, I_3, I_1$ , if you assume  $I_5$  is known, e.g.,  $I_5 = I_6 = 1A$ . However, the voltage for the voltage source obtained based on this assumption is of course not as given (120V). In this case, the linearity property  $F(ax + by) = aF(x) + bF(y)$  can be applied. In particular, given  $y = F(x)$ , then  $ay = F(ax) = aF(x)$ . Use this relationship to find the actual values of the currents.



**Solution:**


- use node c as reference (ground), assume  $I_5 = 1$ , then  $V_b = (20 + 2) = 22V$ ,  
 $I_4 = 22/20 = 1.1A$ ,  $I_3 = I_4 + I_5 = 1.1 + 1 = 2.1A$ ,  
 $V_a = 2.1 \times 2 + V_b = 4.2 + 22 = 26.2V$ ,  $I_2 = V_a/20 = 26.2/20 = 1.31A$ ,  
 $I_1 = I_2 + I_3 = 1.31 + 2.1 = 3.41A$ ,  
 $V_0 = I_1 \times 2 + V_a = 2 \times 3.41 + 26.2 = 33.02$ .

- But the given voltage source is 120V, all currents should be scaled up by a factor  $120/33.02 = 3.634$ ,  $I_1 = 12.39$ ,  $I_2 = 4.76$ ,  $I_3 = 7.63$ ,  $I_4 = 4.00$ ,  $I_5 = 3.63$
- 

5. In the circuit below,  $R_1 = 1\Omega$ ,  $V_2 = 2V$ ,  $R_3 = 1\Omega$ ,  $R_4 = 3\Omega$ ,  $I_5 = 5A$ ,  $V_6 = 2V$ , and  $R_6 = 1\Omega$ . Find

- current through voltage source  $V_2$ .
- current through resistor  $R_3$

(Hint: consider superposition theorem.)

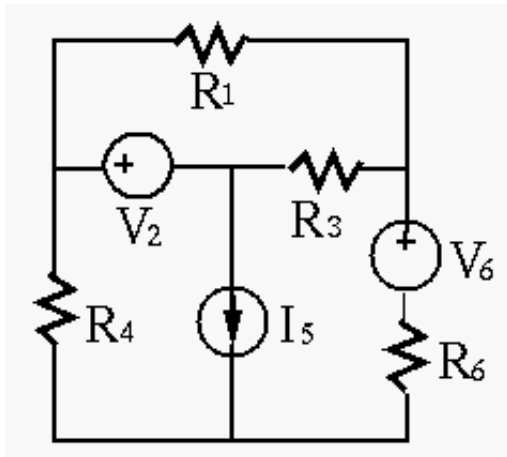

**Solution:** Consider each of the three sources alone:

- V2 alone ( $I_5$  open,  $V_6$  short):  

$$I' = V_2 / [R_1 + R_3 // (R_3 + R_6)] = 2 / (1 + 1 // 4) = 2 / (1 + 4/5) = 10/9$$
 (left).
- V6 alone ( $I_5$  open,  $V_2$  short):  

$$I'' = 0.5 \times V_6 / (R_6 + R_4 + R_1 // R_3) = 1 / (1 + 3 + 0.5) = 1/4.5 = 2/9$$
 (left)
- $I_5$  alone ( $V_2$ ,  $V_6$  both short):

$$\text{current thru } R_6: I_5 \times R_4 / [R_4 + (R_6 + R_1 // R_3)] = 5 \times 3 / 4.5 = 10/3$$


---

current thru  $R_4$ :

$$I_5 \times (R_6 + R_1 // R_3) / [R_4 + (R_6 + R_1 // R_3)] = 5 \times 1.5 / 4.5 = 5/3$$


---

current thru  $R_1$  is (half of that thru  $R_6$ ):  $5/3$

- $I'''$  is the sum of current thru  $R_4$ , current thru  $R_1 = 5/3 + 5/3 = 10/3$  (right)  
 and current thru  $V_2$ :  $I' + I'' + I''' = 10/9 + 2/9 - 10/3 = -2$  (left) or 2 (right)
- currents thru  $R_3$  due to  $V_2$  and  $V_6$  respectively are the same as that thru  $V_2$  currents

thru  $R_3$  due to  $I_5$  is (half of current thru  $R_6$  above):  $5/3$  (left)


- total current thru  $R_3$ :  $\underline{10/9 + 2/9 + 5/3 = 3}$  (left)

- The sum of two currents is equal to  $I_5 = 2 + 3 = 5$

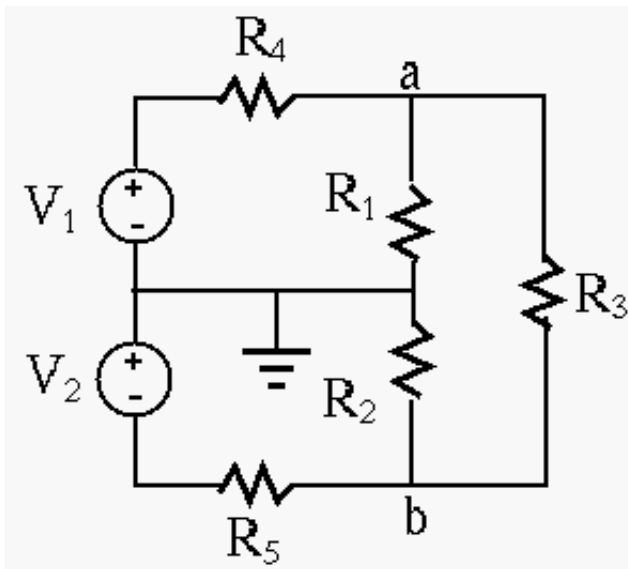6. In the circuit below,  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 3\Omega$ ,  $R_4 = 4\Omega$ ,  $R_5 = 5\Omega$ ,  $V_1 = 4V$ ,  $V_2 = 5V$ . Find voltage  $V$  across and current  $I$  through the load resistor  $R_3$  by converting the rest of the circuit into a

- Thevenin's voltage source  $V_T$  with  $R_T$
- Norton's current source  $I_N$  with  $R_N$

Verify your results by converting the current source into a voltage source (or vice versa). Then find voltage  $V$  and current  $I$  associated with load  $R_3$ .



**Solution:**

- Find Thevenin's voltage source  $V_T$  with  $R_T$ . First turn voltage sources off and find  $R_T$  between nodes  $a$  and  $b$ :

$$R_T = R_1 || R_4 + R_2 || R_5 = \frac{R_1 R_4}{R_1 + R_4} + \frac{R_2 R_5}{R_2 + R_5} = 78/35$$

Find  $V_{oc}$ :

$$V_a = V_1 \frac{R_1}{R_1 + R_4} = 4/5, \quad V_b = -V_2 \frac{R_2}{R_2 + R_5} = -10/7$$

$$V_{oc} = V_a - V_b = 78/35$$

- Norton's current source  $I_N$  with  $R_N$ . First  $R_N = R_T = 78/35$ . Then use loop current method to find  $I_N = I_{sc}$ . Assume loop currents  $I_a$  (top-left loop),  $I_b$  (bottom left loop) and  $I_c = I_{sc} = I_N$  (right loop), and we have these loop current equations:

$$\begin{cases} 5I_a & & -I_c = 4 \\ & 7I_b & -2I_c = 5 \\ -I_a & -2I_b & +3I_c = 0 \end{cases}$$

Solving this to get  $I_N = I_{sc} = I_c = 1$ .

- Verify your results by converting the current source into a voltage source (or vise versa).

$$I_N R_N = 78/35 = V_T$$

Finally,

$$I = \frac{V_T}{R_T + R_3} = \frac{78/35}{78/35 + 3} = \frac{78}{183} = 0.426$$

$$V = IR_3 = 1.28V$$

- 
- [About this document ...](#)
- 

[Next](#) [Up](#) [Previous](#)

**Next:** [About this document ...](#)

Ruye Wang 2011-06-20