

# Basic Electrical Measurements

Matthew Spencer


E80 Lecture 4

2016-01-27

Many thanks to Prof. Lee for her excellent work on the lecture figures


# Why are We Talking?

GIVEN: Schematics

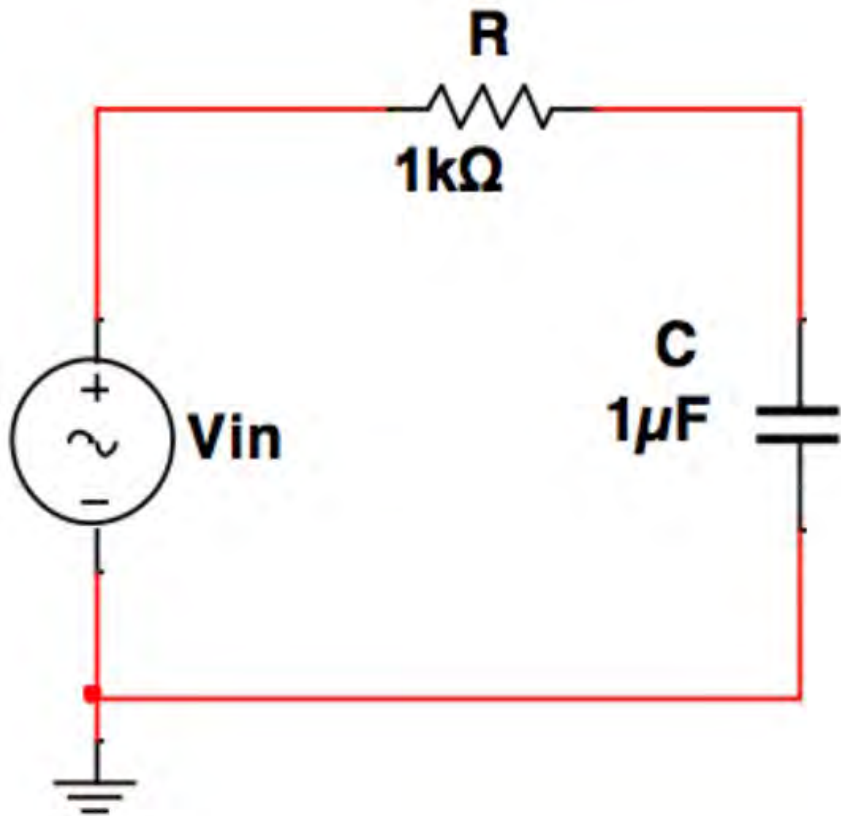


+  
 $V_C$   
-

DESIRE: Experiments

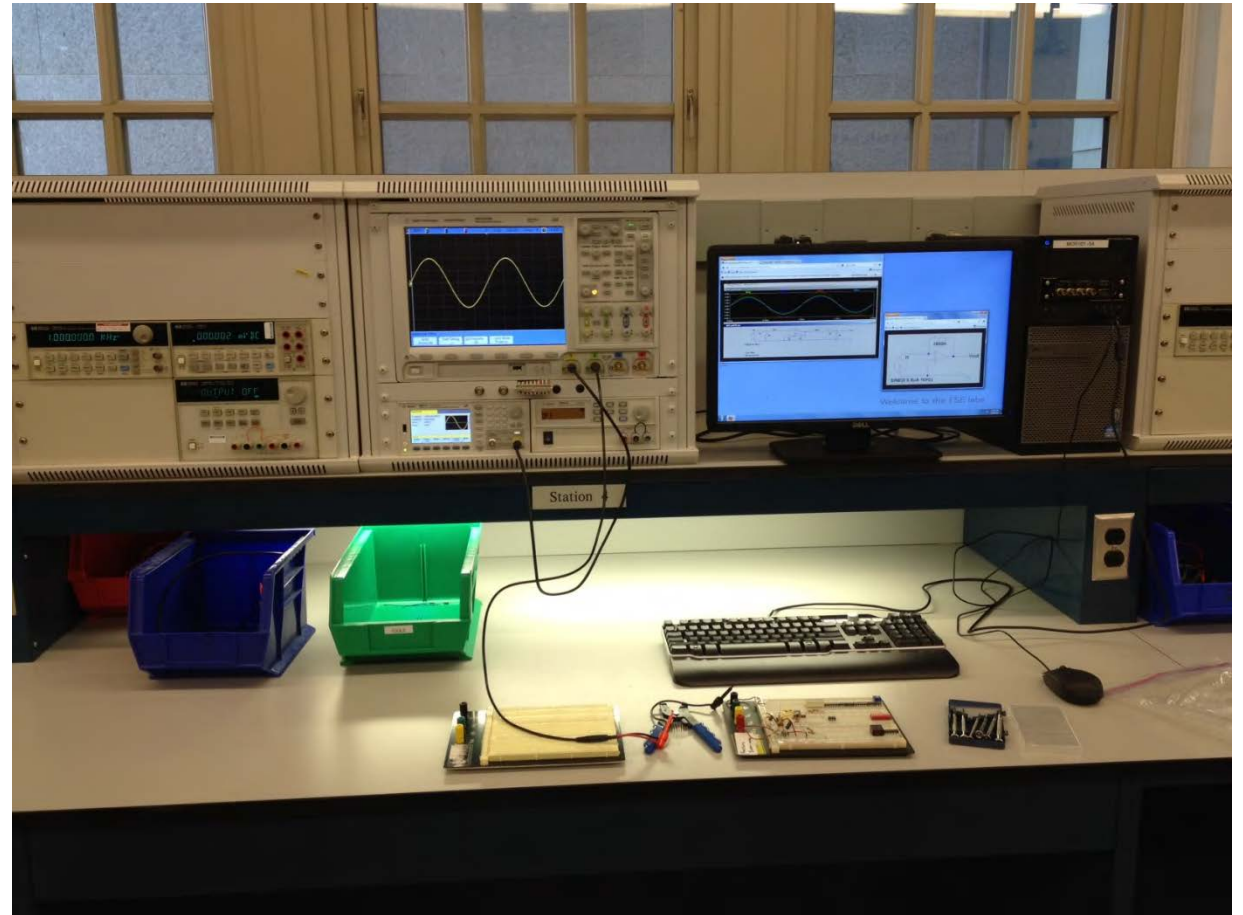


# The Three Parts of a Schematic

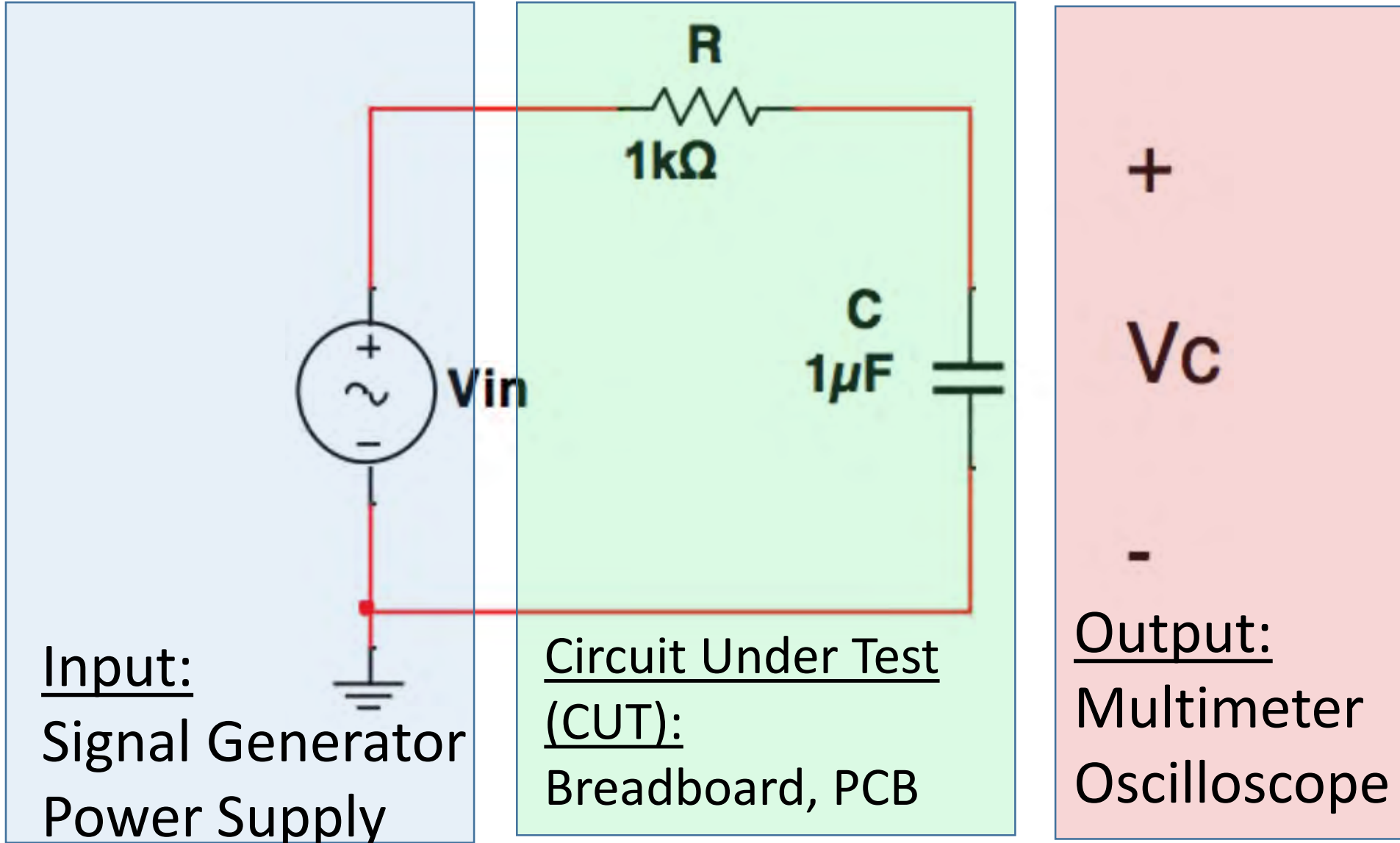
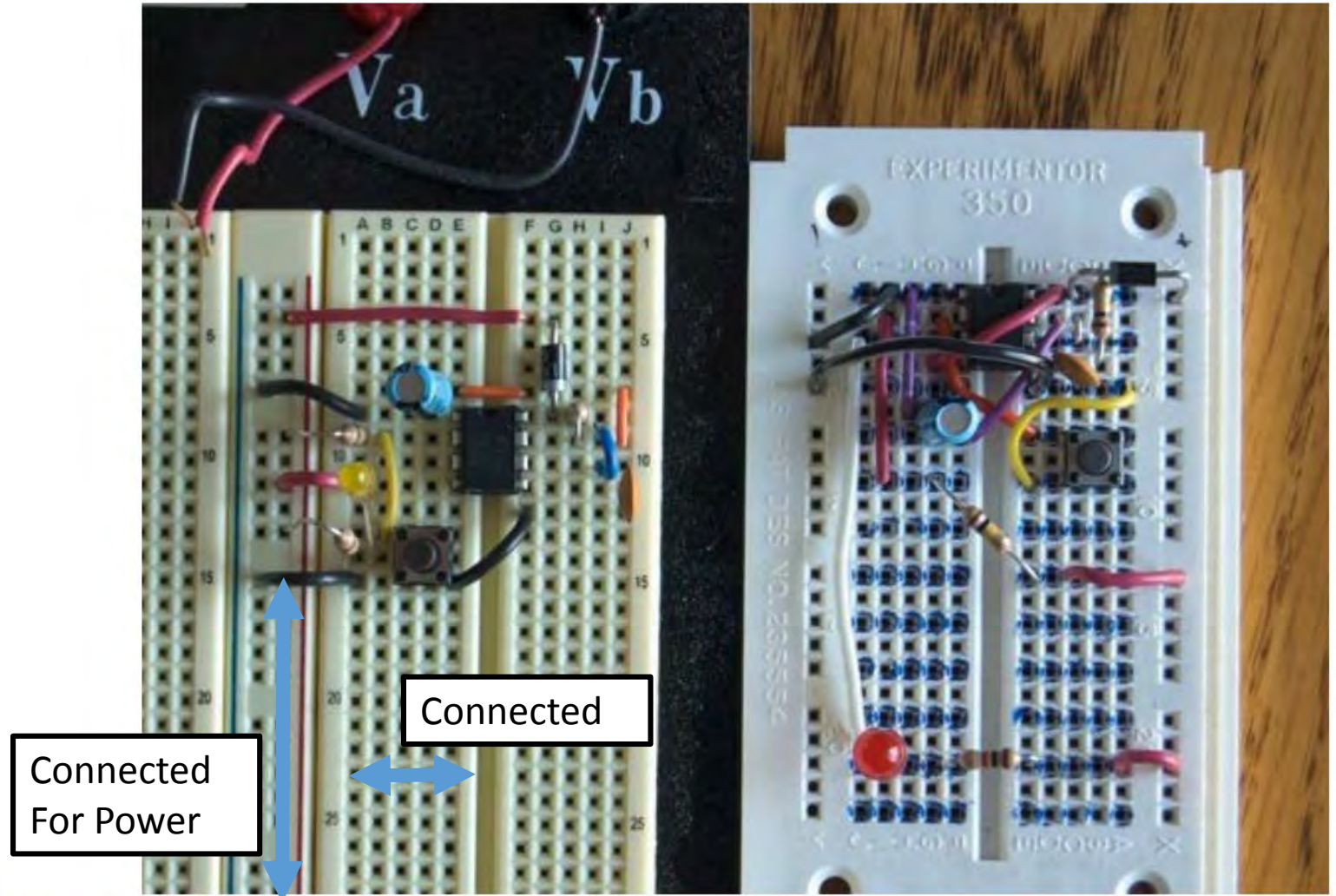
# A Circuit Under Test

Stuff to notice:

- Breadboard Routing
- Layout Sins
- Parasitic Elements
- Color Coding



# Multimeter

Don't forget this




# Two Tricky Things

- What the heck does AC RMS Mean?
  - To the board!
  - It is one number that describes the amplitude of a sine wave\*
  - Specifically, it is the DC voltage which dissipates the same power in a resistor as a sine wave of amplitude  $V_{ZeroPeak}$
  - $V_{RMS} = V_{ZeroPeak} / \sqrt{2}$  in a sinusoidal wave
- Why are there so many plug holes?
  - Next few slides

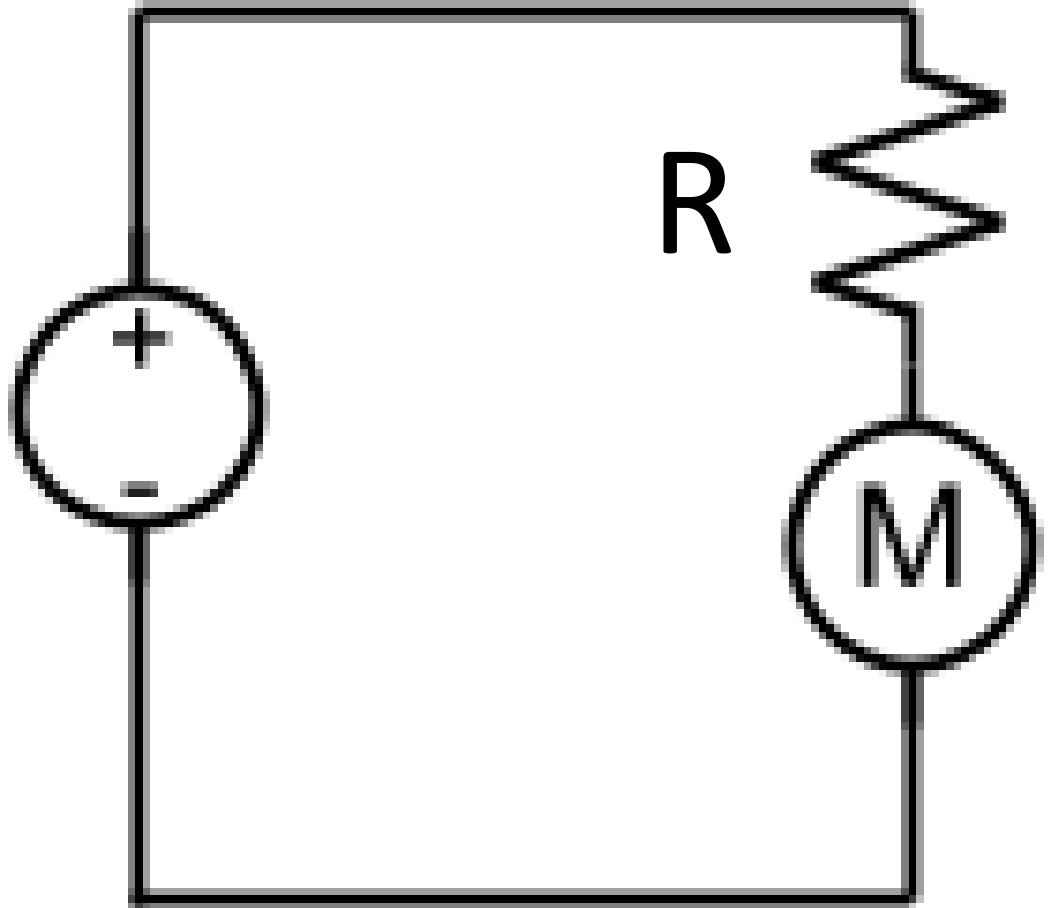
# Let's Do a Current Measurement

- Put multimeter in series
- Current flows through it
- Multimeter must look like a wire to be non-invasive


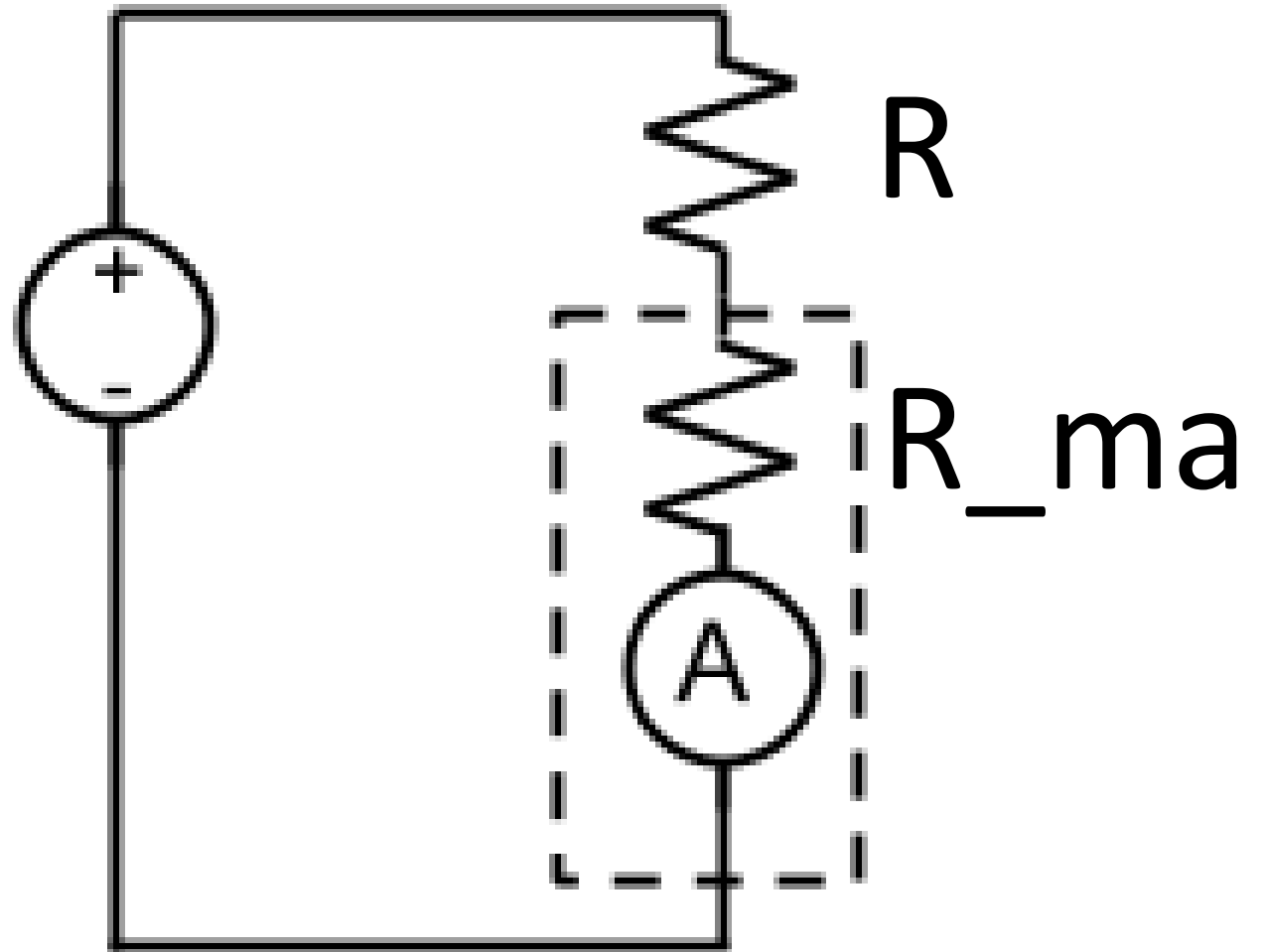
# The Multimeter has Impedance


- $R_{ma}$  is needed to take a measurement.
- Most of the time, this won't matter. It could for small  $R$ .
- Do analysis with equivalent circuit model if necessary.






# Let's do a Voltage Measurement



Schematic

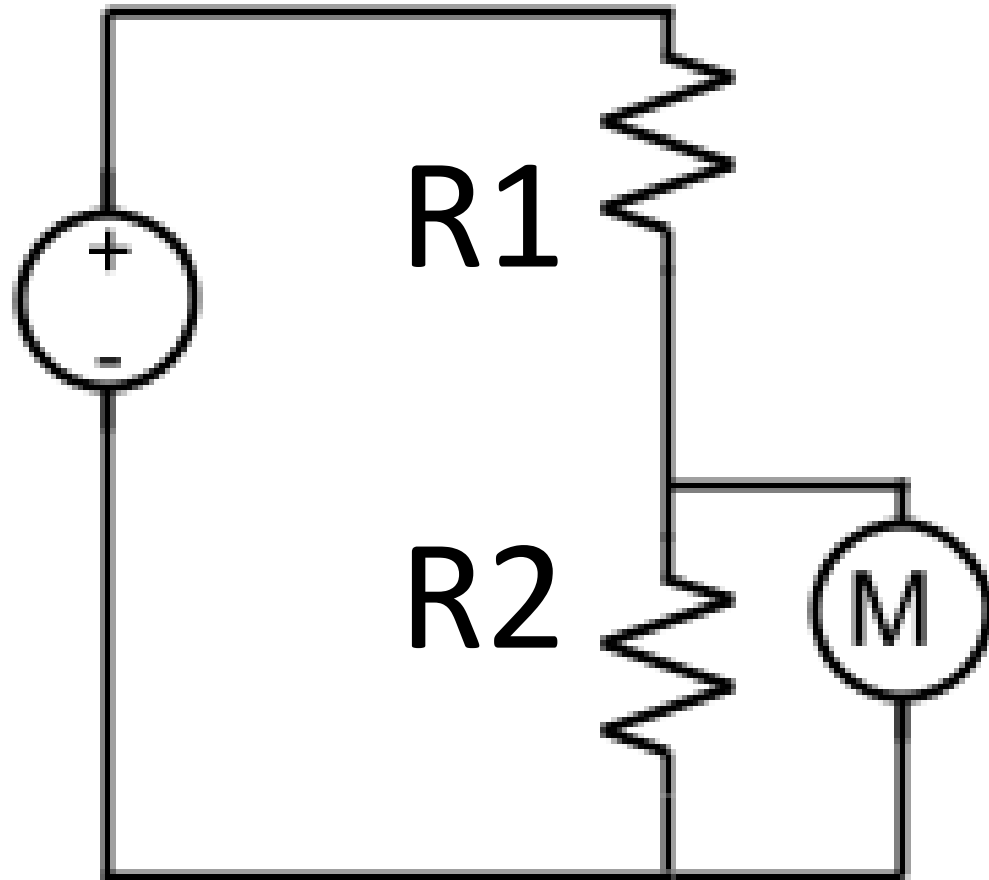

Schematic w/ Eq. Ckt Model


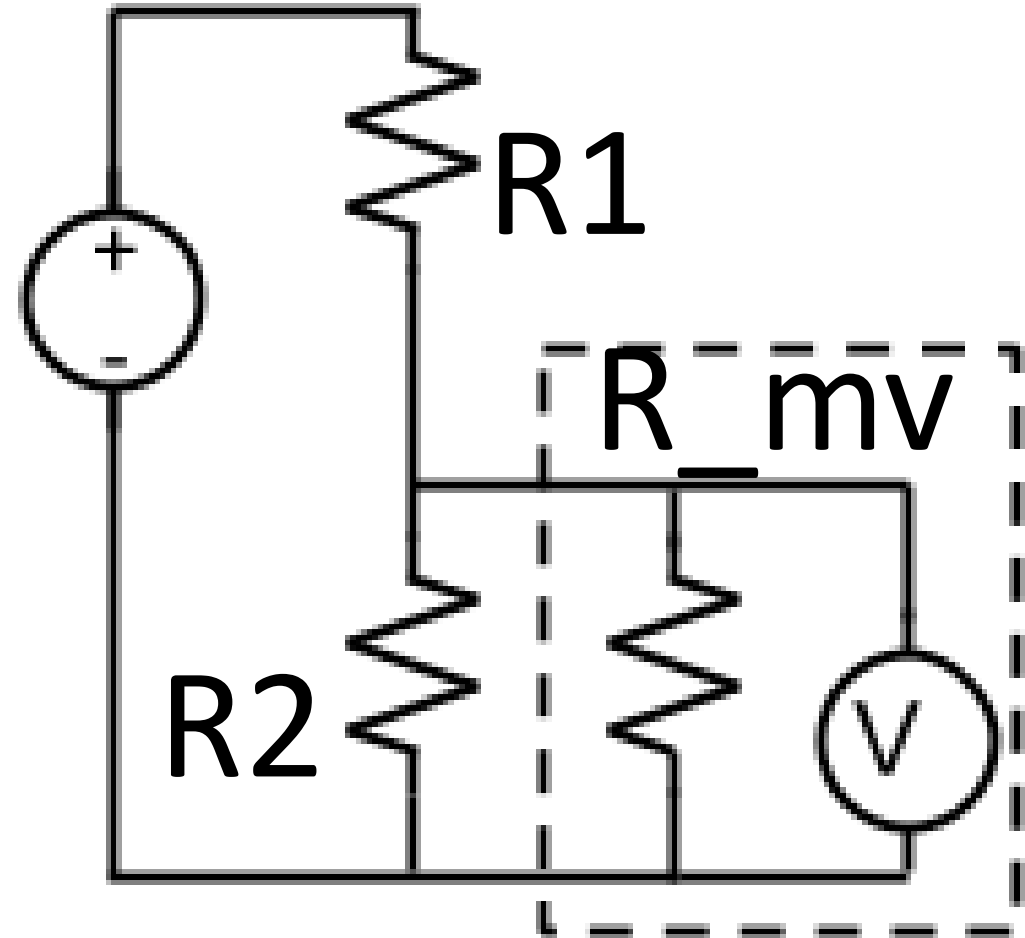


# Let's do a Resistance Measurement

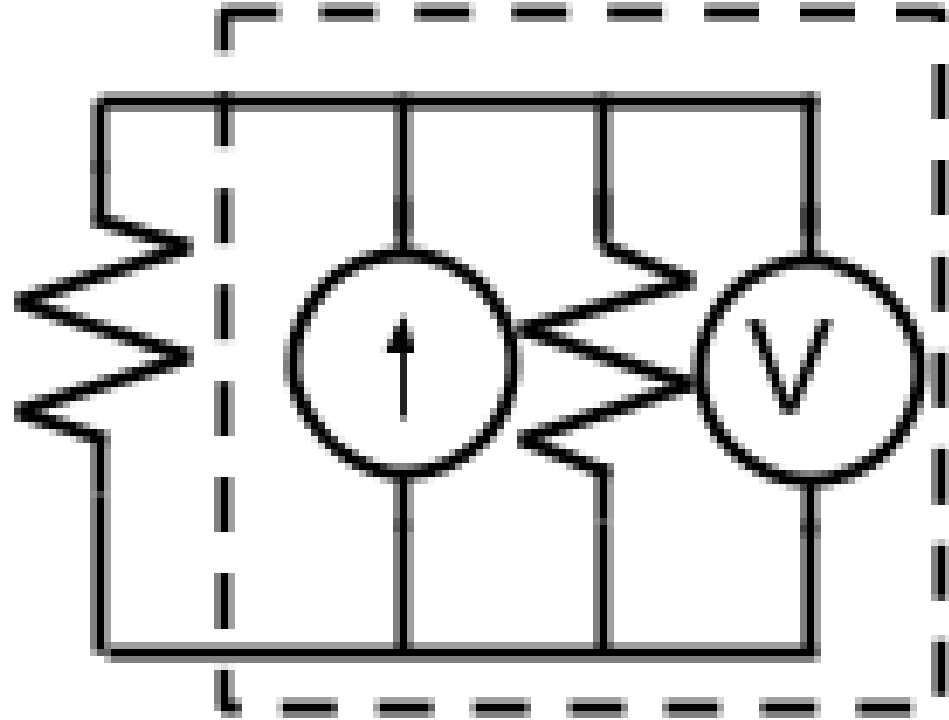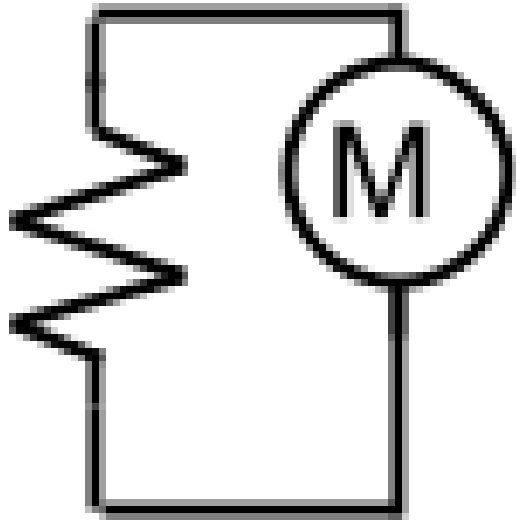

- Current source will do weird stuff if it interacts with chips

# Oscilloscopes

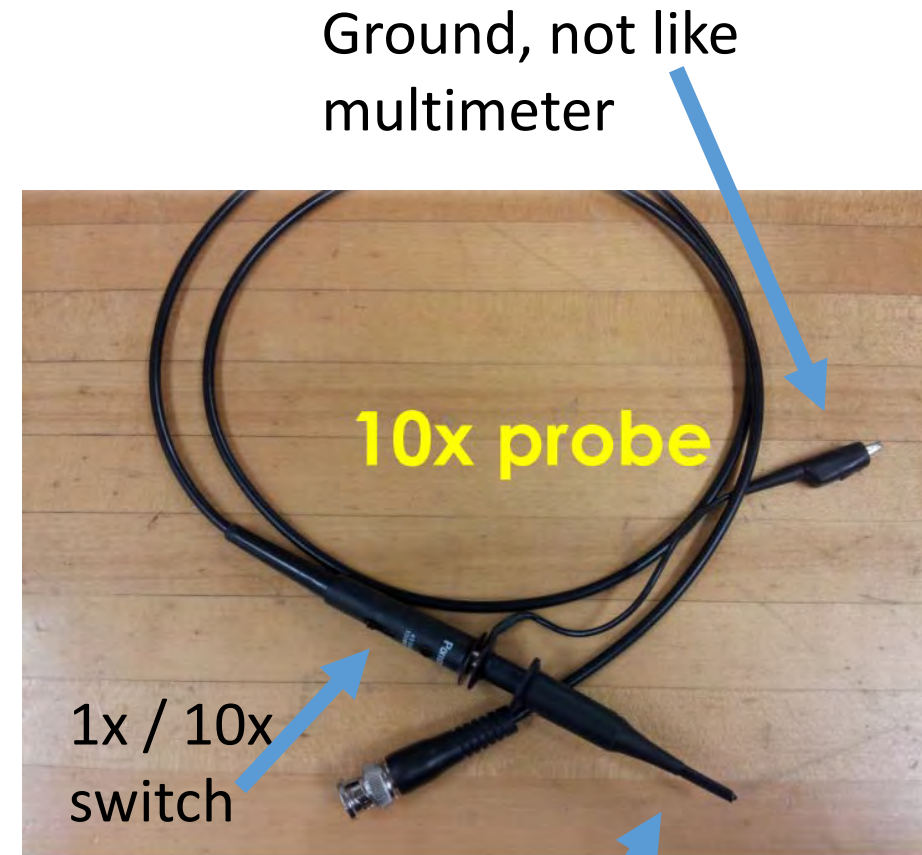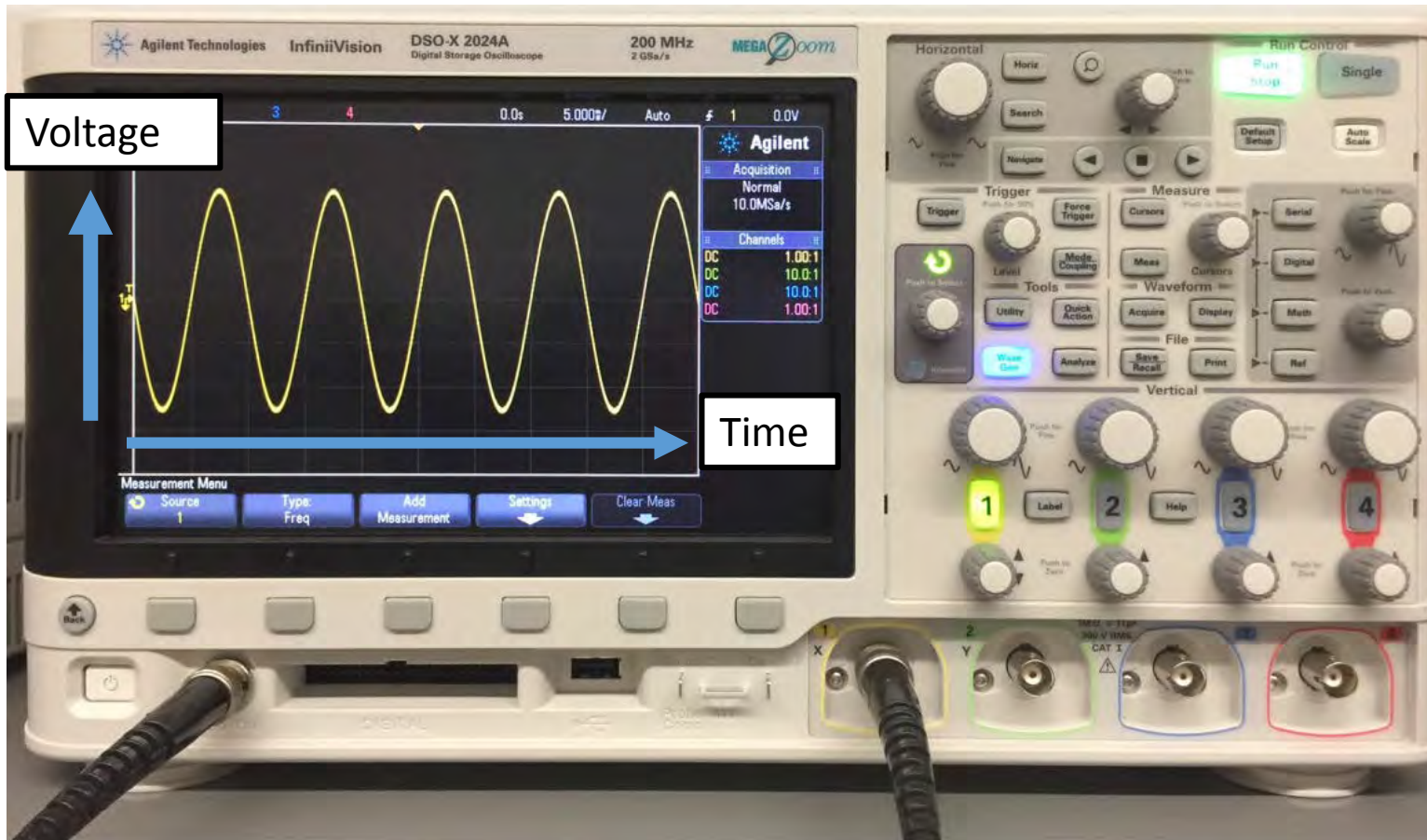

- Leave wires in your board, don't wrap around probes
- Don't lose probe hats!

# Power Supplies Make DC Voltage

Use this to make negative V  
Sets  $-1 * V_{-20}/V_{+20}$



Circuit Ground  
"Common" Node


Earth Ground  
Connects to wire in wall

# Old Signal Generators




Bad Habit to use these for oscilloscopes


# New Signal Generators

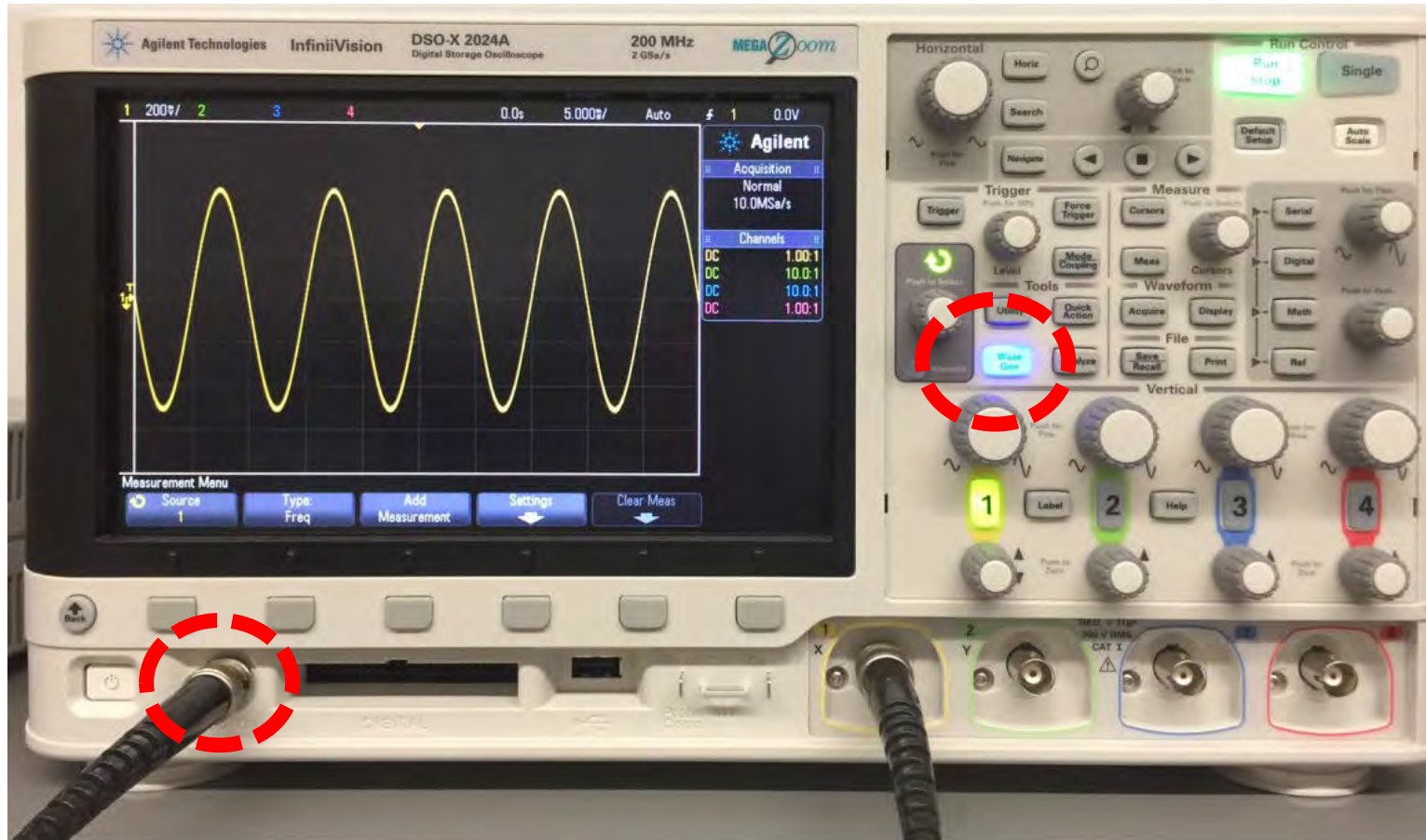
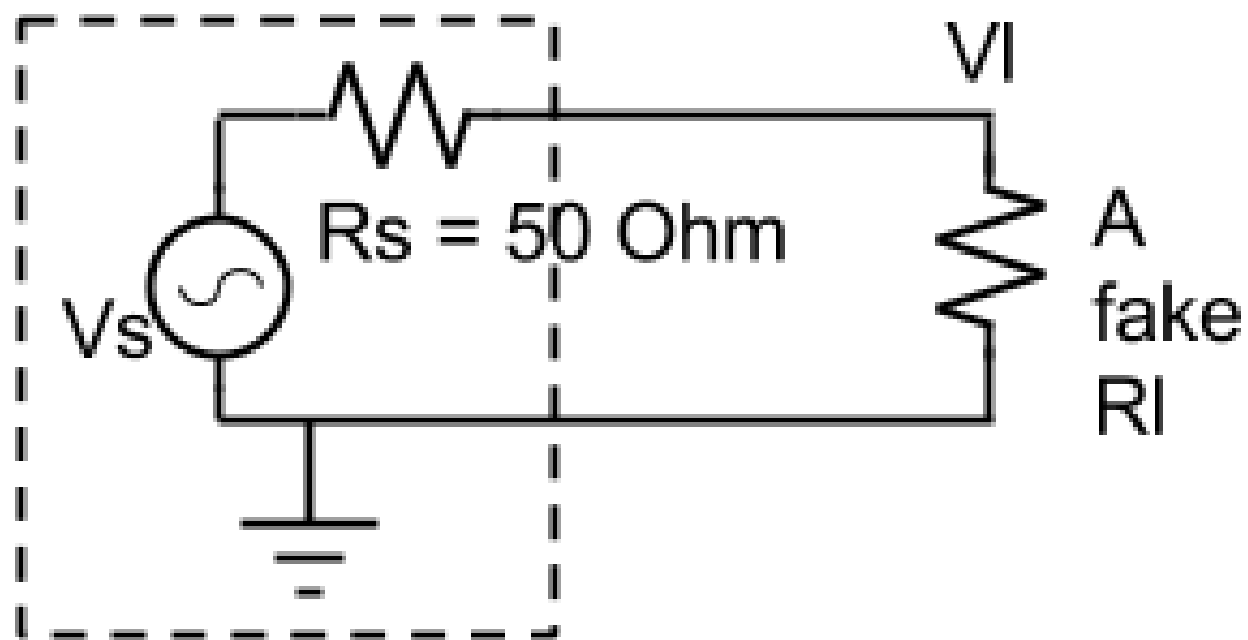
# Model of Signal Generators and 50 Ohm/Hi Z



Output term set to 50 Ohm

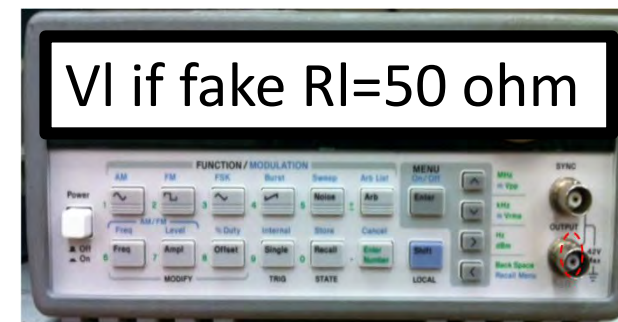

Output term set to Hi Z



- Output term has NO PHYSICAL EFFECT
- This confuses lots of people. Use Hi-Z.
- I hate the 50 Ohm setting, but it has some historical significance related to high speed measurements.