


E80 Spring 2014

# Op Amps Circuits

# Agenda: Operational Amplifier

- Recap: Non-inverting amplifier and unity gain buffer
- Inverting amplifier (multiplication)
- Summing amplifier (add and subtract)
- Differentiator and integrator
- Difference amplifier
- Instrumentation amplifier
- Transimpedance amplifier
- Active filters


# Recap: Opamp Model

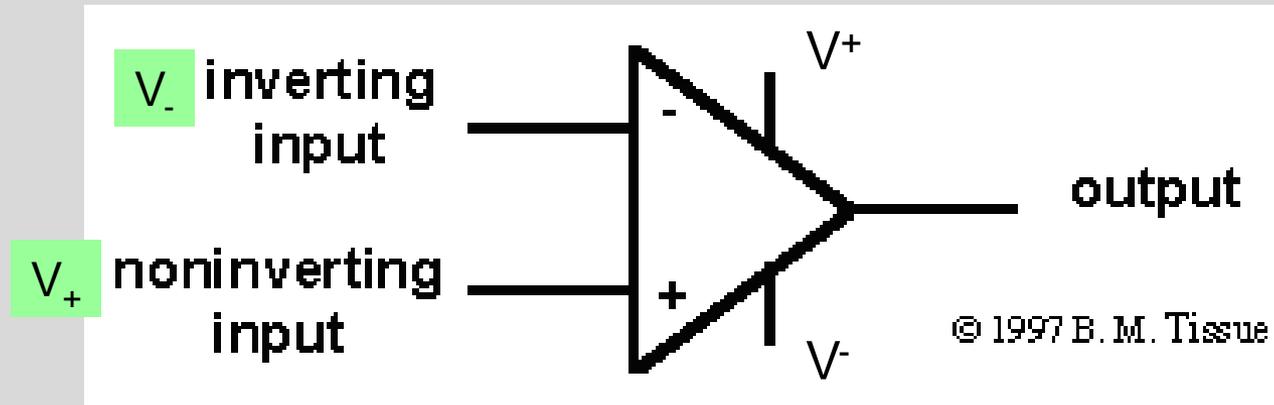


$$(1) v_+ = v_- \quad (2) i_+ = 0, \quad i_- = 0$$
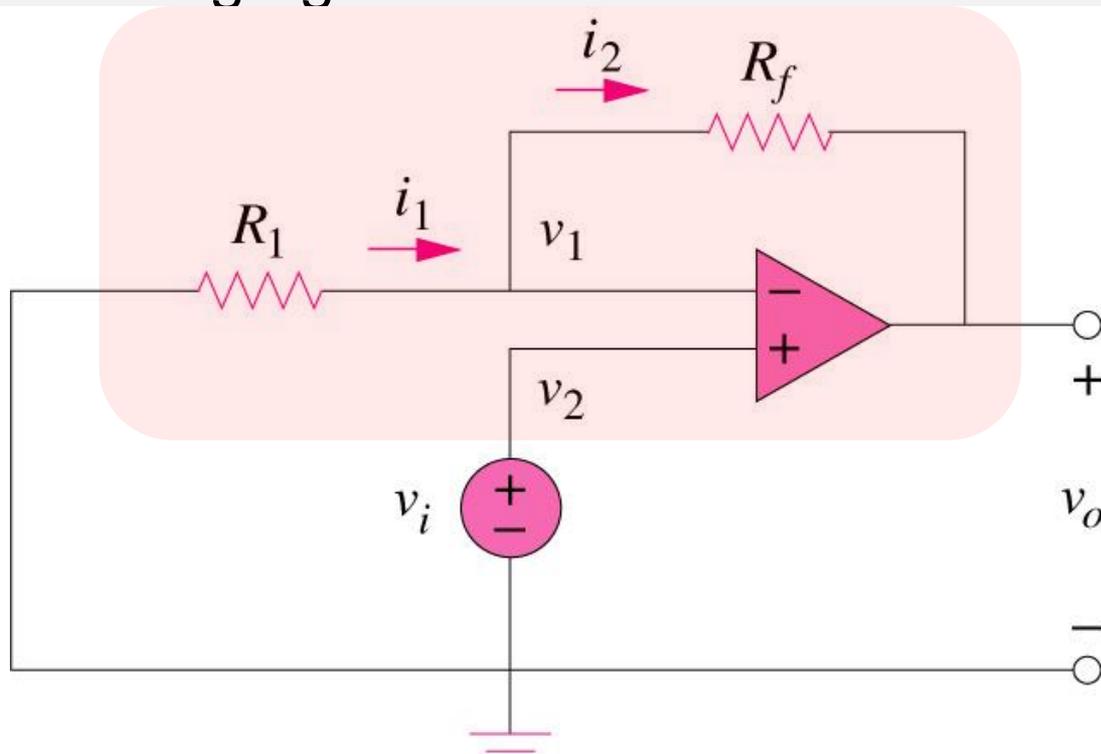
# Recap: Non-inverting Amplifier

- Non-inverting amplifier is designed to produce positive voltage gain



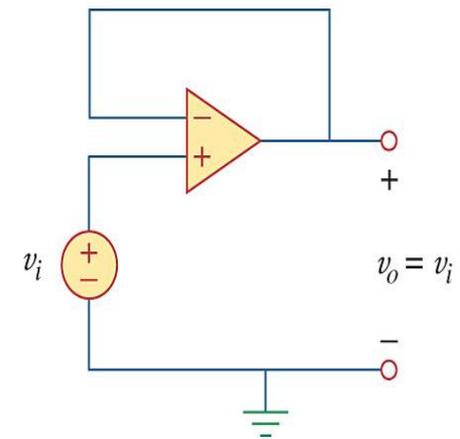
$$v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$$



Special case:  
 $R_1 = \infty$ ,  $R_f = 0$   
Unity-gain buffer
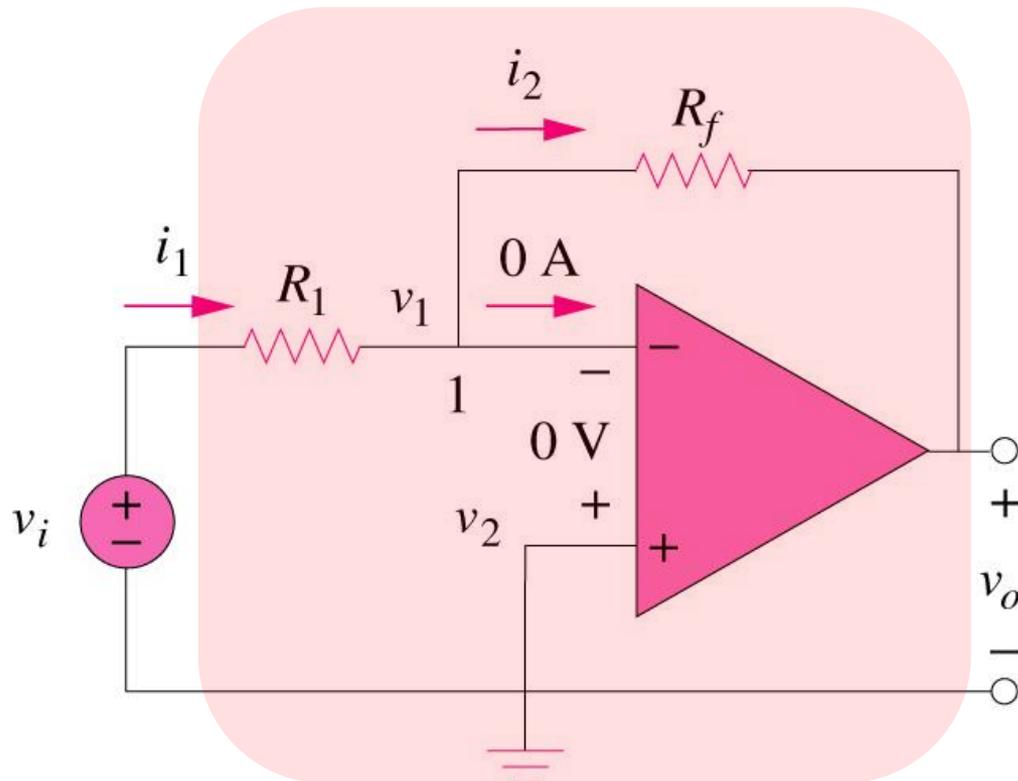
# Inverting amplifier


- Inverting amplifier reverses the polarity of the input signal while amplifying (or attenuating) it



$$v_o = -\frac{R_f}{R_1} v_i$$
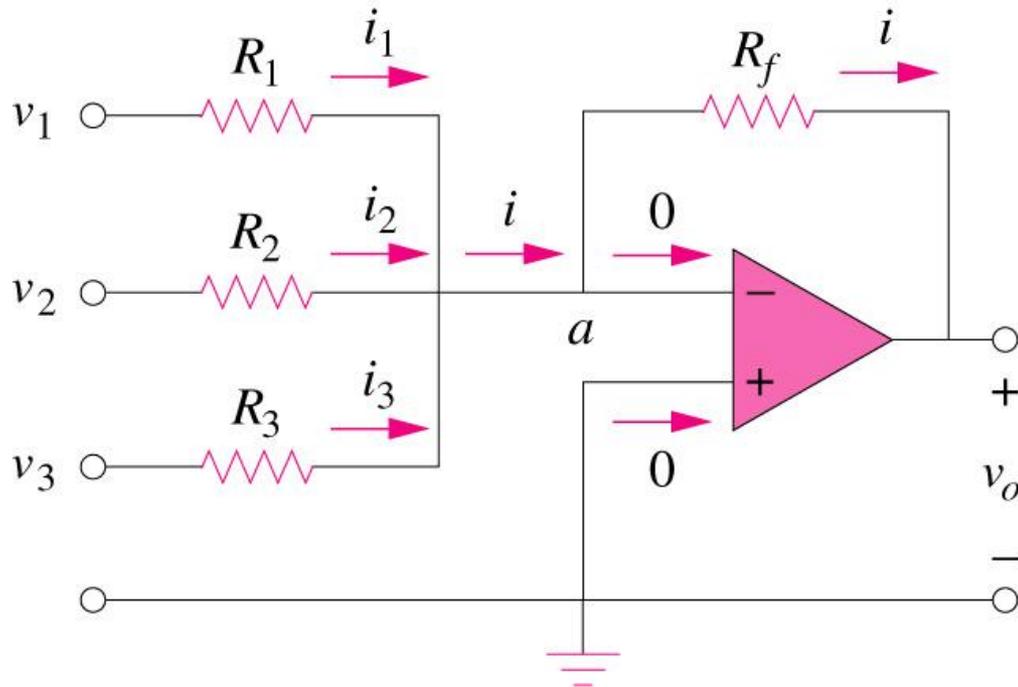
# Summing amplifier

- Summing Amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.




$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

**Q: Is it possible to construct a non-inverting summing amp?**

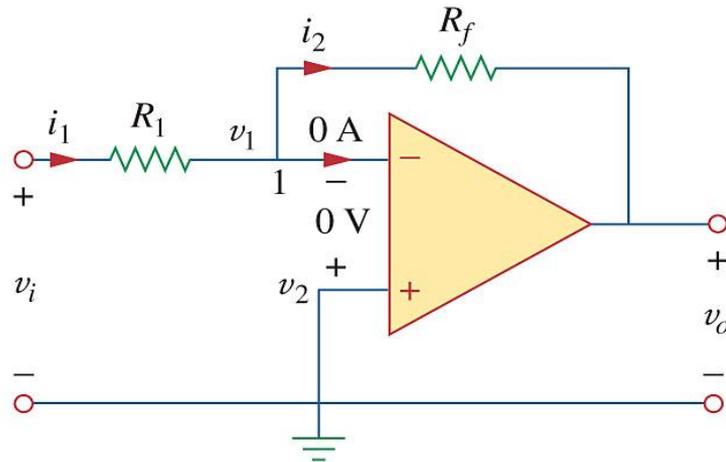
# Opamp Circuit With Capacitor

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)


Inverting amplifier

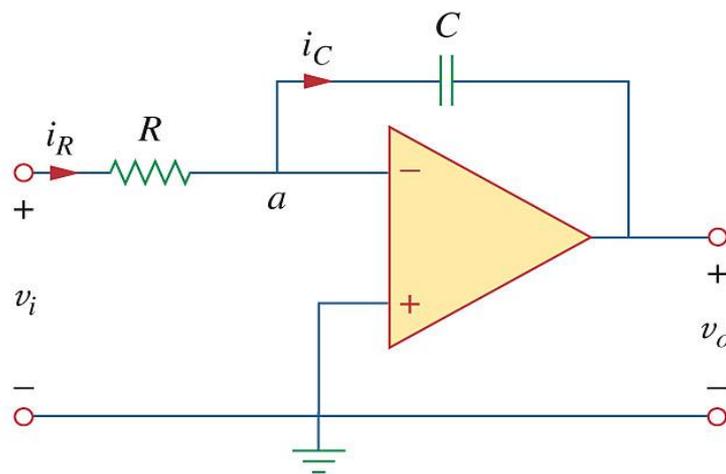

(b)


What does this circuit do?  
How is  $V_o$  related to  $V_i$ ?

# Opamp Circuit With Capacitor

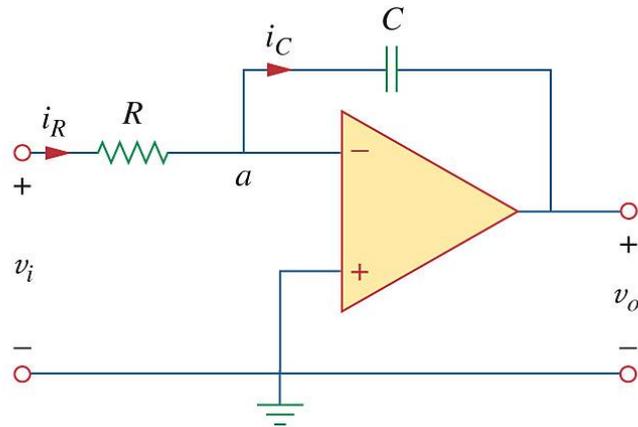

Integrator circuit

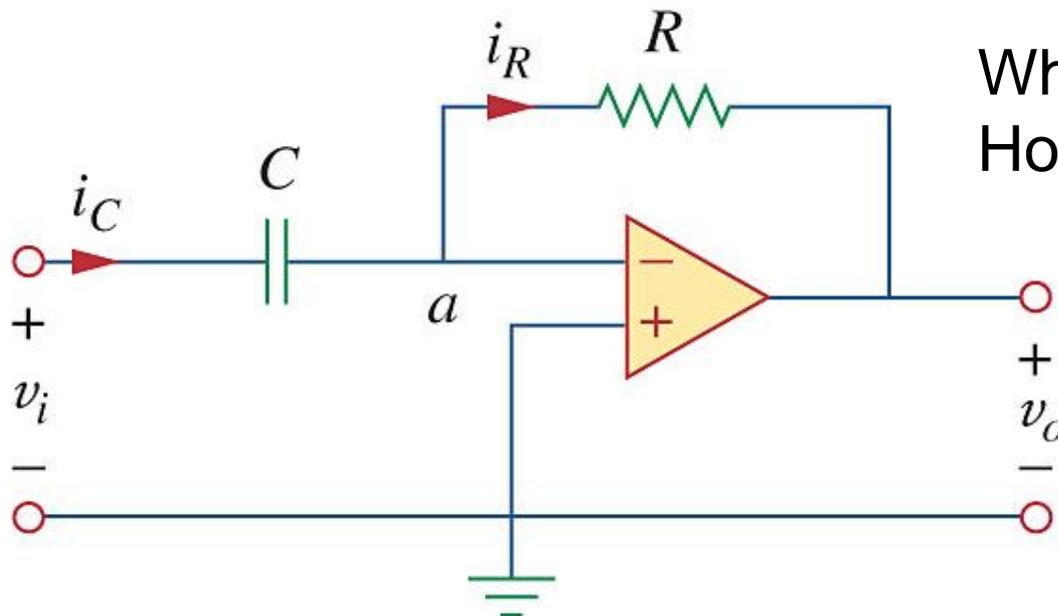
$$v_o(t) = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau + v_C(0)$$




What does this circuit do?  
How is  $V_o$  related to  $V_i$ ?

# Example

What does the output waveform look like?

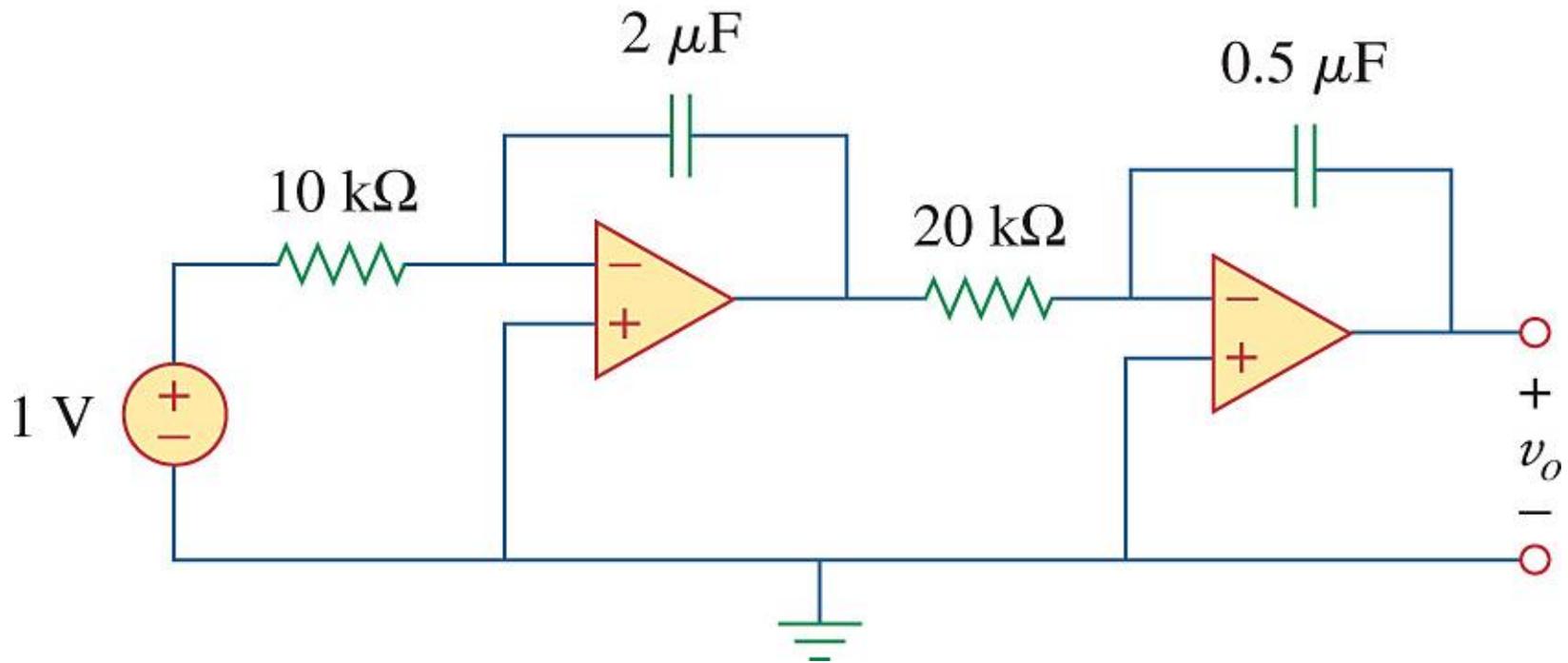
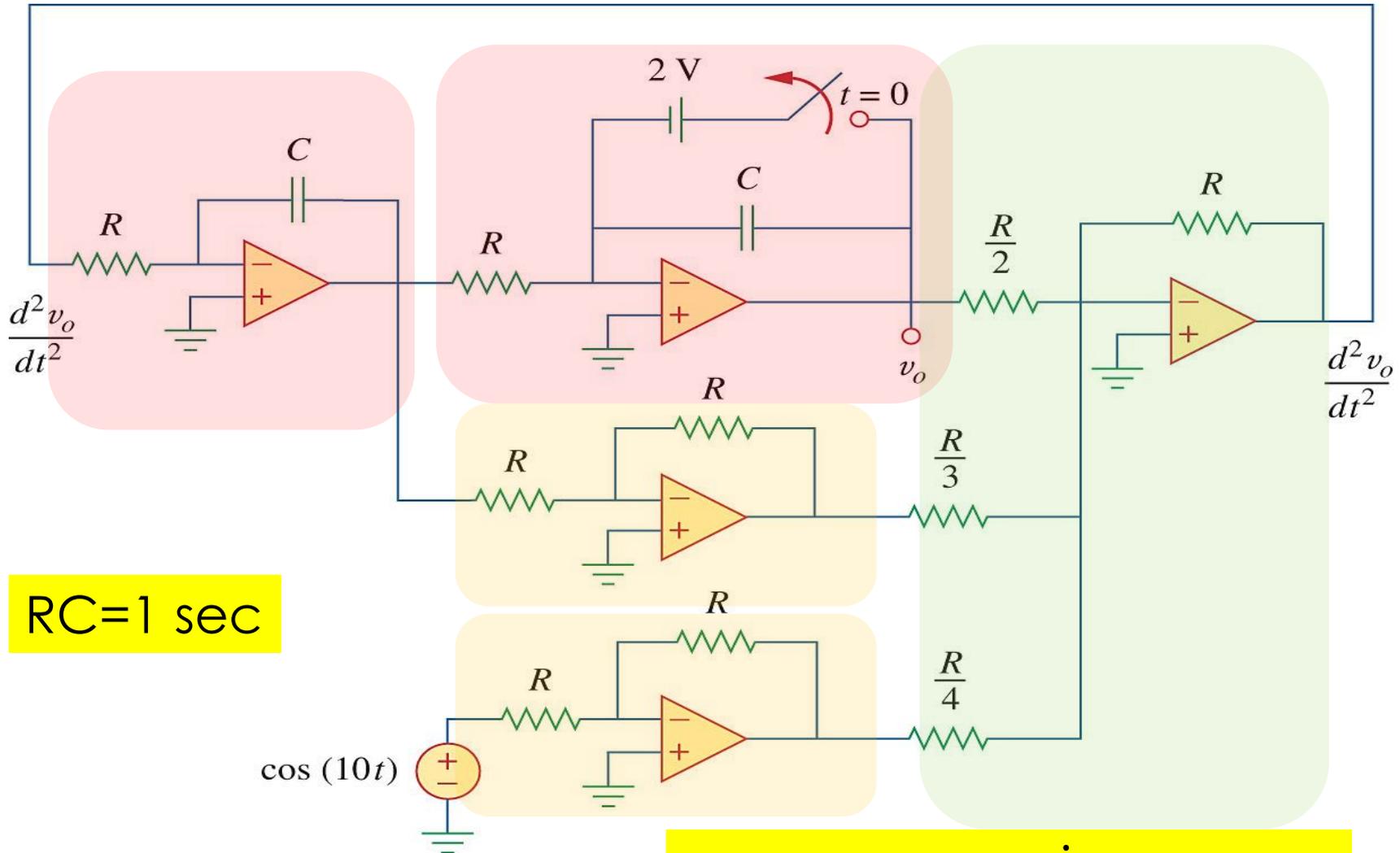
# Solving Differential Equation Using Opamp Circuit




$RC=1 \text{ sec}$

$$\ddot{v}_o + 3\dot{v}_o + 2v_o = 4\cos(10t)$$
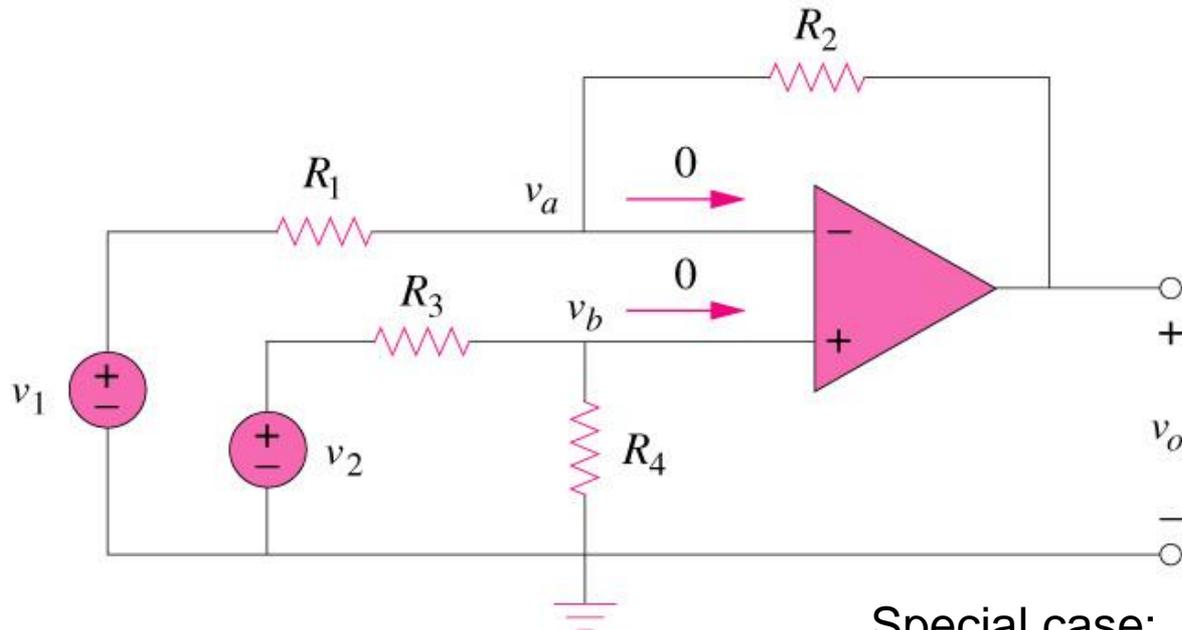
# Difference Amplifier

- Difference amplifier is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.




Special case:



$$v_0 = \frac{1 + R_2/R_1}{1 + R_3/R_4} v_2 - \frac{R_2}{R_1} v_1$$

$$R_1 = R_2 \text{ and } R_3 = R_4 \\ v_0 = v_2 - v_1$$


# Instrumentation Amplifier

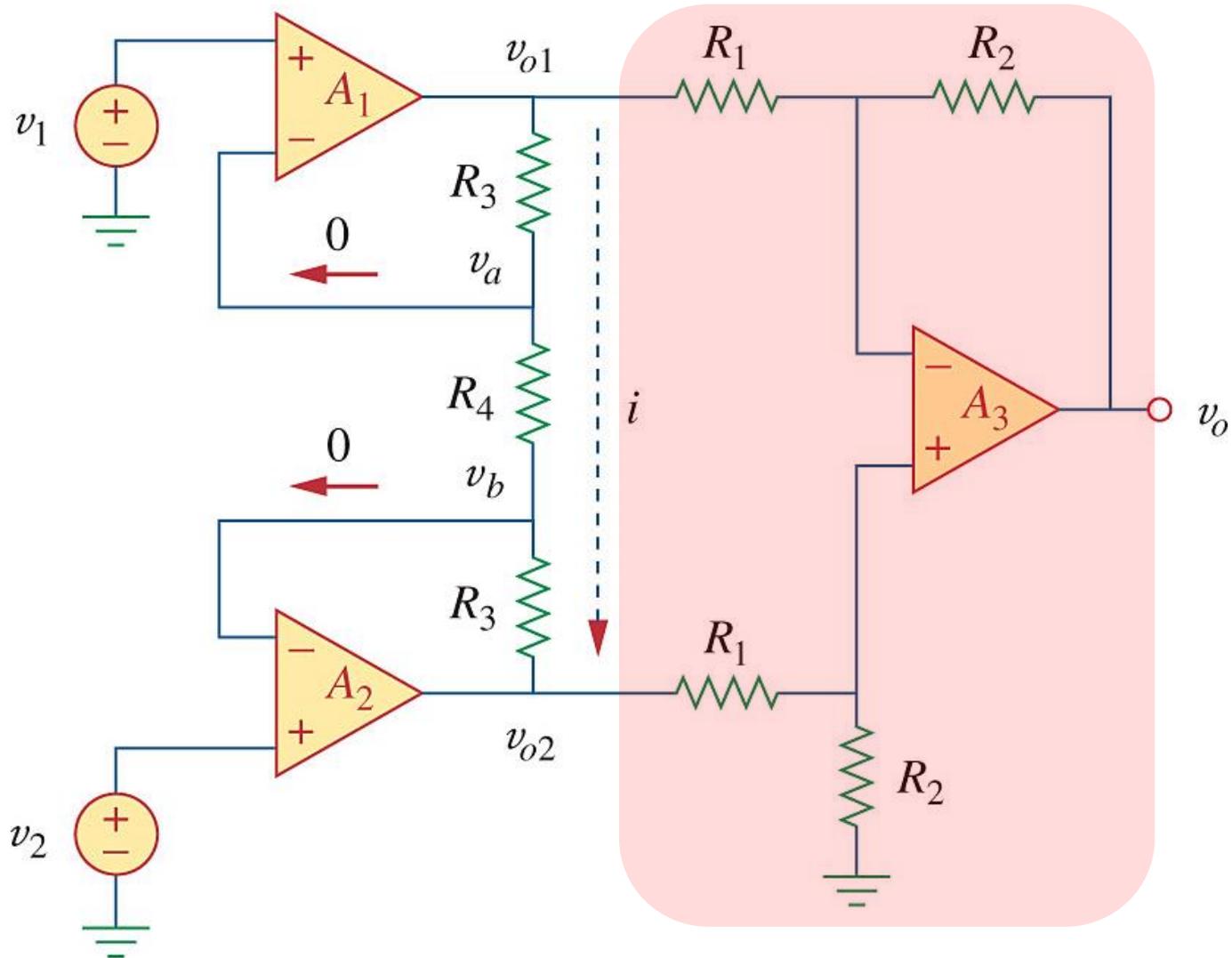


# Instrumentation Amplifier Application

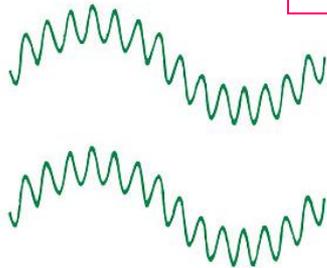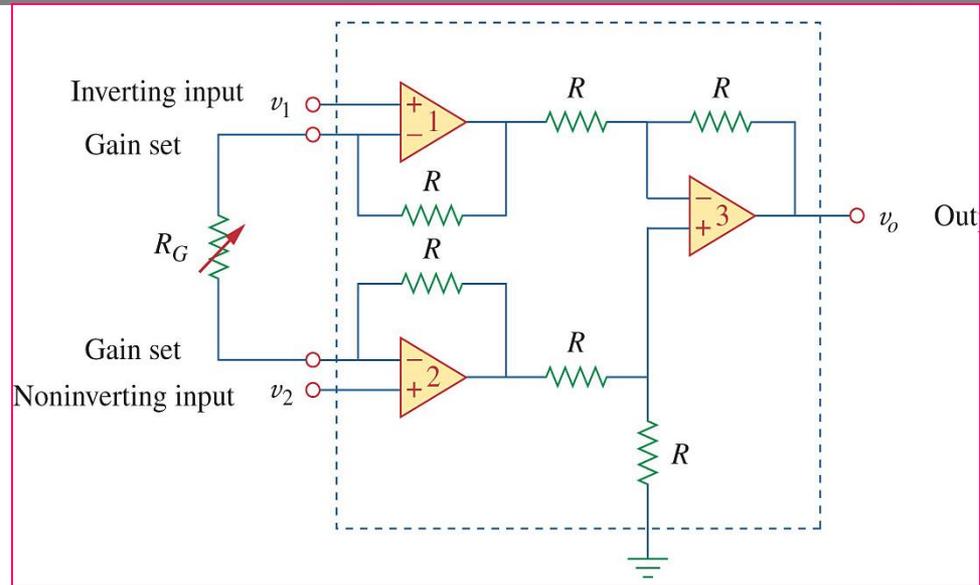

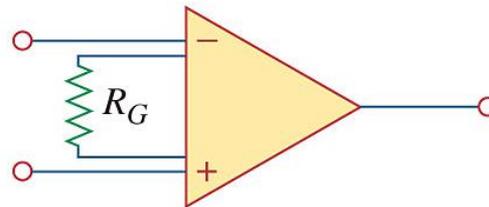Small differential signals riding on larger common-mode signals




Instrumentation amplifier

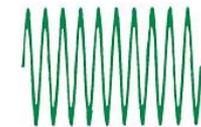

Amplified differential signal, No common-mode signal

- (1) Only amplify difference
- (2) Infinite Input resistance & zero Output resistance
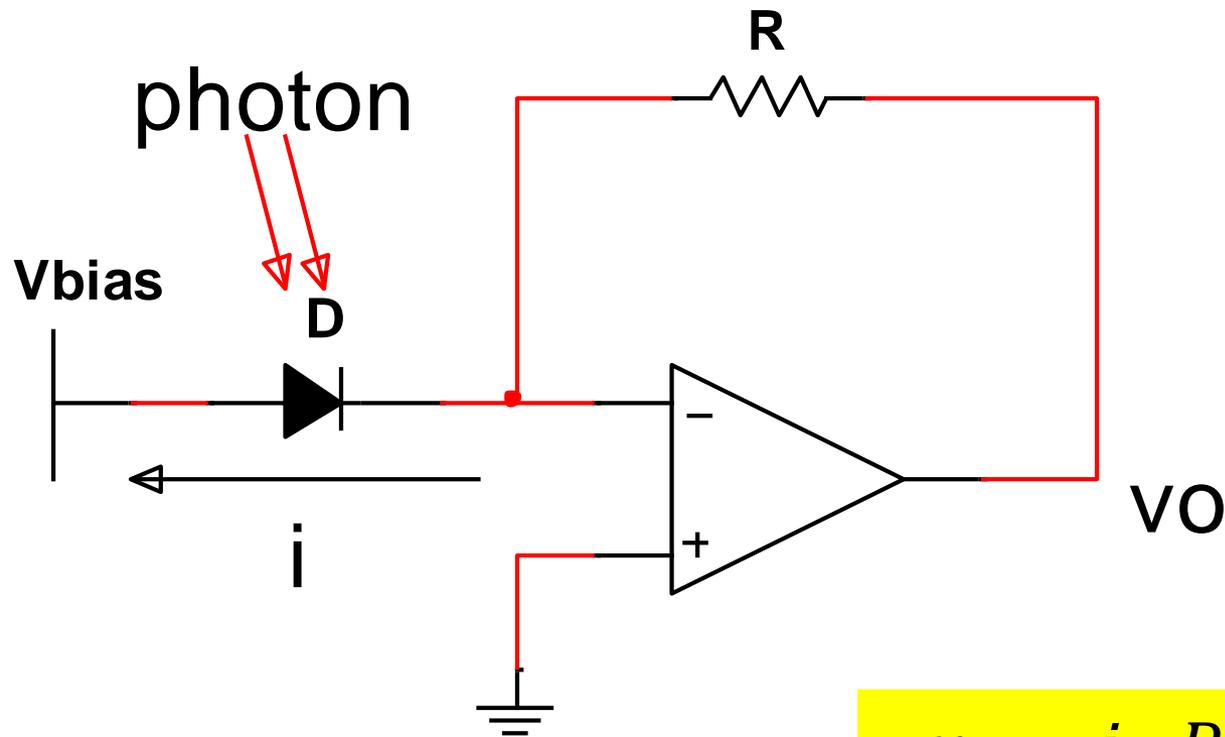
# Transimpedance amplifier for photodiode



$$v_o = i \cdot R$$


- Much easier to measure voltage than current
- Provide large amplification

# Active filter

- RC and OpAmp (<1MHz, bulky inductor in RLC filters)
- 1<sup>st</sup> order filters
  - Low pass
  - High pass
  - Inverting
  - Non-inverting
- 2<sup>nd</sup> order low pass filter

# Active Filter Example

Say  $R_f > R_i$

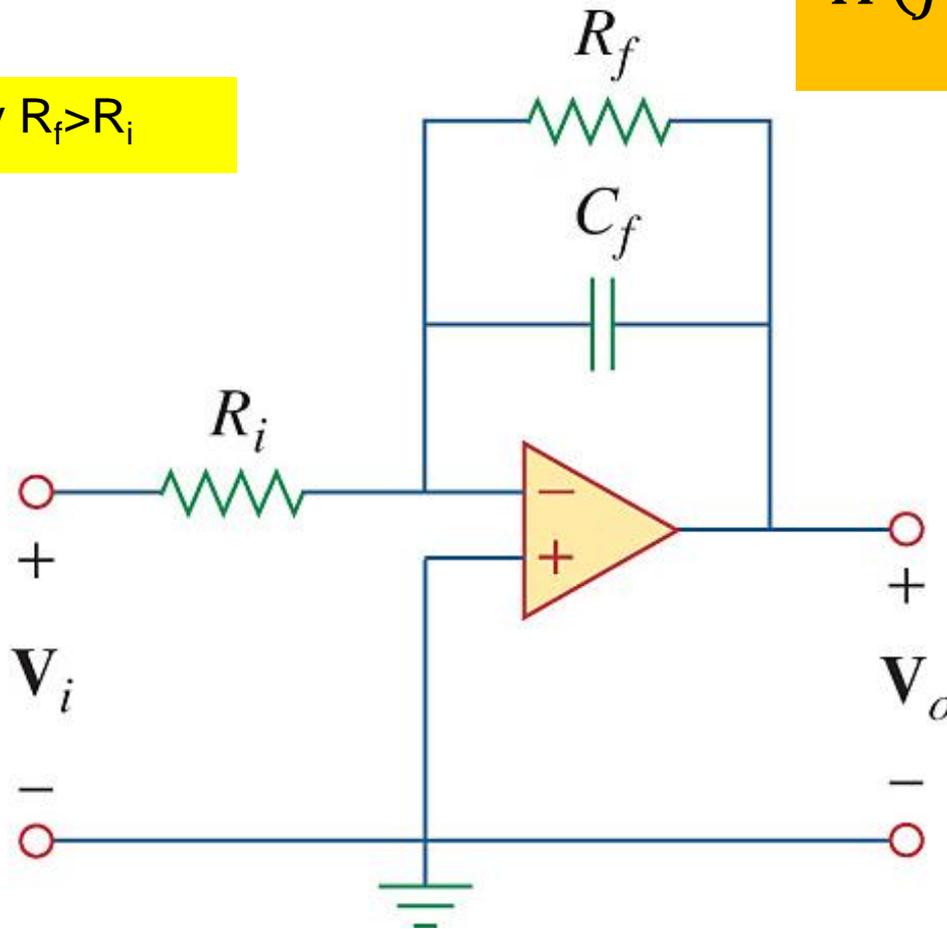


$$H(j\omega) = -\frac{R_f/R_i}{1 + j\omega R_f C_f}$$

Low pass filter

Sketch Bode Plot
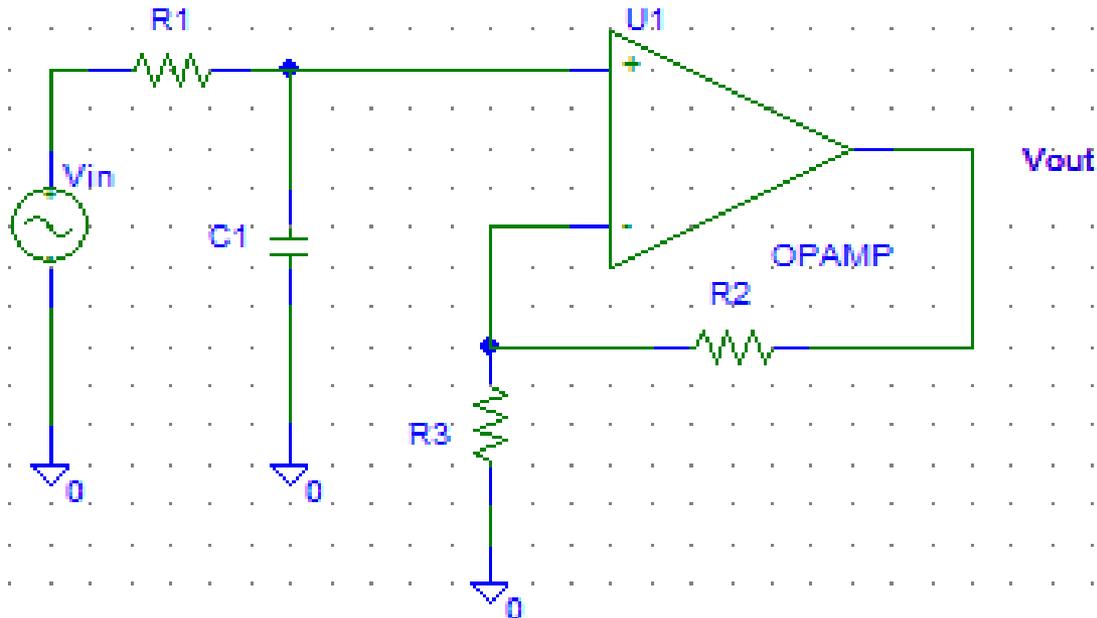
# Active Filter Example

$$H(j\omega) = \frac{1 + R_2/R_3}{1 + j\omega R_1 C_1}$$




Non-inverting 1<sup>st</sup> order low pass active filter
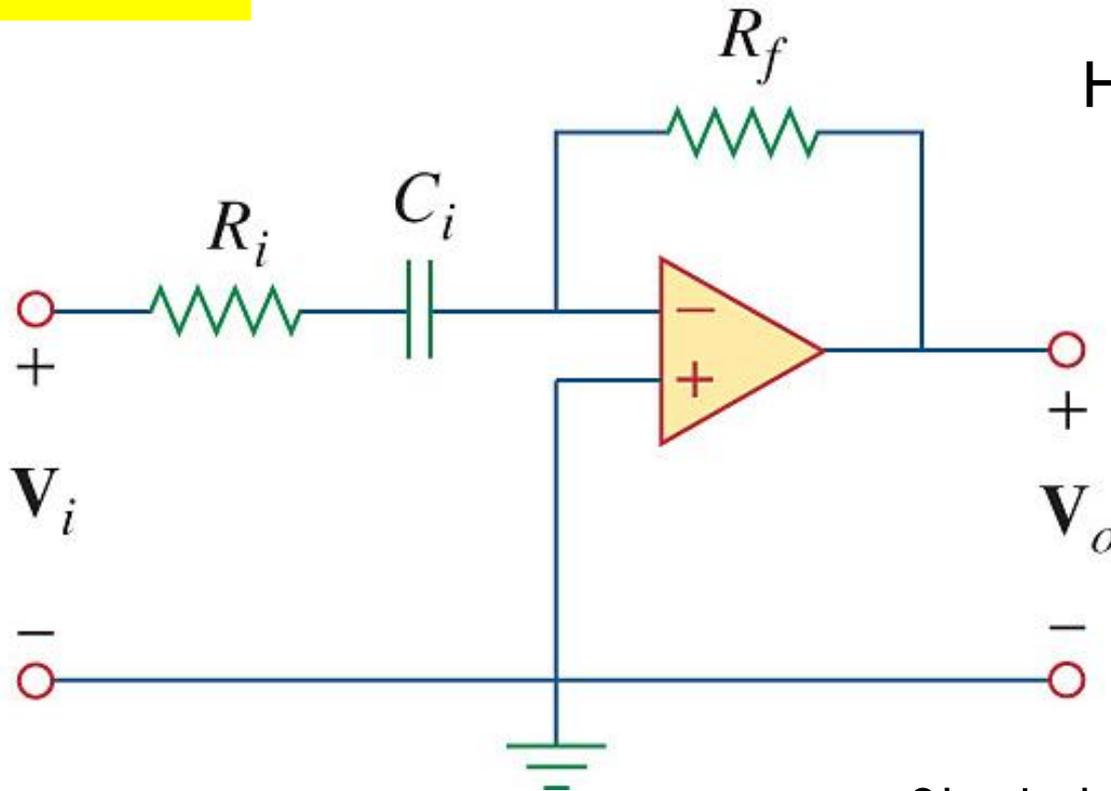
# Active Filter Example

Say  $R_f > R_i$

$$H(j\omega) = -\frac{j\omega R_f C_i}{1 + j\omega R_i C_i}$$




High pass filter

Sketch Bode Plot
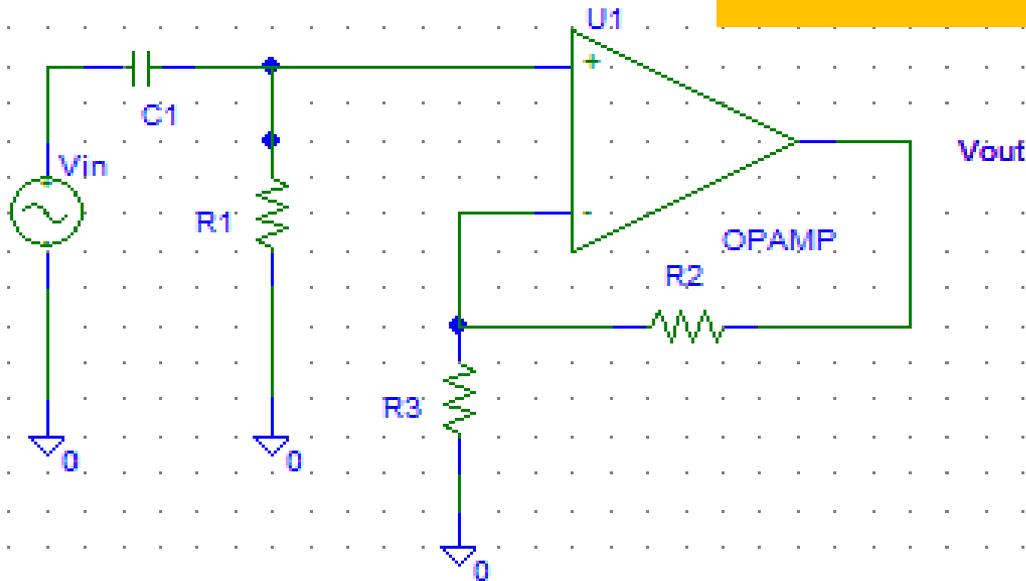
# Active Filter Example

$$H(j\omega) = \frac{j\omega R_1 C_1 \left(1 + \frac{R_2}{R_3}\right)}{1 + j\omega R_1 C_1}$$




Non-inverting 1<sup>st</sup> order high pass active filter.
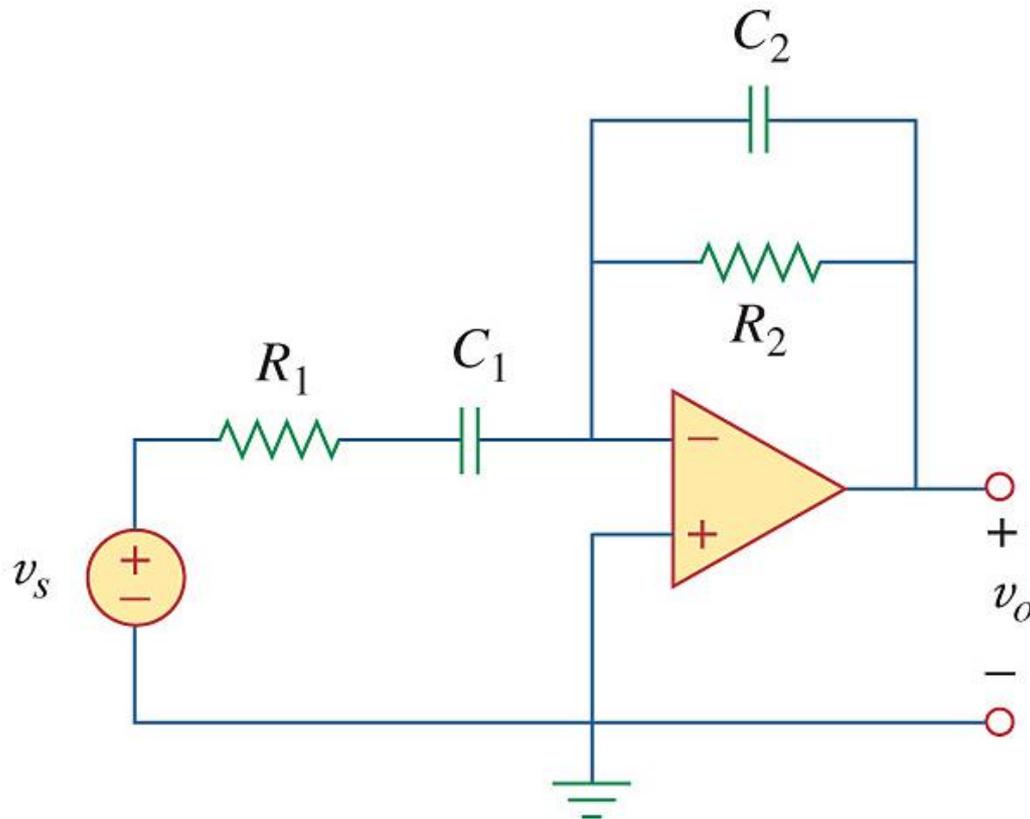
# Active Filter Example

Say  $R_2 > R_1$

$$H(j\omega) = \frac{-j\omega R_2 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$




Bandpass filter

Sketch Bode Plot
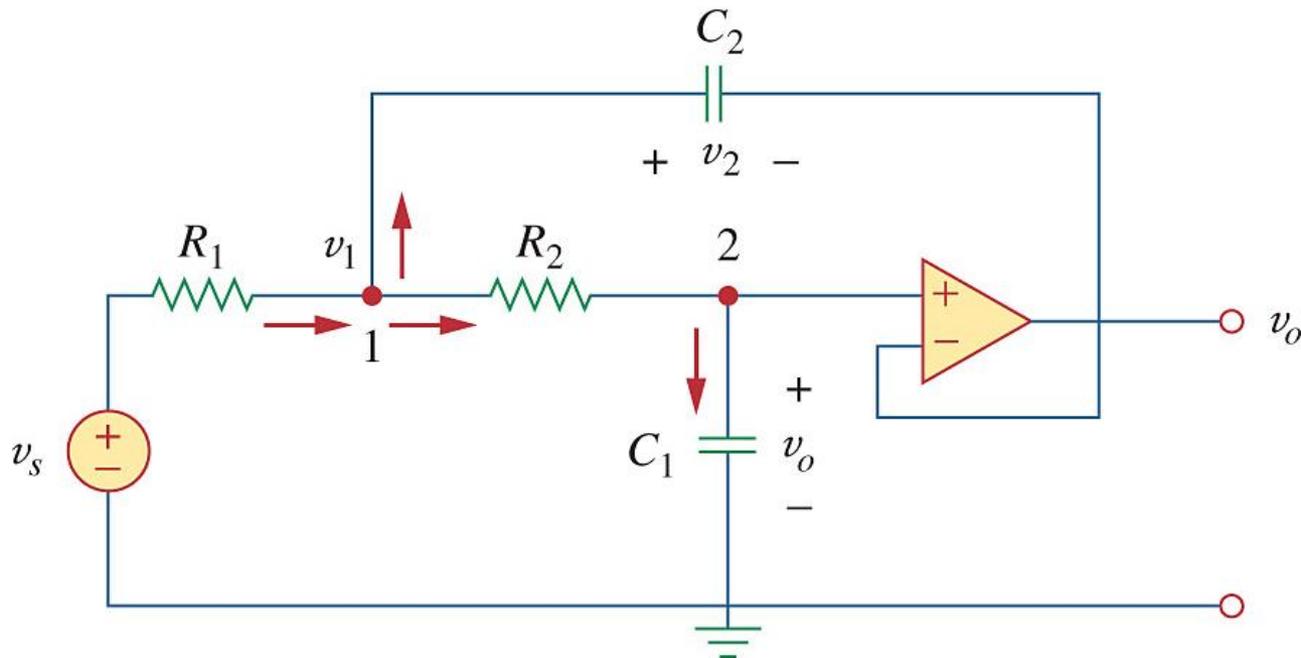
# 2<sup>nd</sup> order Active Filter Sallen-Key Low Pass Filter

Find frequency response function of unity-gain Sallen Key Topology



$$H(j\omega) = \frac{1}{1 + j\omega(R_1 + R_2)C_1 - \omega^2 R_1 R_2 C_1 C_2}$$