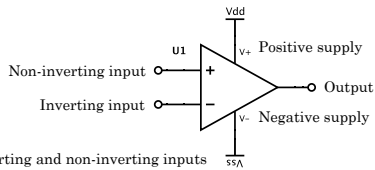


Op Amps and Signal Conditioning

E80 Spring 2015
Erik Spjut

5 wire diagram




Inverting and non-inverting inputs are often flipped in the schematic. Be sure you check.

2

Sample Op Amp Internals

For the curious.
Not needed for E80

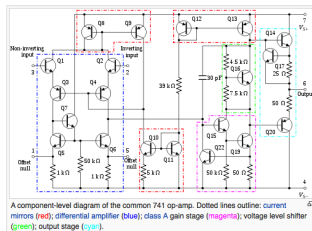

A component-level diagram of the common 741 op-amp. Dotted lines outline: current mirrors (red); differential amplifier (blue); class A gain stage (magenta); voltage level shifter (green); output stage (cyan).

*OpAmpTransistorLevel_Colored_Labels by Daniel Braun - redrawn png file from User:Omegatron, database. Licensed under CC BY 2.5 via Wikimedia Commons - http://commons.wikimedia.org/wiki/File:OpAmpTransistorLevel_Colored_Labels.svg#/media/File:OpAmpTransistorLevel_Colored_Labels.svg

3

Simulink Op Amp Model

For the curious.
Not needed
for E80


- Rate limited integrator followed by a range limit block.
- Ask Prof. Spjut if you ever need it.

4

Simplified Real Op Amp Model

For the curious.
Not needed
for E80

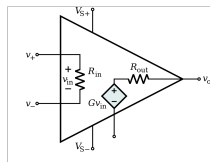
- The internally generated voltage is the gain times the difference of the input voltages.
- The input impedance is very large.
- The output impedance is very small.
- The ideal op amp is derived by assuming the gain approaches ∞ , the output impedance approaches 0, and the input impedance approaches ∞ .



$$V_{out} = G(V_{+} - V_{-})$$

5

TL081 Datasheet

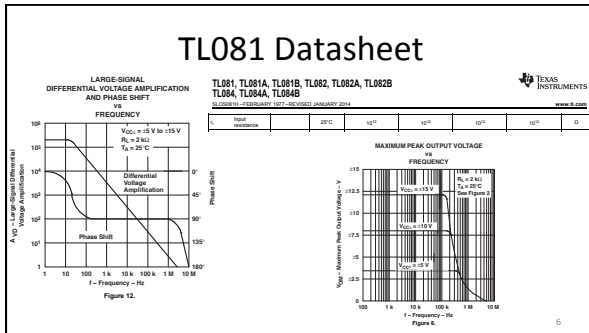

6

Ideal Op Amp Model

- Input impedance: $\infty\Omega$
- Output impedance: 0Ω
- With negative feedback, gain so high that $V_+ = V_-$

7


Operational Amplifier

- Can be configured to perform mathematical operations on a signal.
 - Multiply by a constant (change gain)
 - Change sign
 - Add two or more signals
 - Subtract one signal from another
 - Integrate a signal
 - Differentiate a signal
 - Many others

8

Unity Gain Buffer

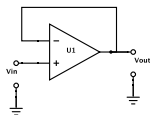- Your go-to circuit. It solves many problems.
- Analyze circuit.
- Draws no current at input (ideal model).
- Provides needed current at output (ideal model).
- Transfers voltage with no circuit loading.




9

Non-Inverting

$$V_{out} = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

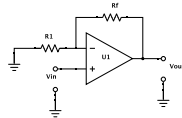- High impedance input, great for measuring voltages
- Gains ≥ 1
- Do you see the voltage divider?
- Analyze circuit.




10

Inverting

$$V_{out} = -\frac{R_f}{R_1} V_{in}$$

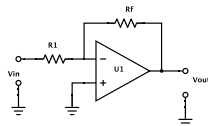- Input impedance is R_1 (ideal model).
- Flips sign (or phase) of input.
- Full gain range
- Analyze circuit.




11

Inverting Summing Amp

$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$

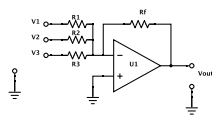- How would you sum three signals?
- How would you average three signals?
- What is the input impedance?
- Analyze circuit.
- Non-inverting summer exists.




12

General Impedance Model

$$V_{out} = -\frac{Z_1}{Z_2} V_{in}$$

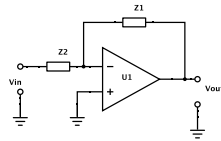- Analyze circuit.
- Do you see the voltage divider?
- What is the input impedance?




13

Integrator

$$V_{out} = -\frac{Z_1}{Z_2} V_{in} = -\frac{1/j\omega C_1}{R_1} V_{in} = -\frac{1}{jR_1 C_1 \omega} V_{in}$$

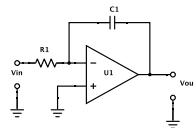
- What is the time-domain version?
- How do you set initial condition?
- How do you reset?



14

Differentiator
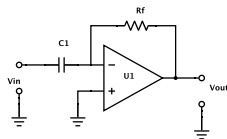
$$V_{out} = -\frac{Z_1}{Z_2} V_{in} = -\frac{R_f}{1/j\omega C_1} V_{in} = -(jR_f C_1 \omega) V_{in}$$



15

Filters – LP, HP

$$\frac{V_{out}}{V_{in}} = H(j\omega) = -\frac{R_1/R_2}{1 + j\omega R_1 C_1}$$

$$\frac{V_{out}}{V_{in}} = H(j\omega) = -\frac{j\omega R_1 C_2}{1 + j\omega R_2 C_2}$$

16

Filters – BP

$$H(j\omega) = \frac{-j\omega R_1 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

17

A Step Up – Sallen & Key


$$\frac{V_{out}}{V_{in}} = \frac{Z_2 Z_4}{Z_1 Z_2 + Z_3(Z_1 + Z_2) + Z_3 Z_4}$$

18

Difference Amplifier

$$V_{out} = \left(\frac{R_2}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} \right) V_2 - \left(\frac{R_2}{R_1} \right) V_1$$

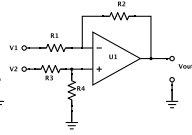If $R_3 = R_1$ and $R_4 = R_2$ then $V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$




19

Instrumentation Amplifier

$$V_{out} - V_{ref} = \left(1 + \frac{2R_1}{R_{gain}} \right) \frac{R_2}{R_2} (V_{non-inv} - V_{inv})$$

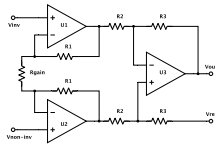- Set gain with R_{gain} .
- V_{ref} must be a low-impedance source.
- Never make one. Use a commercial one.




20

Transimpedance Amp

$$V_{out} = iR_f$$

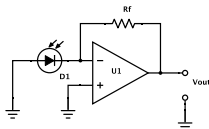- If V_{out} has the wrong sign, flip the diode.
- The far side of the photodiode can be tied to V_{bias} instead of ground.



21

Logarithmic Amp

$$V_{out} = -V_T \ln\left(\frac{V_{in}}{i_s R}\right)$$

V_T and i_s are diode properties.

- Thermal voltage
- Saturation current

22

Exponential Amp

$$V_{out} = -R_1 i_s \exp\left(\frac{V_{in}}{V_T}\right)$$

V_T and i_s are diode properties.

- Thermal voltage
- Saturation current

23

What Does It Do?

- What does the first voltage divider do?
- Can you find the unity gain buffer?
- Where is the instrumentation amp?
- Can you find the modified difference amp?
- What are G and K ?
- Don't use a circuit you don't understand.

$$V_{out} = G(V_2 - V_4) + K$$

24

LabVIEW File Naming Convention:

Your file name should be (Last Name)_(First Initial)_A(Assignment Number)_S(Section Number). (vi or llb). For example, if I were Greg Lake in Section 4 and I was turning in Assignment 3, my file would be named Lake_G_A3_S4.llb. **If your file does not have the correct naming convention, it will not be graded.**

Professors have asked that you submit lab reports as PDF files. There are too many Mac/Win formatting battles to submit Word files.

25
