

Lecture 19: Packaging, Power, & Clock

Outline

- ☐ Packaging
- ☐ Power Distribution
- ☐ Clock Distribution


Packages

□ Package functions

- Electrical connection of signals and power from chip to board
- Little delay or distortion
- Mechanical connection of chip to board
- Removes heat produced on chip
- Protects chip from mechanical damage
- Compatible with thermal expansion
- Inexpensive to manufacture and test


Package Types

□ Through-hole vs. surface mount

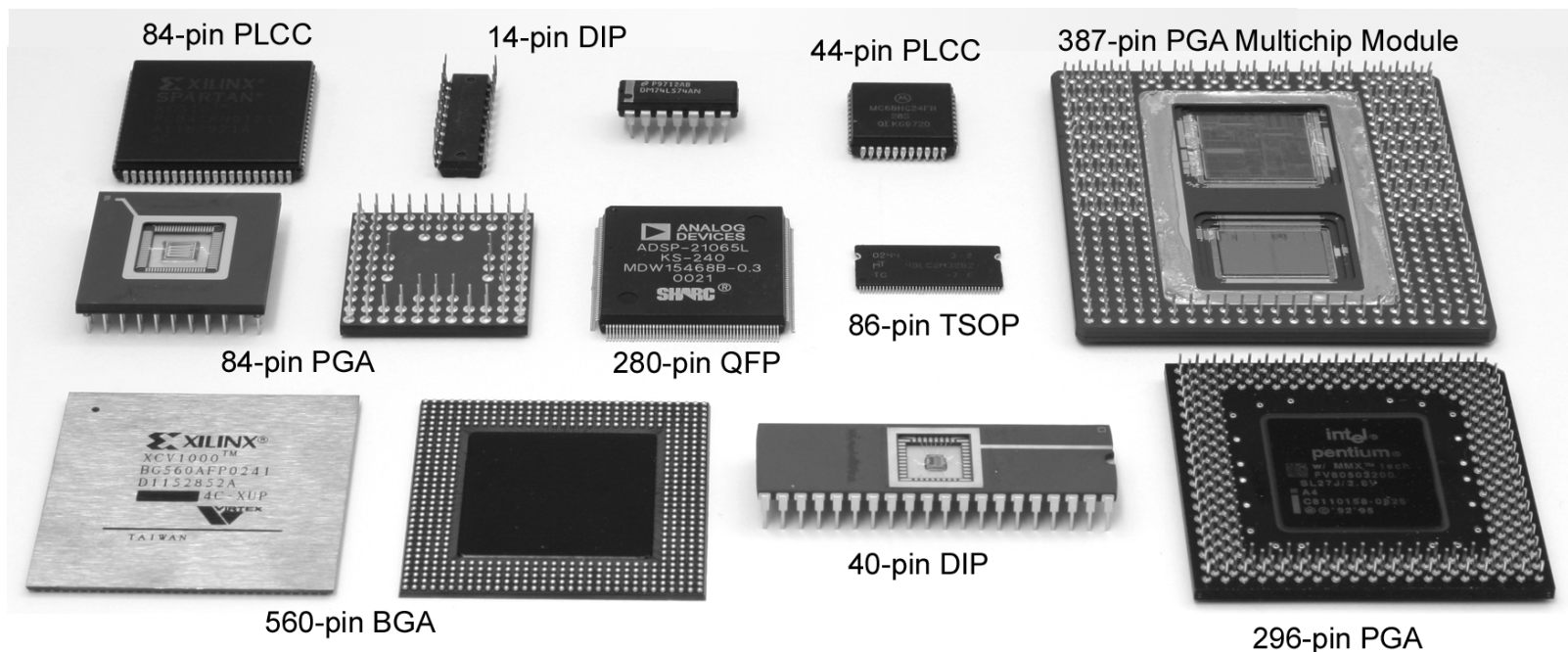

Chip-to-Package Bonding

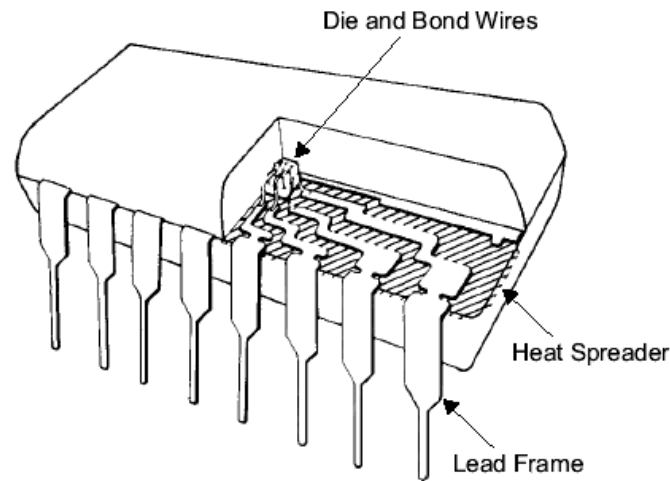- ❑ Traditionally, chip is surrounded by *pad frame*
 - Metal pads on 100 – 200 μm pitch
 - Gold *bond wires* attach pads to package
 - *Lead frame* distributes signals in package
 - Metal *heat spreader* helps with cooling




Advanced Packages

- ❑ Bond wires contribute parasitic inductance
- ❑ Fancy packages have many signal, power layers
 - Like tiny printed circuit boards
- ❑ *Flip-chip* places connections across surface of die rather than around periphery
 - Top level metal pads covered with solder balls
 - Chip flips upside down
 - Carefully aligned to package (done blind!)
 - Heated to melt balls
 - Also called *C4* (Controlled Collapse Chip Connection)

Package Parasitics

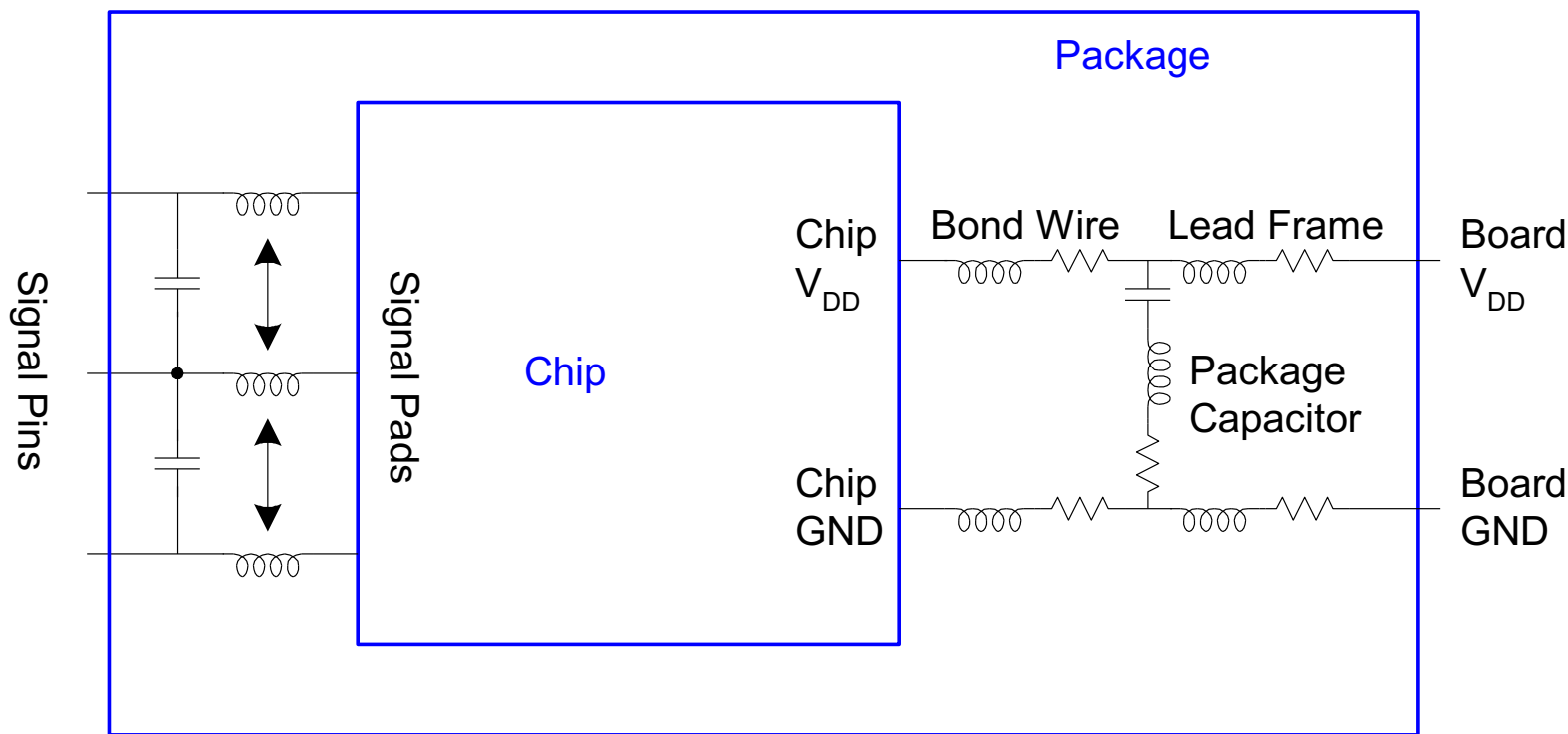- ❑ Use many V_{DD} , GND in parallel
 - Inductance, I_{DD}



Heat Dissipation

- ❑ 60 W light bulb has surface area of 120 cm²
- ❑ Itanium 2 die dissipates 130 W over 4 cm²
 - Chips have enormous power densities
 - Cooling is a serious challenge
- ❑ Package spreads heat to larger surface area
 - Heat sinks may increase surface area further
 - Fans increase airflow rate over surface area
 - Liquid cooling used in extreme cases (\$\$\$)

Thermal Resistance

- ❑ $\Delta T = \Theta_{ja} P$
 - ΔT : temperature rise on chip
 - Θ_{ja} : thermal resistance of chip junction to ambient
 - P : power dissipation on chip
- ❑ Thermal resistances combine like resistors
 - Series and parallel
- ❑ $\Theta_{ja} = \Theta_{jp} + \Theta_{pa}$
 - Series combination

Example

- ❑ Your chip has a heat sink with a thermal resistance to the package of 4.0° C/W .
- ❑ The resistance from chip to package is 1° C/W .
- ❑ The system box ambient temperature may reach 55° C .
- ❑ The chip temperature must not exceed 100° C .
- ❑ What is the maximum chip power dissipation?



- ❑ $(100 - 55 \text{ C}) / (4 + 1 \text{ C/W}) = 9 \text{ W}$

Temperature Sensor

- ❑ Monitor die temperature and throttle performance if it gets too hot
- ❑ Use a pair of pnp bipolar transistors
 - Vertical pnp available in CMOS

$$I_c = I_s e^{\frac{qV_{BE}}{kT}} \rightarrow V_{BE} = \frac{kT}{q} \ln \frac{I_c}{I_s}$$
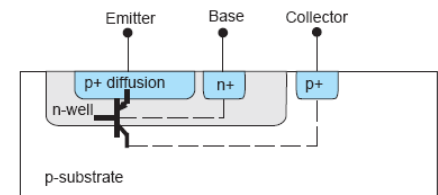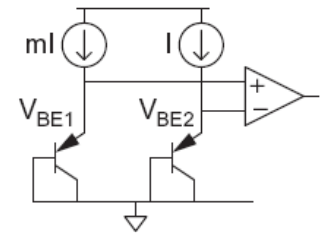
$$\Delta V_{BE} = V_{BE1} - V_{BE2} = \frac{kT}{q} \left(\ln \frac{I_{c1}}{I_s} - \ln \frac{I_{c2}}{I_s} \right) = \frac{kT}{q} \left(\ln \frac{I_{c1}}{I_{c2}} \right) = \frac{kT}{q} \ln m$$




- ❑ Voltage difference is proportional to absolute temp
 - Measure with on-chip A/D converter

Power Distribution

- ❑ Power Distribution Network functions
 - Carry current from pads to transistors on chip
 - Maintain stable voltage with low noise
 - Provide average and peak power demands
 - Provide current return paths for signals
 - Avoid electromigration & self-heating wearout
 - Consume little chip area and wire
 - Easy to lay out

Power Requirements

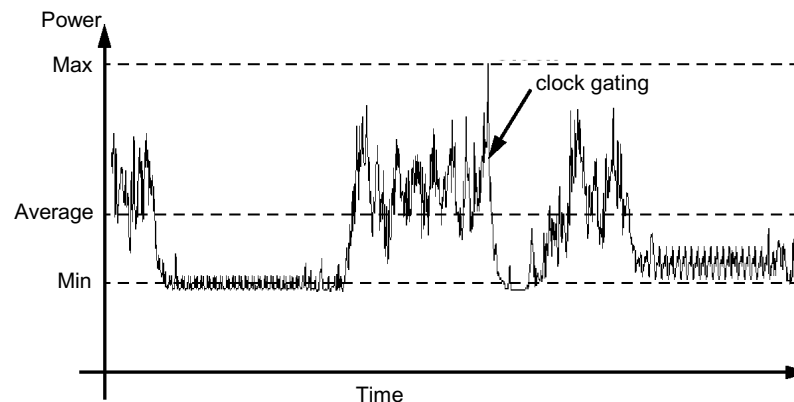- ❑ $V_{DD} = V_{DDnominal} - V_{droop}$
- ❑ Want $V_{droop} < +/- 10\%$ of V_{DD}
- ❑ Sources of V_{droop}
 - IR drops
 - L di/dt noise
- ❑ I_{DD} changes on many time scales



IR Drop

- ☐ A chip draws 24 W from a 1.2 V supply. The power supply impedance is 5 m Ω . What is the IR drop?
- ☐
- ☐


L di/dt Noise

- ❑ A 1.2 V chip switches from an idle mode consuming 5W to a full-power mode consuming 53 W. The transition takes 10 clock cycles at 1 GHz. The supply inductance is 0.1 nH. What is the L di/dt droop?




Bypass Capacitors

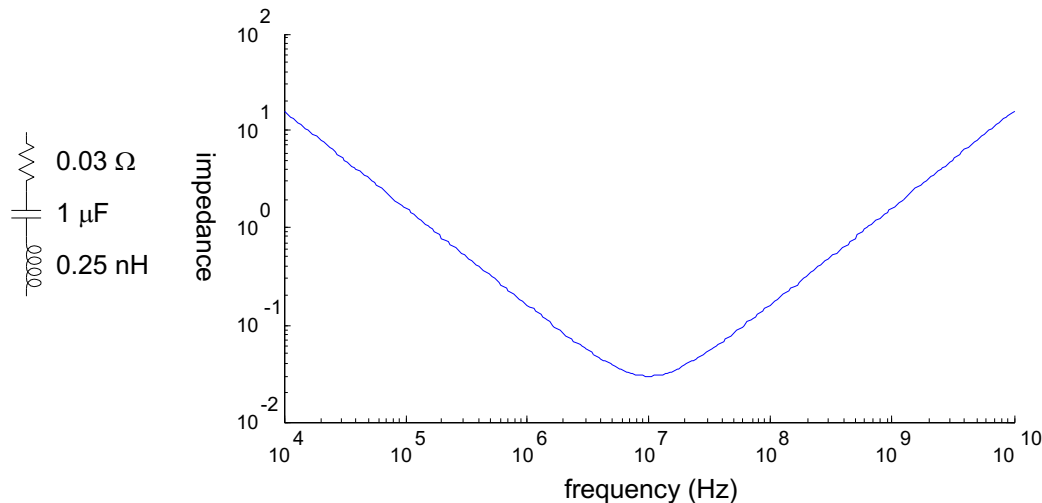- ❑ Need low supply impedance at all frequencies
- ❑ Ideal capacitors have impedance decreasing with ω
- ❑ Real capacitors have parasitic R and L
 - Leads to resonant frequency of capacitor




Power System Model

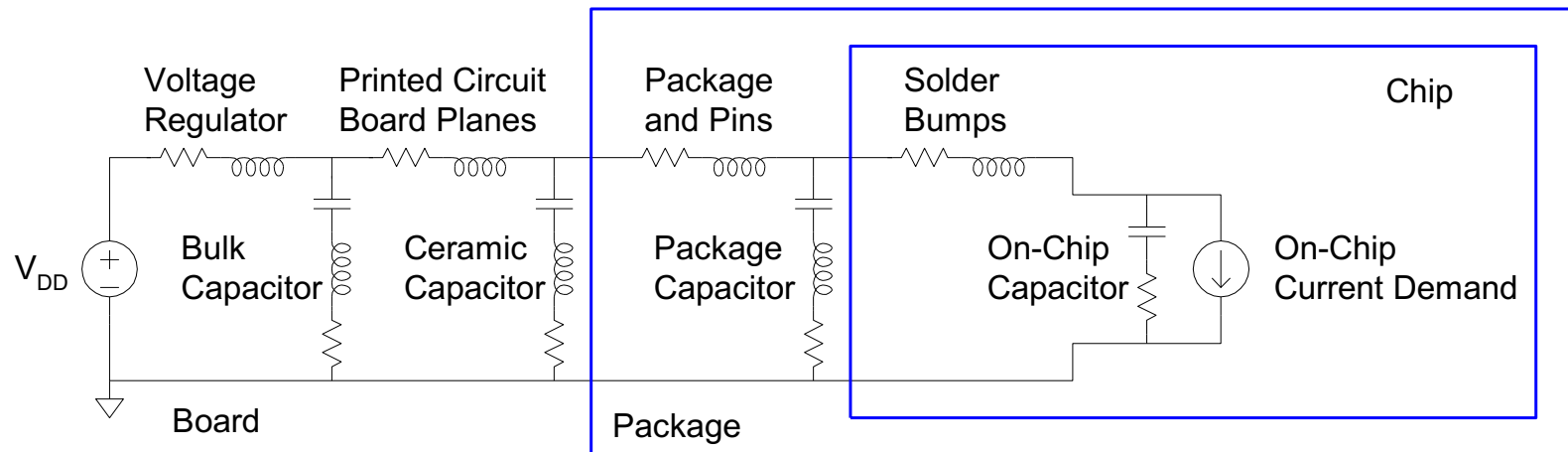- ❑ Power comes from regulator on system board
 - Board and package add parasitic R and L
 - Bypass capacitors help stabilize supply voltage
 - But capacitors also have parasitic R and L
- ❑ Simulate system for time and frequency responses





Frequency Response

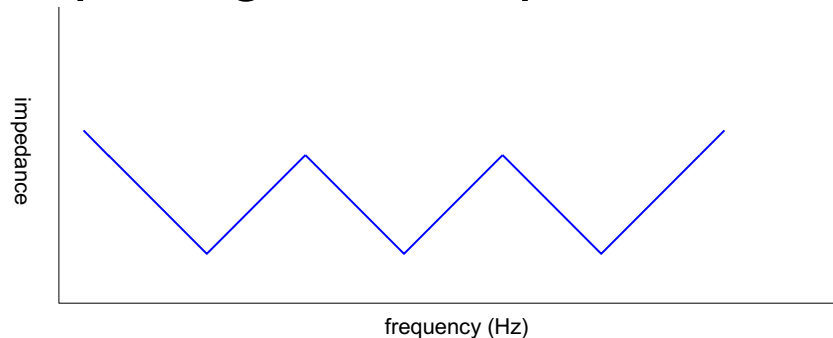- ❑ Multiple capacitors in parallel
 - Large capacitor near regulator has low impedance at low frequencies
 - But also has a low self-resonant frequency
 - Small capacitors near chip and on chip have low impedance at high frequencies
- ❑ Choose caps to get low impedance at all frequencies



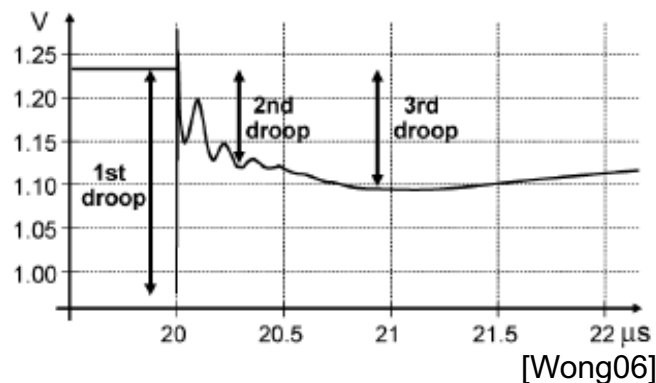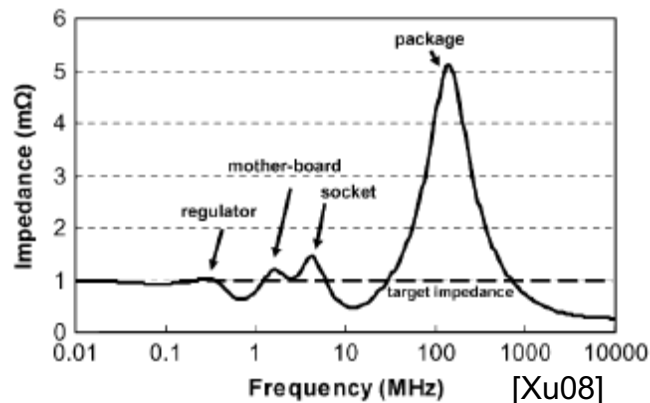
Example: Pentium 4

- ❑ Power supply impedance for Pentium 4
 - Spike near 100 MHz caused by package L
- ❑ Step response to sudden supply current chain
 - 1st droop: on-chip bypass caps
 - 2nd droop: package capacitance
 - 3rd droop: board capacitance



Charge Pumps

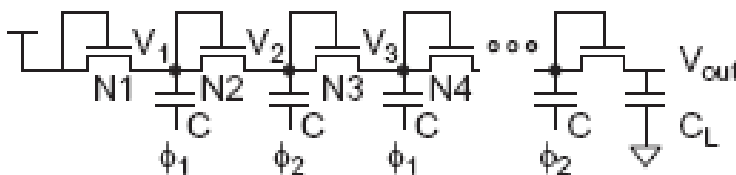- ❑ Sometimes a different supply voltage is needed but little current is required
 - 20 V for Flash memory programming
 - Negative body bias for leakage control during sleep
- ❑ Generate the voltage on-chip with a charge pump



$$V_{\text{out}} = N \left[\frac{CV_{DD} - \frac{I_{\text{out}}}{f}}{C + C_s} - V_t \right]$$

Energy Scavenging


- ❑ Ultra-low power systems can scavenge their energy from the environment rather than needing batteries
 - Solar calculator (solar cells)
 - RFID tags (antenna)
 - Tire pressure monitors powered by vibrational energy of tires (piezoelectric generator)
- ❑ Thin film microbatteries deposited on the chip can store energy for times of peak demand

Clock Distribution

- ❑ On a small chip, the clock distribution network is just a wire
 - And possibly an inverter for clkb
- ❑ On practical chips, the RC delay of the wire resistance and gate load is very long
 - Variations in this delay cause clock to get to different elements at different times
 - This is called *clock skew*
- ❑ Most chips use repeaters to buffer the clock and equalize the delay
 - Reduces but doesn't eliminate skew

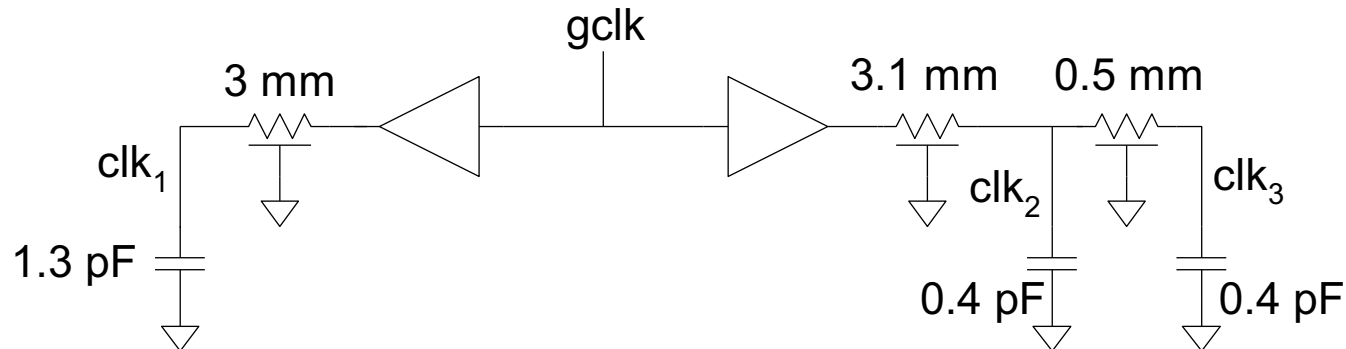Example

- ❑ Skew comes from differences in gate and wire delay
 - With right buffer sizing, clk_1 and clk_2 could ideally arrive at the same time.
 - But power supply noise changes buffer delays
 - clk_2 and clk_3 will always see RC skew




Review: Skew Impact

- ❑ Ideally full cycle is available for work
- ❑ Skew adds sequencing overhead
- ❑ Increases hold time too

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
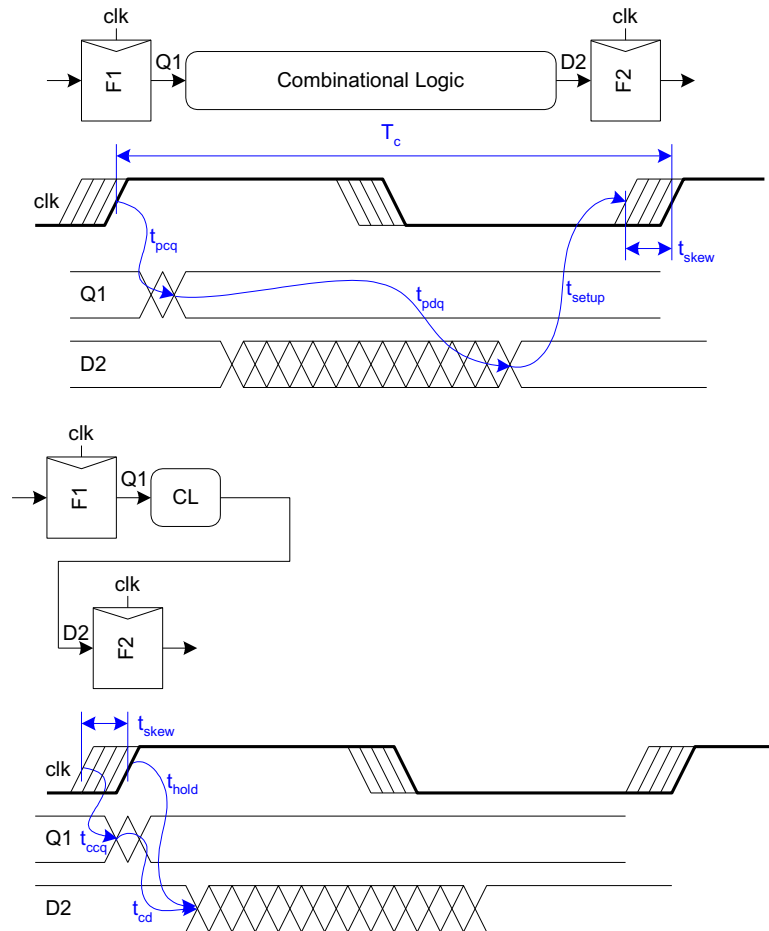
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$



Solutions

- ❑ Reduce clock skew
 - Careful clock distribution network design
 - Plenty of metal wiring resources
- ❑ Analyze clock skew
 - Only budget actual, not worst case skews
 - Local vs. global skew budgets
- ❑ Tolerate clock skew
 - Choose circuit structures insensitive to skew

Clock Dist. Networks




- ☐ *Ad hoc*
- ☐ Grids
- ☐ H-tree
- ☐ Hybrid

Clock Grids

- ☐ Use grid on two or more levels to carry clock
- ☐ Make wires wide to reduce RC delay
- ☐ Ensures low skew between nearby points
- ☐ But possibly large skew across die



Alpha Clock Grids

Alpha 21064

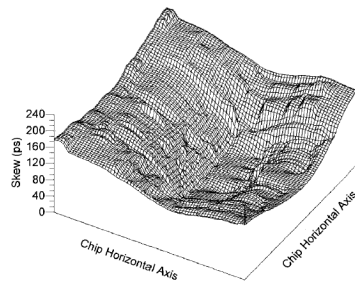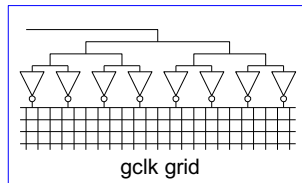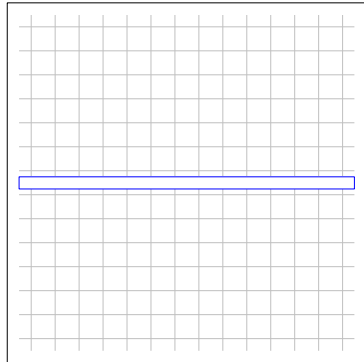




Alpha 21064

Alpha 21164

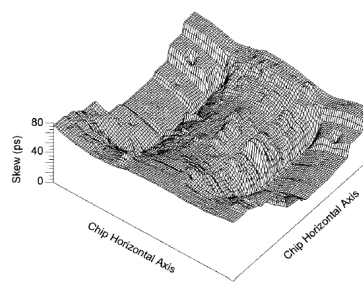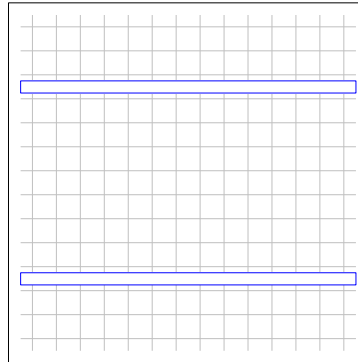

Alpha 21164


Alpha 21264

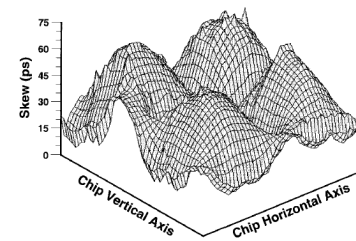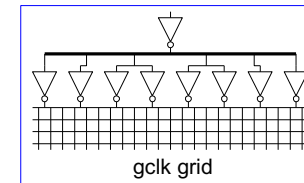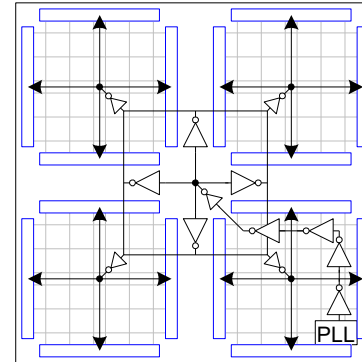

Alpha 21264

H-Trees

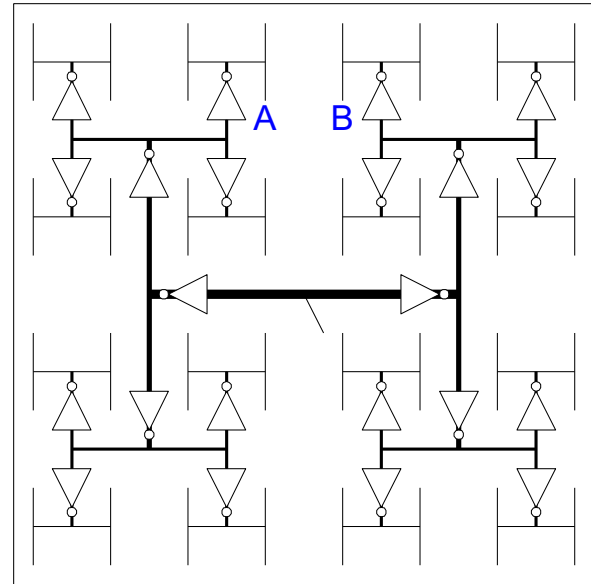- ❑ Fractal structure
 - Gets clock arbitrarily close to any point
 - Matched delay along all paths
- ❑ Delay variations cause skew
- ❑ A and B might see big skew




Itanium 2 H-Tree

❑ Four levels of buffering:

- Primary driver
- Repeater
- Second-level clock buffer
- Gater

❑ Route around obstructions

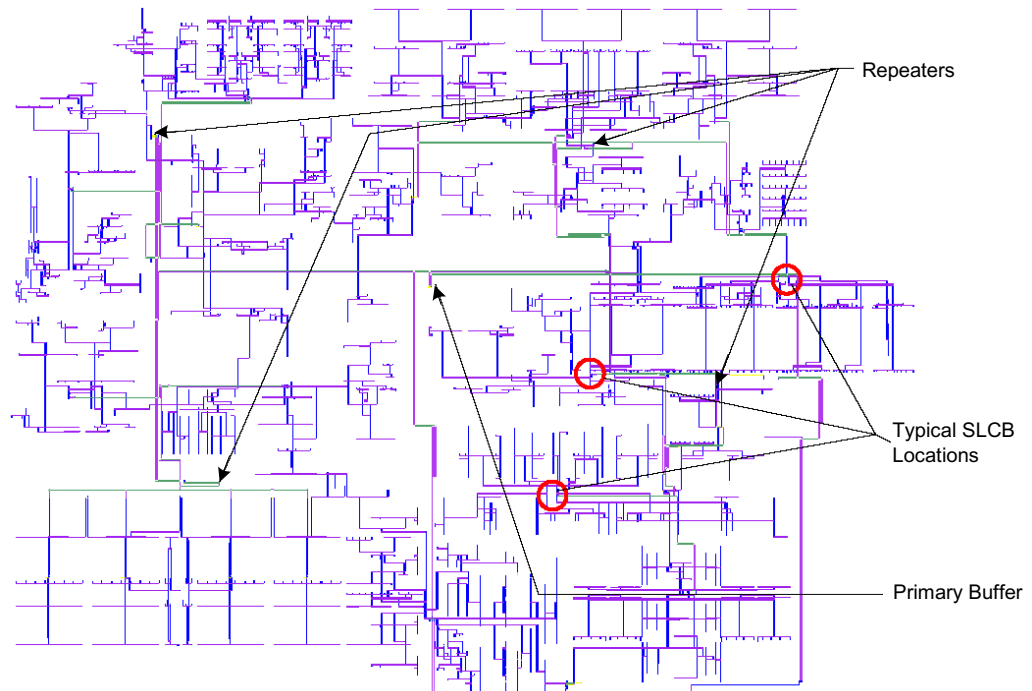

Hybrid Networks

- ❑ Use H-tree to distribute clock to many points
- ❑ Tie these points together with a grid

- ❑ Ex: IBM Power4, PowerPC
 - H-tree drives 16-64 sector buffers
 - Buffers drive total of 1024 points
 - All points shorted together with grid